

## FEEDBACKS

\* Two Kinds of feedback:-

- (i) negative or degenerative.
- (ii) positive or regenerative.

\* Types of amplifiers:-

- (i) Voltage-in  $\rightarrow$  Voltage-out  $\Rightarrow A_v$ .
- (ii) Current-in  $\rightarrow$  Current-out  $\Rightarrow A_i$ .
- (iii) Voltage-in  $\rightarrow$  Current-out  $\Rightarrow G_m$
- (iv) Current-in  $\rightarrow$  Voltage-out  $\Rightarrow R_m$ .

\*  $A_v$  = Voltage gain (dimensionless)

\*  $A_i$  = Current gain (dimensionless)

\*  $G_m$  = Transconductance (Siemens or Mhos)

\*  $R_m$  = Transresistance (Ohms).

\* Negative-Feedback is used to realize amplifiers (any of the above four topologies) so that the following properties are achieved:-


- (i) Gain Desensitization  $\Rightarrow$  make sure that the gain is not sensitive to process, voltage, and temperature (PVT)
- (ii) Non-linearity Reduction  $\Rightarrow$  Make the output linearly proportional to input.
- (iii) Improvement in Input and Output impedances.
- (iv) Enhance the bandwidth.
- (v) Reduce the effect of noise  $\Rightarrow$  Not discussed & is little subtle.

(2)

- \* Positive Feedback is used to
  - ⇒ realize oscillators which serve as clock sources.
  - ⇒ realize regenerative amplifiers used in latches and sense-amplifiers and find extensive application in Memories and digital sequential circuits.

NOTE:- All the goodies of negative-feedback come at the expense of reduction in gain. (No free lunch). ☹️☹️!!!

### GENERAL FEEDBACK STRUCTURE:-

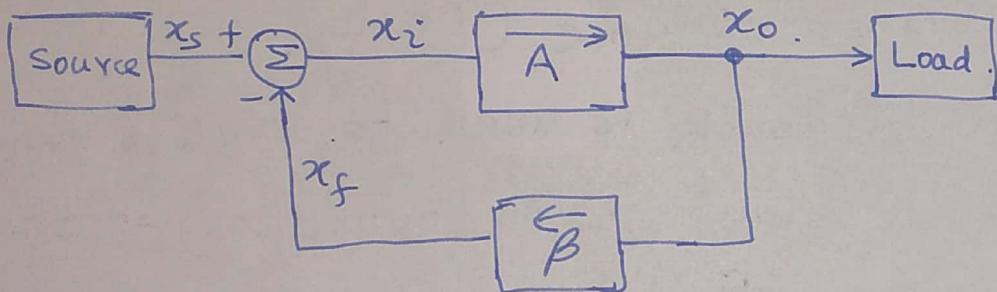

Signal-flow diagram

$A$  = open-loop amplifier gain (i.e.,  $A_u, A_i, G_m$ , or  $B_m$ )

$\beta$  = feedback factor.

Now,  $x_o = A x_i$ ,  $x_f = \beta x_o$ , and  $x_i = x_s - x_f$ .

Thus,

$$A_f = \frac{x_o}{x_s} = \frac{A}{1 + A\beta}$$

$A\beta$  = loop-gain.

If,  $A\beta \gg 1$ , then,  $A_f = \frac{1}{\beta}$ .  $\Rightarrow$  gain is determined by feedback network

$A_f$  = Closed Loop Gain.

\* If  $\beta$  is realized using passive circuit then it does not vary with P.V.T significantly resulting in stable gain.

Properties of Negative Feedback.

① Gain Desensitization:-

$$A_f = \frac{A}{1 + A\beta}$$

If  $A$  changes by 20% then  $A_f$  changes by 0.025%.

$$\frac{dA_f}{A_f} = \frac{1}{1 + A\beta} \frac{dA}{A}$$

$(1 + A\beta)$  is called desensitivity factor.

② Bandwidth Extension:-

$$\text{Let, } A(s) = \frac{A_M}{1 + \frac{s}{\omega_H}}$$

where,  $\omega_H$  is the upper 3-dB cut-off frequency.

Thus,

$$A_f(s) = \frac{A(s)}{1 + \beta A(s)} \quad \dots \quad \text{where } \beta \text{ is assumed to be frequency independent.}$$

$$\Rightarrow A_f(s) = \frac{\frac{A_M}{1 + A_M \beta}}{1 + \frac{s}{\omega_H(1 + A_M \beta)}}$$


$$\Rightarrow \omega_{Hf} = (1 + A\beta) \omega_H$$

④ If the open-loop amplifier has lower 3-dB cut-off frequency of  $\omega_L$ , then after feedback we get,

$$\omega_{Lf} = \frac{\omega_L}{(1 + A_M \beta)}$$

\* Since we assumed a single-pole system the gain-bandwidth product is maintained constant.

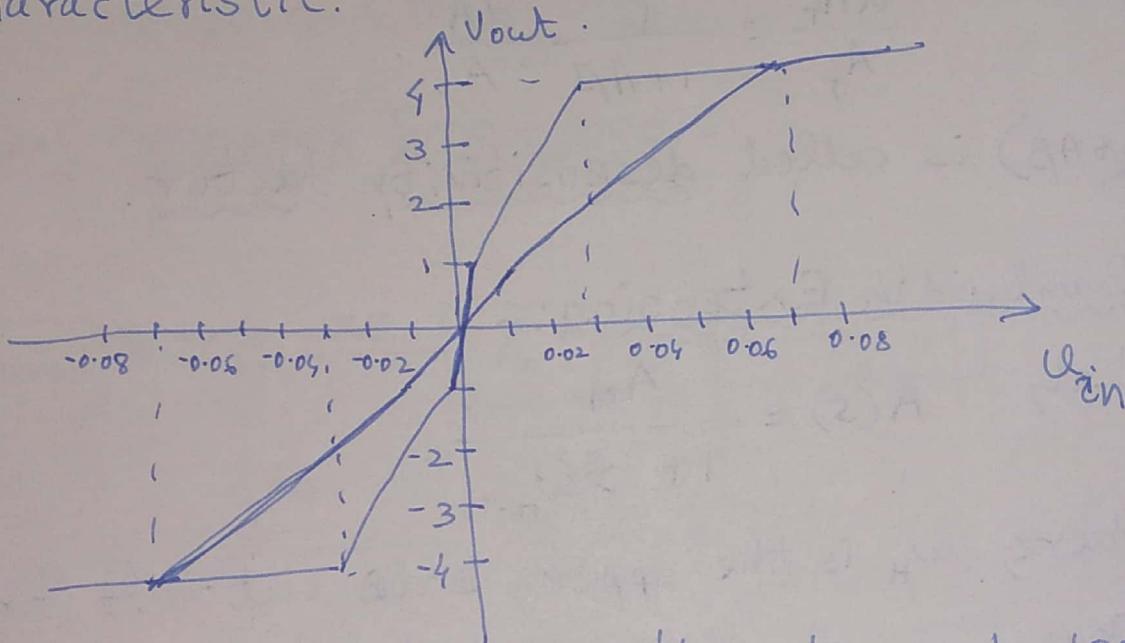③ Reduction in Non-Linear Distortion:- Negative feedback significantly linearizes the input-output characteristic.




$A = 1000$  in beginning and then changes to 100. If  $\beta = 0.01$  then the closed loop gain varies from 90.9 to 50.

④ Enhancement of Input-Output Impedances:- To be discussed for various topologies of feedback.

## (5)

## VOLTAGE AMPLIFIER :-

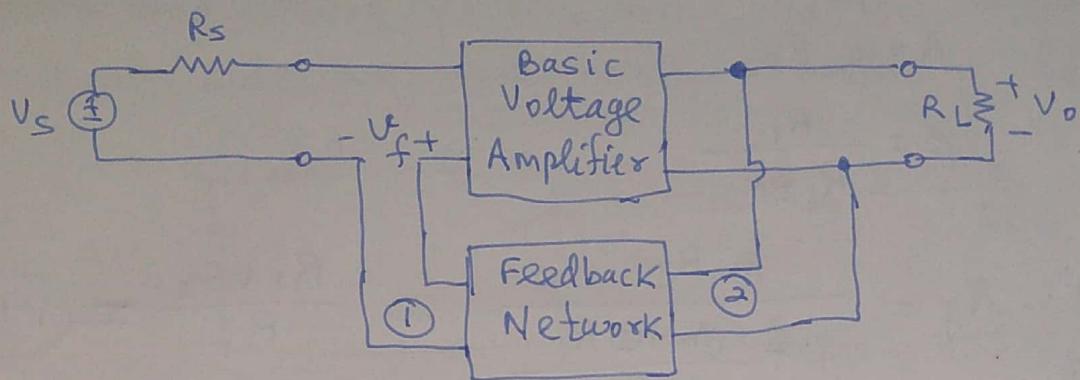

$\Rightarrow$  Voltage-Mixing at input & voltage-sampling in the output.

$\Rightarrow$  Series-Shunt.

\* So feedback topology will have some mixing in the input and some sampling at output.




\* Voltage mixing  $\Rightarrow$  series.

Current sampling  $\Rightarrow$  shunt.

\* Voltage Sampling  $\Rightarrow$  shunt.

Current sampling  $\Rightarrow$  series.

Examples:-

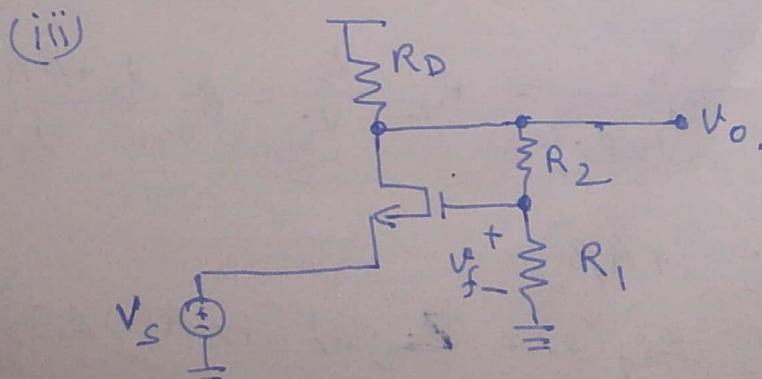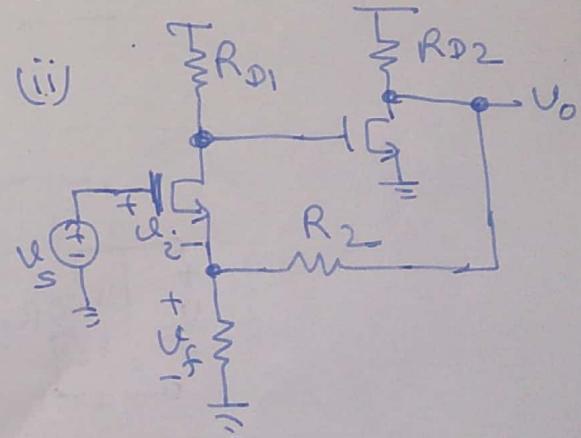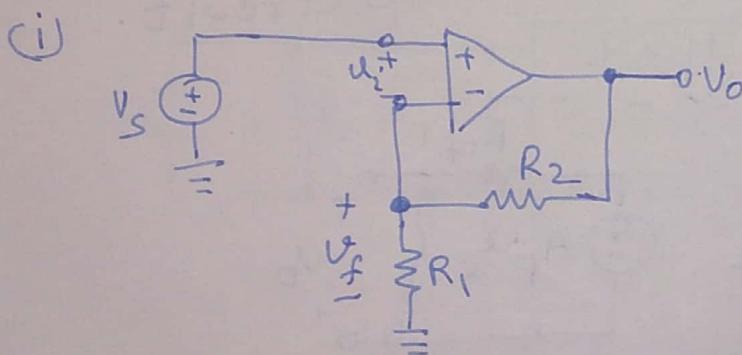

⑥



In. example (iii) if  $(R_1 + R_2) \gg R_D$

$$A = g_m R_D$$

$$\beta = \frac{R_1}{R_1 + R_2}$$

$$\therefore A_f = \frac{g_m R_D}{1 + \frac{g_m R_D R_1}{R_1 + R_2}} \approx \frac{R_1 + R_2}{R_1} = \left(1 + \frac{R_2}{R_1}\right)$$

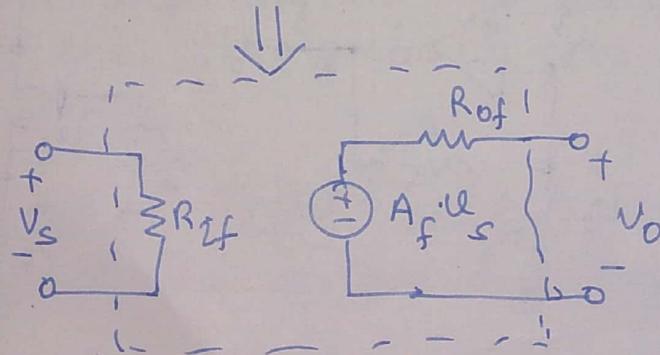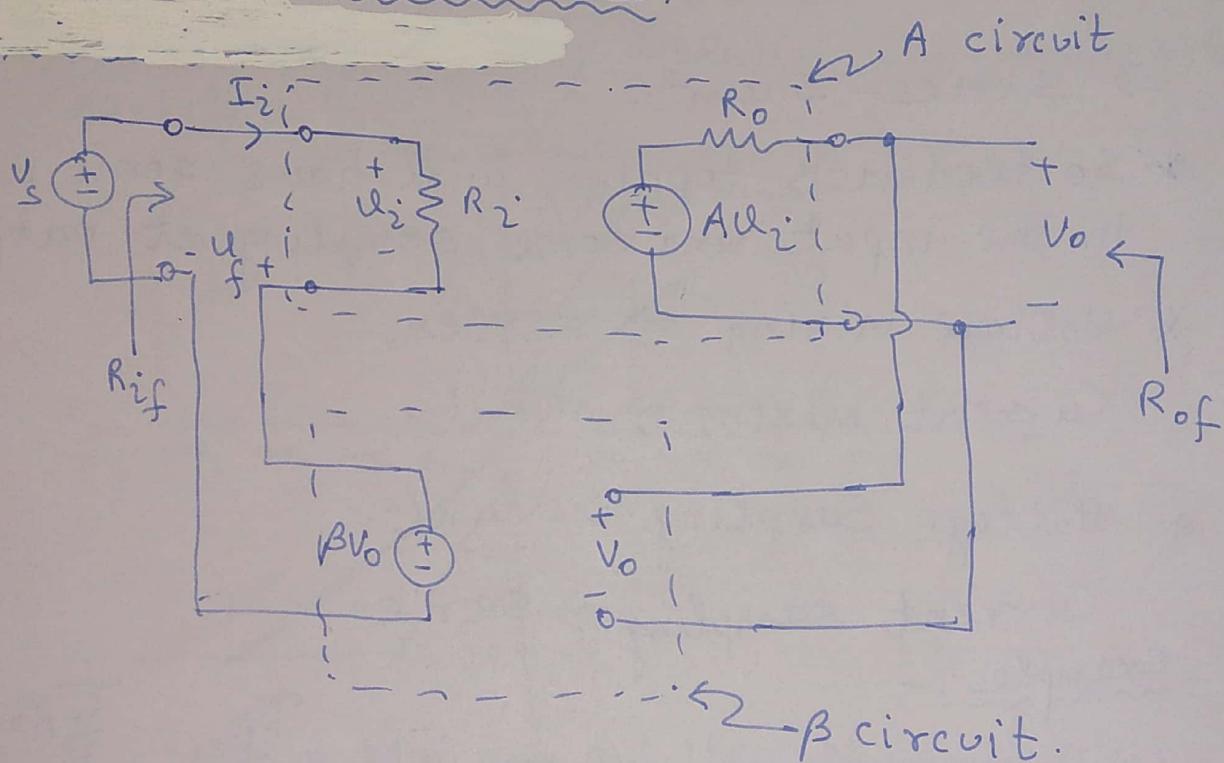if,  $A\beta \gg 1$   
CALCULATION OF I/O IMPEDANCES:-




$$\text{Now, } R_{if} = \frac{V_s}{I_i} = \frac{V_s}{(V_i/R_i)} = R_i \frac{V_s}{V_i} = R_i \frac{V_i + \beta A V_o}{V_i} = R_i \frac{V_i + A \beta V_o}{V_i}$$

$$\Rightarrow R_{if} = R_i (1 + A\beta)$$

$$\text{Generalized impedance, } Z_{if}(s) = Z_i(s) (1 + A(s)\beta(s))$$

7

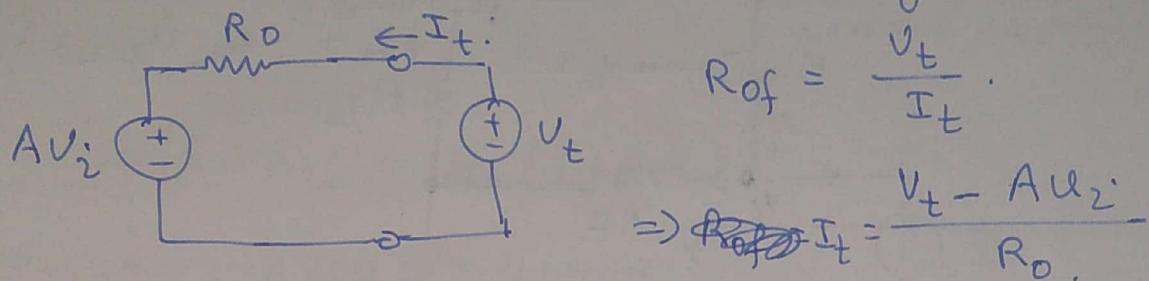In order to compute  $R_{of}$  apply  $V_t$  at the output port and short  $V_s$ . i.e., make  $V_s = 0$ . Thus, at the output side we will have something like this,



Since,  $V_s = 0 \Rightarrow V_2 = -\beta V_o = -\beta V_t$ , resulting in

$$I_t = \frac{V_t + A\beta V_t}{R_o}$$


$$\Rightarrow \frac{V_t}{I_t} = \frac{R_o}{1 + A\beta}$$

$$\Rightarrow R_{of} = \frac{R_o}{1 + A\beta}$$

which can be generalized to,

$$Z_{of}(s) = \frac{Z_o(s)}{1 + A(s)\beta(s)}$$


### CURRENT AMPLIFIERS:-

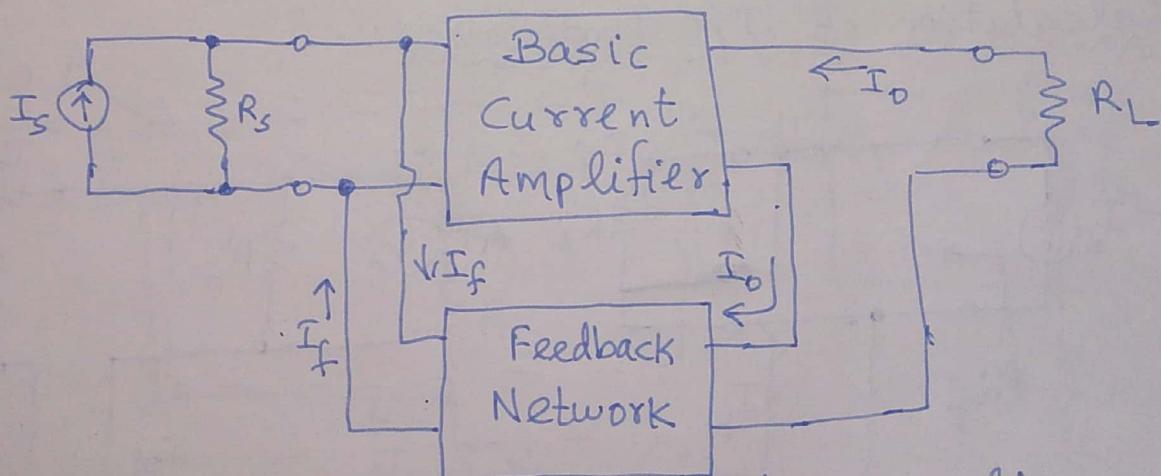

\* Current-mixing shunt & Current-sampling series.

shunt-series feedback.

⑧ Example :-

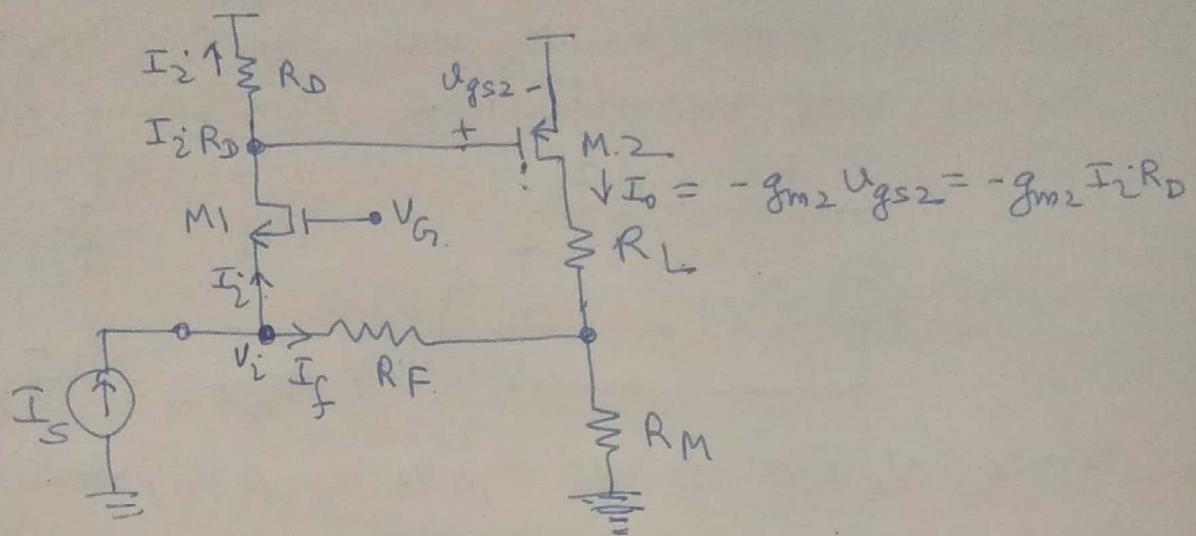


\* Impedance seen at source of  $Q_1$  is very small  
 $\Rightarrow v_i$  is very small and hence can be considered "0". to compute  $I_f$ . Thus,

$$\beta = \frac{I_f}{I_o} \approx -\frac{R_M}{R_f + R_M}$$

Here,  $A = \frac{I_o}{I_i} = -g_m R_D$ . resulting in,

$$\frac{I_o}{I_s} = A_f = -\frac{g_m R_D}{1 + g_m R_D / (1 + \frac{R_f}{R_M})}$$

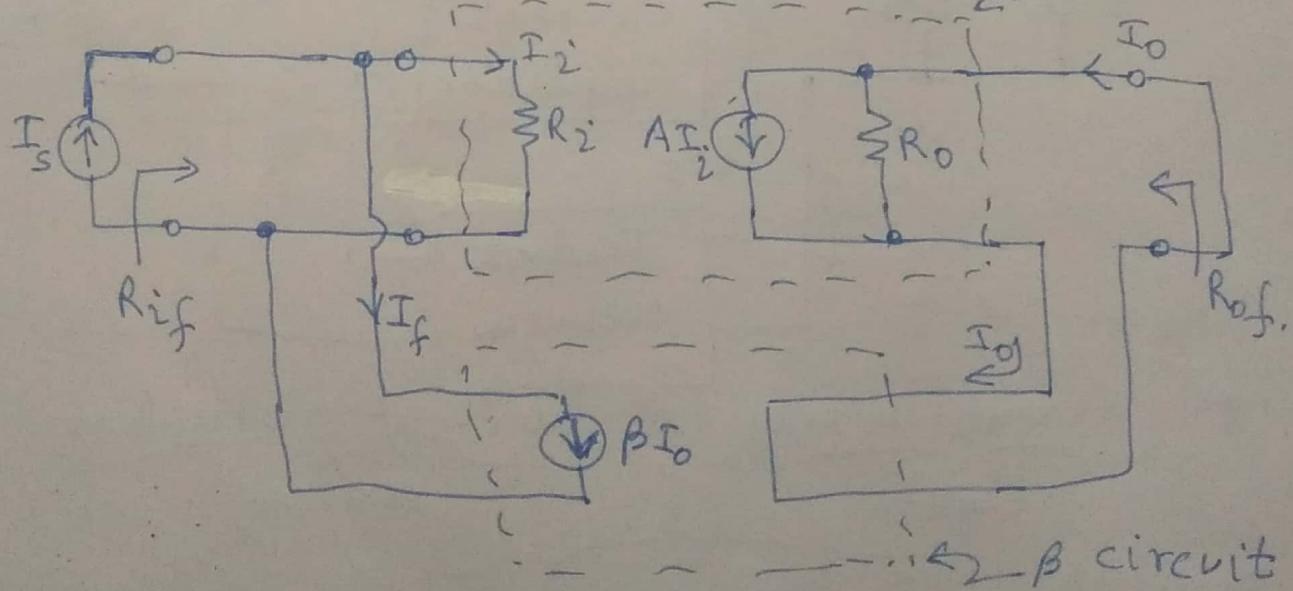Calculation of I/O Impedance :- A circuit.



(9)


$$A_f = \frac{I_o}{I_s} = \frac{A}{1+A\beta}$$

and hence,  $R_{if} = \frac{R_2}{1+A\beta}$

and  $R_{of} = R_o(1+A\beta)$ .


- \* Source & load resistances have been absorbed in A-circuit.
- \*  $\beta$  network does not load the A-circuit  $\Rightarrow$  it samples the short-circuit current.

### TRANSCONDUCTANCE AMPLIFIER:-

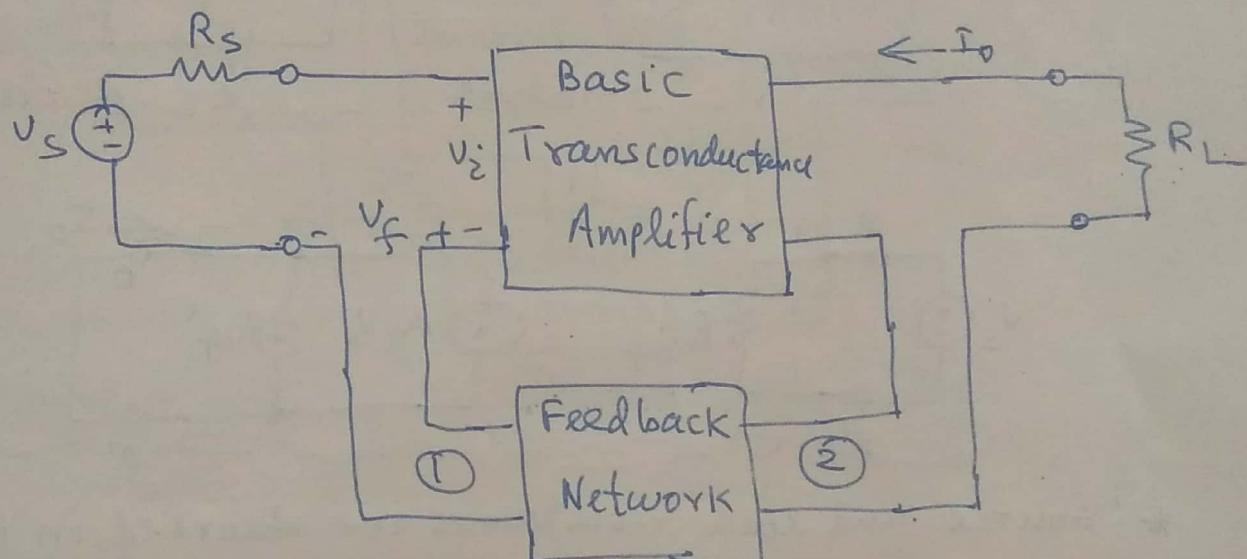

\* Voltage-Mixing & Current Sampling series.

Example:-


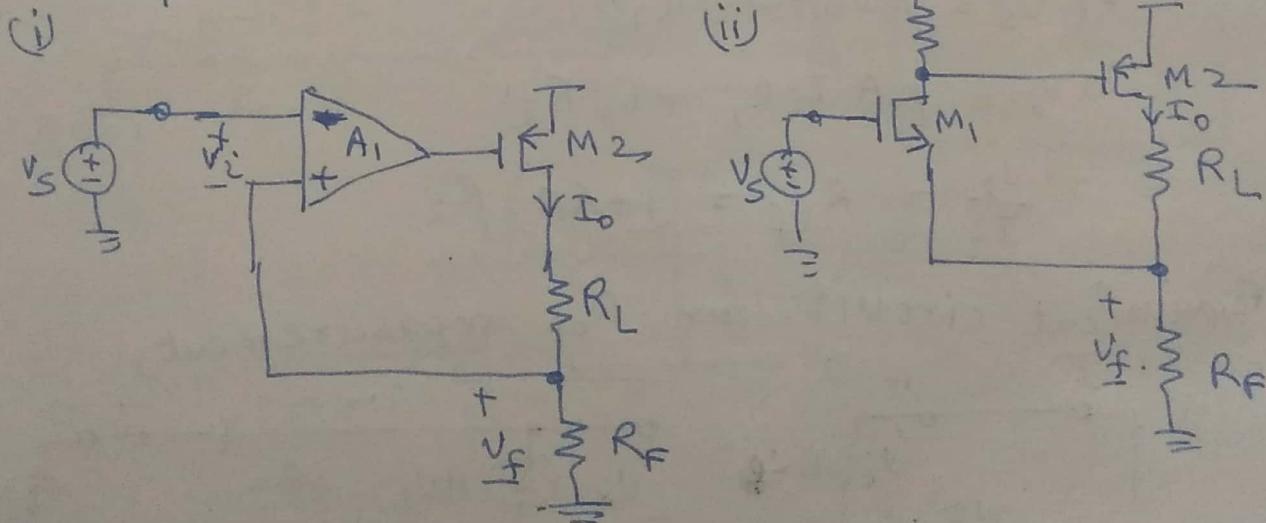


Here,  $\frac{I_o}{v_i} = g_m A_1$ .  
 $\beta = R_F$

and  $A_f = \frac{I_o}{v_s} = \frac{A_1 g_m}{1 + A_1 g_m R_F} \approx \frac{1}{R_F}$ .

(10)

COMPUTE THE I/O IMPEDANCE:-

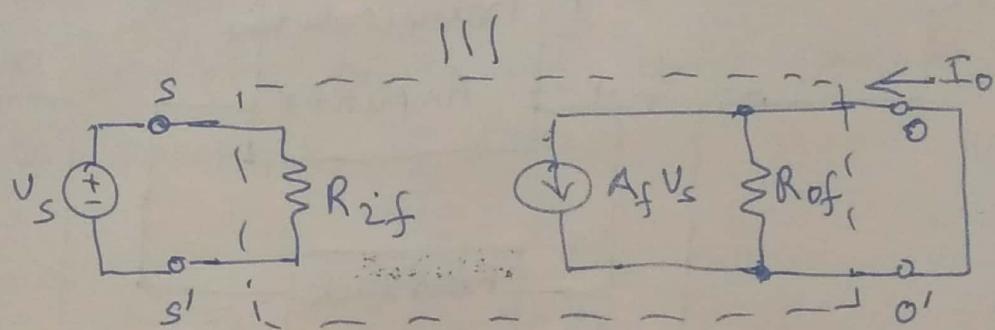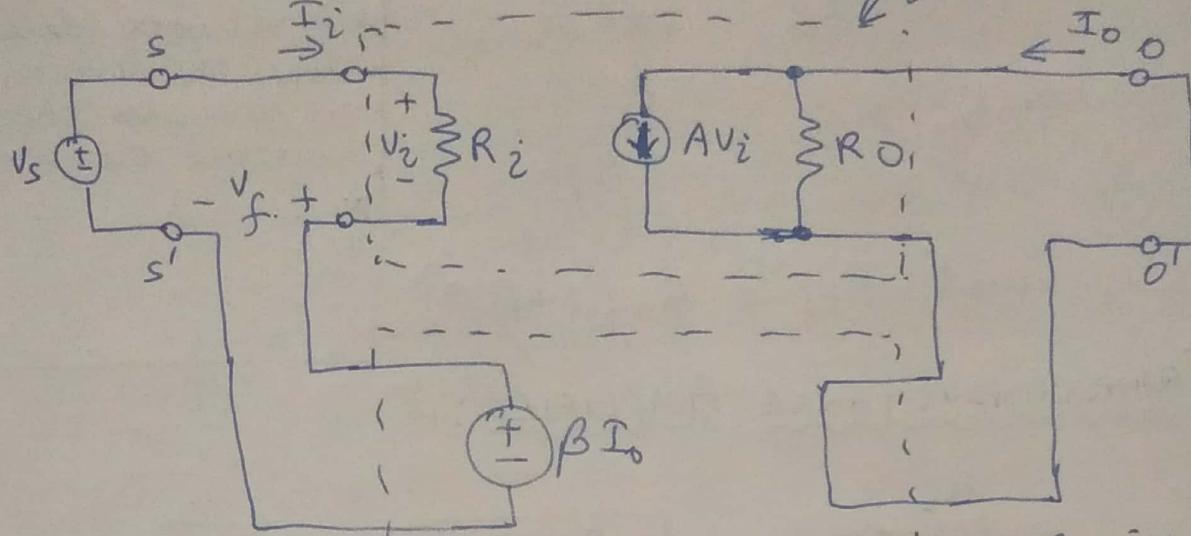

\* source and load resistances are absorbed in the ~~source~~ A-circuit.

\*  $A_f$  is short circuit transconductance.


$$\text{Now, } V_s = V_f + V_i$$

$$\Rightarrow V_s = \beta I_o + I_i R_i$$

$$\Rightarrow V_s = \beta A I_i R_i + I_i R_i$$

$$\Rightarrow \frac{V_s}{I_i} = R_{if} = (1 + \beta A) R_i$$

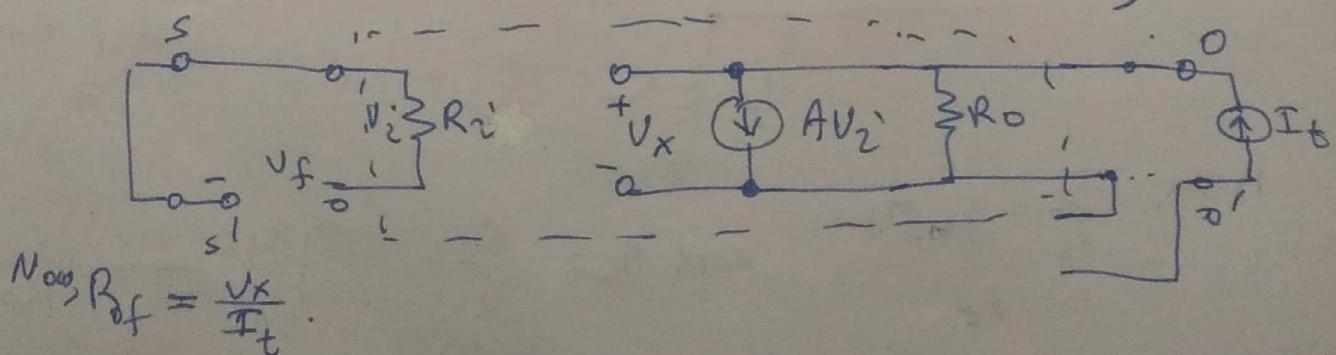
Equivalent circuit for  $R_{of}$  measurement,



(11)

Here,  $V_Z = -V_f = -\beta I_D = \beta I_2$ . Thus,  
 $V_x = (I_t - A V_Z) R_o = I_t (1 + A\beta) R_o$ .  
 $\Rightarrow \frac{V_x}{I_t} = R_o (1 + A\beta)$ .


### TRANSRESISTANCE AMPLIFIER:-

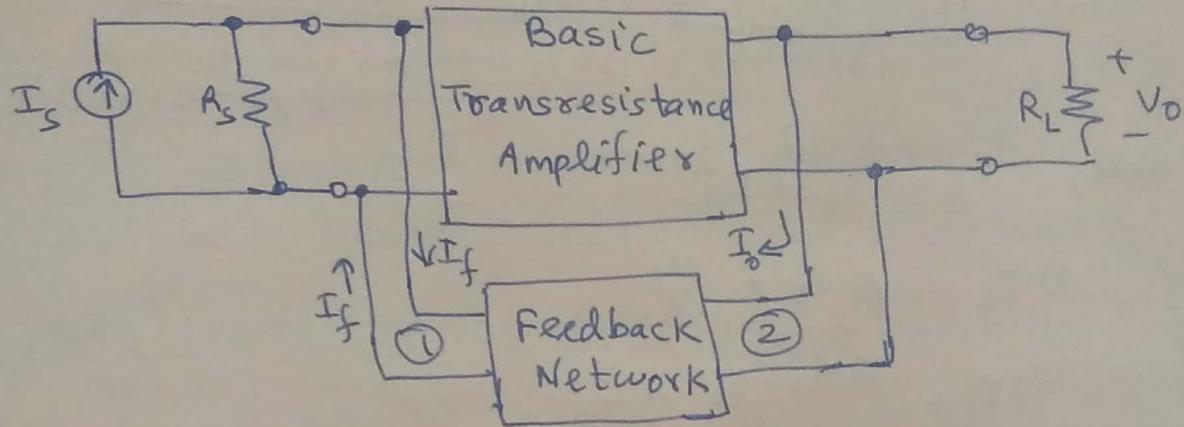


\* Current-mixing & VOLTAGE sampling.  
 shunt shunt.

Example:-


(i)

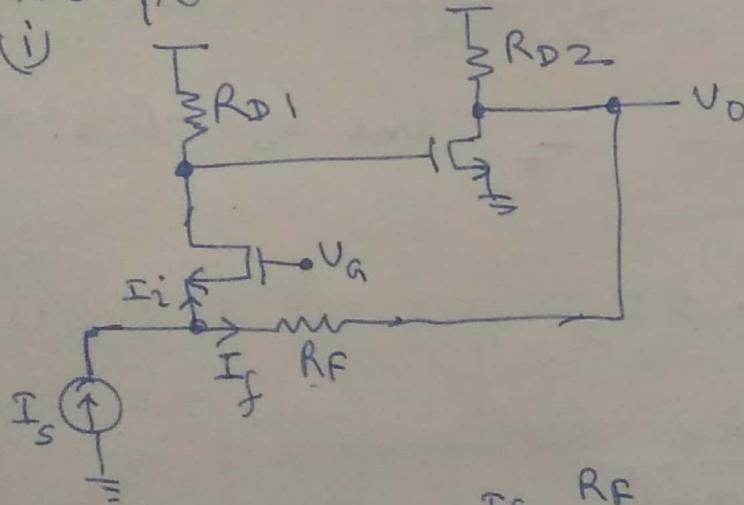


(ii)

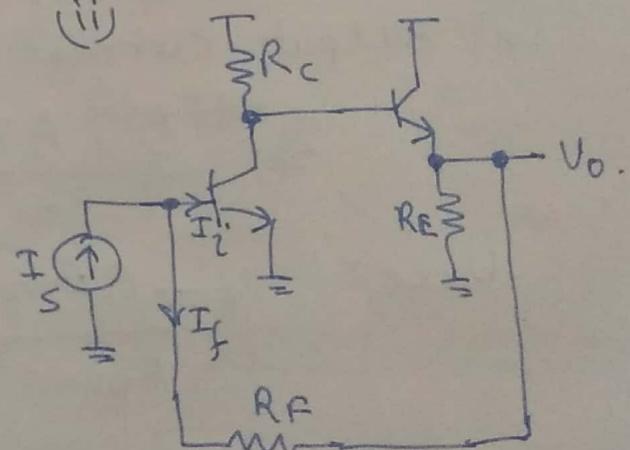

(iii)

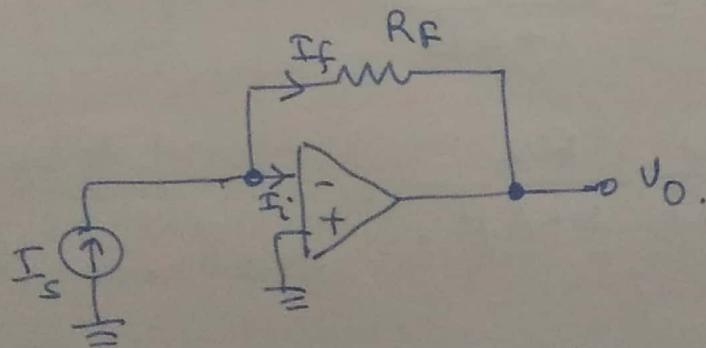

(12) COMPUTE I/O Impedance:-

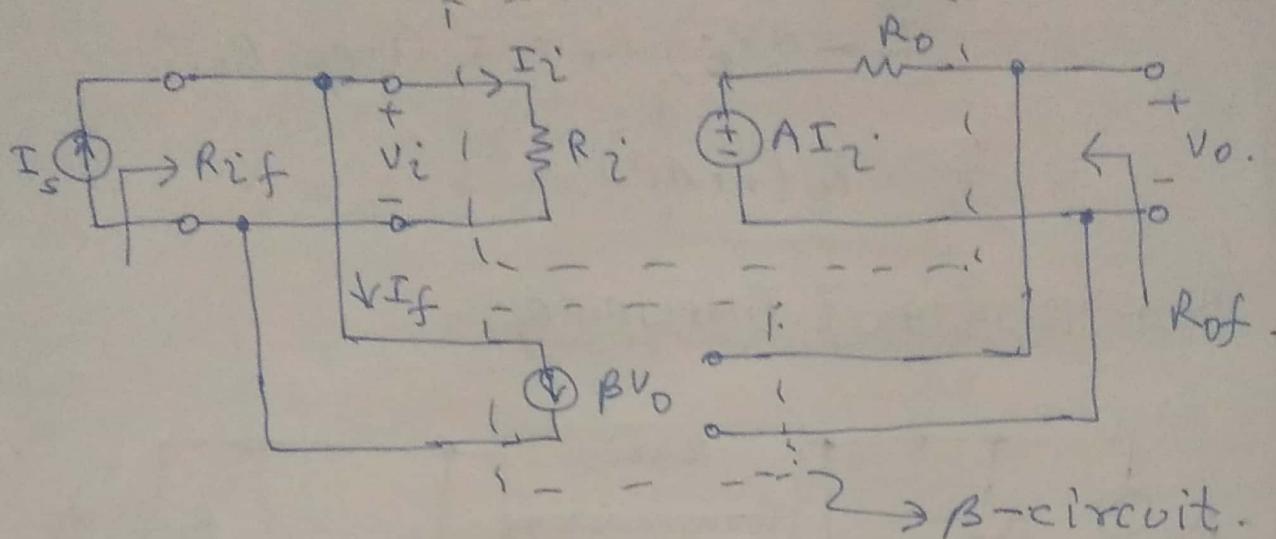

$$\text{Note, } I_s = I_f + I_i$$

$$\Rightarrow I_s = \beta V_o + \frac{V_i}{R_i}$$

$$\Rightarrow I_s = \beta A_i \frac{V_i}{R_i} + \frac{V_i}{R_i}$$

$$\Rightarrow \frac{V_i}{I_s} = \frac{R_i}{1+A\beta} = R_{if}.$$

To compute  $R_{of}$  open  $I_s$  and apply  $V_t$  at output.  
Let output current be  $I_t$ . Thus,

$$\frac{V_t - A I_2}{R_o} = I_t \quad \text{and } I_2 = -\beta V_o = -\beta V_t.$$

$$\text{Hence, } \frac{V_t + A\beta V_t}{R_o} = I_t.$$

$$\Rightarrow \frac{V_t}{I_t} = \frac{R_o}{1+A\beta}$$

$$\Rightarrow R_{of} = \frac{R_o}{1+A\beta}$$

## SUMMARY:-

### \* VOLTAGE AMPLIFIER :-

- ⇒ series - shunt feedback.
- ⇒ Voltage - voltage feedback.  
sense return.

### \* CURRENT AMPLIFIER :-

- ⇒ shunt-series feedback
- ⇒ current - current feedback.  
sense return.



### \* TRANSCONDUCTANCE AMPLIFIER :-

- ⇒ series-series feedback
- ⇒ current - voltage feedback.  
sense return.



### \* TRANSRESISTANCE AMPLIFIER :-

- ⇒ shunt-shunt feedback.
- ⇒ voltage-current feedback.  
sense return.
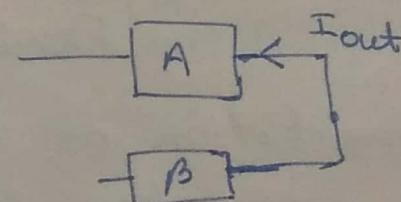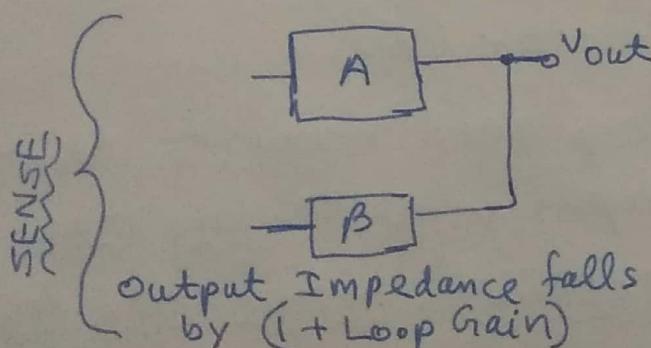
## EFFECT OF FEEDBACK ON INPUT AND OUTPUT IMPEDANCE



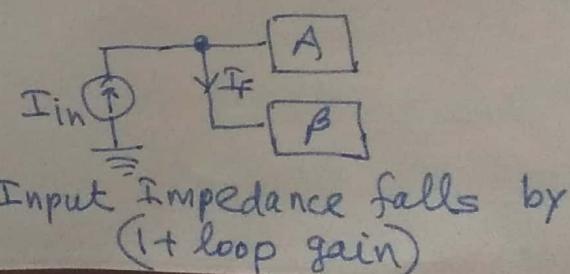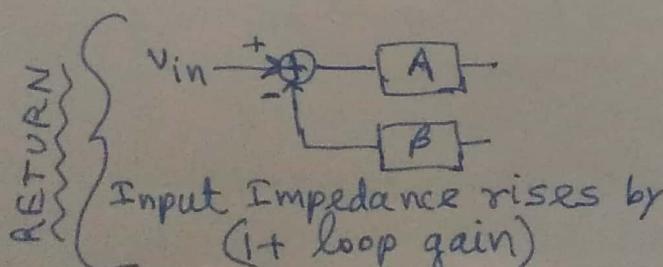
Output Impedance rises by  $(1 + \text{loop gain})$ .



(14)
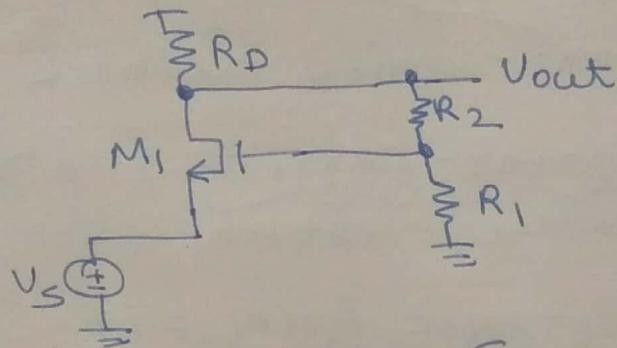
## LOADING EFFECT :-

- \* Till now we have assumed that the I/O impedance of feedback-network does not affect the forward amplifier.
- \* However this is not the case.
- \* For example in the following figure :-




we have assumed that  $(R_2 + R_1) \gg R_D$  so as to not load the forward amplifier comprising of  $M_1$  and  $R_D$ .

If  $(R_2 + R_1) \nparallel R_D$  then the gain of the forward amplifier will reduce from  $g_{m1} R_D$  to  $g_{m1} [R_D \parallel (R_1 + R_2)]$

- \* Computation of the closed-loop gain requires that we compute the following things:-
  - (i) Open-loop gain ( $A$ )
  - (ii) Feedback-factor ( $\beta$ ).
- \* Computation of open-loop gain requires that we break the loop properly  $\Rightarrow$  taking the loading effect into account. break the loop


RULES FOR BREAKING THE Loop:- We will illustrate this using signal-flow graph.

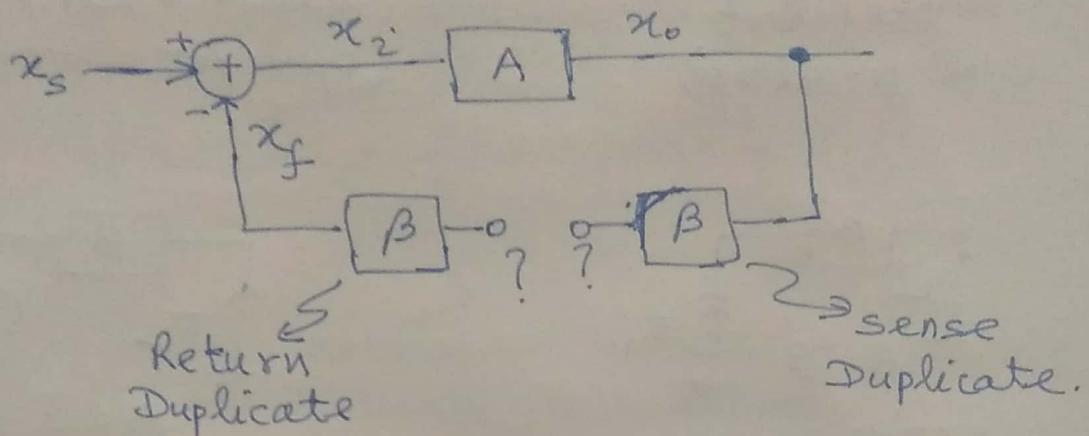- \* The loop is broken by duplicating the feedback network at both the input and the output of the overall system as shown below:-




- \* But, what do you do with the output port of  $\beta$ -network in the sense duplicate and the input port of the  $\beta$ -network in the return duplicate.


This depends on kind of feedback.

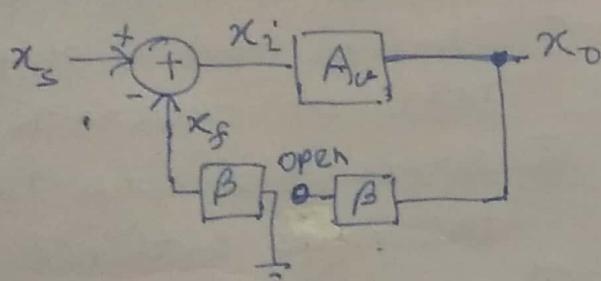


series - shunt  
(voltage - voltage)

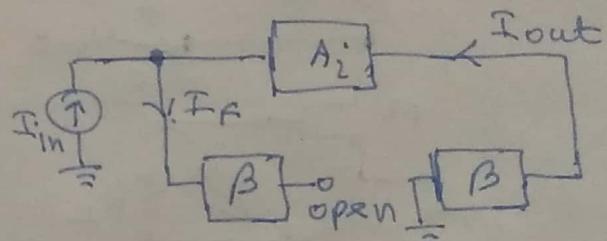

shunt - series  
(current - current)

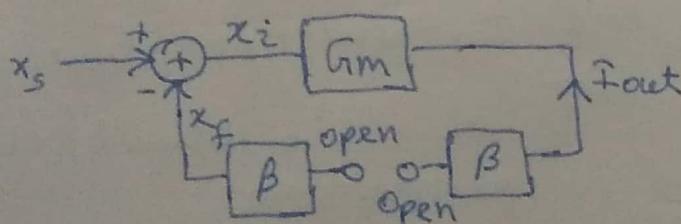


series - series  
(current - voltage)

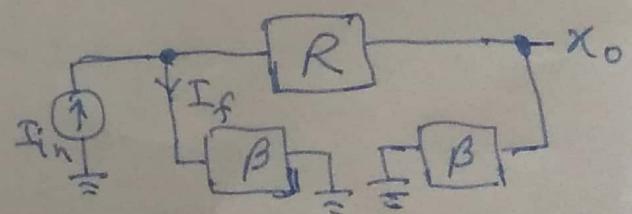

shunt - shunt  
(voltage - current)


(16)
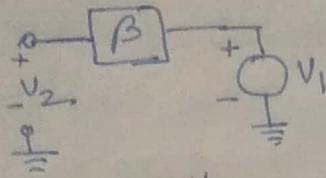
## COMPUTATION OF FEEDBACK FACTOR ( $\beta$ ):-




$$\beta = \frac{V_2}{V_1}$$

series-shunt  
(Voltage-voltage)

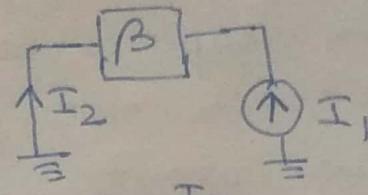


$$\beta = \frac{I_2}{I_1}$$

shunt-series  
(current-current)

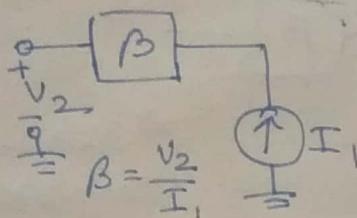


series-series  
(current-voltage)

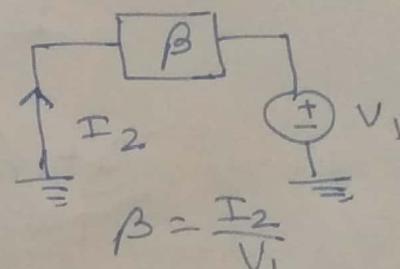

shunt-shunt  
(voltage-current)

### Examples:-

#### ① SERIES-SHUNT:-

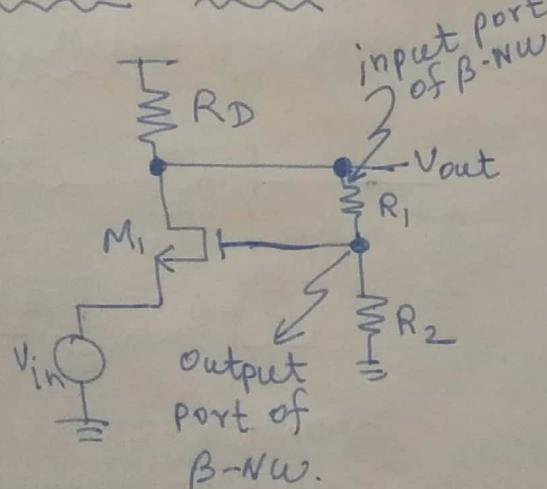

#### steps:-

- ① Identify feedback network.
- ② Identify forward amplifier.
- ③ Identify input & output port of feedback network.
- ④ Break the loop following the rules outlined earlier.
- ⑤ Obtain  $\beta$  following the rules given earlier.
- ⑥ Obtain open-loop gain
- ⑦ Calculate closed-loop parameters.


(17)

Step-1 :- Feedback-network comprises of  $R_1$  and  $R_2$ .


Step-2 :- Ideal forward amplifier comprises of  $M_1$  and  $R_D$ .

Step-3 :- I/O port of  $\beta$ -network is annotated.

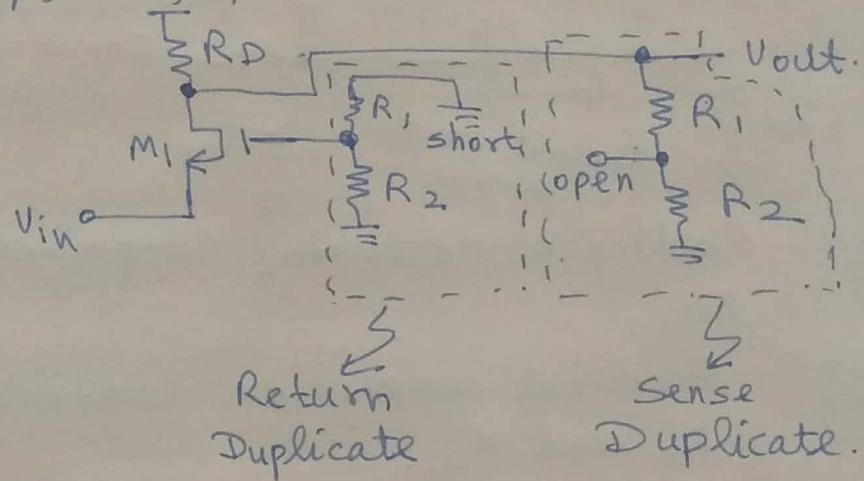Step-4 :- Breaking the loop properly, i.e. at output port of  $\beta$ -nw.



Step-5 :- Obtaining  $\beta$ .

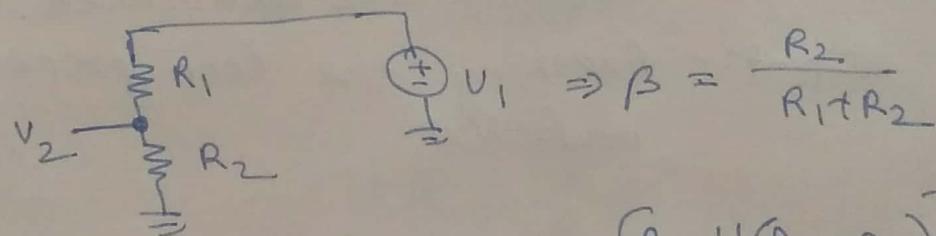

Step-6 :- Open-loop gain,  $A_u = g_{m1} [R_D \parallel (R_1 + R_2)]$ .

$$\text{Step-7} :- A_{u, \text{closed}} = \frac{g_{m1} [R_D \parallel (R_1 + R_2)]}{1 + \frac{R_2}{R_1 + R_2} g_{m1} [R_D \parallel (R_1 + R_2)]}$$

$$R_{in, \text{open}} = \frac{1}{g_{m1}} \quad (\lambda=0)$$


$$R_{out, \text{open}} = R_D \parallel (R_1 + R_2) \quad (\lambda=0)$$

$$\therefore R_{in, \text{closed}} = \frac{1}{g_{m1}} \left[ 1 + \frac{R_2}{R_1 + R_2} g_{m1} [R_D \parallel (R_1 + R_2)] \right]$$

$$R_{out, \text{closed}} = \frac{[R_D \parallel (R_1 + R_2)]}{1 + \frac{R_2}{R_1 + R_2} g_{m1} [R_D \parallel (R_1 + R_2)]}$$

(18)

② SHUNT - SERIES FEEDBACK :-

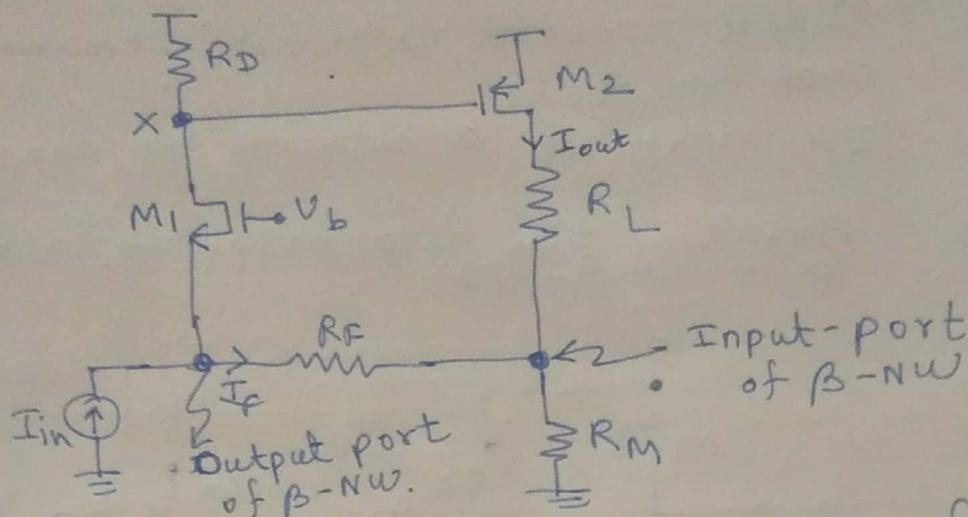


Step-1:- Feedback network comprises of  $R_F$  and  $R_M$ .


Step-2:- Forward amplifier consists of  $M_1$ ,  ~~$M_2$~~ ,  $R_D$  and  $M_2$ .

Step-3:- The input and output port of  $\beta$ -network are annotated.

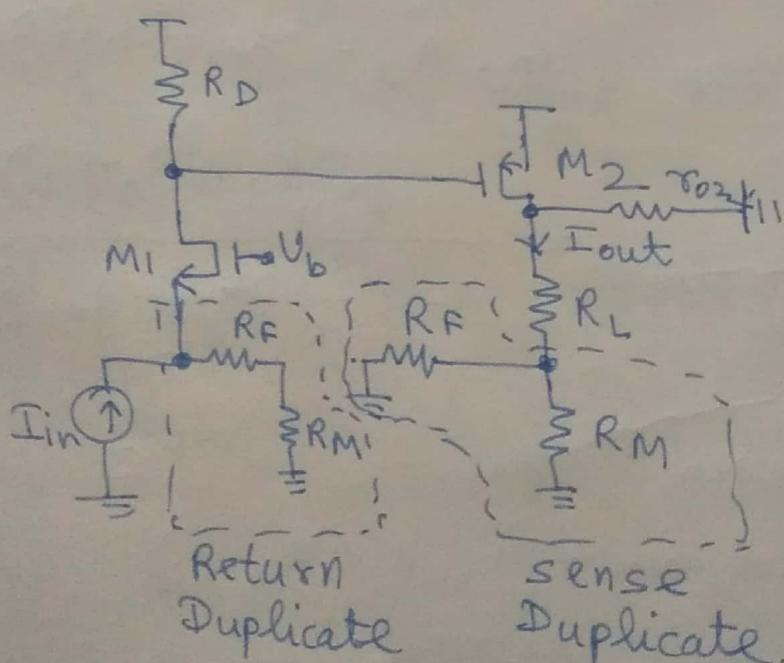Step-4:- Breaking the loop properly, i.e., at o/p of  $\beta$ -NW.



Step - 5 :- Obtaining  $\beta$ .

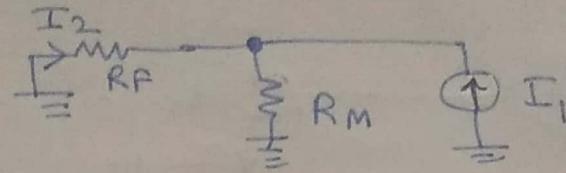

$$\beta = -\frac{R_M}{R_F + R_M}$$

Step - 6 :- Obtain open-loop parameters.

$$A_{i,open} = \frac{(R_F + R_M) R_D}{R_F + R_M + \frac{1}{g_{m1}}} \cdot \frac{-g_{m2} r_{o2}}{r_{o2} + R_L + (R_M || R_F)}$$

$$R_{in,open} = \frac{1}{g_{m1}} || (R_F + R_M)$$

$$R_{out,open} = r_{o2} + (R_F || R_M)$$

Step - 7 :-


$$A_{i,closed} = \frac{A_{i,open}}{1 + A_{i,open} \beta}$$

$$R_{in,closed} = \frac{R_{in,open}}{1 + A_{i,open} \beta}$$

$$R_{out,closed} = R_{out,open} (1 + A_{i,open} \beta)$$

(20)

③ SERIES-SERIES FEEDBACK:-

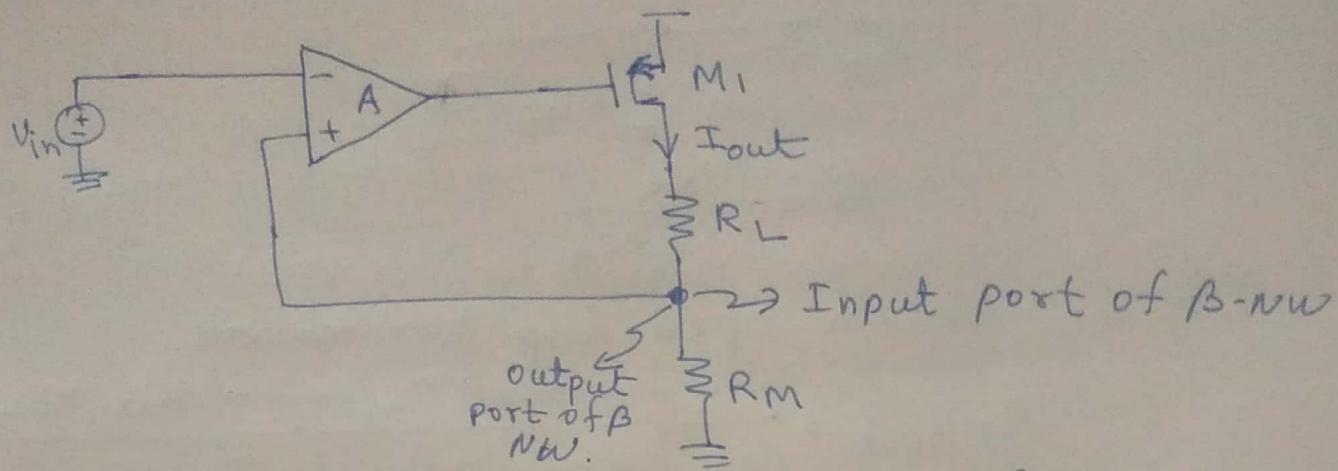


Step-1:- Feedback network comprises of  $R_M$ .


Step-2:- Feedforward network comprises of  $A$  and  $M_1$ .

Step-3:- I/O port of  $\beta$ -NW are annotated.

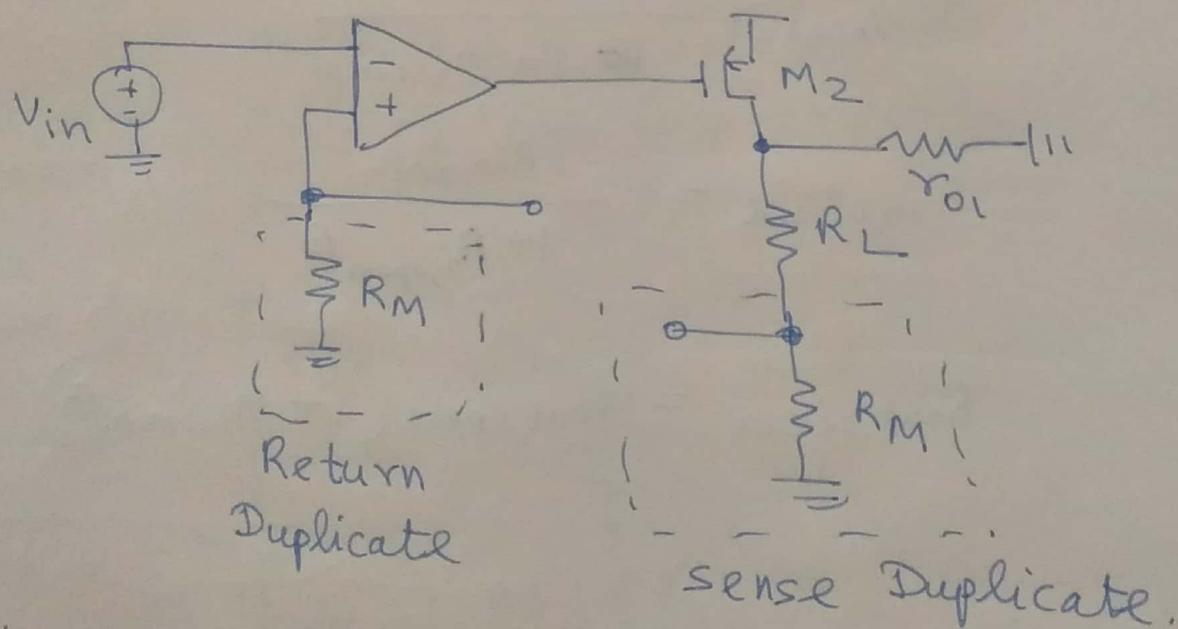Step-4:- Breaking the loop properly, i.e., at output port of  $\beta$ -NW.



Step-5:- Obtaining  $\beta$

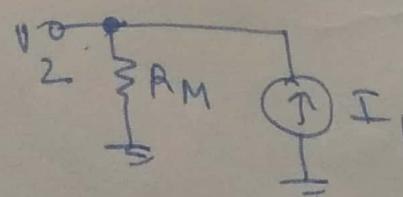

$$\beta = R_M.$$

Step-6:- Obtain open loop parameters.

$$G_{m,\text{open}} = \frac{g_{m2} A_1 \cdot r_{o1}}{r_{o1} + R_L + R_M}$$

$$R_{in,\text{open}} = \infty$$

$$R_{out,\text{open}} = (R_M + r_{o1})$$


Step-7:-

$$G_{m,\text{closed}} = \frac{G_{m,\text{open}}}{1 + G_{m,\text{open}}\beta}$$

$$R_{in,\text{closed}} = \infty$$

$$R_{out,\text{open}} = (r_{o1} + R_M) (1 + R_M G_{m,\text{open}})$$

#### ④ SHUNT-SHUNT FEEDBACK :-

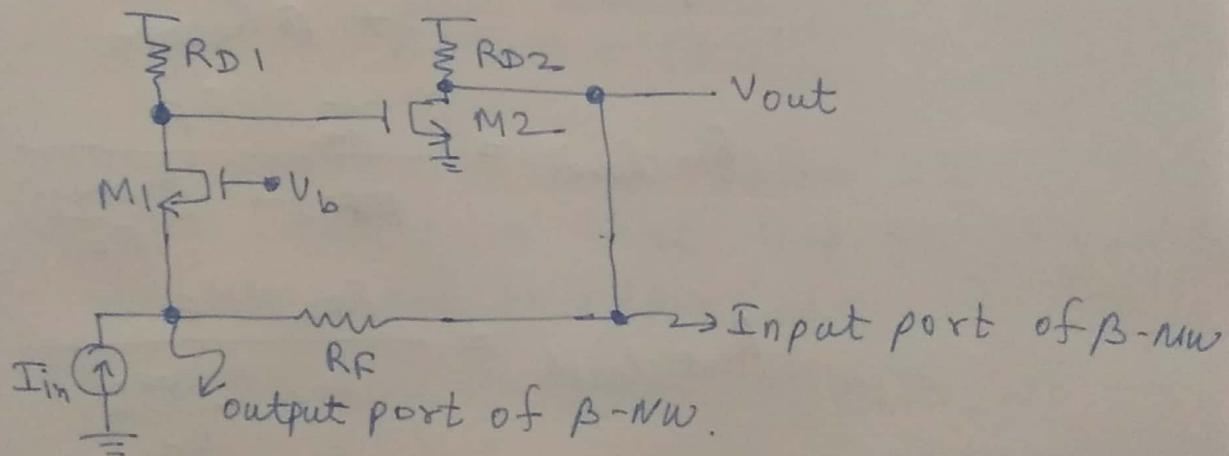


Step-1:- Feedback network comprises of  $R_F$ .


Step-2:- Forward amplifier comprises of  $M_1$ ,  $R_{D1}$ ,  $M_2$  and  $R_{D2}$ .

Step-3:- I/O port of  $\beta$ -NW is annotated.

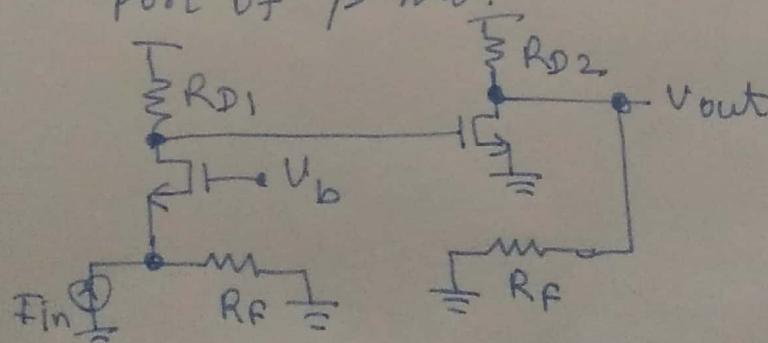Step-4:- Break the loop properly, i.e. at the o/p port of  $\beta$ -NW.



(22)

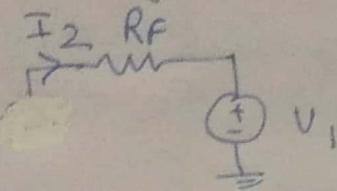Step - 5 :- obtaining  $\beta$ .

$$\beta = -\frac{1}{R_F}$$

Step - 6 :- Obtain open-loop parameters.

$$R_{o,open} = \frac{R_F R_{D1}}{R_F + \frac{1}{g_m 1}} \left[ -g_m 2 (R_{D2} || R_F) \right]$$

$$R_{in,open} = \frac{L}{g_m 1} || R_F$$

$$R_{out,open} = R_{D2} || R_F$$


Step - 7 :-

$$R_{o,closed} = \frac{R_{o,open}}{1 + \beta R_{o,open}}$$

$$R_{in,closed} = \frac{\frac{1}{g_m 1} || R_F}{\cancel{1} - \frac{R_{o,open}}{R_F}}$$

$$R_{out,closed} = \frac{R_{D2} || R_F}{1 - \frac{R_{o,open}}{R_F}}$$

## PROBLEM OF INSTABILITY:-

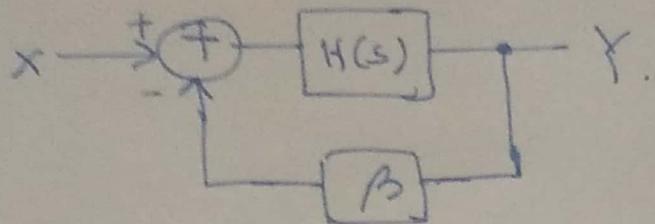

$$\frac{Y}{X}(s) = \frac{H(s)}{1 + \beta H(s)}$$

If  $\beta H(s)$  or loop gain has a value of  $-1$  at particular frequency  $\omega_1$ , then  $\frac{Y}{X}(s) \rightarrow \infty$  resulting in oscillation.



## Barkhausen's Criteria for Oscillation:-

$$|\beta H(j\omega_1)| = 1$$

$$\angle \beta H(j\omega_1) = -180^\circ$$



\* So to make the closed-loop system stable we have to make sure that loop-gain  $< 1$  when the loop-phase is  $180^\circ$ .

## Onset of Oscillation in Slow Motion:-

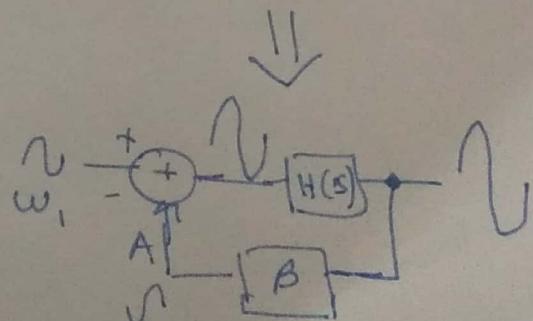
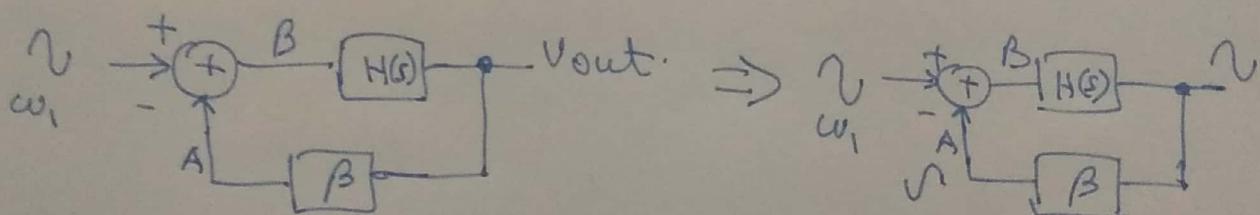


## 24 BODE PLOT REVIEW



① 1-Pole System:-

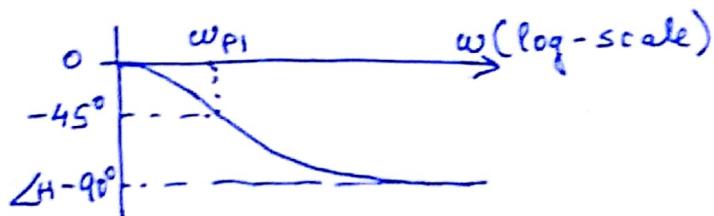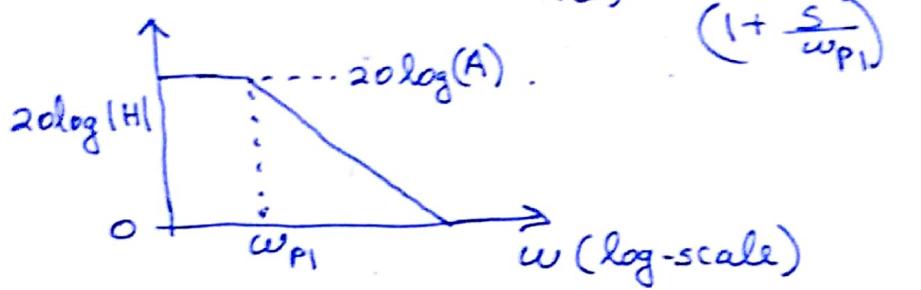

② 2-Pole System:-

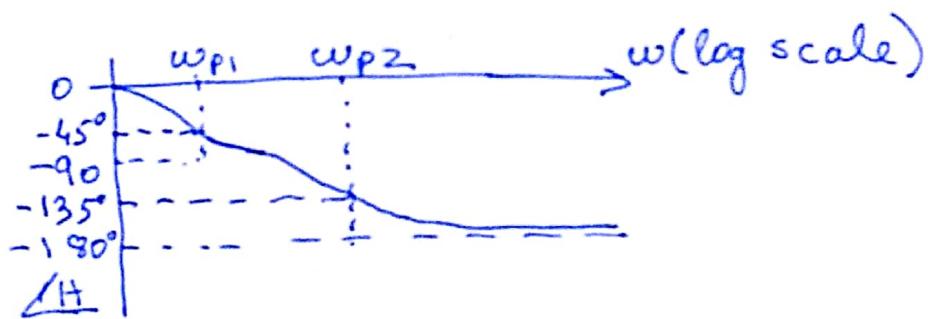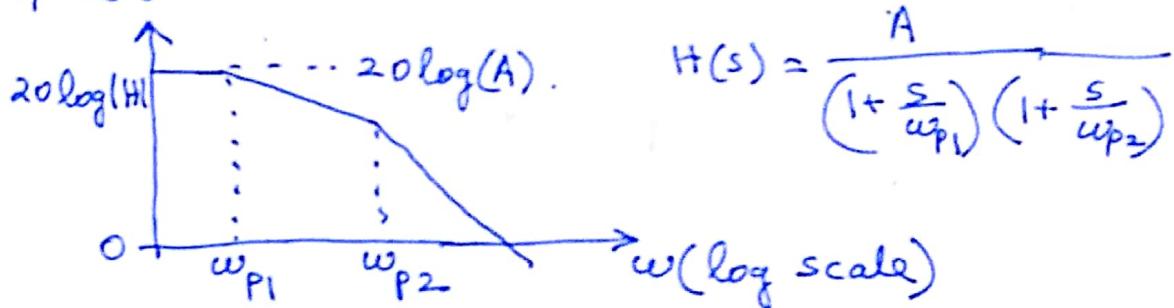

③ 3-pole System:-

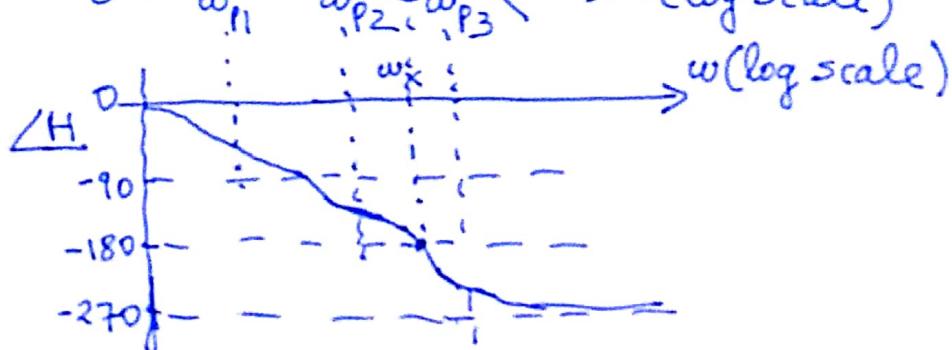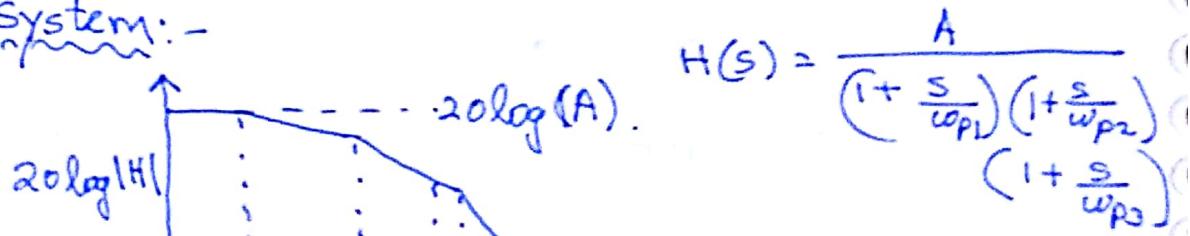

- \* As can be clearly seen for a 3-pole system the phase hits  $180^\circ$  at  $\omega_x$  and gain  $> 1$ .
- \* So, if we ~~put~~ put feedback around that system there could be oscillation.
- \* In a ~~feedback~~ feedback system as mentioned earlier if the following condition is satisfied then oscillation happens at  $\omega_1$ .



$$|\beta H(j\omega_1)| = 1$$

$$\underline{\angle \beta H(j\omega_1)} = -180^\circ$$

- \* If  $|\beta H(j\omega)| < 1$  then the output cannot grow indefinitely.

### STABILITY CONDITION:-

- \* If  $|\beta H(j\omega_1)| > 1$  and  $\underline{\angle \beta H(j\omega_1)} = -180^\circ$  the negative feedback system oscillates.
- \* To avoid this we have to make sure that both the gain and phase conditions do not get satisfied at any ~~any~~ frequency.

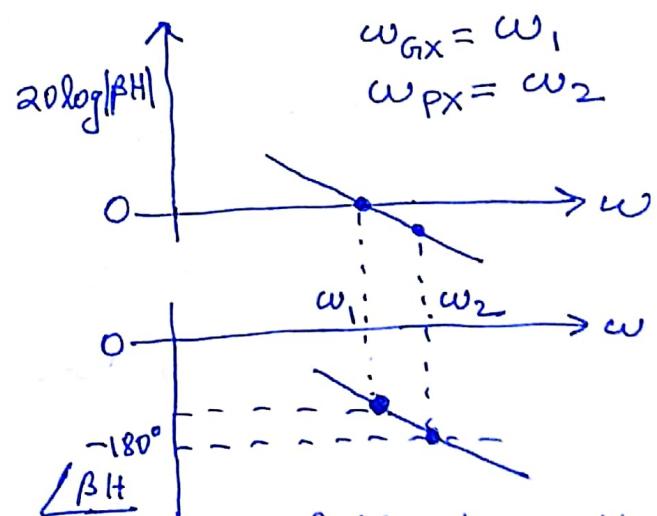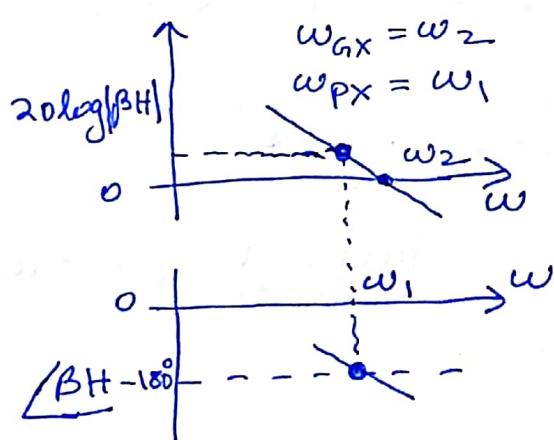


- \* Frequency at which the loop-gain falls to unity is called gain crossover frequency,  $\omega_{GX}$ .
- \* Frequency at which phase reaches  $-180^\circ$  is called phase crossover frequency,  $\omega_{PX}$ .

- \* In the above example  $\omega_{ax}$  and  $\omega_{px}$  are annotated. Based on that we conclude that a negative-feedback system would be stable if,

$$\omega_{ax} < \omega_{px}.$$

and is called stability criteria based on Bode-Plot.  $\Rightarrow$  Guarantee that "Barkhausen's Criteria" is not satisfied at any frequency.

Example:-

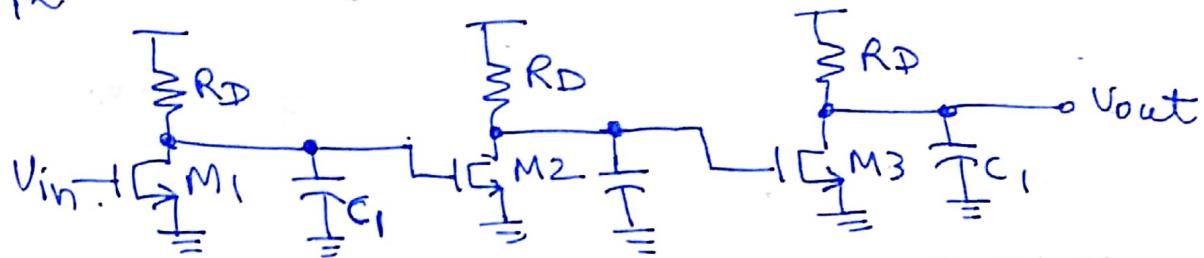

If we put negative feedback with  $\beta = 1$  in the above circuit derive the condition of stability. Assume  $\gamma = 0$ ,  $M_1, M_2$  and  $M_3$  are identical and ignore parasitic capacitances.

Ans:-


$$\text{Low frequency gain} = (g_m R_D)^3.$$

$$\text{Each stage has a pole at } \omega_p = (R_D C_1)^{-1}.$$

$$\text{Thus, } H(s) = \frac{(g_m R_D)^3}{\left(1 + \frac{s}{\omega_p}\right)^3}$$

and  $\beta = 1$  ... as given in question.

There loop gain  $= \beta H(s) = H(s)$ .

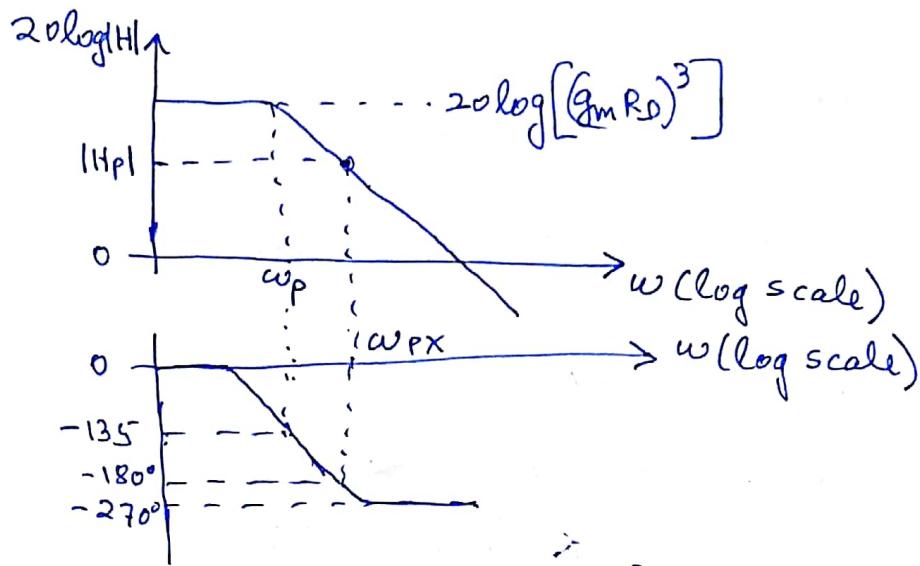

At,  $\omega_{px}$  the phase is  $-180^\circ$ .

Thus,

$$-3 \tan^{-1} \left( \frac{\omega_{px}}{\omega_p} \right) = -180^\circ$$

$$\Rightarrow \omega_{px} = \sqrt{3} \omega_p.$$


At  $\omega_{px}$  the ~~gain~~ loop-gain  $< 1$ . Thus,

$$\frac{(g_m R_D)^3}{\left[ 1 + \left( \frac{\omega_{px}}{\omega_p} \right)^2 \right]^3} < 1$$

$$\Rightarrow g_m R_D < 2.$$

If  $g_m R_D$  exceeds 2 then oscillation can set-in.

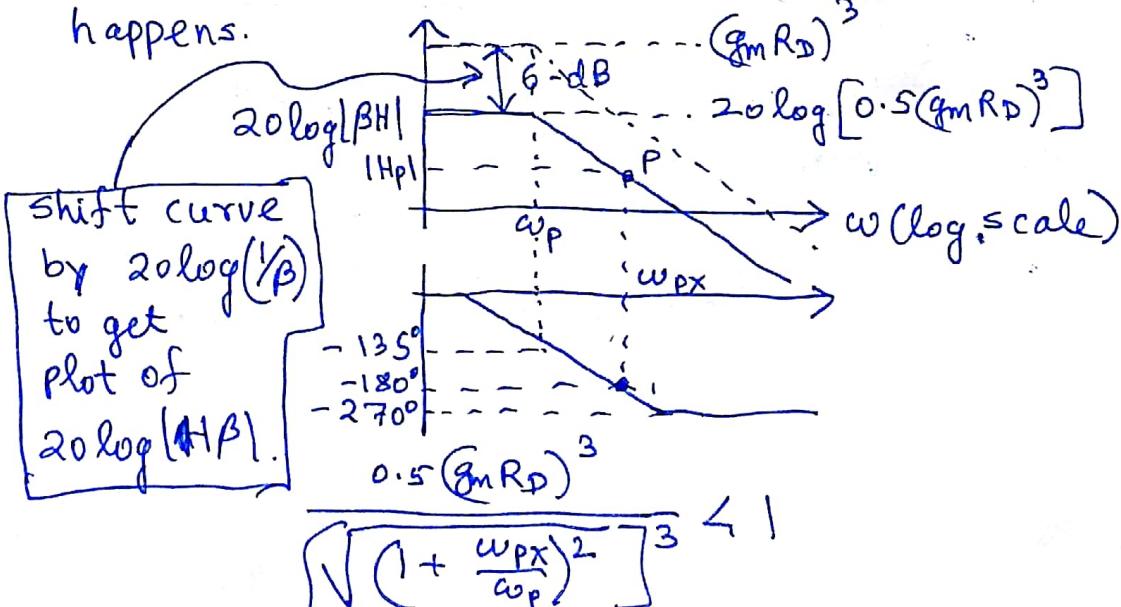\* In the above example if  $\beta = 0.5$  what happens.





(28)

$$\text{Thus, } (gm RD)^3 < \frac{2^3}{0.5}$$




\* Hence, weaker feedback allows greater open-loop gain.
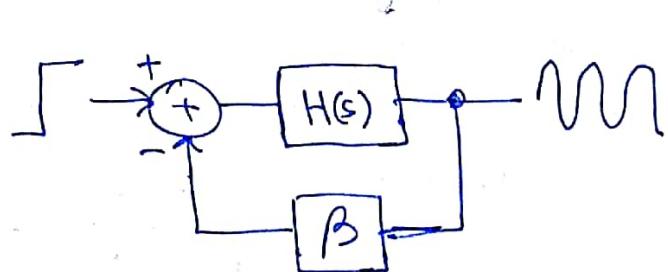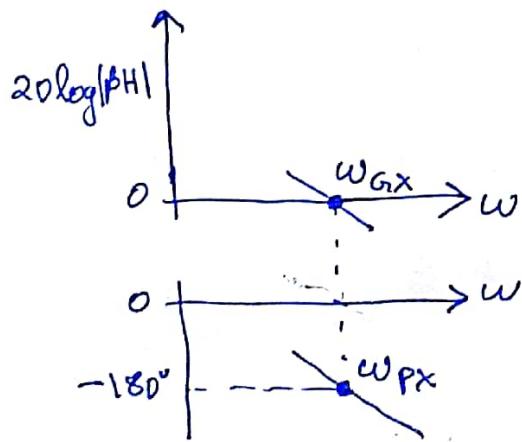
### SOME KEY OBSERVATIONS:-

- ① Feedback factor  $\beta \leq 1$ . with  $\beta=1$  called unity-feedback, i.e., strongest amount of feedback.
- ② ~~Since~~ changing the feedback factor translates the gain plot (Bode) ~~upward~~ down.
- ③ Changing feedback factor does not alter the phase-plot (Bode) much.
- ④ If a system can be made stable with  $\beta=1$ , then the system is guaranteed to be stable for any  $\beta$ .


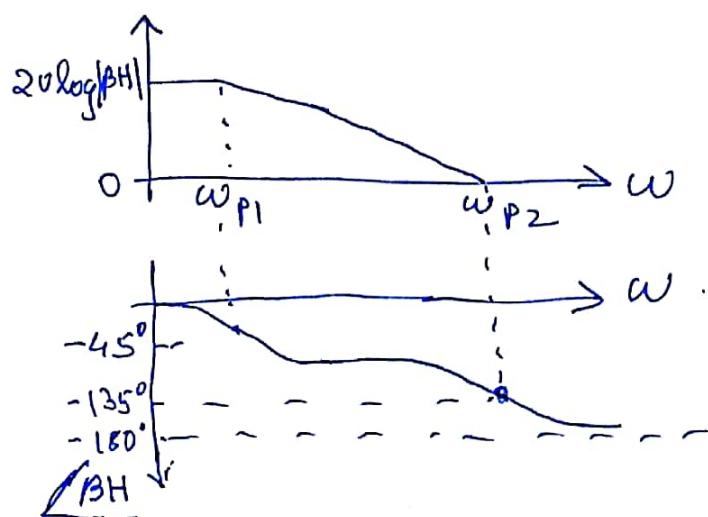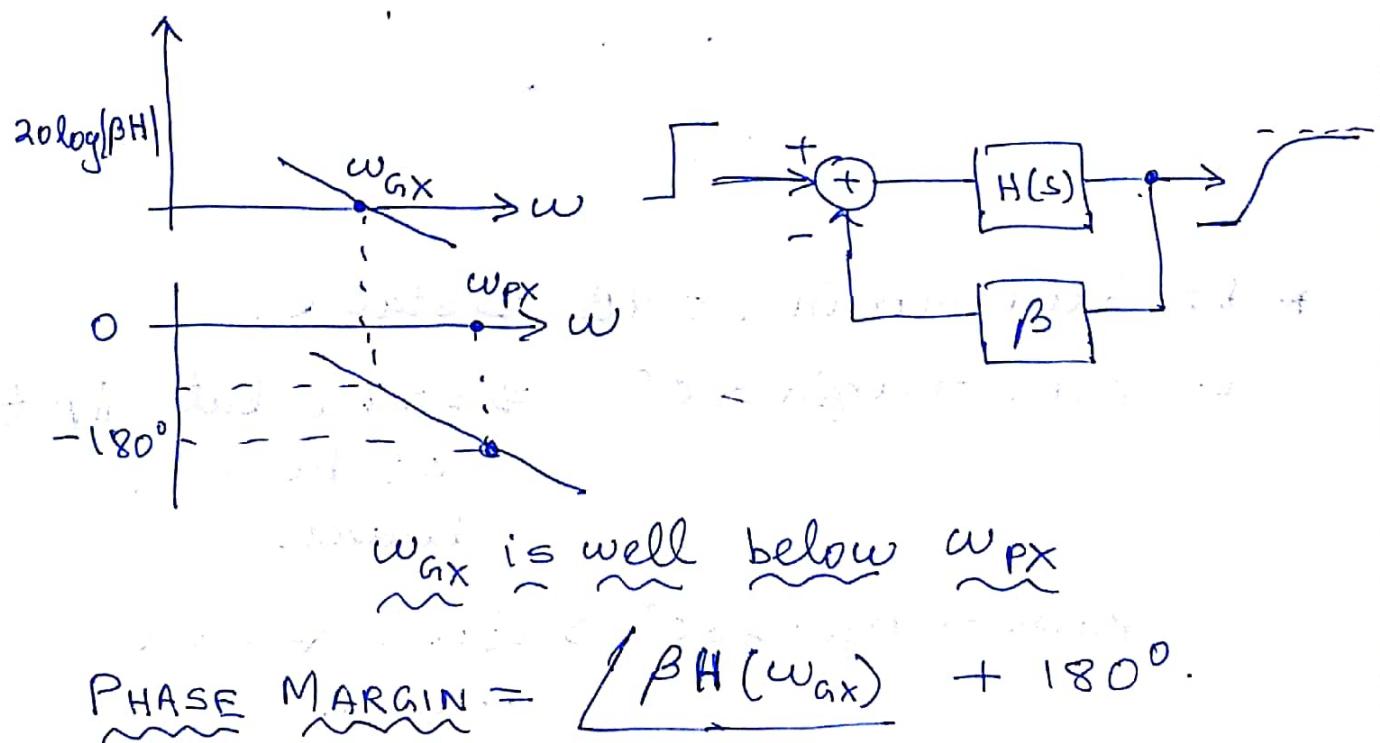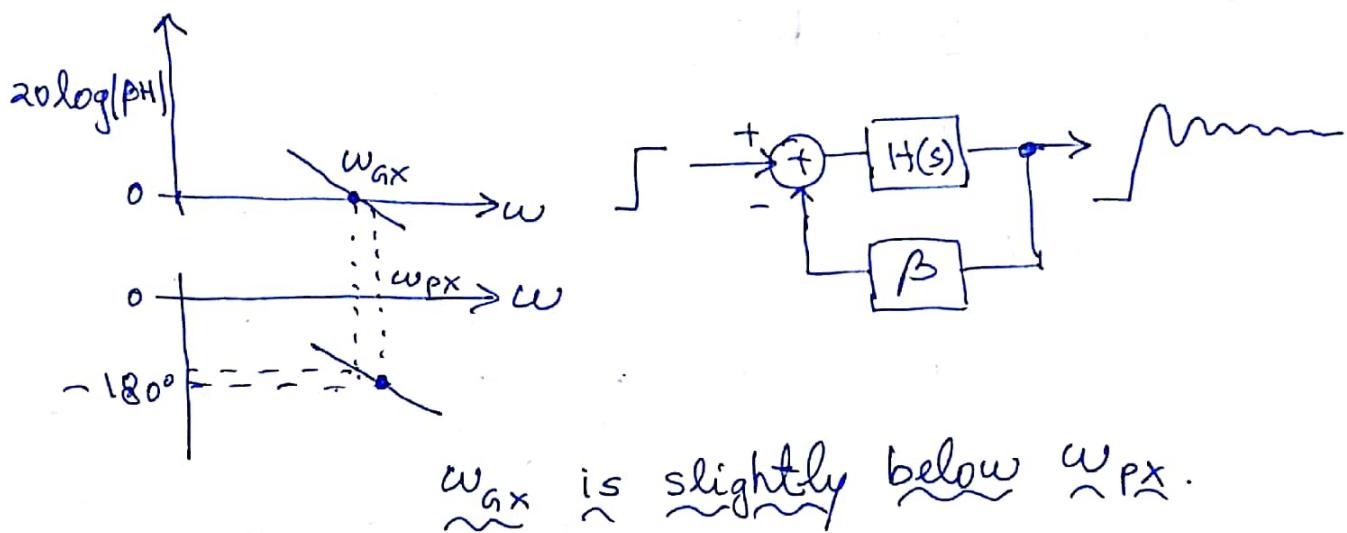
$$\omega_{Gx} = \omega_{Px} \Rightarrow \text{Oscillatory.}$$




$$\text{Phase margin} = 45^\circ.$$

\* For well behaved system typical Phase Margin required is 60°.

(30)

$$\text{GAIN MARGIN} = |\beta H| \omega_{px}$$

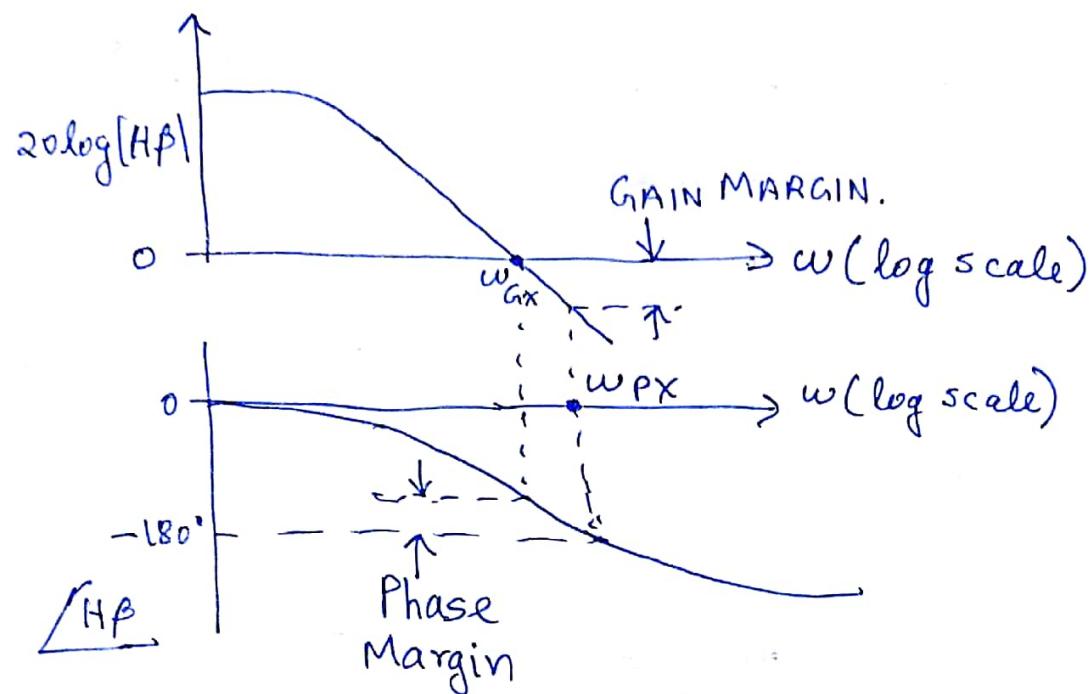

\* If Gain-margin < 0 dB  $\Rightarrow$  stable.

If Phase-margin  $> 0^\circ$   $\Rightarrow$  stable but might not be well behaved.

Phase-margin  $> 60^\circ \Rightarrow$  stable & well behaved.

Example 1 :- One-pole open-loop transfer function is given by,

$$H(s) = \frac{A_0}{1 + \frac{s}{\omega_0}}.$$


What is the phase-margin if  $\beta = 1$ .

Ans:- A single pole system rolls off at a rate of  $-20\text{dB/dec}$  in case of Bode-Gain Plot.


$$\text{DC gain} = 20\log(A_0) \text{ dB.}$$

$\omega_{gx}$  = gain-cross over frequency is  $10^{\frac{\log A_0}{20}}$  decades away from  $\omega_0$ .

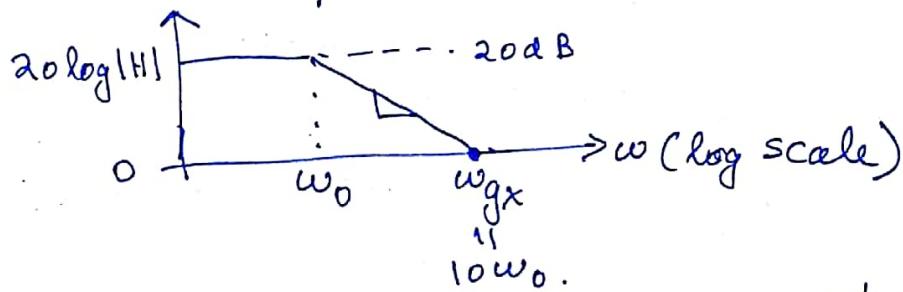For example if  ~~$20\log A_0 = 20\text{dB}$~~  then  $\omega_{gx}$  is 1 decade away from  $\omega_0$  as shown below:-



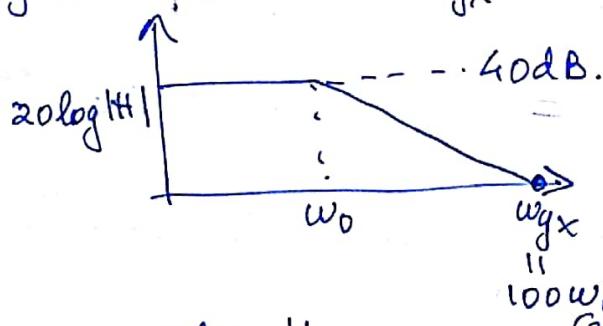If  $20\log A_0 = 40\text{dB}$  then  $\omega_{gx} = 100\omega_0$  as shown below.



If  $20\log A_0 = 30\text{dB}$  then  $\omega_{gx} = 10^{\frac{30-20}{20}}\omega_0 = 31.62\omega_0$ .

Thus, phase at  $\omega_{gx}$  is given by,


$$\angle H(\omega_{gx}) = -\tan^{-1} \left[ 10^{\frac{\log A_0}{20}} \frac{\omega_0}{\omega_{gx}} \right]$$

$$\Rightarrow \angle H(\omega_{gx}) = -\tan^{-1} \left[ 10^{\frac{\log A_0}{20}} \right].$$

Therefore, Phase Margin =  $180^\circ - \tan^{-1} \left[ 10^{\frac{\log A_0}{20}} \right]$ , if  $\beta = 1$ .

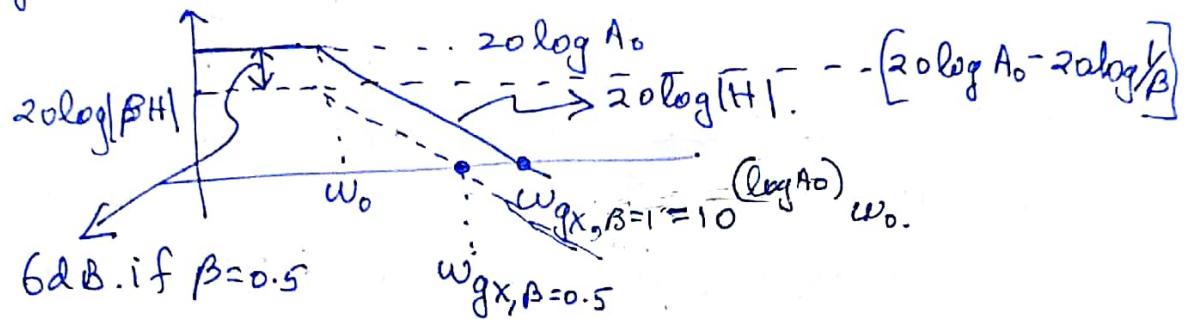(32)

\* What if  $\beta = 0.5$  then the loop gain Bode-plot is going to look as follows:-



$$\text{Now, } \omega_{gX, \beta=1} = 10^{\log A_0} \omega_0.$$

$$\omega_{gX, \beta=0.5} = 10^{\frac{\log A_0 - \log(\beta)}{2}} \omega_0.$$

Hence, for  $\beta = 0.5$  we get,

$$\omega_{gX, \beta=0.5} = 10^{\frac{\log A_0 - 0.3}{2}} \omega_0.$$


$$\Rightarrow \omega_{gX, \beta=0.5} = 0.5 \cdot 10^{\frac{\log A_0}{2}} \omega_0.$$

$$\Rightarrow \omega_{gX, \beta=0.5} = 0.5 \omega_{gX, \beta=1}.$$

$$\therefore \text{Phase Margin} = 180^\circ - \tan^{-1}(0.5 \cdot 10^{\frac{\log A_0}{2}})$$

\* Thus, as feedback factor reduces the phase margin increases.

Example-2:-

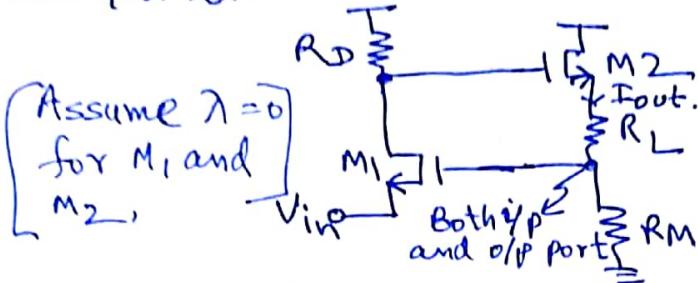

(i) What is the kind of feedback?

(ii) Derive various parameters like  $R_{in, closed}$ ,  $R_{out, closed}$  and  $G_{m, closed}$ .

\* Sensing Current  $\Rightarrow$  series sampling

\* Returning Voltage  $\Rightarrow$  series mixing.


Thus, series-series feedback or current-voltage feedback

Step-1:- Feedback network comprises of  $R_M$ .


Step-2:- Forward amplifier consists of  $M_1$ ,  $R_D$  ~~and~~ and  $M_2$ .

Step-3:- The input and output port of feedback network is annotated.

Step-4:- Break the loop properly.

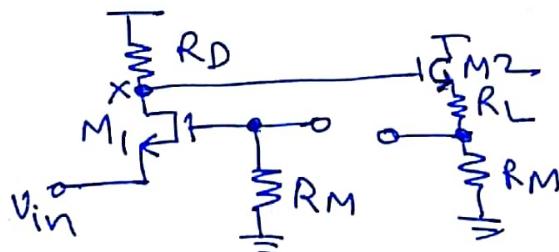

Step 5:- Compute  $\beta$ .

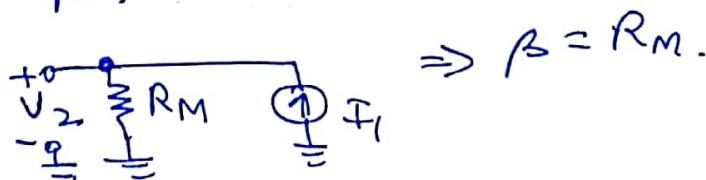

Step 6:- Open loop gain is,

$$G_{m, open-loop} = \left( \frac{V_x}{V_{in}} \right) \cdot \left( \frac{I_{out}}{V_x} \right)$$

Let, source of  $M_2$  be called node "A". Thus,

$$\frac{V_A}{V_x} = \frac{R_L + R_M}{R_L + R_M + \frac{1}{g_m 2}}$$

$$\text{Thus, } I_{out} = \frac{V_A}{R_L + R_M} = \frac{V_x}{R_L + R_M + \frac{1}{g_m 2}}$$


(34)

Hence,

$$G_{m, \text{open-loop}} = \frac{g_m R_D}{R_L + R_M + \frac{1}{g_m 2}}$$

$$R_{in, \text{open-loop}} = \frac{1}{g_m 1}$$

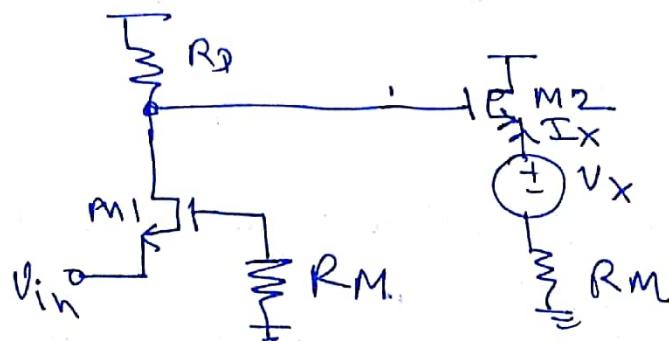To find ~~Rout~~  $R_{out, \text{open-loop}}$  we apply the test voltage  $V_x$  as shown below and measure  $I_x$ .



$$\text{Thus, } R_{out, \text{open-loop}} = \frac{1}{g_m 2} + R_M.$$


Step 7:-

$$G_{m, \text{closed-loop}} = \frac{G_{m, \text{open-loop}}}{1 + R_M G_{m, \text{open-loop}}}$$

$$R_{in, \text{closed}} = \frac{1}{g_m 1} (1 + R_M G_m)$$

$$R_{out, \text{closed}} = \left( \frac{1}{g_m 2} + R_M \right) (1 + R_M G_m)$$

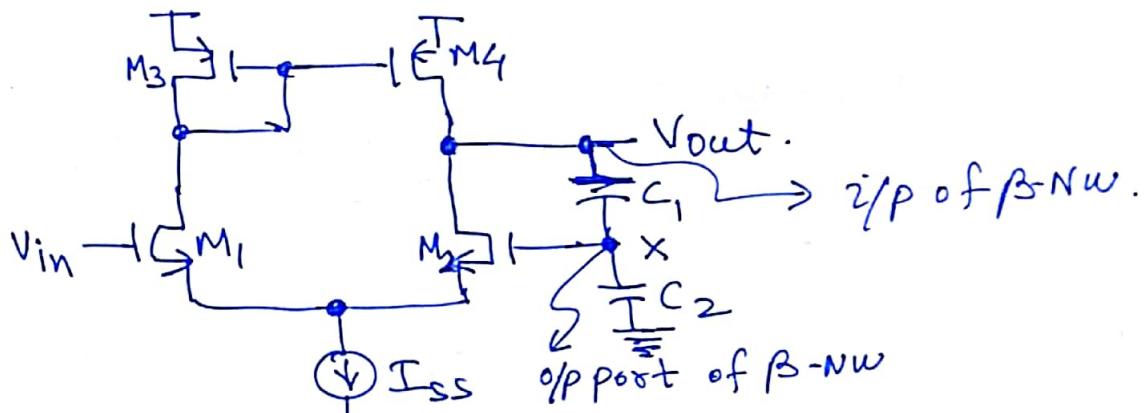Example 3:- Identify the type of feedback in the following circuit. At low frequencies, is there any loading effect? Compute the loop gain and the closed loop gain, input-impedance, and output impedance.



Ans:- Voltage sensing  $\Rightarrow$  shunt sampling.

Voltage mixing  $\Rightarrow$  series. mixing.

series-shunt feedback

or.

Voltage - voltage feedback.

- \* ~~C<sub>1</sub>~~ and C<sub>2</sub> comprise the feedback network.
- \* At low frequencies current through feedback network is negligible  $\Rightarrow$  no-loading effect
- \* U<sub>X</sub> is feedback and it is a fraction of output voltage. Thus,

$$\beta = \frac{U_X}{V_{out}} = \frac{C_1}{C_1 + C_2},$$

- \* ~~when~~ when there is no loading effect you can break the loop ~~anywhere~~ either at the i/p port or o/p port of β-network.
- \* Forward path consists of M<sub>1</sub>, M<sub>2</sub>, M<sub>3</sub>, and M<sub>4</sub>. having a voltage gain of,  $A_u = g_m(\tau_{o2} || \tau_{o4})$


(36) Thus,  $A_{\text{closed}} = \frac{g_m (\tau_{o2} || \tau_{o4})}{1 + \frac{C_1}{C_1 + C_2} g_m (\tau_{o2} || \tau_{o4})}$

where,  $g_m = g_{m1} = g_{m2}$ .

\*  $R_{\text{out, open}} = (\tau_{o2} || \tau_{o4})$ .

$$\Rightarrow R_{\text{out, closed}} = \frac{\tau_{o2} || \tau_{o4}}{1 + \frac{C_1}{C_1 + C_2} g_m (\tau_{o2} || \tau_{o4})}$$

Example 4:-

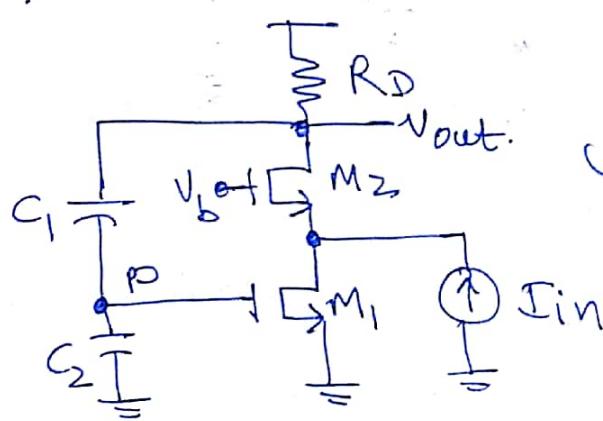

- (i) Identify the type of feedback.
- (ii) Is there loading effect at low freq.
- (iii) Compute  $k_{\text{closed}}$ ,  $R_{\text{in, closed-loop}}$ , and  $R_{\text{out, closed-loop}}$ .

\* Assume  $\tau = 0$ .

Ans:-  $V_{\text{out}}$  is sensed  $\Rightarrow$  shunt-sampling.

Part of  $V_{\text{out}}$  shows up at  $V_P$  modulating the  $V_{\text{ds}}$  of  $M_1$ , thus subtracting current from  $I_{\text{in}}$ .

Hence, Current mixing  $\Rightarrow$  shunt-mixing.

Thus, shunt-shunt feedback.

voltage-current feedback.

\* At low frequency the feedback network  $C_1$  and  $C_2$  ~~are open~~ do not draw current from output.  $\Rightarrow$  No loading effect.

\* Forward amplifier comprises of  $M_2$  and  $R_D$ .

\* Feedback network includes  $C_1$ ,  $C_2$  and  $M_1$ .

Thus,  $\beta = \frac{C_1}{C_1 + C_2} g_{m1}$ .

and,  $R_{open} = \frac{V_{out}}{I_{in}} = R_D$ .

resulting in,

$$R_{closed} = \frac{R_D}{1 + \frac{C_1}{C_1 + C_2} g_{m1} R_D}$$

Now,  $R_{in, open} = \frac{1}{g_{m2}}$ .

and,  $R_{out, open} = R_D$ .

Thus,

$$R_{in, closed-loop} = \frac{1}{g_{m2}} - \frac{1}{1 + \frac{C_1}{C_1 + C_2} g_{m1} R_D}$$

and,  $R_{out, closed-loop} = \frac{R_D}{1 + \frac{C_1}{C_1 + C_2} g_{m1} R_D}$ .