

1.8) $\Delta_1 = 8 \text{ mod } 10 = 8$
 $I_S = (S + \frac{\Delta_1}{10}) \times 10^{-14} \text{ A}$
 $= 5.8 \times 10^{-13} \text{ mA}$

$\beta = 100 + 8 = 108$

$V_X = \infty$

$V_T = 26 \text{ mV}$

$V_{DD} = 5 + \frac{\Delta_1}{10} = 5.8 \text{ V}$

a) $V_{BE} = 0.7 \text{ V}$

$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) = 5.8 \times 10^{-13} \exp\left(\frac{0.7}{0.026}\right)$
 $= 0.2857 \text{ mA}$

$g_m = \frac{I_C}{V_T} = \frac{0.2857 \text{ mA}}{0.026 \text{ V}} = 10.99 \text{ (k}\Omega\text{)}^{-1}$

$\approx 11 \text{ k}\Omega^{-1} \text{ (Ans)}$

b) $V_{R_C} = \frac{V_{DD}}{2} = 2.9 \text{ V}$

$I_C = 0.2857 \text{ mA}$

$R_C = 10.15 \text{ k}\Omega \text{ (Ans)}$

c) $V_{BE} \sim 0.1 \sim 0.3 V_{CC}$

\therefore voltage drop across R_E for bias stability

~~$= 0.29 \text{ V}$~~

$\sim 0.58 \text{ V approx}$ or 0.5 V approx

bias currents must be negligible to reduce loss through bleeding of power.

d) if bias current is negligible


$\frac{V_{DD}}{R_1 + R_2} \gg I_B$

$I_B = \frac{I_C}{\beta} = 2.64 \times 10^{-3} \text{ mA}$

or $\frac{V_{DD}}{R_1 + R_2} = 10 I_B$

or $\frac{V_{DD}}{R_1 + R_2} = 26.4 \times 10^{-3}$

or $R_1 + R_2 = 219.25 \text{ k}\Omega$

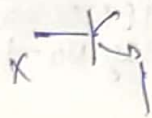

$$\begin{aligned} V_{RE} &= 0.5 \text{ V} \\ V_{BE} &= 0.7 \text{ V} \\ \therefore V_X &= 1.2 \text{ V} \end{aligned}$$

$$\begin{aligned} V_{RE} &= 0.5 \text{ V} \\ I_E &= 0.2857 \text{ mA} \\ R_E &= 1.75 \text{ k}\Omega \end{aligned}$$

$$V_X = (10I_B)R_2$$

$$\text{or } R_2 = \frac{1.2}{10 \times 2.64 \times 10^{-3}}$$

$$\text{or } R_2 = \frac{500}{11} = 45.45 \text{ k}\Omega \quad (\text{Ans})$$

$$R_1 = 219.25 - 45.45 = 173.79 \text{ k}\Omega \quad (\text{Ans})$$

$$\frac{V_X}{R_2} = 10I_B \quad \text{implies bias current is less than current through } R_2$$

$$\begin{aligned} A_V &= - \frac{R_C}{\frac{1}{g_m}} = -g_m R_C \\ &= -10.99 \times 10.15 \\ &= -111.54 \end{aligned}$$

Since there are 3 capacitors we expect 3 poles one associated with each node.

$$|\omega_{p1}| = \frac{1}{C_1(R_1 || R_2)} = 5.9 \text{ rad/s}$$

$$|\omega_{p2}| = \frac{1}{R_E C_E} = \frac{1}{1.75 \times 47 \times 10^{-3} \times 10^3} = 121.57 \text{ rad/s}$$

$$|\omega_{p3}| = \frac{1}{C_2(R_C)} = 20.96 \text{ rad/s}$$