



Indian Institute of Technology
Kharagpur, India

Op Amp Design LT-SPICE Expts


Bibhu Datta Sahoo

(Prepared by Shruti Konwar and Senorita Deb)

Department of Electronics and Electrical Communication Engineering
Indian Institute of Technology Kharagpur, India



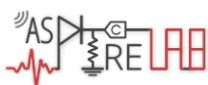
Indian Institute of Technology
Kharagpur, India



Analog Signal Processing, Integrated circuit
Research and Engineering LAB,
Department of E&ECE, IIT Kharagpur



Fully Differential Two stage OpAmp

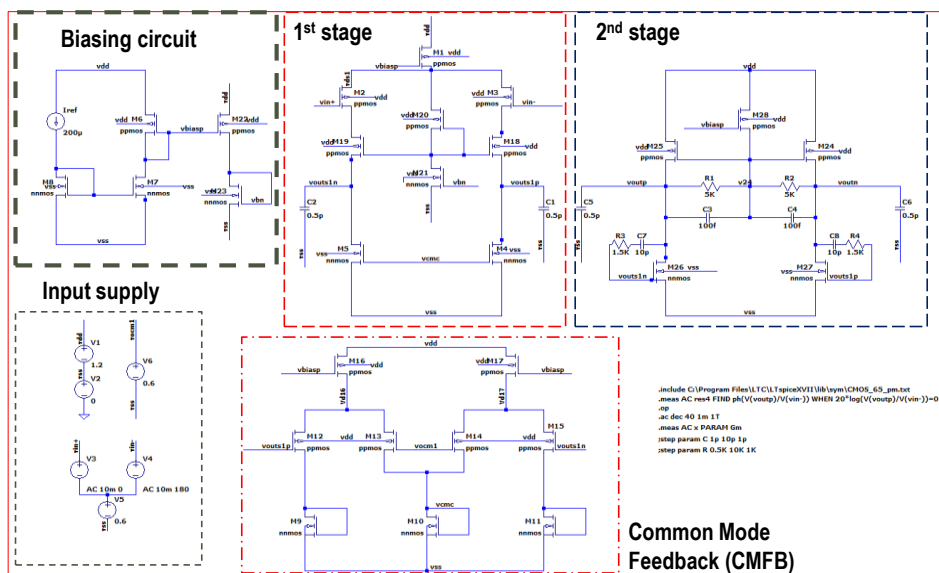

Indian Institute Of Technology, Kharagpur, India

Bibhu Datta Sahoo




Analog Signal Processing, Integrated circuit Research
and Engineering LAB, Department of E&ECE

2



Design criteria to be followed

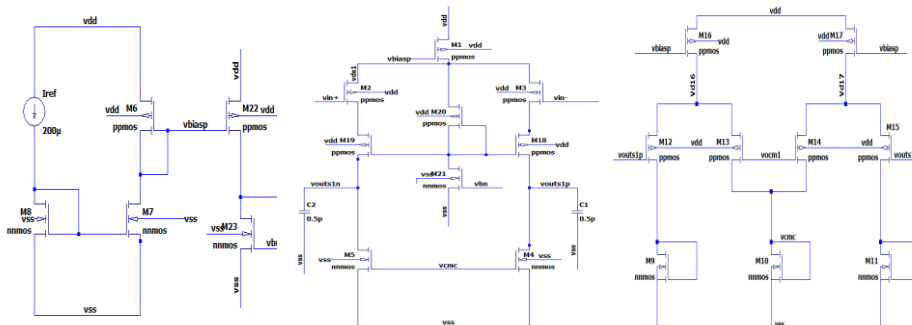

- Channel length of the current mirror devices : $L \gg L_{\min}$ (minimum channel length of the technology node) to minimize CLM effect (λV_{DS} small).
- Input devices :
 - Channel length of Input devices should be near to L_{\min} (To increase transit frequency f_T)
 - For higher gain, transconductance (g_m) of input devices should be more, so Width can be kept high.
- Tail Current source (as required in the other circuits) are biased from the current mirror circuit according to 1:K ratio of width keeping L constant w.r.t. current mirror load.



First stage with CMFB



- Uses a CMFB circuitry with two differential pairs.
- CMFB circuit controls the Gate voltage of M5 and M4 which further controls the output common mode voltage of the stage.
- First approach: First stage without cascode transistors ; with CMFB (Fig. 1)
- Design approach:

Length of load transistors M_{16}, M_{17} kept high $\rightarrow R_{out}$ increases

- The input and load devices are sized to have sufficient overdrive voltage to remain in saturation
- Observation: $R_{out} = R_{up} \parallel R_{down}$ so R_{up} needs to be increased; Consequence : Use of PMOS cascode transistors M18, M19

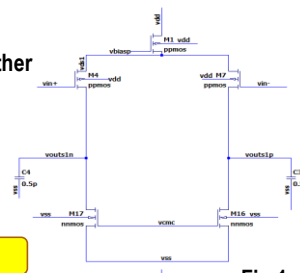


Fig.1

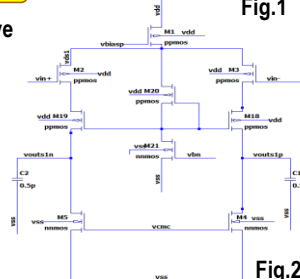


Fig.2





First stage with CMFB



Transistor pairs M12-M13 and M14-M15 together sense the common mode output voltage $V_{OC} = (V_{outS1P} + V_{outS1N})/2$

And generates an output proportional to the difference between $V_{outS1P/n}$ and V_{ocm1} which controls the gate voltage of transistors M4 and M5 of the first stage.


Assuming the differential inputs $V_{outS1P} - V_{ocm1}$ and $V_{outS1N} - V_{ocm1}$ to the two source coupled pairs M12-M13 and M14-M15 to be small enough for small signal analysis, we can write

$$I_{D14} = -I_{D17} - gm_{14} \frac{V_{outS1N} - V_{CM}}{2}$$

$$I_{D13} = -I_{D16} - gm_{13} \frac{V_{outS1P} - V_{CM}}{2}$$

These two currents are summed up in the diode connected NMOS M10 and give the common mode sensor output current, $I_{D10} = I_{D13} + I_{D14}$ $I_{D10} = I_{D16,17} + gm_{13,14}(V_{OC} - V_{CM})$

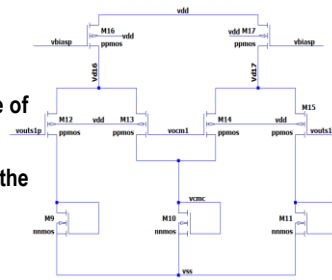This current is mirrored by M4-M5 to produce the tail current of the op-amp first stage which controls the output common mode voltage of V_{outS1P} and V_{outS1N}



Design approach :

Transistors M12,M13,M14,M15 are kept at same L_{min}

Transistors M9,10,11 are kept at same L as that of M4-M5 (corresponding mirrors)




Second stage with Frequency compensation



- Uses a resistive divider feedback ($R1,R2$) to set the output common mode voltage to $V_{DD}/2$.

Design procedure : Without the presence of the current source M13 \rightarrow no flow of current through $R1$ and $R2$. This gives an overdrive voltage of $V_{DSAT11,12} = V_{SG11,12} - |V_{thp}|$ where $|V_{thp}|$ is the threshold of the pmos transistors. This limits the output maximum swing to $V_{outp,max} = V_{outn,max} = V_{DD} - V_{DSAT11,12}$

- This increases the swing, but V_{SD} approach towards V_{DD} i.e. the output swing is not symmetric and the dc operating point is not obtained to be at $V_{DD}/2$.
- Thus a current source M28 is included \rightarrow allows some current to flow through $R1,R2$ \rightarrow pushes V_{outp} or V_{outn} to lower value than the gate voltage of the pmos transistors .
- $R1,R2$ and M13 can be sized such that
 - condition $V_{outp} = V_{outn} = V_{DD}/2$ satisfies
 - should not modify the output impedance of the stage to a great extent.
 - should not increase the RC ($R1C_{gs}$ or $R2C_{gs}$)time constant of the stage

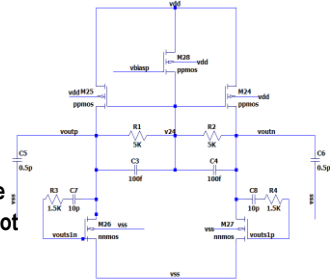



Second stage with Frequency compensation



Typical choice of $R_1 = R_2 = (5 - 10)(R_{out25} || R_{out26})$

For the current source, a typical design criteria is to keep the current (1/10)th of the total current through the two differential branches

R1, R2 resistors along with the gate capacitances $C_{gs24,25}$ introduce a pole in the common mode feedback loop limiting the high frequency response.

Solution: Capacitor C3, C4 are added in parallel to each sense resistor

This introduces a left-half plane zero in the common mode sense circuit.

C3, C4 acts as HPF respectively reducing the effect of the pole at high frequencies and is chosen so as not to load the output.



Second stage with Frequency compensation



Design approach for Frequency compensation

Dominant pole and lead compensation used

Resistor R3,R4 , controls the lead compensation

Capacitors C7,C8 controls the dominant first pole

Steps to follow :

Consider $R3=R4=R_c$ and $C7=C8=C_c$


Sweep C_c and R_c for wide range (coarse sweeping)

Use LTspice commands

```
.step PARAM <exp> <initial value> <final value> <increment>
.ac dec <points per decade> <initial frequency> <final frequency>
.meas AC <variable> PARAM <measured quantity>
.meas AC res4 FIND ph(V(voutp)/V(vin-)) WHEN 20*log(V(voutp)/V(vin-))=0
  • Run → View → SPICE Error Log
```

Check the phase angle Φ (provided in dB) for $PM \approx 60^\circ (180^\circ - \Phi) \rightarrow$ corresponding R_c and C_c are the desired coarse values.

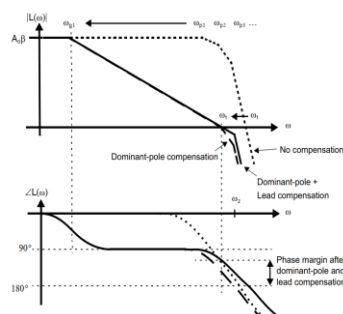Fine sweeping for a smaller range of R_c and C_c is to be done for final values.




NB: Phase angles are shown as 20log(phase) dB, with 180° or 0° phase shift.





Frequency Response

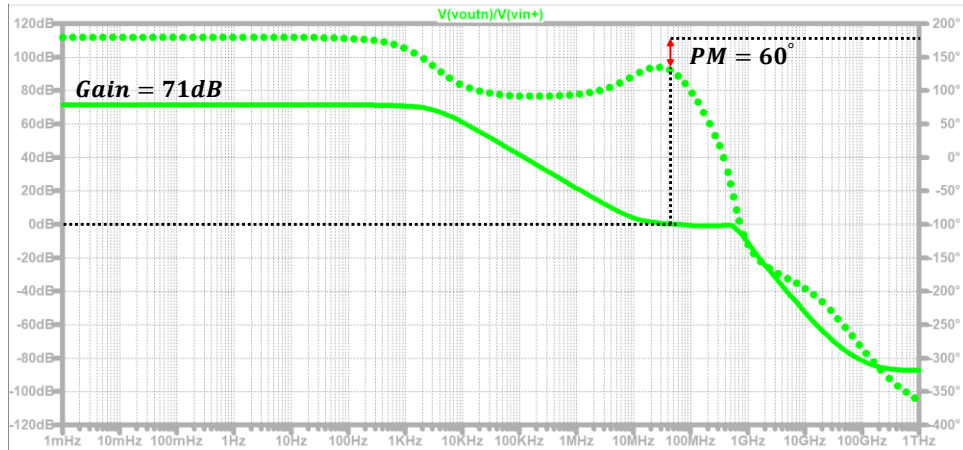

Indian Institute Of Technology, Kharagpur, India

Bibhu Datta Sahoo



Analog Signal Processing, Integrated circuit Research and Engineering LAB, Department of E&ECE