

## CMOS Inverter: DC Analysis


- Analyze DC Characteristics of CMOS Gates by studying an Inverter

$$\text{pFET: } V_{Tp} < 0$$
$$\beta_p = k'_p \left(\frac{W}{L}\right)_p$$

- DC Analysis
  - DC value of a signal in static conditions

- DC Analysis of CMOS Inverter

 - $V_{in}$ , input voltage
- $V_{out}$ , output voltage
- single power supply, VDD
- Ground reference
- find  $V_{out} = f(V_{in})$




- Voltage Transfer Characteristic (VTC)
  - plot of  $V_{out}$  as a function of  $V_{in}$
  - vary  $V_{in}$  from 0 to VDD (**and in reverse!**)
  - find  $V_{out}$  at each value of  $V_{in}$

$$\text{nFET: } V_{Tn} > 0$$
$$\beta_n = k'_n \left(\frac{W}{L}\right)_n$$


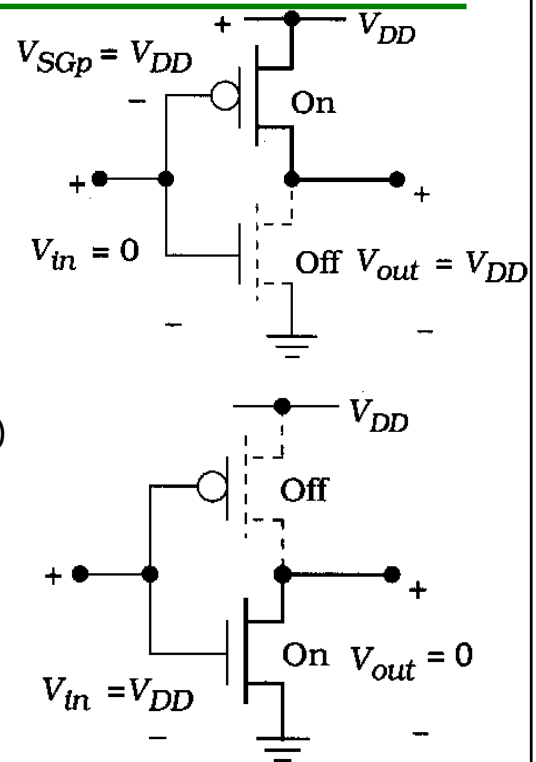
# Inverter Voltage Transfer Characteristics

- Output High Voltage,  $V_{OH}$ 
  - maximum output voltage
    - occurs when input is low ( $V_{in} = 0V$ )
    - pMOS is ON, nMOS is OFF
    - pMOS pulls  $V_{out}$  to  $V_{DD}$
  - $V_{OH} = V_{DD}$
- Output Low Voltage,  $V_{OL}$ 
  - minimum output voltage
    - occurs when input is high ( $V_{in} = V_{DD}$ )
    - pMOS is OFF, nMOS is ON
    - nMOS pulls  $V_{out}$  to Ground
  - $V_{OL} = 0V$
- Logic Swing
  - Max swing of output signal
    - $V_L = V_{OH} - V_{OL}$
    - $V_L = V_{DD}$




# Inverter Voltage Transfer Characteristics

- Gate Voltage,  $f(V_{in})$ 
  - $V_{GSn} = V_{in}$ ,  $V_{SGp} = V_{DD} - V_{in}$
- Drain Voltage,  $f(V_{out})$ 
  - $V_{DSn} = V_{out}$ ,  $V_{SDp} = V_{DD} - V_{out}$


- Transition Region (between  $V_{OH}$  and  $V_{OL}$ )

- $V_{in}$  low
  - $V_{in} < V_{tn}$ 
    - Mn in Cutoff, OFF
    - Mp in Triode,  $V_{out}$  pulled to  $V_{DD}$
  - $V_{in} > V_{tn} < \sim V_{out}$ 
    - Mn in Saturation, strong current
    - Mp in Triode,  $V_{SG}$  & current reducing
    - $V_{out}$  decreases via current through Mn
- $V_{in} = V_{out}$  (mid point)  $\approx \frac{1}{2} V_{DD}$ 
  - Mn and Mp both in Saturation
  - maximum current at  $V_{in} = V_{out}$
- $V_{in}$  high
  - $V_{in} > \sim V_{out}$ ,  $V_{in} < V_{DD} - |V_{tp}|$ 
    - Mn in Triode, Mp in Saturation
  - $V_{in} > V_{DD} - |V_{tp}|$ 
    - Mn in Triode, Mp in Cutoff

 


$V_{in} < V_{IL}$   
input logic LOW

$V_{in} > V_{IH}$   
input logic HIGH

 
 
## Noise Margin


- Input Low Voltage,  $V_{IL}$ 
  - $V_{in}$  such that  $V_{in} < V_{IL} = \text{logic 0}$
  - point 'a' on the plot
    - where slope,  $\frac{\partial V_{in}}{\partial V_{out}} = -1$
- Input High Voltage,  $V_{IH}$ 
  - $V_{in}$  such that  $V_{in} > V_{IH} = \text{logic 1}$
  - point 'b' on the plot
    - where slope = -1
- Voltage Noise Margins
  - measure of how stable inputs are with respect to signal interference
  - $VNM_H = V_{OH} - V_{IH} = V_{DD} - V_{IH}$
  - $VNM_L = V_{IL} - V_{OL} = V_{IL}$
  - desire large  $VNM_H$  and  $VNM_L$  for best noise immunity


 
## Switching Threshold

- Switching threshold = point on VTC where  $V_{out} = V_{in}$ 
  - also called midpoint voltage,  $V_M$
  - here,  $V_{in} = V_{out} = V_M$

- Calculating  $V_M$ 
  - at  $V_M$ , both nMOS and pMOS in Saturation
  - in an inverter,  $I_{Dn} = I_{Dp}$ , always!
  - solve equation for  $V_M$



$$I_{Dn} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GSn} - V_{tn})^2 = \frac{\beta_n}{2} (V_{GSn} - V_{tn})^2 = \frac{\beta_p}{2} (V_{SGp} - |V_{tp}|)^2 = I_{Dp}$$

- express in terms of  $V_M$

$$\frac{\beta_n}{2} (V_M - V_{tn})^2 = \frac{\beta_p}{2} (V_{DD} - V_M - |V_{tp}|)^2 \Rightarrow \sqrt{\frac{\beta_n}{\beta_p}} (V_M - V_{tn}) = V_{DD} - V_M - |V_{tp}|$$

- solve for  $V_M$

$$V_M = \frac{V_{DD} - |V_{tp}| + V_{tn} \sqrt{\frac{\beta_n}{\beta_p}}}{1 + \sqrt{\frac{\beta_n}{\beta_p}}}$$



## Effect of Transistor Size on VTC

- Recall

$$\beta_n = k'_n \frac{W}{L} \quad \frac{\beta_n}{\beta_p} = \frac{k'_n \left(\frac{W}{L}\right)_n}{k'_p \left(\frac{W}{L}\right)_p}$$

$$V_M = \frac{V_{DD} - |V_{tp}| + V_m \sqrt{\frac{\beta_n}{\beta_p}}}{1 + \sqrt{\frac{\beta_n}{\beta_p}}}$$

- If nMOS and pMOS are same size

-  $(W/L)_n = (W/L)_p$

-  $C_{oxn} = C_{oxp}$  (always)

$$\frac{\beta_n}{\beta_p} = \frac{\mu_n C_{oxn} \left(\frac{W}{L}\right)_n}{\mu_p C_{oxp} \left(\frac{W}{L}\right)_p} = \frac{\mu_n}{\mu_p} \cong 2 \text{ or } 3$$

- If  $\frac{\mu_n}{\mu_p} = \frac{\left(\frac{W}{L}\right)_p}{\left(\frac{W}{L}\right)_n}$ , then  $\frac{\beta_n}{\beta_p} = 1$

since  $L$  normally min. size for all tx,  
can get betas equal by making  $W_p$  larger than  $W_n$

- Effect on switching threshold

- if  $\beta_n \approx \beta_p$  and  $V_{tn} = |V_{tp}|$ ,  $V_M = V_{DD}/2$ , exactly in the middle


- Effect on noise margin

- if  $\beta_n \approx \beta_p$ ,  $V_{IH}$  and  $V_{IL}$  both close to  $V_M$  and noise margin is good



 
## Example

- Given
  - $k'_n = 140 \mu\text{A}/\text{V}^2$ ,  $V_{tn} = 0.7\text{V}$ ,  $V_{DD} = 3\text{V}$
  - $k'_p = 60 \mu\text{A}/\text{V}^2$ ,  $V_{tp} = -0.7\text{V}$
- Find
  - a) tx size ratio so that  $V_M = 1.5\text{V}$
  - b)  $V_M$  if tx are same size



(a) Larger pFET design

(b) Equal aspect ratios


 


transition pushed lower  
as beta ratio increases


  
## CMOS Inverter: Transient Analysis

- Analyze Transient Characteristics of CMOS Gates by studying an Inverter
- Transient Analysis
  - signal value as a function of time
- Transient Analysis of CMOS Inverter
  - $V_{in}(t)$ , input voltage, function of time
  - $V_{out}(t)$ , output voltage, function of time
  - $V_{DD}$  and Ground, DC (not function of time)
  - find  $V_{out}(t) = f(V_{in}(t))$
- Transient Parameters
  - output signal **rise and fall time**
  - propagation delay**





## Transient Response

- Response to step change in input
  - delays in output due to parasitic R & C

- Inverter RC Model

- Resistances

- $R_n = 1/[\beta_n(V_{DD} - V_{tn})]$

- $R_p = 1/[\beta_p(V_{DD} - |V_{tp}|)]$

- Output Cap. (only output is important)

- $C_{Dn}$  (nMOS drain capacitance)

- $C_{Dn} = \frac{1}{2} C_{ox} W_n L + C_j A_{Dnbot} + C_{jsw} P_{Dnsw}$

- $C_{Dp}$  (pMOS drain capacitance)


- $C_{Dp} = \frac{1}{2} C_{ox} W_p L + C_j A_{Dpbot} + C_{jsw} P_{Dpsw}$

- Load capacitance, due to gates attached at the output

- $C_L = 3 C_{in} = 3 (C_{Gn} + C_{Gp})$ , 3 is a "typical" load

- Total Output Capacitance

- $C_{out} = C_{Dn} + C_{Dp} + C_L$

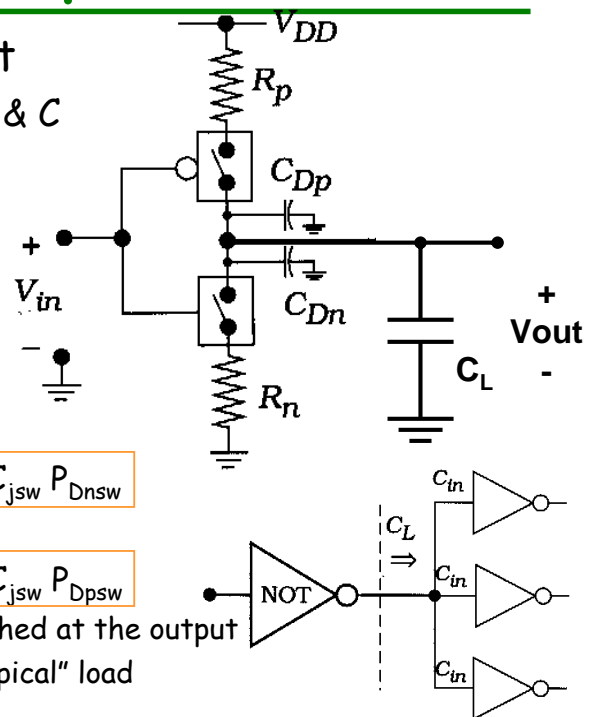

term "fan-out" describes  
# gates attached at output



## Fall Time

- Fall Time,  $t_f$

- time for output to **fall** from '1' to '0'

- derivation:

$$i = -C_{out} \frac{\partial V_{out}}{\partial t} = \frac{V_{out}}{R_n}$$

- initial condition,  $V_{out}(0) = V_{DD}$

- solution

$$V_{out}(t) = V_{DD} e^{-t/\tau_n} \quad \tau_n = R_n C_{out} \quad \text{time constant}$$

$$t = \tau_n \ln\left(\frac{V_{DD}}{V_{out}}\right)$$



- definition

- $t_f$  is time to fall from


- 90% value  $[V_1, t_x]$  to 10% value  $[V_0, t_y]$

$$t = \tau_n \left[ \ln\left(\frac{V_{DD}}{0.1V_{DD}}\right) - \ln\left(\frac{V_{DD}}{0.9V_{DD}}\right) \right]$$

- $t_f = 2.2 \tau_n$

  

(a) Discharge circuit

 

(b) Output waveform



## Rise Time

- Rise Time,  $t_r$

- time for output to **rise** from '0' to '1'

- derivation: 
$$i = C_{out} \frac{\partial V_{out}}{\partial t} = \frac{V_{DD} - V_{out}}{R_p}$$

- initial condition,  $V_{out}(0) = 0V$

- solution

$$V_{out}(t) = V_{DD} \left[ 1 - e^{-t/\tau_p} \right] \quad \tau_p = R_p C_{out} \quad \text{time constant}$$

- definition

- $t_f$  is time to rise from



- 10% value  $[V_0, t_u]$  to 90% value  $[V_1, t_v]$

- $t_r = 2.2 \tau_p$


- Maximum Signal Frequency

- $f_{max} = 1/(t_r + t_f)$

  - faster than this and the output can't settle



(a) Charge circuit

 


(b) Output waveform


 
## Propagation Delay

- Propagation Delay,  $t_p$ 
  - measures speed of output reaction to input change
  - $t_p = \frac{1}{2} (t_{pf} + t_{pr})$
- Fall propagation delay,  $t_{pf}$ 
  - time for output to fall by 50%
    - reference to input **switch**
- Rise propagation delay,  $t_{pr}$ 
  - time for output to rise by 50%
    - reference to input **switch**
- Ideal expression (if input is step change)
  - $t_{pf} = \ln(2) \tau_n$
  - $t_{pr} = \ln(2) \tau_p$
- Total Propagation Delay
  - $t_p = 0.35(\tau_n + \tau_p)$



Propagation delay measurement:  
 - from time input reaches 50% value  
 - to time output reaches 50% value

Add rise and fall propagation delays for total value



## Switching Speed -Resistance

- Rise & Fall Time
  - $t_f = 2.2 \tau_n, t_r = 2.2 \tau_p,$

$$\tau_n = R_n C_{out}$$

$$\tau_p = R_p C_{out}$$

- Propagation Delay

$$t_p = 0.35(\tau_n + \tau_p)$$

$$R_n = 1/[\beta_n(V_{DD} - V_{tn})]$$

$$\beta = \mu C_{ox} (W/L)$$

$$R_p = 1/[\beta_p(V_{DD} - |V_{tp}|)]$$

- In General

$$\text{delay} \propto \tau_n + \tau_p$$

$$\tau_n + \tau_p = C_{out} (R_n + R_p)$$

$$C_{out} = C_{Dn} + C_{Dp} + C_L$$

- Define delay in terms of design parameters

$$R_n + R_p = \frac{(V_{DD} - V_t)(\beta_n + \beta_p)}{\beta_n \beta_p (V_{DD} - V_t)^2}$$

Beta Matched if  $\beta_n = \beta_p = \beta,$

$$R_n + R_p = \frac{2}{\beta (V_{DD} - V_t)} = \frac{2L}{\mu C_{ox} W (V_{DD} - V_t)}$$

Width Matched if  $W_n = W_p = W,$  and  $L = L_n = L_p$

$$R_n + R_p = \frac{\beta_n + \beta_p}{\beta_n \beta_p (V_{DD} - V_t)}$$

$$R_n + R_p = \frac{L (\mu_n + \mu_p)}{(\mu_n \mu_p) C_{ox} W (V_{DD} - V_t)}$$

$$\text{if } V_t = V_{tn} = |V_{tp}|$$

To decrease R's,  $\downarrow L, \uparrow W, \uparrow V_{DD}, (\uparrow \mu_p, \uparrow C_{ox})$



## Switching Speed -Capacitance

- From Resistance we have

- $\downarrow L$ ,  $\uparrow W$ ,  $\uparrow VDD$ , (  $\uparrow \mu_p$ ,  $\uparrow Cox$  )
- but  $\uparrow VDD$  increases power
- $\uparrow W$  increases  $C_{out}$

- $C_{out}$

- $C_{out} = \frac{1}{2} Cox L (W_n + W_p) + C_j 2L (W_n + W_p) + 3 Cox L (W_n + W_p)$ 
  - assuming junction area  $\sim W \cdot 2L$
  - neglecting sidewall capacitance
- $C_{out} \approx L (W_n + W_p) [3 \frac{1}{2} Cox + 2 C_j]$
- $C_{out} \propto L (W_n + W_p)$

To decrease  $C_{out}$ ,  $\downarrow L$ ,  $\downarrow W$ , ( $\downarrow C_j$ ,  $\downarrow Cox$ )

- Delay  $\propto C_{out}(R_n + R_p) \propto L W \frac{L}{W VDD} = \frac{L^2}{VDD}$

$$C_{out} = C_{Dn} + C_{Dp} + C_L$$


if  $L = L_n = L_p$

estimate

$$C_L = 3 (C_{Gn} + C_{Gp}) = 3 Cox (W_n L + W_p L)$$

$$C_{Dn} = \frac{1}{2} Cox W_n L + C_j A_{Dnbot} + C_{jsw} P_{Dnsw}$$
 
$$C_{Dp} = \frac{1}{2} Cox W_p L + C_j A_{Dpbot} + C_{jsw} P_{Dpsw}$$



Decreasing  $L$  (reducing feature size) is best way to improve speed!


## Switching Speed -Local Modification

- Previous analysis applies to the overall design
  - shows that reducing feature size is critical for higher speed
  - general result useful for creating cell libraries
- How do you improve speed within a specific gate?
  - increasing  $W$  in one gate will not increase  $C_G$  of the load gates
    - $C_{out} = C_{Dn} + C_{Dp} + C_L$
    - increasing  $W$  in one logic gate will increase  $C_{Dn/p}$  but not  $C_L$ 
      - $C_L$  depends on the size of the tx gates at the output
      - as long as they keep minimum  $W$ ,  $C_L$  will be constant
  - thus, **increasing  $W$  is a good way to improve the speed within a local point**
  - But, **increasing  $W$  increases chip area needed**, which is bad
    - fast circuits need more chip area (chip "real estate")
- Increasing  $V_{DD}$  is not a good choice because it **increases power consumption**


 
## CMOS Power Consumption

- $P = P_{DC} + P_{dyn}$ 
  - $P_{DC}$ : DC (static) term
  - $P_{dyn}$ : dynamic (signal changing) term
- $P_{DC}$ 
  - $P = I_{DD} V_{DD}$ 
    - $I_{DD}$  DC current from power supply
    - ideally,  $I_{DD} = 0$  in CMOS: ideally only current during switching action
    - leakage currents cause  $I_{DD} > 0$ , define **quiescent** leakage current,  $I_{DDQ}$  (due largely to leakage at substrate junctions)
  - $P_{DC} = I_{DDQ} V_{DD}$
- $P_{dyn}$ , power required to switch the state of a gate
  - charge transferred during transition,  $Q_e = C_{out} V_{DD}$
  - assume each gate must transfer this charge 1x/clock cycle
  - $P_{average} = V_{DD} Q_e f = C_{out} V_{DD}^2 f$ ,  $f$  = frequency of signal change



- Total Power,  $P = I_{DDQ} V_{DD} + C_{out} V_{DD}^2 f$

Power increases with  $C_{out}$  and frequency, and **strongly** with  $V_{DD}$  (second order).






## Multi-Input Gate Signal Transitions

- In multi-input gates multiple signal transitions produce output changes
- What signal transitions need to be analyzed?
  - for a general N-input gate with  $M_0$  low output states and  $M_1$  high output states
    - # high-to-low output transitions =  $M_0 \cdot M_1$
    - # low-to-high output transitions =  $M_1 \cdot M_0$
    - total transitions to be characterized =  $2 \cdot M_0 \cdot M_1$
    - example: NAND has  $M_0 = 1$ ,  $M_1 = 3$
  - don't test/characterize cases without output transitions
- Worst-case delay** is the slowest of all possible cases
  - worst-case high-to-low
  - worst-case low-to-high
  - often different input transitions for each of these cases

	$V_A$	$V_B$	$V_{out}$
(i)	0	0	$V_{DD}$
(ii)	0	$V_{DD}$	$V_{DD}$
(iii)	$V_{DD}$	0	$V_{DD}$
	$V_{DD}$	$V_{DD}$	0

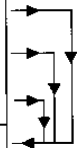

(a) Transition table





# Series/Parallel Equivalent Circuits

- Scale both  $W$  and  $L$ 
  - no effective change in  $W/L$
  - increases gate capacitance



$$Q_1 \text{ with } W/L \equiv Q_{eq} \text{ with } (KW)/(KL) \text{ for any } K$$

inputs must be at same value/voltage

  - Series Transistors
  - increases effective  $L$



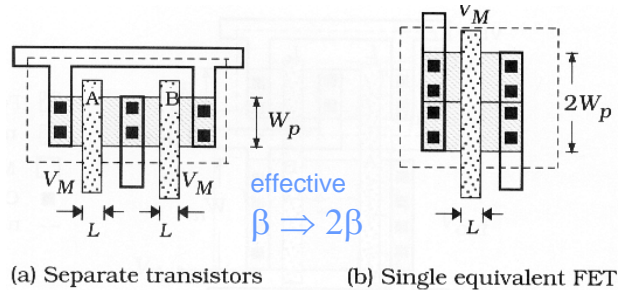 - Parallel Transistors
  - increases effective  $W$



## NAND: DC Analysis

- Multiple Inputs
- Multiple Transitions
- Multiple VTCs

- VTC varies with transition

- transition from 0,0 to 1,1 pushed right of others
- why?


- $V_M$  varies with transition

- assume all tx have same  $L$
- $V_M = V_A = V_B = V_{out}$ 
  - can merge transistors at this point
- if  $W_{pA}=W_{pB}$  and  $W_{nA}=W_{nB}$ 
  - series nMOS,  $\beta_n \Rightarrow \frac{1}{2} \beta_n$
  - parallel pMOS,  $\beta_p \Rightarrow 2 \beta_p$


- can now calculate the NAND  $V_M$

	$V_A$	$V_B$	$V_{out}$
(i)	0	0	$V_{DD}$
(ii)	0	$V_{DD}$	$V_{DD}$
(iii)	$V_{DD}$	0	$V_{DD}$
	$V_{DD}$	$V_{DD}$	0

(a) Transition table

 

(b) VTC family

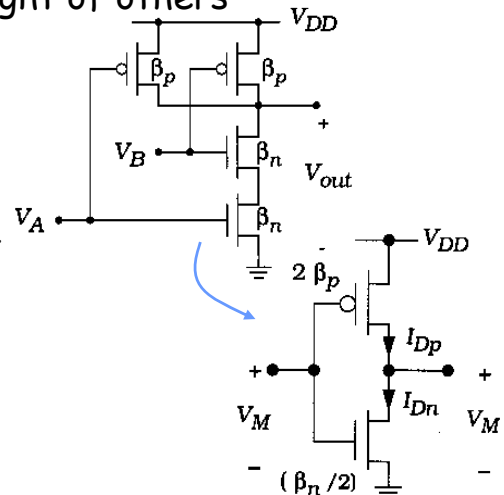

# NAND Switching Point

- Calculate  $V_M$  for NAND
  - 0,0 to 1,1 transition
    - all tx change states (on, off)
    - in other transitions, only 2 change
  - $V_M = V_A = V_B = V_{out}$
  - set  $I_{Dn} = I_{Dp}$ , solve for  $V_M$

$$V_M = \frac{V_{DD} - |V_{tp}| + V_m \frac{1}{2} \sqrt{\frac{\beta_n}{\beta_p}}}{1 + \frac{1}{2} \sqrt{\frac{\beta_n}{\beta_p}}}$$

- denominator reduced more
  - VTC shifts right




- For NAND with N inputs

$$V_M = \frac{V_{DD} - |V_{tp}| + V_m \frac{1}{N} \sqrt{\frac{\beta_n}{\beta_p}}}{1 + \frac{1}{N} \sqrt{\frac{\beta_n}{\beta_p}}}$$

series nMOS means  
more resistance to  
output **falling**,  
shifts VTC to right

to balance this effect  
and set  $V_M$  to  $V_{DD}/2$ ,  
can increase  $\beta$  by  
increasing  $W_n$

   but, since  $\mu_n > \mu_p$ ,  $V_M \approx V_{DD}/2$   
when  $W_n = W_p$




## NOR: DC Analysis

- Similar Analysis to NAND
- Critical Transition
  - 0,0 to 1,1
  - when all transistors change
- $V_M$  for NOR2 critical transition
  - if  $W_{pA}=W_{pB}$  and  $W_{nA}=W_{nB}$ 
    - parallel nMOS,  $\beta_n \Rightarrow 2\beta_n$
    - series pMOS,  $\beta_p \Rightarrow \frac{1}{2}\beta_p$

	$V_A$	$V_B$	$V_{out}$
	0	0	$V_{DD}$
(iii)	0	$V_{DD}$	0
(ii)	$V_{DD}$	0	0
(i)	$V_{DD}$	$V_{DD}$	0

(a) Transition table

 

(b) VTC family


$$V_M = \frac{V_{DD} - |V_{tp}| + 2V_m \sqrt{\frac{\beta_n}{\beta_p}}}{1 + 2\sqrt{\frac{\beta_n}{\beta_p}}}$$

for NOR2

$$V_M = \frac{V_{DD} - |V_{tp}| + NV_m \sqrt{\frac{\beta_n}{\beta_p}}}{1 + N\sqrt{\frac{\beta_n}{\beta_p}}}$$

for NOR-N

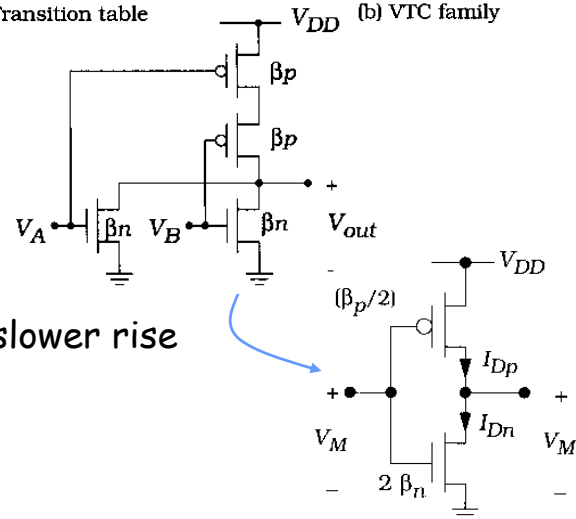
- series pMOS resistance means slower rise
- VTC shifted to the left
- to set  $V_M$  to  $V_{DD}/2$ , increase  $W_p$ 
  - this will increase  $\beta_p$


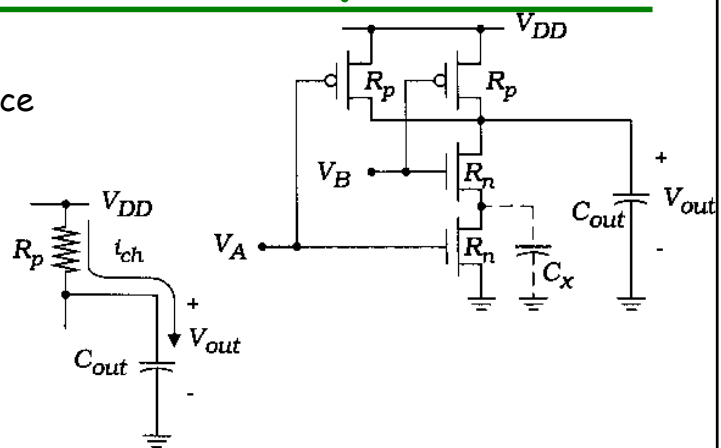
## NAND: Transient Analysis


- NAND RC Circuit
  - R: standard channel resistance
  - C:  $C_{out} = C_L + C_{Dn} + 2C_{Dp}$

- Rise Time,  $t_r$ 
  - Worst case charge circuit
    - 1 pMOS ON
  - $t_r = 2.2 \tau_p$ 
    - $\tau_p = R_p C_{out}$
  - best case charge circuit
    - 2 pMOS ON,  $R_p \Rightarrow R_p/2$



 (a) Charging circuit

- Fall Time,  $t_f$ 
  - Discharge Circuit
    - 2 series nMOS,  $R_n \Rightarrow 2R_n$
    - must account for internal cap,  $C_x$
  - $t_f = 2.2 \tau_n$ 
    - $\tau_n = C_{out} (2 R_n) + C_x R_n$




$$C_x = C_{Sn} + C_{Dn}$$

(b) Discharging circuit


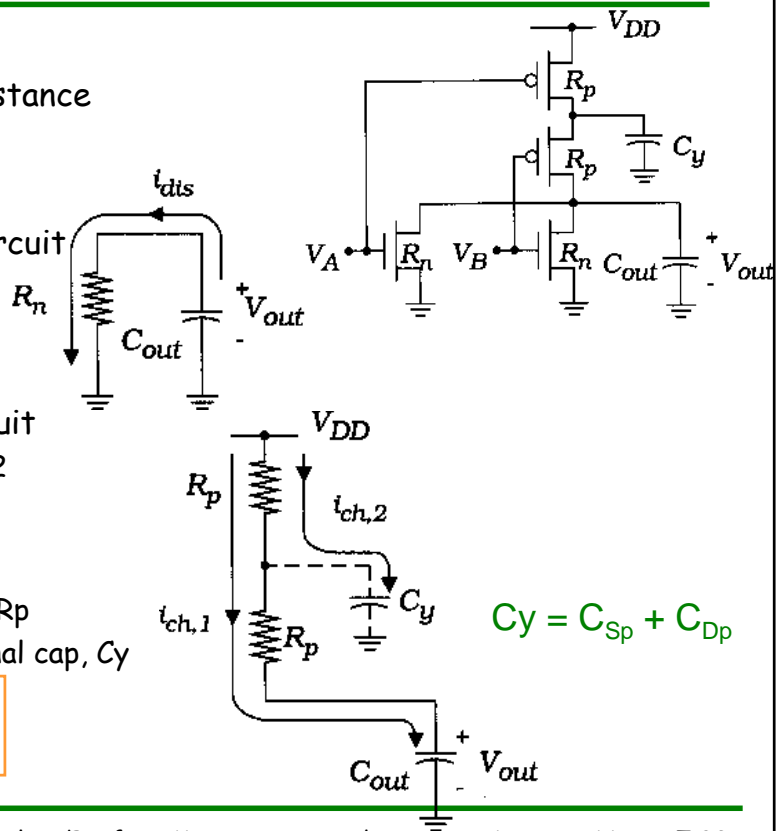
## NOR: Transient Analysis

- NAND RC Circuit
  - R: standard channel resistance
  - C:  $C_{out} = C_L + 2C_{Dn} + C_{Dp}$
- Fall Time,  $t_f$ 
  - Worst case discharge circuit
    - 1 nMOS ON
  - $t_f = 2.2 \tau_n$ 
    - $\tau_n = R_n C_{out}$
  - best case discharge circuit
    - 2 nMOS ON,  $R_n \Rightarrow R_n/2$
- Rise Time,  $t_r$ 
  - Charge Circuit
    - 2 series pMOS,  $R_p \Rightarrow 2R_p$
    - must account for internal cap,  $C_y$
  - $t_r = 2.2 \tau_p$ 
    - $\tau_p = C_{out} (2 R_p) + C_y R_p$




## NAND/NOR Performance

- Inverter: symmetry ( $V_M = V_{DD}/2$ ),  $\beta_n = \beta_p$ 
  - $(W/L)_p = \mu_n/\mu_p (W/L)_n$
- Match INV performance with **NAND**
  - pMOS,  $\beta_p = \beta_p$ , same as inverter
  - nMOS,  $\beta_N = 2\beta_n$ , to balance for 2 series nMOS
- Match INV performance with **NOR**
  - pMOS,  $\beta_p = 2\beta_p$ , to balance for 2 series pMOS
  - nMOS,  $\beta_N = \beta_n$ , same as inverter

$\beta$  is adjusted by changing transistor size (width)

NAND and NOR will still be slower due to **larger  $C_{out}$**

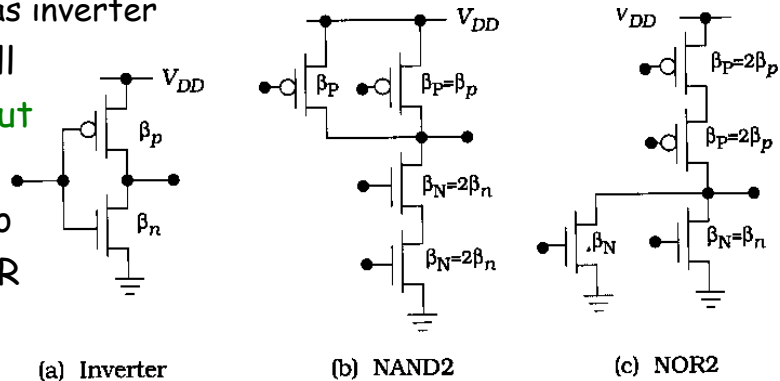
- This can be extended to 3, 4, ... N input NAND/NOR gates





 
## NAND/NOR Transient Summary

- Critical Delay Path
  - paths through series transistors will be slower
  - more series transistors means worse delays
- Tx Sizing Considerations
  - increase  $W$  in series transistors
  - balance  $\beta_n/\beta_p$  for each cell
- Worst Case Transition
  - when all series transistor go from OFF to ON
  - and all internal caps have to be
    - charged (NOR)
    - discharged (NAND)


 
## Performance Considerations

- Speed based on  $\beta_n$ ,  $\beta_p$  and parasitic caps
- DC performance ( $V_M$ , noise) based on  $\beta_n/\beta_p$
- Design for speed not necessarily provide good DC performance
- Generally set tx size to optimize speed and then test DC characteristics to ensure adequate noise immunity
- Review Inverter: Our performance reference point
  - for symmetry ( $V_M = V_{DD}/2$ ),  $\beta_n = \beta_p$ 
    - which requires  $(W/L)_p = \mu_n/\mu_p (W/L)_n$
- Use inverter as reference point for more complex gates
- Apply slowest arriving inputs to series node closest to output
  - let faster signals begin to charge/discharge nodes closer to VDD and Ground



## Timing in Complex Logic Gates

- **Critical delay path** is due to series-connected transistors

- Example:  $f = x(y+z)$

- assume all tx are same size

- Fall time critical delay

- worst case, x ON, and y or z ON

- $t_f = 2.2 \tau_n$


- $\tau_n = R_n C_n + 2 R_n C_{out}$ 
  - $C_{out} = 2C_{Dp} + C_{Dn} + C_L$
  - $C_n = 2C_{Dn} + C_{Sn}$

- Rise time critical delay

- worst case, y and z ON, x OFF

- $t_r = 2.2 \tau_p$

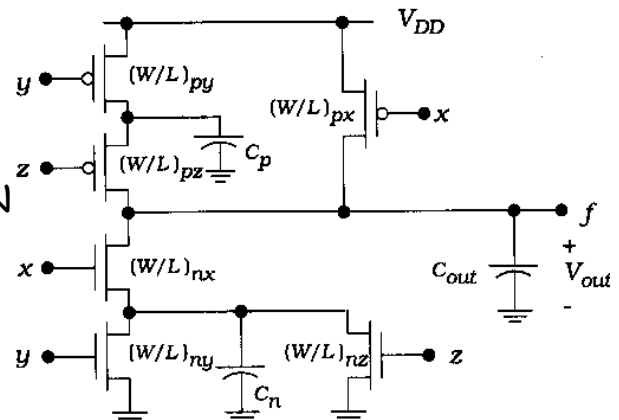- $\tau_p = R_p C_p + 2 R_p C_{out}$ 
  - $C_{out} = 2C_{Dp} + C_{Dn} + C_L$
  - $C_p = C_{Dp} + C_{Sp}$



### size vs. tx speed considerations

$\uparrow W_{nx} \Rightarrow \downarrow R_n$  but  $\uparrow C_{out}$  and  $\uparrow C_n$

$\downarrow W_{ny} \Rightarrow \downarrow C_n$  but  $\uparrow R_n$


$\uparrow W_{pz} \Rightarrow \downarrow R_p$  but  $\uparrow C_{out}$  and  $\uparrow C_p$

$\downarrow W_{px} \Rightarrow$  no effect on critical path



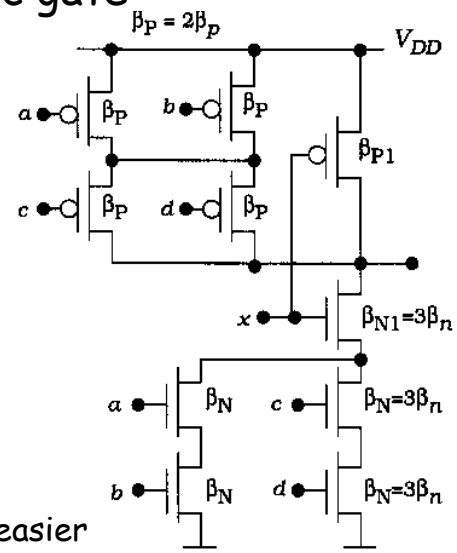
## Sizing in Complex Logic Gates

- Improving speed within a single logic gate
- An Example:  $f = (a b + c d) x$
- nMOS
  - discharge through 3 series nMOS
  - set  $\beta_N = 3\beta_n$
- pMOS
  - charge through 2 series pMOS
  - set  $\beta_p = 2\beta_p$
  - but,  $M_{xp}$  is alone so  $\beta_{p1} = \beta_p$ 
    - but setting  $\beta_{p1} = 2\beta_p$  might make layout easier
- These large transistors will increase capacitance and layout area and may only give a small increase in speed
- Advanced logic structures are best way to improve speed


 
## Timing in Multi-Gate Circuits

- What is the worst-case delay in multi-gate circuits?




- too many transitions to test manually

- Critical Path**

- longest delay through a circuit block
- largest sum of delays, from input to output
- intuitive analysis: signal that passes through most gates
  - not always true. can be slower path through fewer gates

A	B	C	D	F	
0	0	0	0	0	$C \uparrow$
0	0	0	1	0	$C \uparrow D \downarrow$
0	0	1	0	1	$C \downarrow$
1	0	0	0	0	$B \uparrow$
1	1	0	0	1	$B \downarrow$
1	1	1	1	1	

 

path through most gates

critical path if delay at  
D input is very slow



## Power in Multi-Input Logic Gates

- Inverter Power Consumption

- $P = P_{DC} + P_{dyn} = V_{DD}I_{DDQ} + C_{out}V_{DD}^2f$

- assumes gates switches output state once per clock cycle,  $f$

- Multi-Input Gates

- same DC component as inverter,  $P_{DC} = V_{DD}I_{DDQ}$

- for dynamic power, need to estimate "activity" of the gate, how often will the output be switching

- $P_{dyn} = aC_{out}V_{DD}^2f$ ,  $a = \text{activity coefficient}$

NOR    NAND

- estimate activity from truth table

- $a = p_0p_1$

- $p_0$  = prob. output is at 0

- $p_1$  = prob. of transition to 1

A	B	$\overline{A+B}$	$\overline{A \cdot B}$
0	0	1	1
0	1	0	1
1	0	0	1
1	1	0	0

$p_0=0.75$

$p_1=0.25$

$a=3/16$

$p_0=0.25$


$p_1=0.75$

$a=3/16$


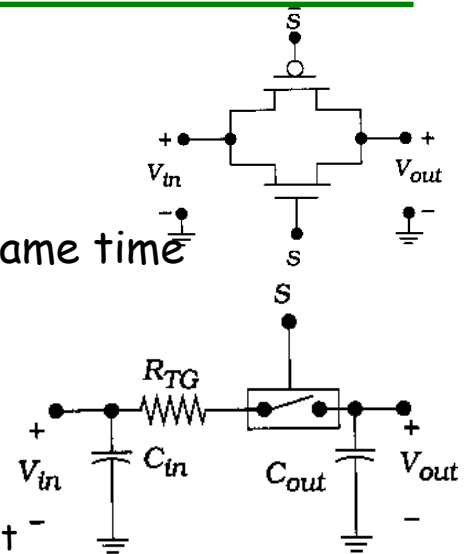
## Timing Analysis of Transmission Gates

- TG = parallel nMOS and pMOS
- RC Model
  - in general, only one tx active at same time
    - nMOS pulls output low
    - pMOS pushes output high
  - $R_{TG} = \max(R_n, R_p)$
  - $C_{in} = C_{Sn} + C_{Dp}$ 
    - if output at higher voltage than input
  - larger  $W$  will decrease  $R$  but increase  $C_{in}$
- Note: no connections to VDD-Ground. Input signal,  $V_{in}$ , must drive TG output; TG just adds extra delay




## Pass Transistor



- Single nMOS or pMOS tx
- Often used in place of TGs
  - less area and wiring
  - can't pull to both VDD and Ground
  - typically use nMOS for better speed

- Rise and Fall Times

- $\tau_n = R_n C_{out}$

 


- $t_f = 2.94 \tau_n$

  

- $t_r = 18 \tau_n$

- much slower than fall time

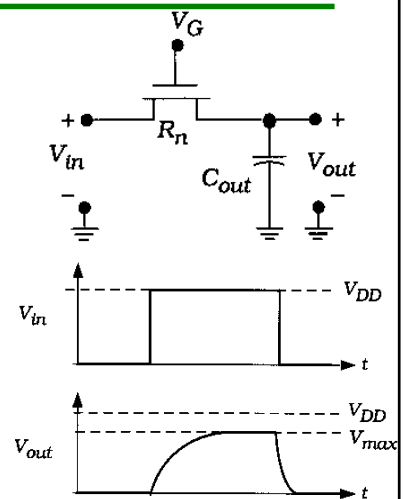

- nMOS can't pull output to VDD
  - rise time suffers from threshold loss in nMOS

