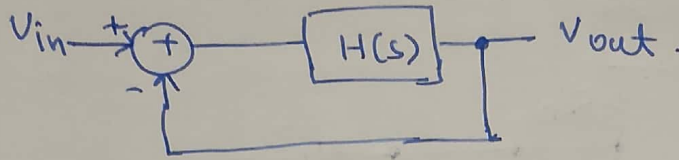


OSCILLATORS

①



* In the above feedback system, where feedback factor, $\beta = 1$, if the amplifier experiences so much phase-shift at high frequencies that the overall feedback becomes positive, then oscillation may occur.

Note:- Oscillation may occur at any β . However, as you know oscillation may occur better as $\beta \rightarrow 1$. \Rightarrow Remember phase-margin reduces as $\beta \rightarrow 1$.

*
$$\frac{V_{out}}{V_{in}}(s) = \frac{H(s)}{1 + H(s)}$$


Barkhausen Criteria for oscillation :-

$$|H(j\omega_0)| \geq 1$$

$$\angle H(j\omega_0) = 180^\circ$$

\Rightarrow At ω_0 forward path gives a phase-shift of 180° and then the negative feedback, i.e., summing node gives another 180° phase-shift. \Rightarrow overall 360° phase-shift in the loop results in positive-feedback or oscillation.

Various Views Of Feedback System :-

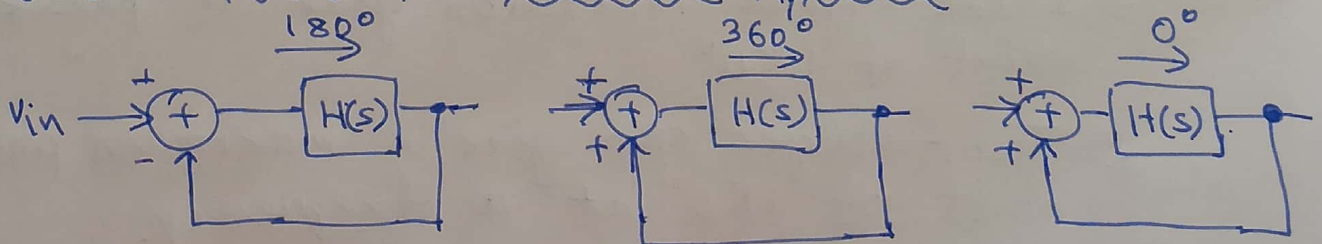


* The above mentioned phase-shifts are happening at the oscillation frequency, ω_0 .

* The summing node gives DC phase-shift.

② RING OSCILLATORS :-

*

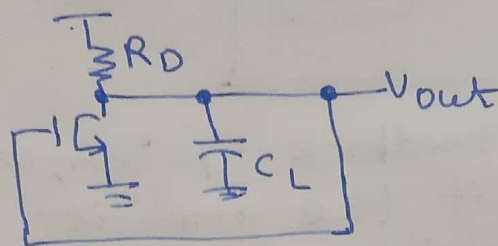


The above single-stage CS amplifier has ~~an~~ negative feedback at DC. ~~why~~ Can it oscillate.

- * Note:- For oscillation to occur we need
- DC phase-shift of 180° . i.e. negative feedback.
 - Frequency dependent phase-shift of 180° .

* The maximum frequency dependent phase-shift that single-stage CS amplifier can give is 90° at ∞ frequency.

⇒ No oscillation.

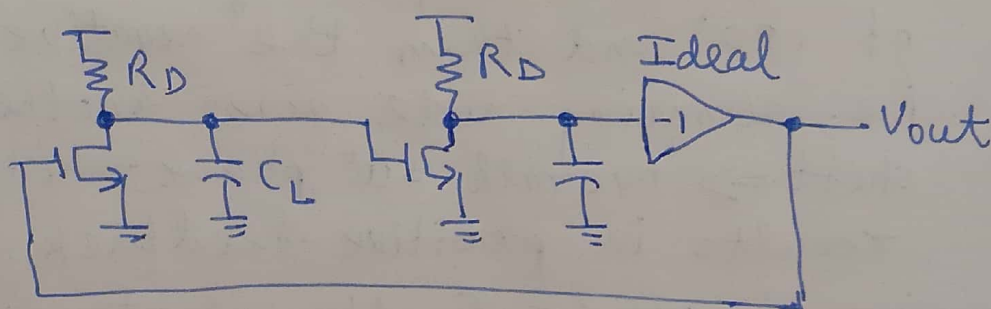- * How about two-stage CS-amplifier in negative-feedback?




⇒ Ideal signal inversion give DC phase shift of 180°

⇒ Two-stages can give a maximum phase-shift of 180° at ∞ frequency.

⇒ No Oscillation

* How about 3-stage CS-amplifier??

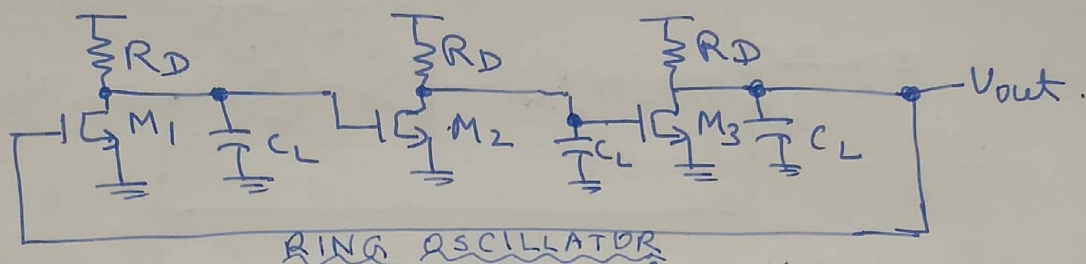

Note: - All stages are decoupled. Hence,

$$H(s) = - \frac{A_0^3}{\left(1 + \frac{s}{\omega_0}\right)^3}$$

where, $A_0 = -g_m R_D$.

At ω_{osc} the phase-shift is $180^\circ \Rightarrow$ each stage gives a phase-shift of 60° . Thus,

$$\tan^{-1}\left(\frac{\omega_{osc}}{\omega_0}\right) = 60^\circ$$

$$\Rightarrow \omega_{osc} = \sqrt{3} \omega_0.$$

Thus, minimum DC gain A_0 required is,

$$\frac{A_0^3}{\left[\sqrt{1 + \left(\frac{\omega_{osc}}{\omega_0}\right)^2}\right]^3} = 1.$$

$$\Rightarrow A_0 = 2.$$

But we want loop gain $\geq 1 \Rightarrow A_0 > 2$.


* If loop-gain = 1 is sufficient for oscillation at ω_{osc} why do we say loop-gain > 1 .

\Rightarrow In order to make sure oscillation is sustained as temperature, ~~and~~ voltage, and process (PVT) change.

\Rightarrow Remember gain is a function of temp., voltage, and process. Why??

\Rightarrow Isn't g_m PVT dependent??

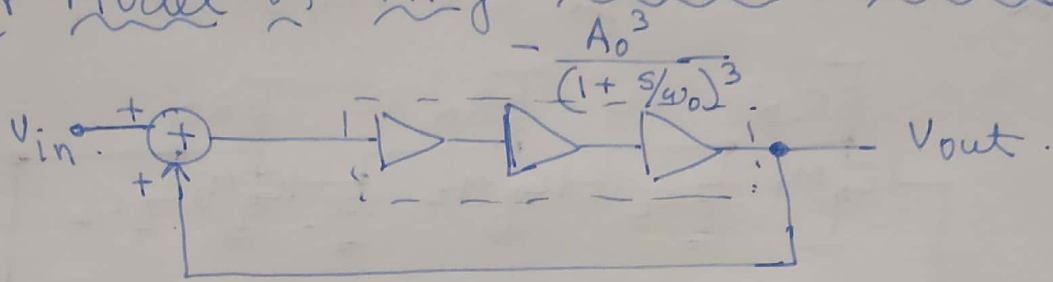④ Linear Model of Ring Oscillator (3-stage)



If $A_0 < 2 \Rightarrow$ no oscillation.

Now,

$$\frac{V_{out}}{V_{in}}(s) = \frac{-A_0^3 / (1 + \frac{s}{\omega_0})^3}{1 + \frac{A_0^3}{(1 + \frac{s}{\omega_0})^3}}$$

$$\Rightarrow \frac{V_{out}}{V_{in}}(s) = \frac{-A_0^3}{(1 + \frac{s}{\omega_0})^3 + A_0^3}$$


The denominator can be expanded as,

$$\left(1 + \frac{s}{\omega_0}\right)^3 + A_0^3 = \left(1 + \frac{s}{\omega_0} + A_0\right) \left[\left(1 + \frac{s}{\omega_0}\right)^2 - \left(1 + \frac{s}{\omega_0}\right)A_0 + A_0^2\right]$$


The 3-poles are,

$$s_1 = (-A_0 - 1)\omega_0$$

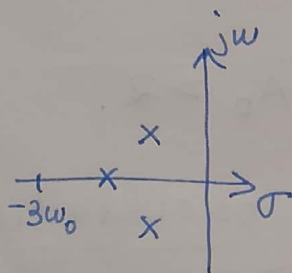
$$s_{2,3} = \left[\frac{A_0(1 \pm j\sqrt{3})}{2} - 1 \right] \omega_0$$



$0 < A_0 < 2$

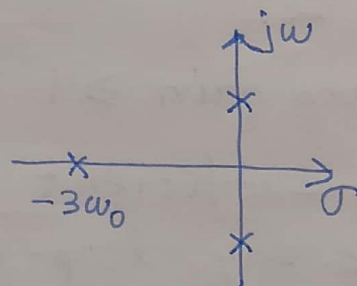

$A_0 = 2$

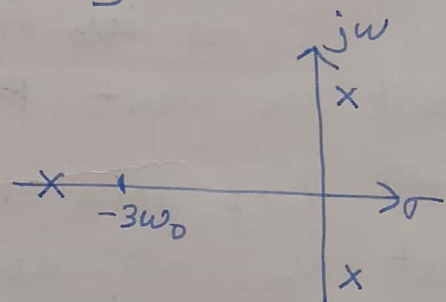

$A_0 > 2$

* The pole, s_1 , gives a decaying exponential which can be ignored as it would eventually die out.


* Thus, neglecting the effect of s_1 , we can express the output waveform as,

$$V_{out} = a \exp\left[\frac{A_0 - 2}{2} \omega_0 t\right] \cdot \cos\left[\frac{A_0}{2} \sqrt{3} \omega_0 t\right]$$

* If $A_0 > 0 \Rightarrow V_{out}$ tends to $\infty \Rightarrow$ but is limited by supply voltage.

* If $A_0 = 2 \Rightarrow$ oscillation sustains.

LC OSCILLATORS:-

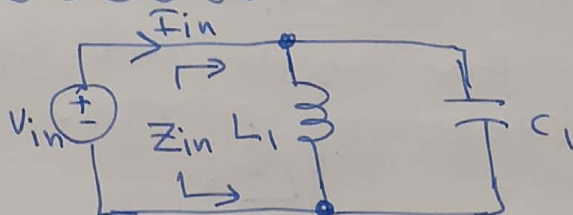



Here,

$$Z_{in} = (L_1 s) \parallel \left(\frac{1}{s C_1}\right)$$

$$\Rightarrow Z_{in} = \frac{j L_1 \omega}{1 - L_1 C_1 \omega^2}$$

$\Rightarrow Z_{in} \rightarrow \infty$ at $\omega_1 = \frac{1}{\sqrt{L_1 C_1}}$ = resonance frequency.

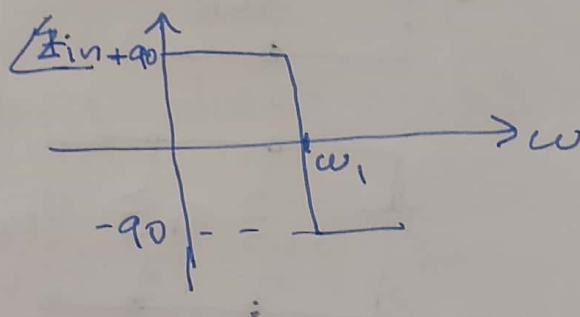
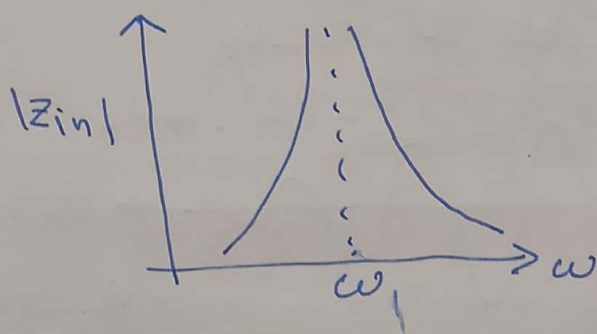
$\Rightarrow V_{in}$ does not supply any current.



* It is difficult to get $Z_{in} = \infty$ at ω_1 , as ~~wires have~~ inductors have finite resistance, resulting in a lossy tank.

why is a parallel LC circuit called an LC-tank??







6

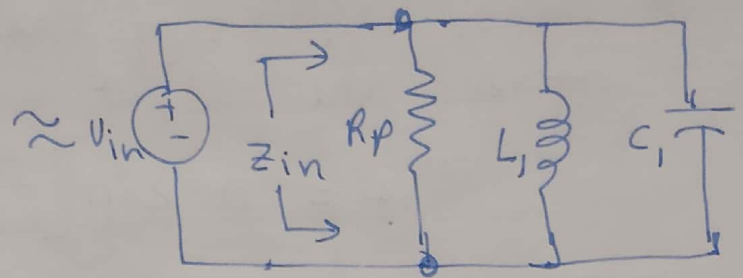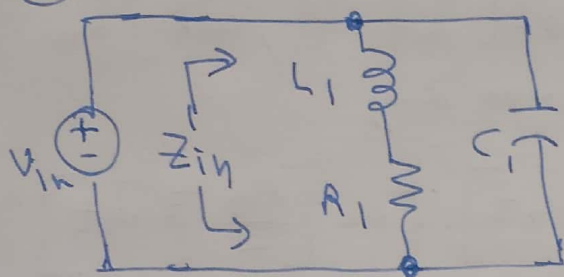

if, $R_p = \frac{L_1^2 \omega^2}{R_1}$ around the resonant frequency.

* How do you obtain that??

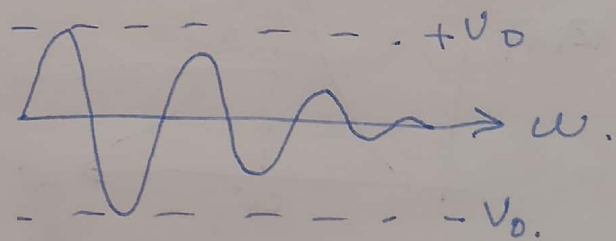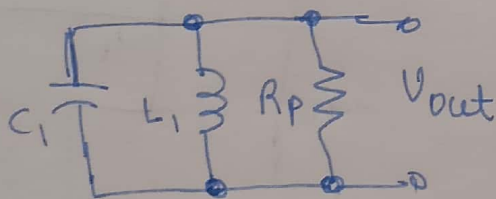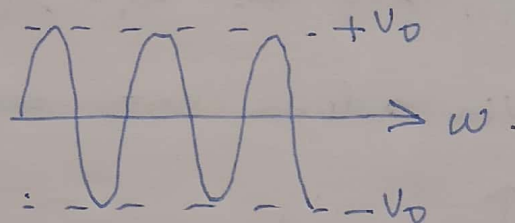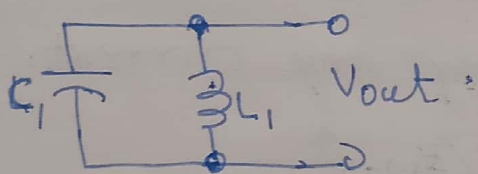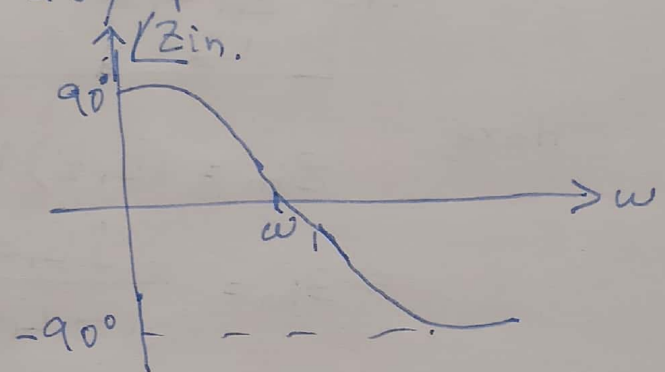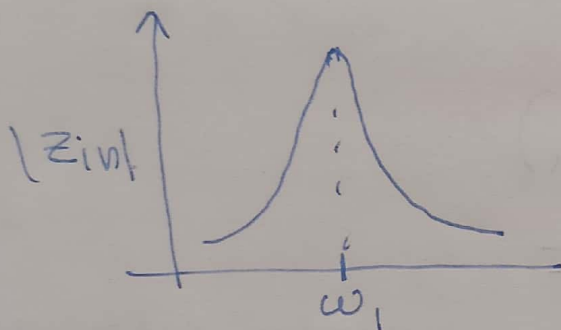
=> Write Z_{in} for both and equate real and imaginary parts.





Time-Domain Behavior

CROSS-COUPLED OSCILLATOR :-

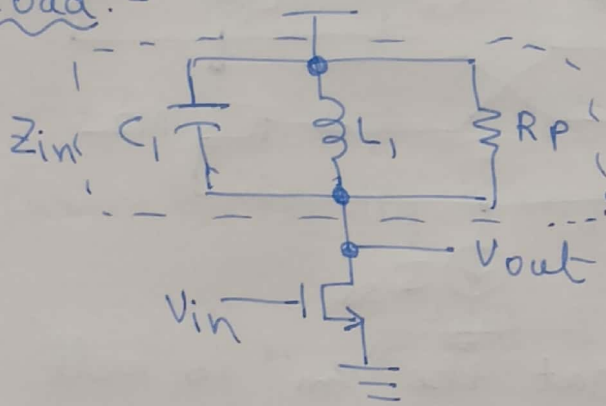Common-Source Amplifier with LC-tank Load :-


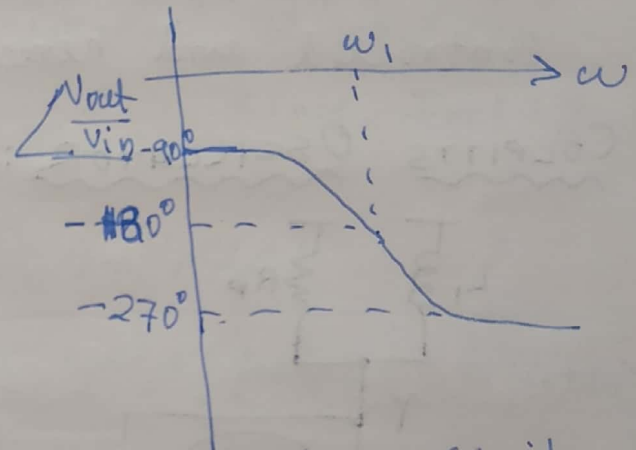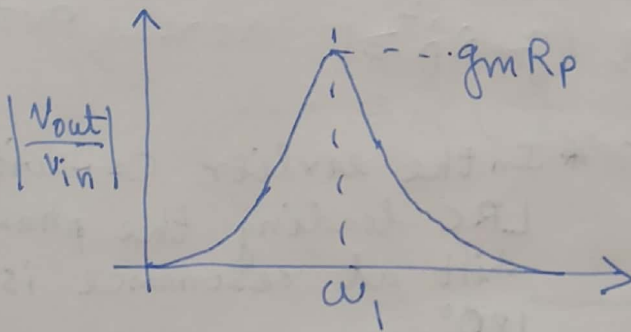
$$\frac{V_{out}}{V_{in}} = -g_m Z_{in}(s)$$




*If we connect output to input will it oscillate.

=> DC phase-shift of 180°

=> Frequency dependent phase shift of -90°

=> total phase-shift of 270° .

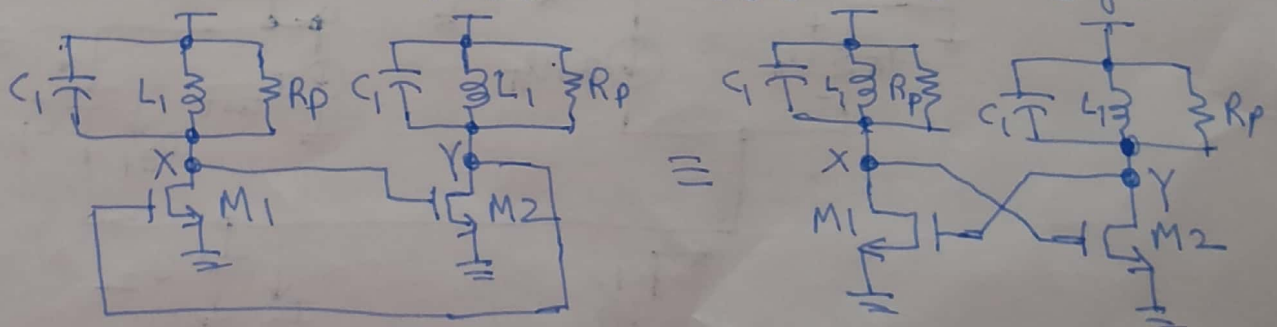
*To make it oscillate connect two stages:-



$$\text{Here, } (g_m R_p)^2 > 1$$


$$\text{or, } (g_m (R_p || r_o))^2 > 1$$

⑧ A better design is as follows:-

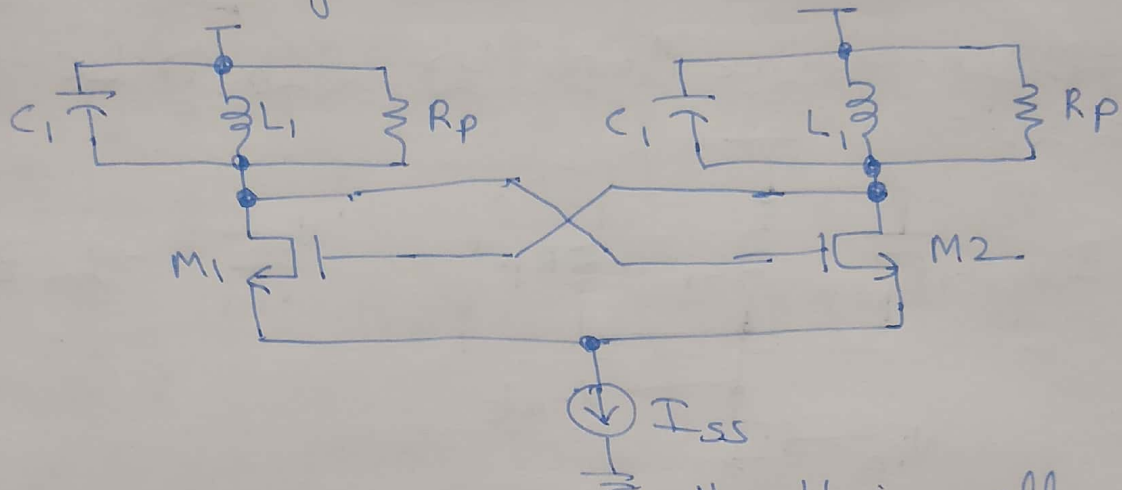

which makes sure that the " g_m " is well controlled and hence, $(g_m R_p)^2 \geq 1$ across PVT.

COLPITTS OSCILLATOR :-

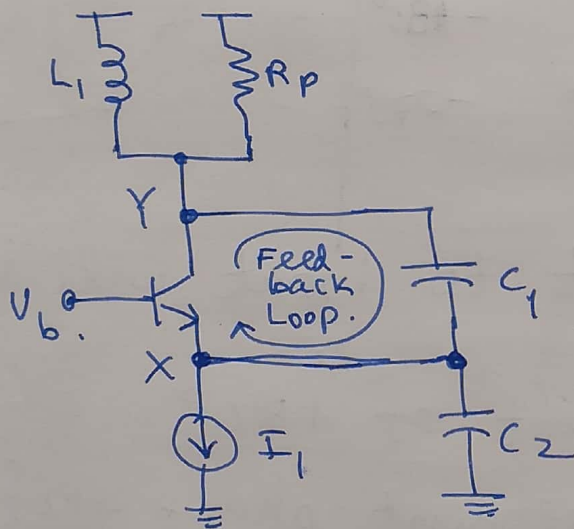


* In the earlier CS - with LRC loading the phase-shift at resonance is 180° .

* However, for oscillation we need total phase shift of 360° at the oscillation frequency.

* Can we instead realize a CB topology to get oscillation.

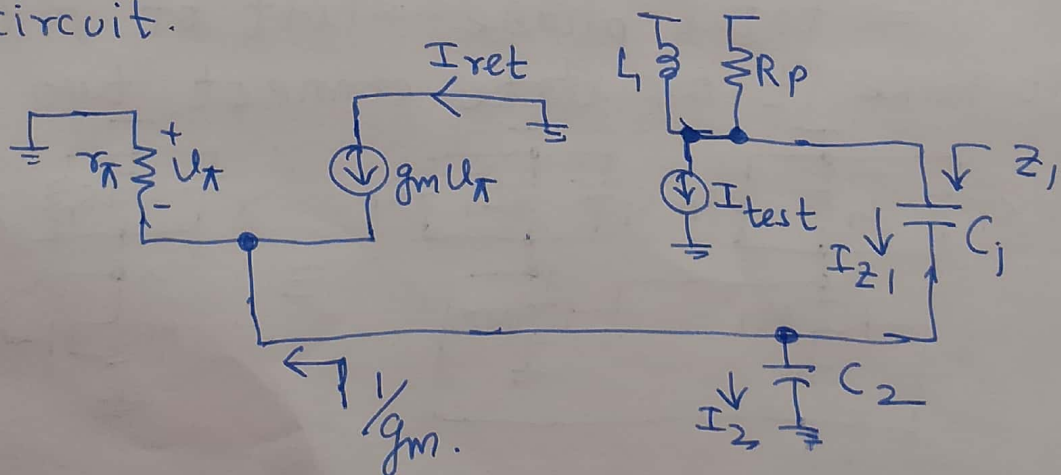Lets, break the loop at Y and analyze the small signal circuit.



(9)
 * Ignoring early effect, we need to make sure that I_{ret}/I_{test} must exhibit a $\geq 60^\circ$ phase-shift and at least unity gain at oscillation frequency.

$$* Z_1 = \frac{1}{C_1 s} + \left(\frac{1}{g_m} \parallel \frac{1}{C_2 s} \right) = \frac{1}{C_1 s} + \frac{1}{C_2 s + g_m}$$

* Current flowing through C_1 is equal to:-

$$I_{Z_1} = -I_{test} \frac{\frac{L_1 R_p s}{L_1 s + R_p}}{\frac{L_1 R_p s}{L_1 s + R_p} + \frac{1}{C_1 s} + \frac{1}{C_2 s + g_m}}$$

Thus, $V_x = I_{Z_1} \left(\frac{1}{s C_2} + \frac{1}{g_m} \right)$. Since, $I_{ret} = g_m V_x$,

we obtain,

$$\frac{I_{ret}}{I_{test}} = \frac{g_m R_p C_1 s^2}{L_1 C_1 C_2 R_p s^3 + [g_m R_p L_1 + L_1 (C_1 + C_2)] s^2 + [g_m L_1 + R_p (C_1 + C_2)] s + g_m R_p}$$

* Loop-gain should be unity, so we set the gain function to unity. ~~The~~ Thus,

$$\frac{I_{ret}}{I_{test}} = \frac{g_m R_p C_1 s^2}{L_1 C_1 C_2 R_p s^3 + [g_m R_p L_1 + L_1 (C_1 + C_2)] s^2 + [g_m L_1 + R_p (C_1 + C_2)] s + g_m R_p}$$

$$L_1 C_1 C_2 R_p s^3 + L_1 (C_1 + C_2) s^2 + [g_m L_1 + R_p (C_1 + C_2)] s + g_m R_p = 0$$

At oscillation frequency both real & imaginary part of above equation should go to "0". Hence,

$$-L_1 (C_1 + C_2) \omega_1^2 + g_m R_p = 0$$

$$\text{and, } -L_1 [C_1 C_2 R_p] \omega_1^3 + [g_m L_1 + R_p (C_1 + C_2)] \omega_1 = 0$$

(10)

Hence,

$$\omega_1^2 = \frac{C_1 + C_2}{C_1 C_2 L_1} + \frac{g_m}{R_p C_1 C_2}$$

Neglecting the 2nd term above we get,

$$\omega_1 = \sqrt{\frac{1}{L_1 \frac{C_1 C_2}{C_1 + C_2}}}$$


* Using the above equation in ~~the~~ resonance we obtain,

$$g_m R_p = \frac{(C_1 + C_2)^2}{C_1 C_2}$$

$$\Rightarrow g_m R_p = \frac{C_2}{C_1} \left[1 + \frac{C_1}{C_2} \right]^2$$


The above is minimum if $C_2/C_1 = 1$. Hence,

$$g_m R_p \geq 4.$$

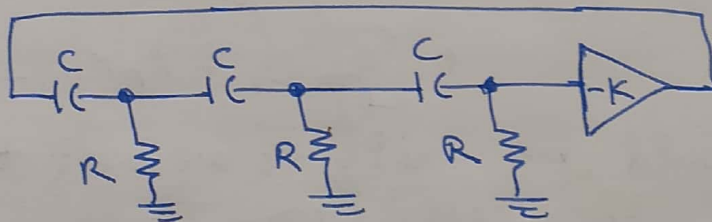~~CR~~CR-Phase SHIFT OSCILLATOR :-

* The above is a CR-phase-shift oscillator which incorporates a phase-shifting network.

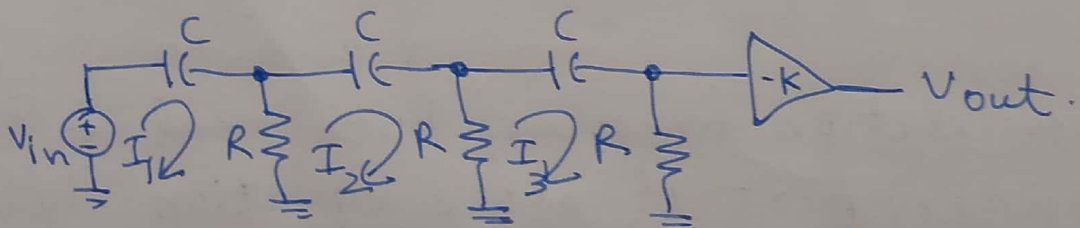* In order to analyze the above circuit we break the loop and find the loop-gain as follows.



Applying KVL in the first three loops we get,

$$I_1 \left(R + \frac{1}{sC} \right) - I_2 R = V_{in} \dots \textcircled{1}$$

$$-I_1 R + I_2 \left(2R + \frac{1}{sC} \right) - I_3 R = 0 \dots \textcircled{2}$$

and, $-I_2 R + I_3 \left(2R + \frac{1}{sC}\right) = 0 \dots \dots \textcircled{3}$

Also, $V_{out} = -K I_3 R \dots \dots \textcircled{4}$

Loop-gain, $A\beta = \frac{V_{out}}{V_{in}} = \frac{-K}{(1 - 5\alpha^2) + j(\alpha^3 - 6\alpha)}$

where, $\alpha = \frac{1}{\omega RC}$

Since loop-gain is a real quantity,

$$\alpha^3 - 6\alpha = 0$$
$$\Rightarrow \alpha = \sqrt{6}$$

$$\Rightarrow \omega_0 = \frac{1}{RC\sqrt{6}}$$


$$\Rightarrow f_0 = \frac{1}{2\pi RC\sqrt{6}}$$

At this frequency loop-gain should be ≥ 1 .


Thus, $|A\beta| = \frac{K}{29} > 1$

$$\Rightarrow K > 29$$

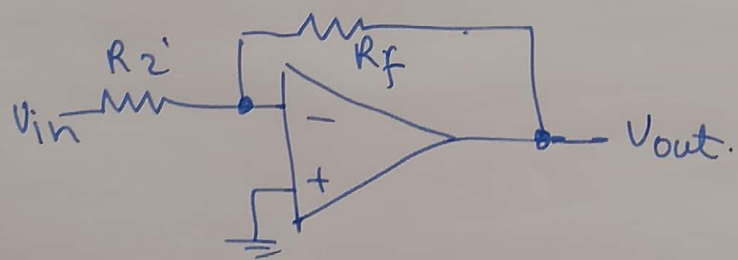The gain K can be realized as follows using op-amp.



Thus, the overall circuit is,

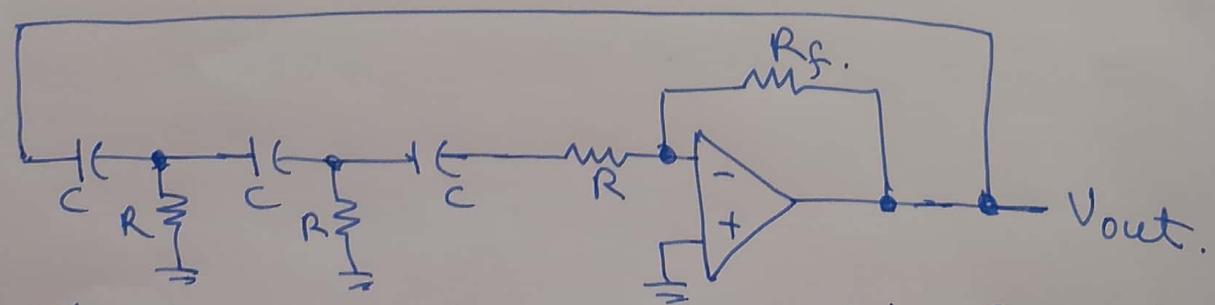

Note:- The last resistor is absorbed in R_i . Why??