
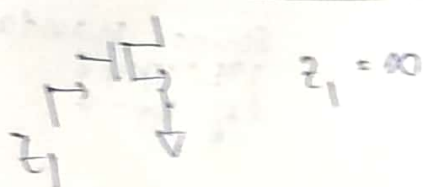


2. i)


Sounak Mandal
19EE10088
Page No - 5

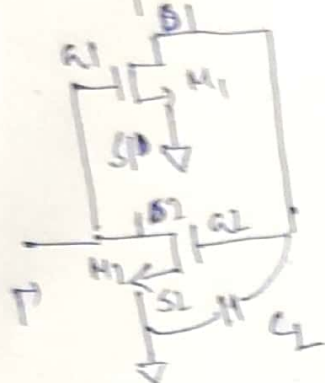


Ac eq circuit



small signal

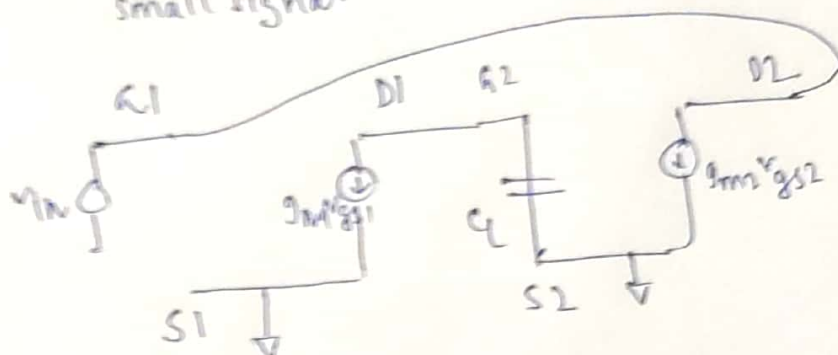

or

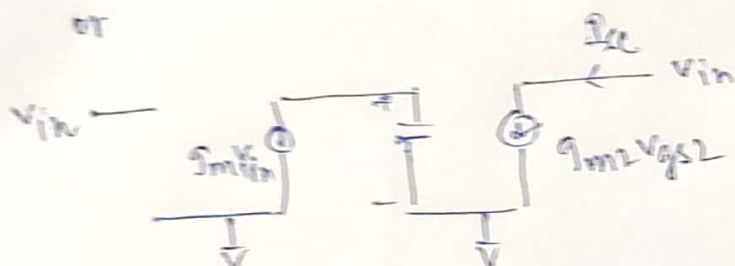

$$V_{gs2} = \frac{g_{m1} V_{in}}{s C_L}$$

$\therefore g_{m1}$

$$I_{sc} = g_{m2} V_{gs2}$$

$$I_{sc} = g_{m2} \times \frac{g_{m1} V_{in}}{s C_L}$$

$$Z_{in} = \frac{V_{in}}{I_{sc}} = \frac{s C_L}{g_{m1} g_{m2}} \text{ (Ans)}$$

$$\text{or } \frac{I_{sc}}{V_{in}} = \frac{g_{m1} g_{m2}}{s C_L}$$

The two transistors come in series as seen from the small signal equivalent along with C_L connected between gate and source of M_2 . Hence such an expression is obtained