
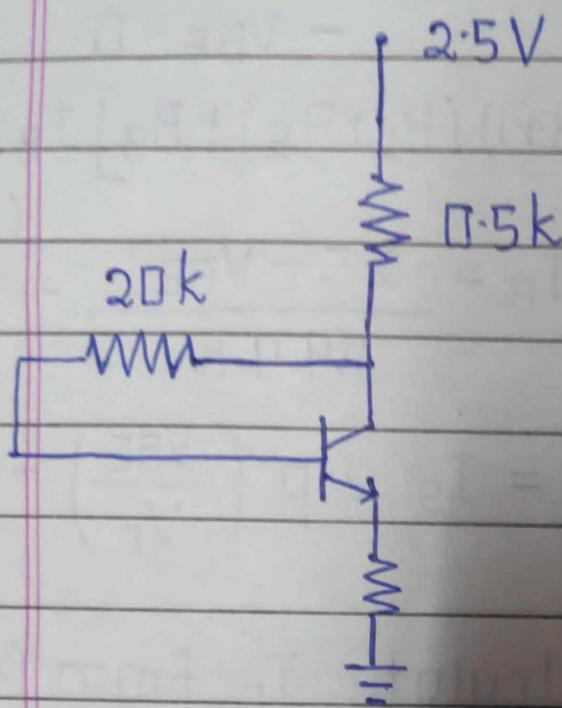


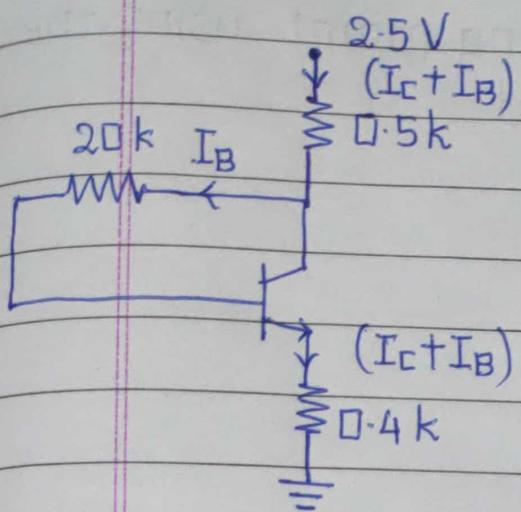Q.1. Given $I_s = 6 \times 10^{-16} A$, $\beta = 10$, $V_{th} = 0.026 V$
calculate the DC operating point using the two approaches discussed.



Solⁿ: Approach 1:



Applying KVL,

$$V_{CC} - (I_E + I_B)(R_E + R_B) - I_B R_B - V_{BE} = 0$$

$$[(\beta + 1)(R_E + R_B) + R_B] I_B = V_{CC} - V_{BE}$$

$$\therefore I_B = \frac{2.5 - V_{BE}}{29.9 \text{ k}} \quad (\because I_E = \beta I_B) \quad \text{--- (1)}$$

$$I_E = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \quad \text{--- (2)}$$

(1) Assume $V_{BE} = 0.7 \text{ V}$, calculate I_E from (2)

$$I_E = 295.59 \mu\text{A}$$

$$(2) \therefore I_B = \frac{I_E}{\beta} = 29.559 \mu\text{A}$$

(3) Recalculate V_{BE} from (1)

$$V_{BE} = 1.616 \text{ V}$$

which diverges greatly from the assumed value

Approach 2:

By KVL, we get $I_B = \frac{2.5 - V_{BE}}{29.9 \text{ k}}$

$$I_E = \beta I_B = 10 \frac{2.5 - V_{BE}}{29.9 \text{ k}} \quad \text{--- (3)}$$

$$V_{BE} = V_T \ln\left(\frac{I_E}{I_S}\right) = 0.026 \ln\left(\frac{I_E}{6 \times 10^{-16}}\right) \quad \text{--- (4)}$$

Assume $V_{BE} = 0.7 \text{ V}$, calculate I_E

$$I_E = 502 \mu\text{A}$$

Using eqⁿ (4), recalculate V_{BE} ($V_{BE} = 0.718 \text{ V}$)

Again calculate I_E

$$I_E = 595.99 \mu A$$

Repeat the steps until convergence.

Finally,

$$V_{BE} = 0.718 V, I_E = 595.99 \mu A$$

Q.2 (i) Calculate the operating pt. (values of V_{BE} and I_c) for the two circuits given below.

Assume $\beta = 100$ and $I_s = 10^{-17} \text{ A}$. Also $V_{th} = 0.026 \text{ V}$

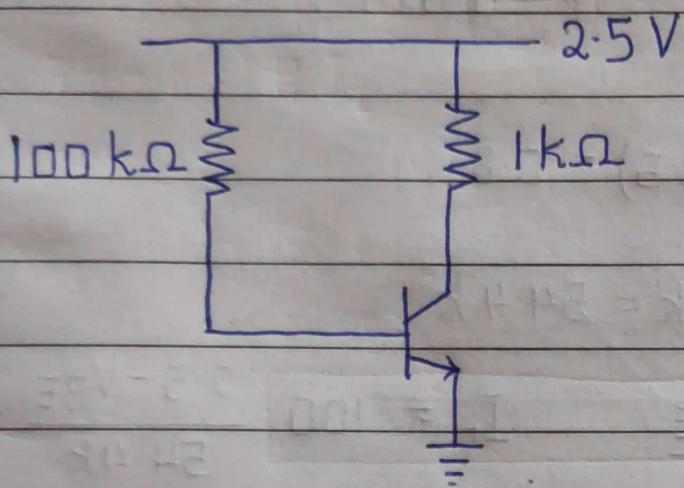


Fig (1) : Simple Biasing


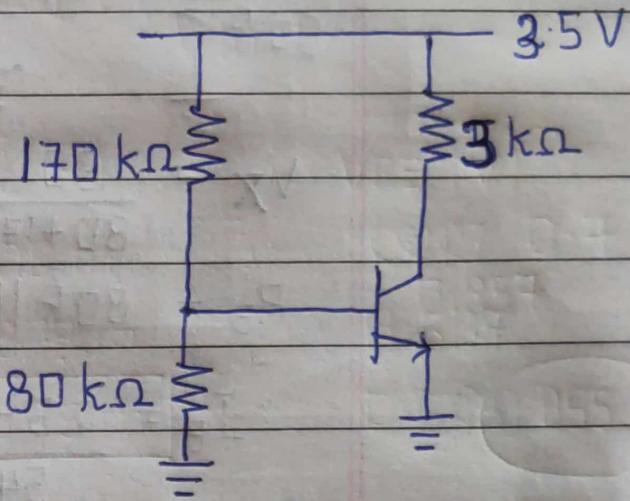


Fig. (2) : Resistive Divider Biasing

- (ii) Now, if the supply voltage decreases by 10%, find the operating point.
- (iii) If the supply voltage increases by 10% from the original value, again calculate the operating point

Soln:

For simple biasing circuit,

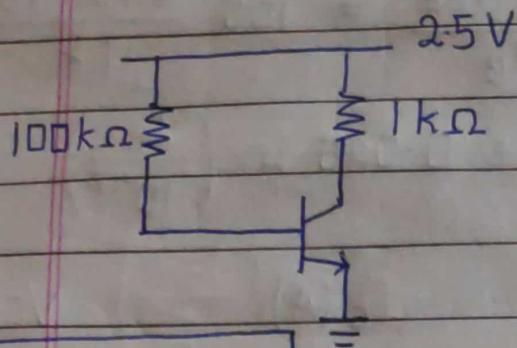

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{2.5 - V_{BE}}{100k}$$

$$I_E = \beta I_B = 100 \frac{2.5 - V_{BE}}{100k} \quad \text{--- (1)}$$

$$\boxed{V_{CE} = V_{CC} - I_E R_C \\ = 2.5 - (1k) I_E}$$

$$V_{BE} = V_T \ln\left(\frac{I_E}{I_S}\right)$$

$$V_{BE} = 0.026 \ln\left(\frac{I_E}{10^{-17}}\right) \quad \text{--- (2)}$$

(i) For $V_{CE} = 2.5V$, assume $V_{BE} = 0.7V$ initially

$V_{BE} (V)$	$I_E (A)$	$V_{CE} (V)$
0.7	1.8mA	0.7
0.853	1.647mA	0.853
<u>0.851</u>	<u>1.649mA</u>	<u>0.851</u>

(i) Assume $V_{BE} = 0.7V$ initially, calculate I_E from (1)

$$I_E = 1.8 \text{ mA}$$

(2) Now substituting $I_E = 1.8 \text{ mA}$ in (2), calculate V_{BE}

$$(3) V_{BE} = 0.853 \text{ V}$$

Repeat the steps until V_{BE} converges.

(ii) For $V_{CC} = 0.9 \times 2.5 = 2.25V$,

$$I_E = \beta I_B = 100 \frac{2.25 - V_{BE}}{100k}$$

$$V_{BE} = 0.026 \ln\left(\frac{I_E}{10^{-17}}\right)$$

$$V_{CE} = 2.25 - (1k) I_E$$

$V_{BE} (V)$	$I_E (A)$	$V_{CE} (V)$
0.7	1.55mA	0.7
0.85	1.4mA	0.85
<u>0.847</u>	<u>1.403mA</u>	<u>0.847</u>

(iii) For $V_{CC} = 2.75 \text{ V}$ ($1.1 \times 2.5 = 2.75 \text{ V}$)

$$I_E = \beta I_B = \beta \frac{V_{CC} - V_{BE}}{R_B} = 100 \frac{2.75 - V_{BE}}{1k}$$

$$V_{BE} = V_T \ln \left(\frac{I_E}{I_S} \right) = 0.026 \ln \left(\frac{I_E}{10^{-17}} \right)$$

$$V_{CE} = 2.75 - (1k) I_E$$

V_{BE} (V)

0.7

0.857

0.855

I_E (A)

2.05 m

1.893 m

1.895 m


V_{CE} (V)

0.405 0.7

0.607 0.857

0.605 0.855

(i) For resistive divider biasing,

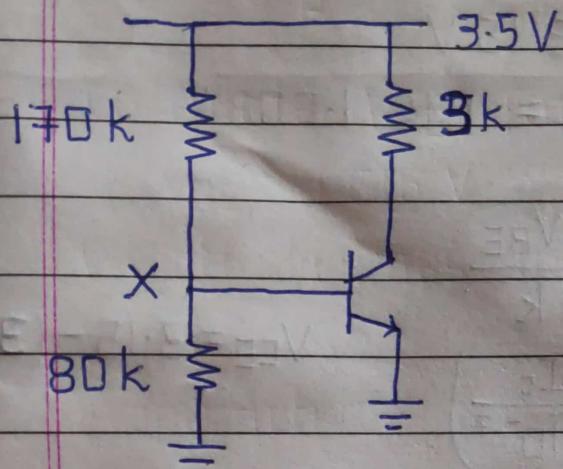

$$V_x = \frac{80}{80+170} (3.5) = 1.12V$$

$$R_{\text{Thev}} = 170k \parallel 80k = 54.4k\Omega$$

$$I_B = \frac{V_x - V_{BE}}{R_{\text{Thev}}} = \frac{1.12 - V_{BE}}{54.4k}$$

$$I_C = \beta I_B = 100 \frac{1.12 - V_{BE}}{54.4k} \quad \text{--- (3)}$$

$$V_{BE} = 0.025 \ln \left(\frac{I_c}{I_s} \right)$$

$$= 0.025 \ln \left(\frac{I_c}{10^{-17}} \right) \quad \text{--- (4)}$$

$$V_{EE} = V_{EE} - I_C R_E = 3.5 - (3k) I_C \quad \text{--- (5)}$$

Follow the same procedure as for simple biasing

(ii) For $V_{CE} = 0.9 \times 3.5 = 3.15 V$

$$V_x = \frac{80}{80+170} (3.15) = 1.008 V$$

$$\therefore I_E = 100 \frac{1.008 - V_{BE}}{54.4 k}$$

$$V_{BE} = 0.026 \ln \left(\frac{I_c}{10^{-17}} \right)$$

$$V_{CE} = 3.15 - (3k) I_E$$

V_{BE} (V)

0.7

0.823

0.81

0.812

I_E (A)

566.18 μ A

340.07 μ A

363.97 μ A

360.29 μ A

V_{CE} (V)

13.49

2.064

(iii) For $V_{CC} = 1.1 \times 3.5 = 3.85 V$

$$V_x = \frac{80}{80+170} (3.85) = 1.232 V$$

$$\therefore I_E = \beta \frac{V_x - V_{BE}}{R_B} = 100 \frac{1.232 - V_{BE}}{54.4 k}$$

$$V_{BE} = V_T \ln \left(\frac{I_E}{I_S} \right) = 0.025 \ln \left(\frac{I_E}{10^{-17}} \right)$$

$$V_{CE} = 3.85 - (3k) I_E$$

$$V_{BE} (V)$$

$$0.7$$

$$0.838$$

$$0.83$$

$$I_E (A)$$

$$977.94 \mu$$

$$724.26 \mu$$


$$738.97 \mu$$

$$V_{CE} (V)$$

$$\cancel{0.155}$$

$$1.633$$

Q.

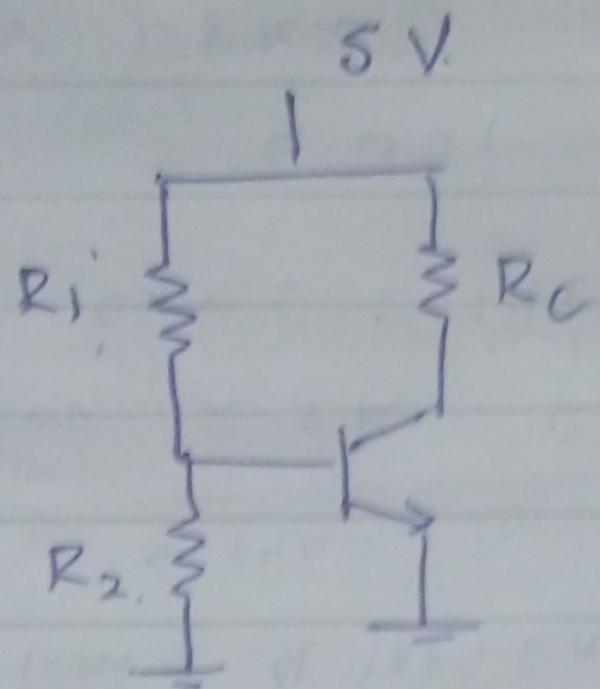

$$Given I_S = 5 \times 10^{-15} A$$

$$\beta = 100$$

$$V_{TH} = 26 mV$$

→ Iterate V_{BE} for stable value starting 0.7V

Find the changes in bias point when

resistance variation of R_2 becomes $1.2R_2$

Take $R_1 = 6.38 k\Omega$, $R_2 = 1.2k\Omega$, $R_C = 1k\Omega$.

$$R_1 = 13.944 k\Omega, R_2 = 2.5 k\Omega$$

Sol: Draw Chevenin's equivalent

$$V_{th} = \frac{V_{cc} \cdot R_2}{R_1 + R_2}$$

$$= \frac{5 \times 8.12}{1.2 + 8.38} = \frac{40.6}{9.6} = 0.7626$$

$$= \frac{5 \times 2.5}{2.5 + 13.944} = 0.760 \text{ V.}$$

$$R_{th} = R_1 \parallel R_2 = \underline{2.12 \text{ k}\Omega}$$

Now find / check for stable V_{BE} , I_c points assuming active mode of operation.

We know,

$$V_{th} = I_B R_{th} + V_{BE} \quad \text{--- (a)}$$

$$\text{Also, } I_B \times \beta = I_c$$

$$I_c = I_s \cdot e^{(V_{BE}/V_T)}$$

$$\text{For, } V_{BE} = 0.7 \text{ V.}, \quad I_c = 2.463 \text{ mA.} \quad \text{--- (1)}$$


$$\text{here } I_B = I_c/\beta = 24.6 \mu\text{A.}$$

Use it in (a),

$$V_{BE} = V_{th} - I_B R_{th} = 0.76 - 24.6 \mu\text{A} \times 2.12 \\ = 0.707 \text{ V.}$$

$$I_c = 5 \times 10^{-15} \times e^{0.707/0.026}$$

$$= 3.22 \text{ mA}$$

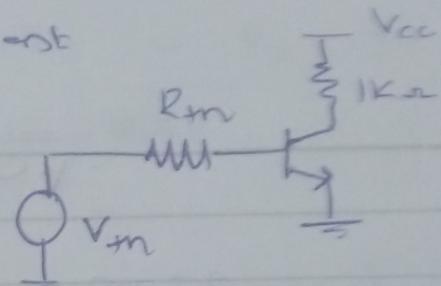

V_{BE} on further iterations can be seen to be stable.

Thus the bias points I_C , V_{CE} calculated,

$$I_C = \underline{3.22 \text{ mA}},$$

$$V_{CE} = V_{CC} - I_C R_C = 5 - 3.22 \text{ mA} \times 1 \text{ k} \\ \Rightarrow 1.78 \text{ V.}$$

=====

2.6 kΩ

$$= 0.707V.$$

Changes R_2 to $1.015R_2$ (1.5%) = $3.5375k\Omega$

$$I_C = I_S e^{V_{BE}/V_T} = 2.463mA$$

$$I_B = 24.6\mu A \quad (\text{using } V_{BE} = 0.7V)$$

Here $R_1 = 13.944k\Omega \Rightarrow R_{th} = \underline{\underline{2.146k\Omega}}$.

$$V_{th} = \underline{\underline{0.77V}}.$$

$$V_{BE} = \underline{\underline{0.717V}}$$

$$I_C = 4.733mA \Rightarrow V_{CE} = V_{CC} - I_C R_C \\ = \underline{\underline{0.27V}}$$

$$V_{TH} = 2.5 \times \frac{10}{25} = 1 \text{ V.}$$

$$R_{TH} = 6 \text{ k}\Omega$$

$$I_c = \beta \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1) R_E}$$

$$V_{BE} (\text{v})$$

$$0.8$$

$$0.78$$

$$0.783$$

$$I_c (\text{mA})$$

$$0.55$$


$$0.606$$

$$0.59$$

$$I_c = 0.59 \text{ mA}$$


$$V_C = 2.5 - (0.59 \times 2)$$

$$V_C = 1.32 \text{ V}$$

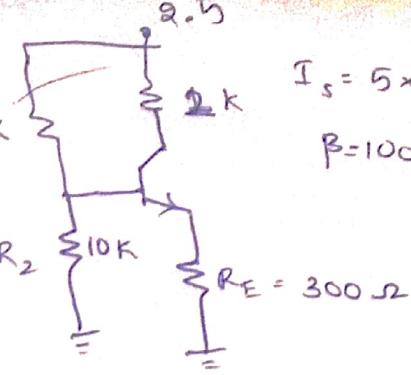

$$I_s = 5 \times 10^{-17} \text{ A}$$

$$\beta = 100$$

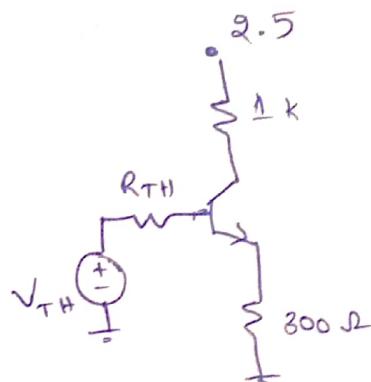

Case (i) change supply voltage by +5% = $2.5 + (2.5 \times 0.05)$
 $= 2.625 \text{ V.}$

$$\therefore V_{TH} = 2.625 \times \frac{10}{25} = 1.05 \text{ V.}$$

V_x changed by 50 mV.

$$V_{BE} (\text{v}) \quad I_c (\text{mA})$$

$$0.8$$

$$0.68$$

$$0.788$$

$$0.72$$

$$0.787$$

$$0.72 \Rightarrow$$

$$I_c = 0.72 \text{ mA}$$

$$\therefore V_C = 2.5 - (0.72 \times 2) = V_C = 1.06 \text{ V.}$$

(ii) Change V_{cc} by -5%

$$V_{cc} = 2.5 - (2.5 \times 0.05) = 2.375$$

$$V_{TH} = 950 \text{ mV}$$

$$V_{BE}$$

$$I_c$$


$$0.8$$

$$0.777$$


$$0.47 \text{ mA}$$

$$V_c = 2.5 - (0.47 \times 2) = 1.56 \text{ V}$$

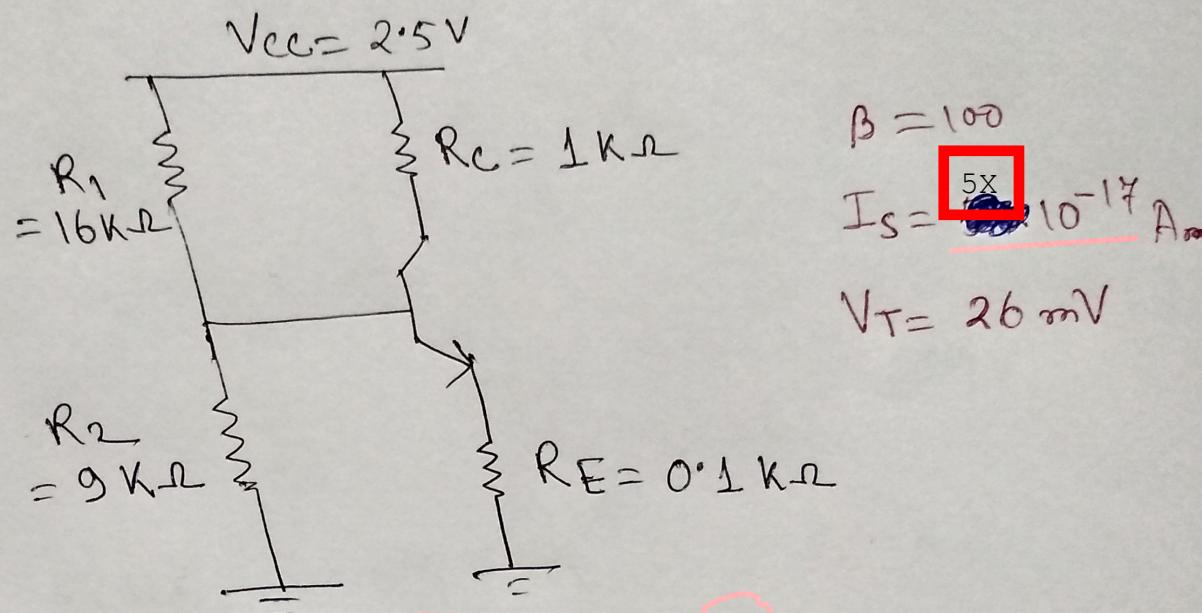Q. Show that the following resistor divider circuit with emitter resistor is very robust and not very sensitive to resistor variation.



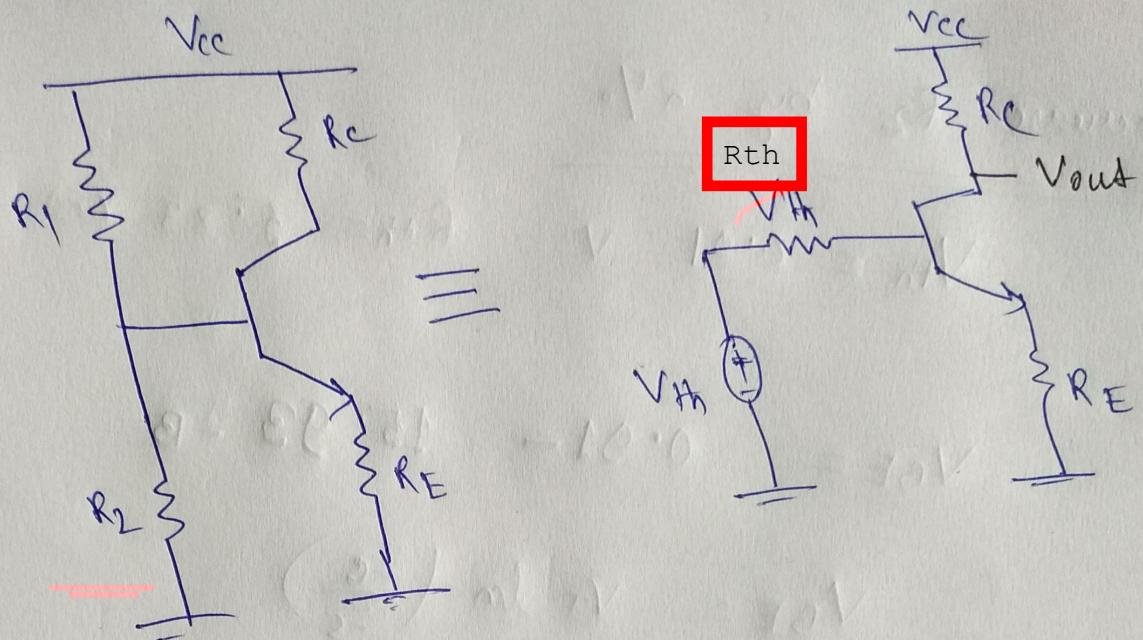- (i) Find V_{BE} and I_c (upto 2 iterations)
- (ii) Increase R_2 by $\boxed{2\%}$ and repeat (i).
- (iii) Find the percentage increase or decrease in V_{BE} . ~~(approx.)~~



$$V_{th} = I_B R_H + V_{BE} + (\beta + 1) R_E I_B \quad (1)$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) \quad (2)$$

$$V_{th} = 0.9 \text{ V}, \quad R_H = 5.76 \text{ k}\Omega$$

$$V_{BE} = 0.9 - 15.86 I_B$$

assume $V_{BE} = 0.8$

$$\frac{V_{BE}}{0.8 \text{ V}} = \frac{I_C}{0.635 \text{ mA}}$$

$$0.785 \text{ V} \quad 0.73 \text{ mA}$$

$$0.788 \text{ V} \quad 0.71 \text{ mA}$$

$$V_{out} = 1.49 \text{ V}$$

Increase R_2 by 2%

$$V_{TH} = 0.91 \text{ V} \quad R_{TH} = 5.83 \text{ k}\Omega$$

$$V_{BE} = 0.91 - 15.93 I_B$$

$$V_{BE} = V_T \ln \left(\frac{I_C}{I_S} \right)$$

assume $V_{BE} = 0.8$

$$\frac{V_{BE}}{0.8 \text{ V}} \quad \frac{I_C}{0.691 \text{ mA}}$$

$$0.787 \quad 0.772 \text{ mA}$$

$$0.789 \quad 0.76 \text{ mA}$$

$$V_{out} = 1.74 \text{ V}$$