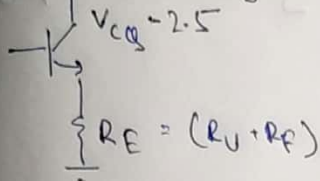


Given $I_{CQ} = 5 \text{ mA}$
 $A = 10 \times 10 \text{ (N/8)}$
 $= 10 \times 10 \text{ (88/8)}$
 $= 10$

$V_{out} = 5 \text{ V}_{pp}$
 $V_{in} = 0.5 \text{ V}_{pp}$

1. The output swings up and down by 2.5V from its quiescent point value. When voltage at output is high, current available is low so low voltage drop across R_E and high V_{CE} , thus circuit is in active.

However when voltage output is low and swings down by 2.5V, current is high and huge drop across R_E . Then we need to see if V_{CE} is high enough.



We set V_{CQ} or $V_{out,Q} = 6 \text{ V} = \frac{V_{CC}}{2} \parallel R_C = \frac{6}{5} = 1.2 \text{ k}\Omega$

It may drop to 3.5V

I_C (instantaneous) = 7.08 mA

$V_{RE, \max} \approx 3.0 \text{ V}$ (0.5 drop across V_{CE} at least)

$R_{E, \max} = 424 \Omega$

2. We ~~need~~ don't need such high R_E , we can set bias at 6V safely.
 $R_E = 0.1 R_C = 120 \Omega$ (for stability)

$|A| = \frac{R_C}{\frac{1}{g_m} + R_U}$

or $10 = \frac{1200}{\frac{26}{5} + R_U}$

or $R_U = 114.8 \Omega$

$R_E = R_U + R_F$
 or $120 = 114.8 + R_F$
 or $R_F = 5.2 \Omega$

3. $I_B \approx \frac{1}{30} \text{ mA}$

$V_B \approx V_{RE} + V_{BE}$

$= 5 \times 0.12 + 0.7$

$= 1.3 \text{ V}$

12 $\frac{R_2}{R_1 + R_2} \approx 1.3$

a $\frac{R_2}{R_1 + R_2} \approx 0.11$

This will lead to some error since we are ignoring base current. Later needs to be fine-tuned

First iteration values

$V_{CQ} = 6 \text{ V}$ (V_{bias})

$R_C = 1.2 \text{ k}\Omega$

$R_U = 114.8 \Omega$

$R_F = 5.2 \Omega$

$R_2 = 11 \text{ k}\Omega$

$R_1 = 89 \text{ k}\Omega$

$C_E = 1 \text{ mF}$

$C_1 = 43 \mu\text{F}$

The lower cut off will be determined by C_E

$f_L \approx \frac{1}{(R_U + \frac{1}{g_m}) \parallel R_F \parallel C_E} \approx \frac{1}{5 \text{ k}\Omega \times 1 \text{ mF}}$

$f_L \approx \frac{1}{31.3 \text{ k}\Omega}$
 $\approx 31.93 \text{ Hz}$
 choosing $C_E = 1 \text{ mF}$
 Hence it becomes mid band

First thing observed after simulation is that current is too small at about 4 mA. This means R_1 and R_2 needs to be changed, specifically R_2 must be \uparrow and R_1 needs to be \downarrow .

A little fine tuning gives

$$R_1 = 12.5 \text{ k}$$

$$R_2 = 87.5 \text{ k}$$

current now is 5 mA

V_{out} obtained is 4.88 V, clearly gain is lower than expected. So we can bypass more of R_E by fine tuning.

A little fine tuning gives

$$R_U = 112 \Omega$$

$$R_F = 8 \Omega$$

To be safer we can make the gain slightly more/slightly

$$R_U = 112 \Omega$$

Then the model obtained is

$$R_C = 1.2 \text{ k}$$

$$C = 47 \mu\text{F}$$

$$R_U = 112 \Omega$$

$$C_E = 1 \text{ mF}$$

$$R_F = 8 \Omega$$

$$R_1 = 87.5 \text{ k}$$

$$R_2 = 12.5 \text{ k}$$

Results obtained for DC condition

$$1. V_{out} = 5 \text{ V}_{PP}$$

$$2. I_C = 5.02 \text{ mA}$$

$$3. V_B = 1.29 \text{ V}$$

$$V_{BE} = 0.69 \text{ V}$$

$$V_C = 5.98 \text{ V}$$

$$V_{CE} = 5.38 \text{ V}$$

$$V_E = 0.60 \text{ V}$$

Results for AC analysis

$$1. V_{in} = 0.15 \text{ V amplitude peak}$$

$$= 0.50 \text{ V}_{PP}$$

$$2. A_V = 20.03 \text{ dB} \approx 10$$

$$3. f_L = 477.38 \text{ MHz}$$

$$f_H = 50.23 \text{ MHz}$$

1k is safely within limits of midband gain bandwidth

$$4. \text{ Harmonic distortion obtained} = 0.47122\% \text{ (according to simulation)}$$