

Introduction to Electronics (Practice paper - 5)

Topic: MOSFET and Amplifiers

1. For the n-channel MOSFET as shown in Fig. 1 has $K_n = 0.2 \text{ mA/V}^2$ and $V_{Th} = 1 \text{ V}$. Given that $V_{DD} = 10 \text{ V}$ and $R_D = 1 \text{ k}\Omega$. Find (a) the region operation, (b) V_{GS} (c) V_{DS} and (d) i_D .

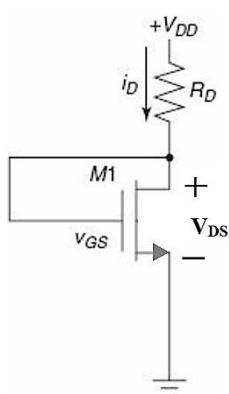


Fig. 1

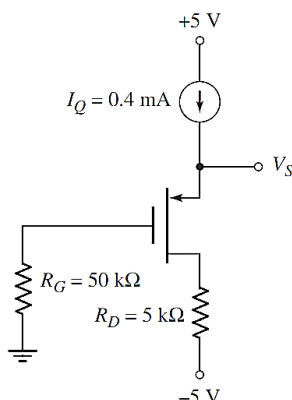


Fig. 2

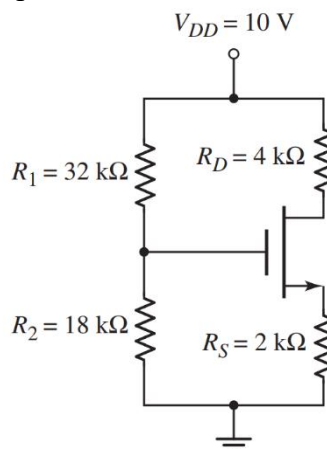


Fig. 3

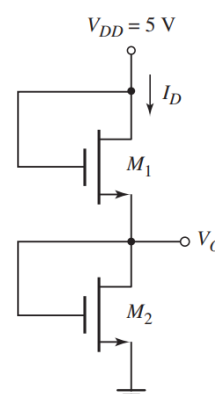


Fig. 4

2. For the circuit in Figure 2, the p-channel transistor has threshold voltage (V_{Th}) = -0.8 V and $K_p = 200 \mu\text{A/V}^2$. Determine V_S and V_{SD} .

3. A particular n-channel MOSFET has parameters $V_{Th} = 0.6 \text{ V}$, $L = 0.8 \mu\text{m}$, $t_{ox} = 200 \text{ \AA}$, and $\mu_n = 600 \text{ cm}^2/\text{V-s}$. A drain current of $I_D = 1.2 \text{ mA}$ is required when the device is biased in the saturation region at $V_{GS} = 3 \text{ V}$. Determine the required channel width of the device.

4. For a p-channel enhancement-mode MOSFET, the parameters are $K_P = 2 \text{ mA/V}^2$ and $V_{TP} = -0.5 \text{ V}$. The gate is at ground potential, and the source terminals is at $+5 \text{ V}$. Determine I_D when the drain terminal voltage is: (a) $V_D = 0 \text{ V}$, (b) $V_D = 2 \text{ V}$, (c) $V_D = 4 \text{ V}$, and (d) $V_D = 5 \text{ V}$.

5. In the circuit shown in Fig. 3, the transistor parameters are $V_{Th} = 0.8 \text{ V}$ and $K_n = 0.5 \text{ mA/V}^2$. Calculate (i) Drain current I_D , (ii) Gate-source voltage (V_{GS}), and (iii) Drain-source voltage (V_{DS}).

6. The transistors (M_1 & M_2) in the circuit shown in Fig. 4 have parameters $V_{Th} = 0.4 \text{ V}$ and $K'_n = 120 \mu\text{A/V}^2$. (a) If the width-to-length ratios of M_1 and M_2 are $(W/L)_1 = (W/L)_2 = 30$, determine V_{GS1} , V_{GS2} , V_O , and I_D . (b) Repeat part (a) if the width-to-length ratios are changed to $(W/L)_1 = 30$ and $(W/L)_2 = 15$.

7. In the circuit shown in Fig. 5, find the value of R_S and R_D when $V_D = -3 \text{ V}$ and $I_D = 0.5 \text{ mA}$. The transistor parameters are given as $K'_p = 30 \mu\text{A/V}^2$, $W/L = 20$ and $V_{Th} = -1.2 \text{ V}$.

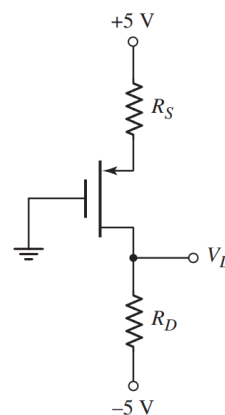


Fig. 5

8. The circuit shown in Fig. 6 have transistor parameters $V_{Th} = -1.75$ V and $K_p = 3$ mA/V². The drain current (I_D) in the circuit is 5 mA, $V_{SD} = 6$ V and $R_{in} = 80$ k Ω . Find R_1 , R_2 and R_D .

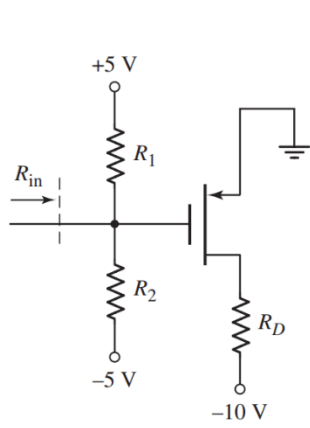


Fig. 6

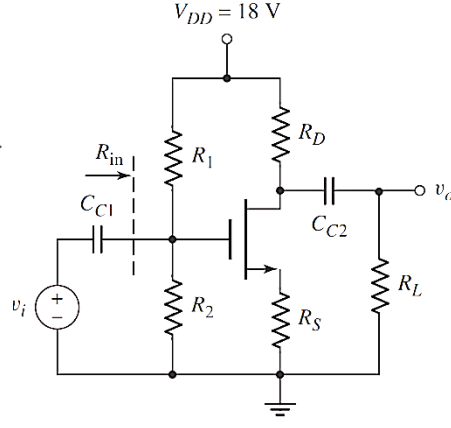


Fig. 7

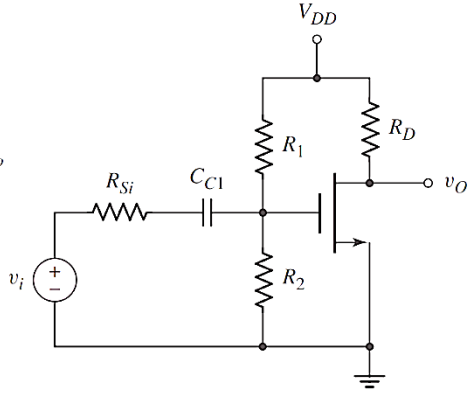


Fig. 8

9. In the common-source amplifier circuit shown in Fig. 7 using an n-channel MOSFET quiescent values are $I_{DQ} = 6$ mA, $V_{GSQ} = 2.8$ V, and $V_{DSQ} = 10$ V. The transconductance is $g_m = 2.2$ mA/V. Consider, $\lambda = 0$, $R_L = 1$ k Ω , $A_v = -1$, and $R_{in} = 100$ k Ω . Find R_1 , R_2 , R_S , R_D , K_n , and V_{Th} .

10. The parameters of the circuit shown in Fig. 8 are $V_{DD} = 5$ V, $R_1 = 520$ k Ω , $R_2 = 320$ k Ω , $R_D = 10$ k Ω , and $R_{Si} = 0$. Assume transistor parameters of $V_{Th} = 0.8$ V, $K_n = 0.20$ mA/V², and $\lambda = 0$. (a) Determine the small-signal transistor parameters g_m and r_o . (b) Find the small-signal voltage gain. (c) Calculate the input and output resistances. (d) Repeat (a) and (b) considering $R_{Si} = 1$ k Ω .

11. Consider the NMOS amplifier with saturated load in Fig. 9. The transistor parameters are $V_{Th_D} = V_{Th_N} = 0.6$ V, $k'_n = 100$ μ A/V², $\lambda = 0$, and $(W/L)_L = 1$. Estimate the W/L ratio of M_D for realizing the overall small-signal voltage gain $|A_v| = 5$.

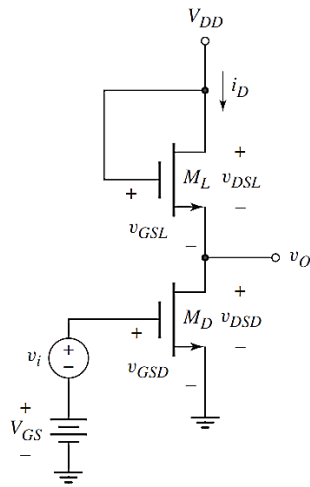


Fig. 9

Please Note: For n-channel MOSFET

$K_n = \frac{1}{2} \mu_n C_{ox} \frac{W}{L}$ is the conduction parameter

$K_n = \frac{1}{2} K'_n \frac{W}{L}$

$K'_n = \mu_n C_{ox}$ is the process conduction parameter