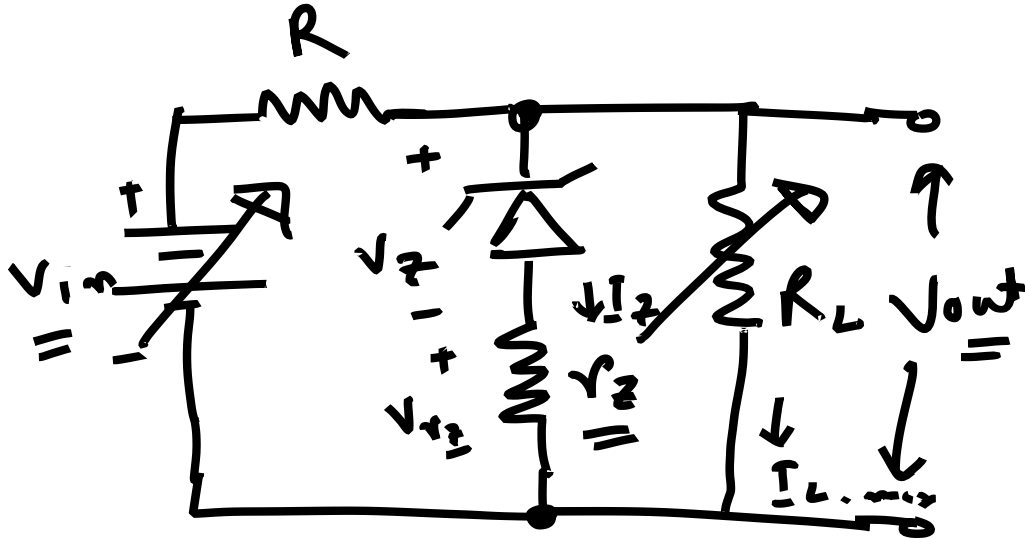


Zener diode as voltage regulator



Figures of Merit


✓ (i) Source regulation = $\frac{\Delta V_{out}}{\Delta V_{in}} \times 100\%$

✓ (ii) Load regulation

$$= \frac{V_{out, no\ load} - V_{out, full\ load}}{V_{out, full\ load}} \times 100\%$$

Zener diode as voltage regulator

example

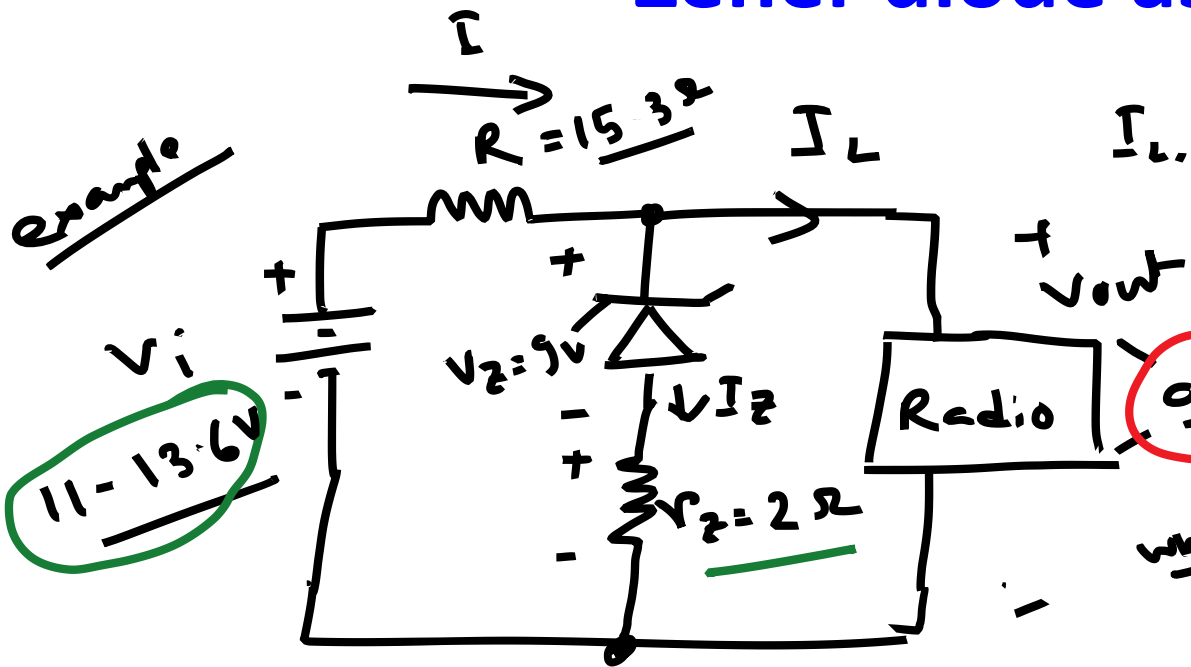

$$I_{L, \min} = 0, \quad I_{L, \max} = 100 \text{ mA}$$

$$\textcircled{1} \text{ Source regulation} = \frac{\Delta V_{out}}{\Delta V_{in}} \times 100\%$$

$$\Delta V_{in} = (13.6 - 11) = \underline{\underline{2.6 \text{ V}}}$$

$$\text{when } I_L = 0, \quad I = I_z = \frac{13.6 - 9}{15.3 + 2} = 0.265 \text{ A}$$

$$V_{out, \max} = 9 + I_z R_2 = 9 + 0.265 \times 2$$

$$\underline{\underline{V_{out, \max} = 9.53 \text{ V}}}$$

$V_{out, \min}$?


$$I = \frac{11 - 9}{15.3 + 2} = 0.115 \text{ A}$$

$$\underline{\underline{V_{out, \min} = 9 + 2 \times 0.115 = 9.23 \text{ V}}}$$

$$\Delta V_{out} = (9.53 - 9.23) \text{ V} = \underline{\underline{0.3 \text{ V}}}$$

$$\text{Source regulation} = \frac{0.3}{2.6} \times 100\% = \underline{\underline{11.53\%}}$$

Zener diode as voltage regulator

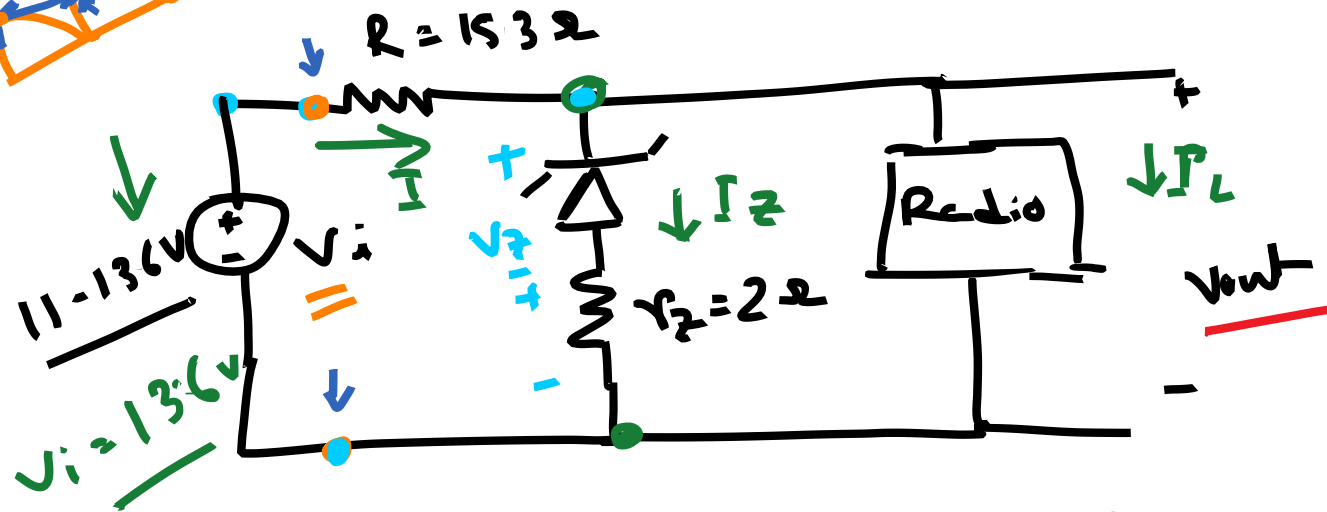

$$\text{Load regulation} = \frac{V_{out, N.L} - V_{out, F.L}}{V_{out, F.L}} \times 100\%$$

No load, $I = I_z$, $I = \frac{13.6 - 9}{15.3 + 2} = 0.265A$

$$V_{out, N.L} = 9 + 2 \times 0.265 = 9.53V$$

Full load, given, $I_{L, max} = 100mA = 0.1A$


$$I_z = I - I_L = \frac{13.6 - (9 + I_z \times 2)}{15.3} - 0.1$$

$$I_z = 0.176A, \quad V_{out, F.L} = 9 + 0.176 \times 2 = 9.35V$$

$$= \frac{9.53 - 9.35}{9.35} \times 100\% \approx 1.9\%$$

Ripple voltage

Ripple voltage in rectified output

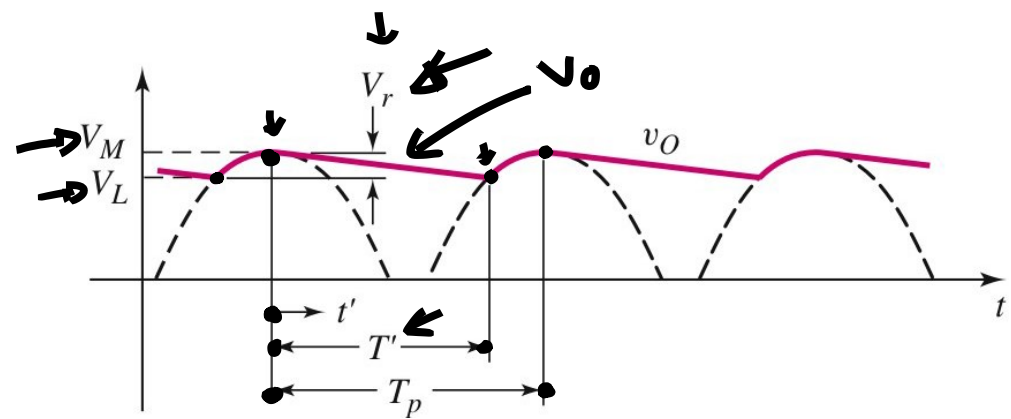

$$v_O(t) = V_M \exp\left(-\frac{t'}{\tau}\right) = V_M \exp\left(-\frac{t'}{RC}\right)$$

$$V_L = v_O(T') = V_M \exp\left(-\frac{T'}{RC}\right)$$

$$V_r = V_M - V_L = V_M - V_M \exp\left(-\frac{T'}{RC}\right)$$

$$V_r = V_M \left[1 - \exp\left(-\frac{T'}{RC}\right) \right]$$


$$\rightarrow V_r = V_M \cdot \frac{T'}{RC}$$

$$\rightarrow V_r = V_M \cdot \frac{T_p}{RC} = \frac{V_M}{2f RC} \leftarrow \text{F.W.R}$$

$RC \gg T$
 $T' \ll RC$
 $\exp\left(-\frac{T'}{RC}\right) \approx 1 - \frac{T'}{RC}$

$$T' = T_p = \frac{1}{2f}$$



$$f = \frac{1}{T}$$

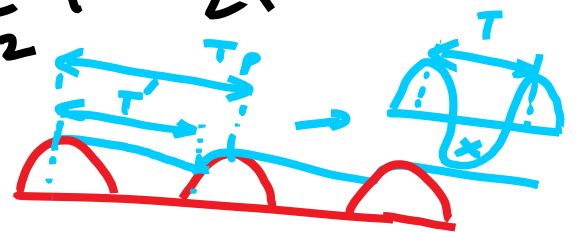

$$\text{H.W.R, } T_p = T, V_r = \frac{V_M}{f RC} \leftarrow \text{H.W.R}$$

→ pn junction diode: switching transient

$$I_F = \frac{V_F - V_T}{R_F}$$

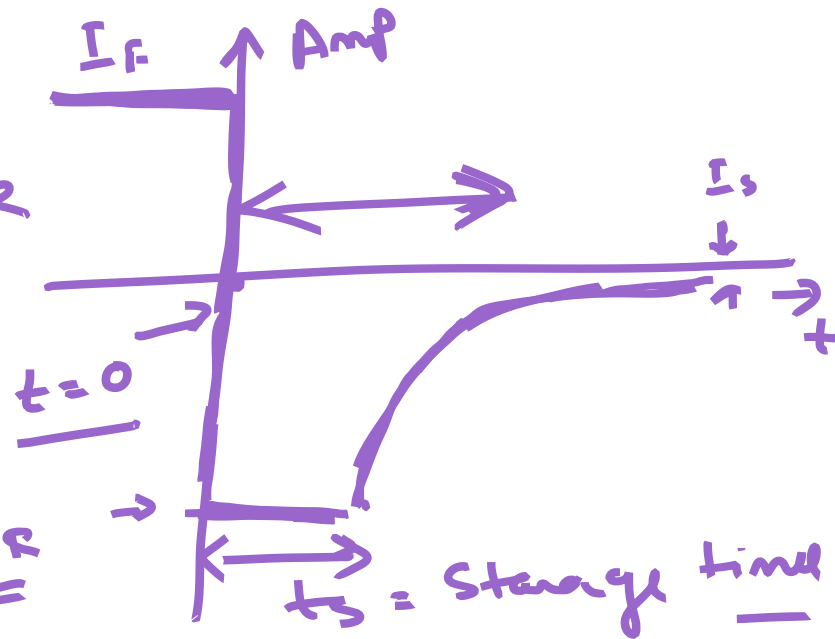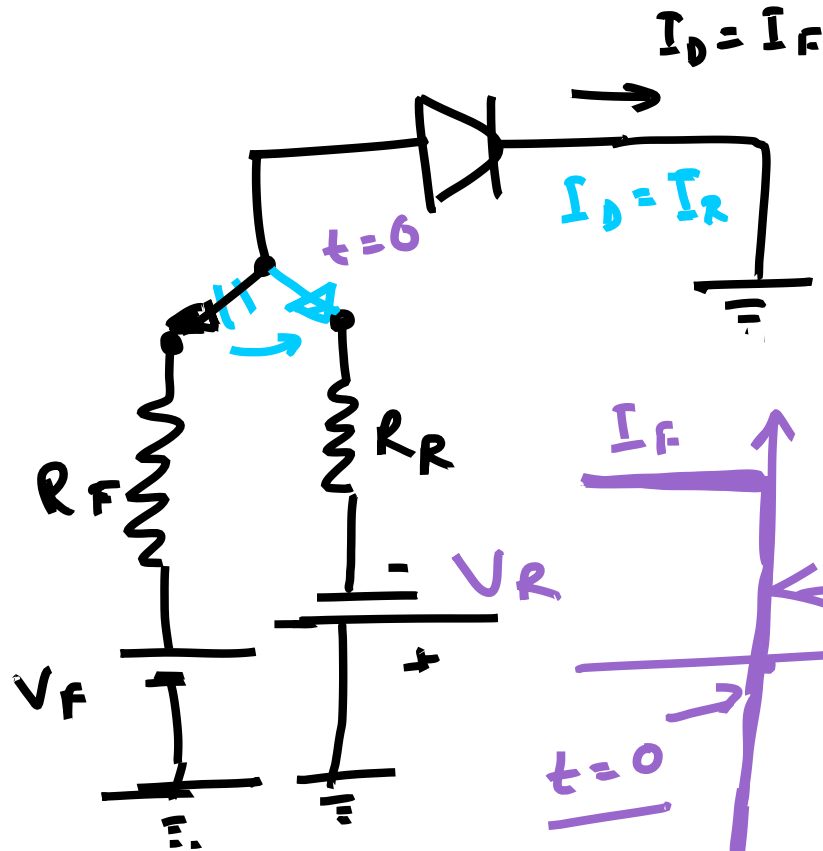

$$I_R \approx \frac{V_R}{R_R}$$

\approx magnitude.

