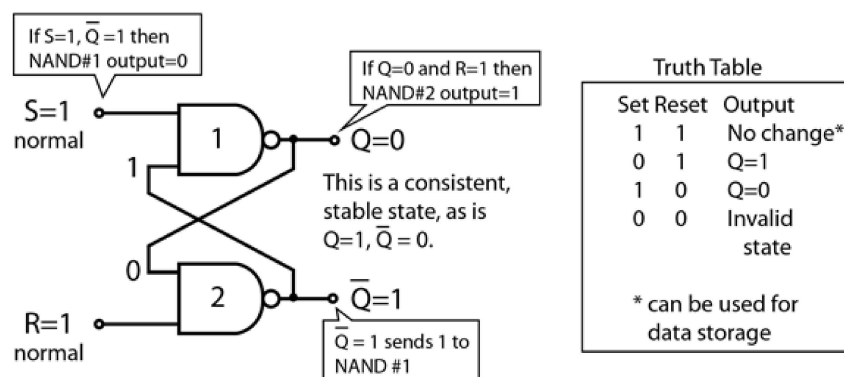



Latches and flip flops

Set-reset (SR) latch


SR latch using NAND gates




SR latch using NOR gates

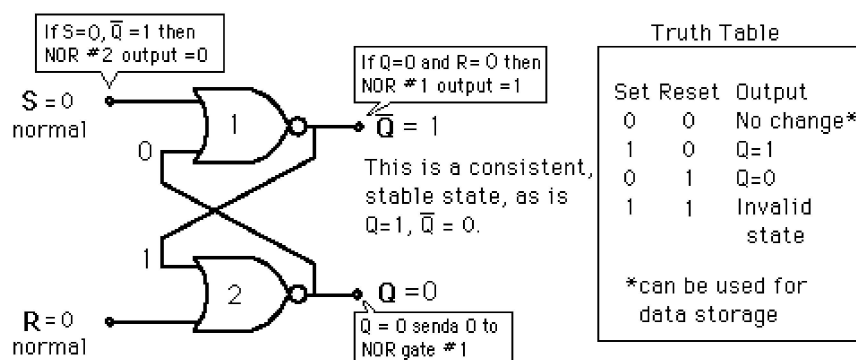

Clocked SR latch (using NAND gates)

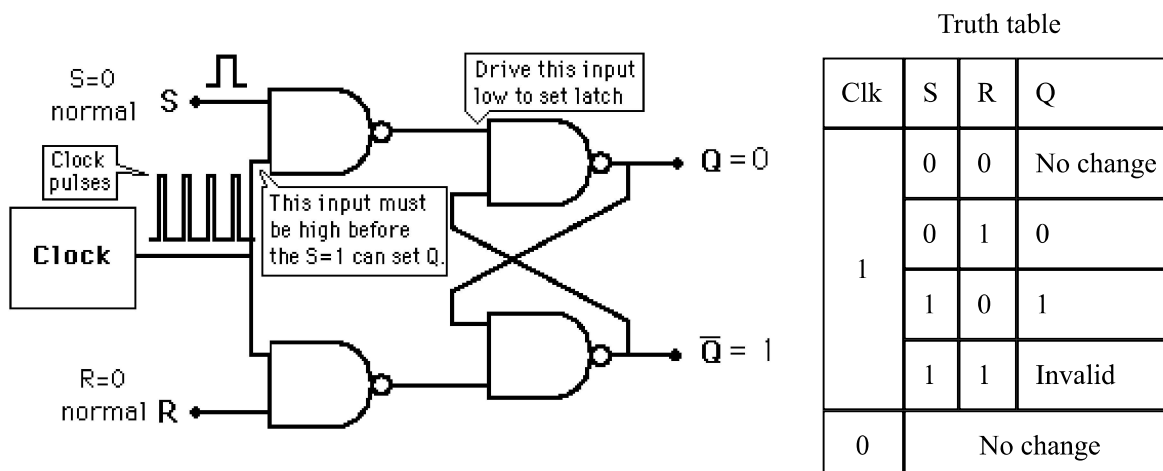

Chatterless switch

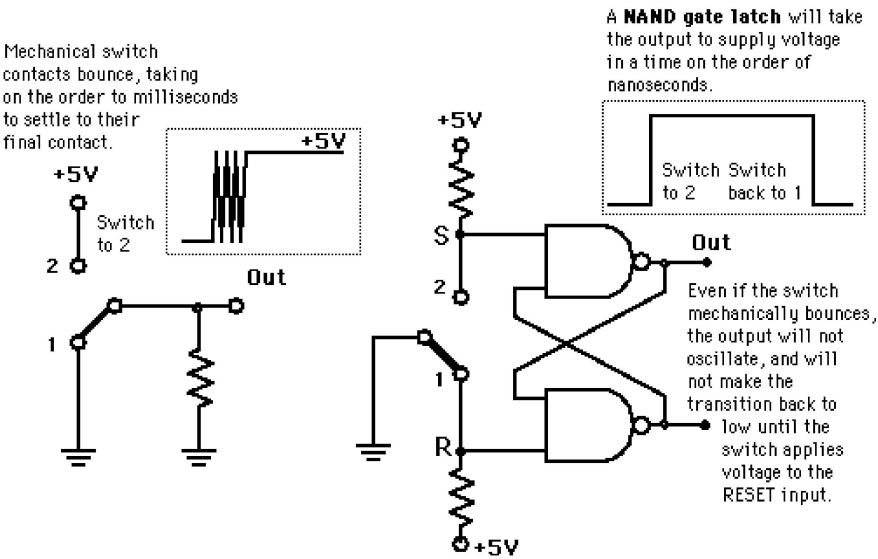

JK flip flop

Basic JK FF

Truth table

Clk	J	K	Q	Q New
1	0	0	—	No change
	0	1	0	0 (NC)
	0	1	1	0 (Q'→1)
	1	0	0	1 (Q→1)
	1	0	1	1 (NC)
	1	1	1	0 (Q'→1)
	1	1	0	1 (Q→1)
0	No change			

Symbol


Circuit

Toggles on leading edge of clock signal

SR flip-flop

Master-slave JK FF


Truth table

 


Active clock edge: 1 → 0 (falling)

Clk	J	K	Q	Q New
0	Master: NC; MLat → SLat			
1	Slave: NC			
1 → 0	0	0	—	MLat → SLat
	0	1	—	0 (S=0, R=1)
	1	0	—	1 (S=1, R=0)
	1	1	1	0 (S=0, R=1)
	1	1	0	1 (S=1, R=0)

D FF with asynchronous preset and clear

 

D FF with synchronous preset and clear

 


Residual problem with above DFF

1. Let the gate delay be Δ
2. Let $D=0$, $Clk=1$
3. Let $D=1$ and just before Δ time, $Clk=0$
4. Master latch has the invalid input combination of 00
5. Before valid inputs could appear at the steering gates of the master latch, $Clk=0$
6. Now, invalid input combination of 11 is presented to the slave steering gates, with $Clock'=1$
7. Slave latch has the invalid input combination of 00
8. Output of DFF is indeterminate

 Problem may be avoided if D remains steady when $Clk=1$, allowed to change only when $Clk=0$


T FF with preset and clear

Similar to DFF, but J and K terminals tied ($J=K=1$)



Huffman model


Schematic diagram

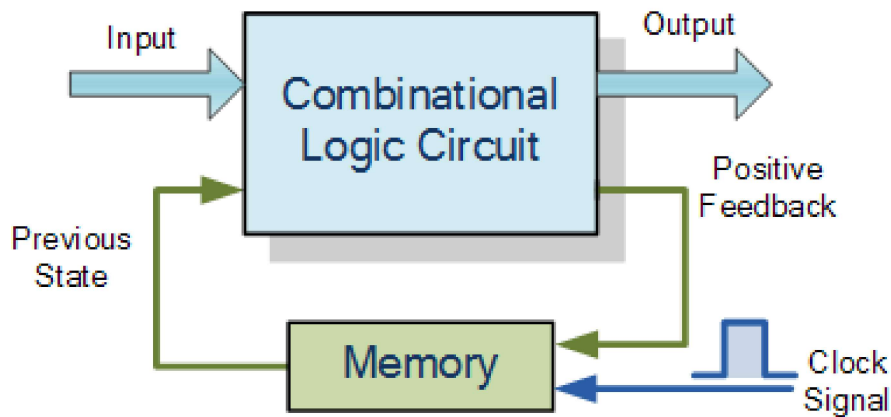

Setup and hold times

Setup time

 It is defined as the minimum amount of time *before* the active clock edge by which the data must be stable for it to be latched correctly; any violation in this required time causes incorrect data to be captured and is known as a setup violation



Time available for data at D2 to reach D1 after active clock edge

$$T_{clk} + T_{skew} - T_{setup}$$

Time needed for data to reach D1 from D2 after active clock edge

$$T_{c2q} + T_{comb}$$

Resulting constraint

$$T_{c2q} + T_{comb} \leq T_{clk} + T_{skew} - T_{setup}$$

$$T_{c2q} + T_{comb} + T_{setup} \leq T_{clk} + T_{skew}$$

Hold time

It is defined as the minimum amount of time *after* the active clock edge by which the data must be stable for it to be latched correctly; any violation in this required time causes incorrect data to be captured and is known as a hold violation

Minimum time for data at D2 to reach D1 after active clock edge

$$T_{c2q} + T_{comb}$$


Time for data to remain steady at D1 after active clock edge

$$T_{skew} + T_{hold}$$

Resulting constraint


$$T_{c2q} + T_{comb} \geq T_{skew} + T_{hold}$$

Example for setup and hold times

 

- What is the minimum clock frequency?
- $T_{clk} + T_{skew} \geq T_{c2q} + T_{comb} + T_{s2}$
- $T_{clk} + 0.25ns \geq 0.1ns + 5ns + 3ns$
- $T_{clk} \geq 7.85ns$

Positive clock edge triggered DFF

 

Transition table

C	D	R	S	R_A	S_A	Q_A
0	—	—	—	1	1	Q
1	0	1	1	0	1	0
	1	1	1	1	0	1
	—	0	1	0	1	0
	—	1	0	1	0	1
	—	0	0	1	0	1

- $S_A = (C \cdot A)' = C' + A' = C' + B \cdot S = C' + (D' + R') \cdot S$
- $R_A = (S \cdot C \cdot B)' = S' + C' + B' = S' + C' + R \cdot D$
- As long as $C = 0$, $R = S = 1$ and the output latch retains its older value
- When C changes from 0 to 1, R and S change as follows:
 - If $D=0$: $R_A = 0$, $S_A = 1$ (from $R = S = 1$) and $Q=0$
 - If $D=1$: $R_A = 1$, $S_A = 0$ (from $R = S = 1$) and $Q=1$
 - Thereafter, R and S remain stable, while $C=1$, irrespective of changes in D
- The invalid state of $R = S = 0$ is never reached
- If somehow $R = S = 0$, state immediately changes to $R = 1$ and $S = 0$

Types of sequential m/cs

Moore m/c


Outputs depend only on the present state

Mealy m/c

Outputs depend on the present state and also on the inputs (transducer)

Both are computationally equivalent

Shift register

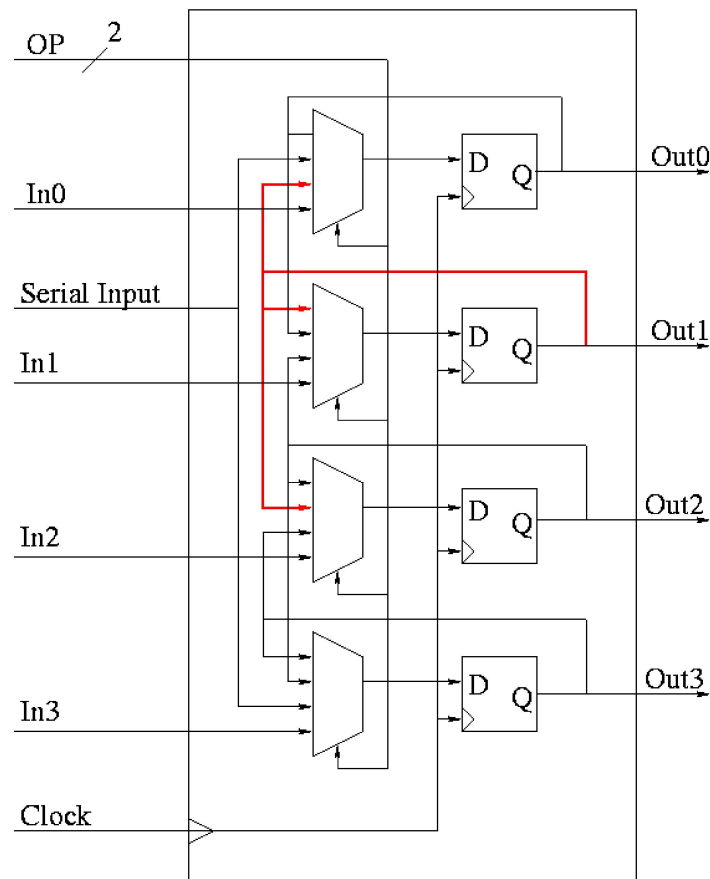

4-bit bidirectional shift register with parallel I/O

OP=00: nop OP=01: left-shift OP=10: right-shift OP=11: load

Barrel shift/rotate

