

## Experiment # 3


### MOSFET Amplifier Characteristics: Common Source

The aim of this experiment is to explore the characteristic of NMOS common source amplifier circuit.

Introduction:

MOSFET is the main active device for modern integrated circuits (ICs). It is mainly used as a switch and also as an amplifier. Here in this experiment NMOS common source amplifier circuit will be characterized.

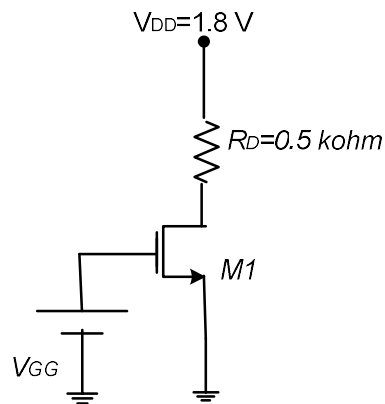
#### 1. DC Characteristics of NMOS circuit:




(i) Take NMOS ( $W=25 \mu\text{m}$ ,  $L=1 \mu\text{m}$ ),  $V_{TH}=0.3\text{V}$

(ii) **Plot  $I_{DS}$  vs  $V_{DS}$ . Plot for five different values of  $V_{GS}$ :  $V_{GS} = 0.6\text{V}, 0.9\text{V}, 1.2\text{V}, 1.5\text{V}$  and  $1.8\text{V}$ .**

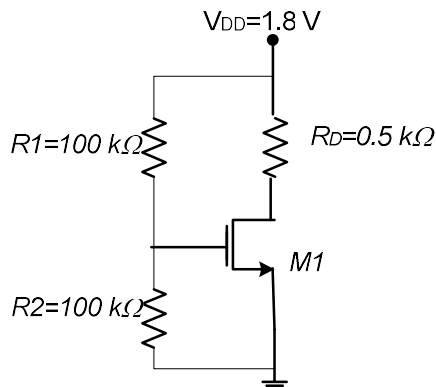2. DC operating point: Find the DC operating point and check whether the circuit is in saturation or not.



### 3. Common Source Amplifier:

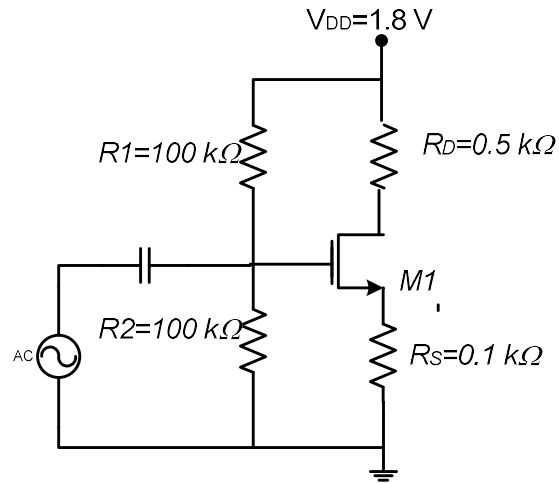

- (i) Apply sine wave (peak to peak 20mV, 10 kHz) through a capacitor 0.1  $\mu$ F. **Plot input and out signal with respect to time. Output is measured at Drain of MOSFET (with and without a capacitor 0.1  $\mu$ F connected at Drain of MOSFET). Take  $R_S=0$  ohm and also  $R_S=100$  ohm.**
- (ii) **Plot Gain (dB) vs Frequency (500 Hz - 5 MHz) of the above circuit (in (i)), take  $R_S=0$  ohm.**
- (iii) Find the Bandwidth of the amplifier.
- (iv) **Repeat the plot (ii) by changing  $R_D = 1$  k $\Omega$ , take  $R_S=0$  ohm.**
- (v) Discuss the effect of  $R_D$  and  $R_S$  on gain.