
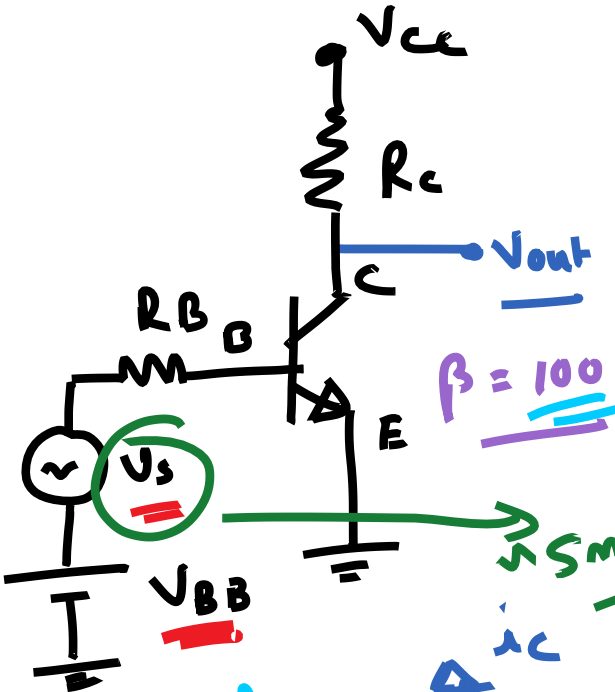



Basic BJT Amplifiers

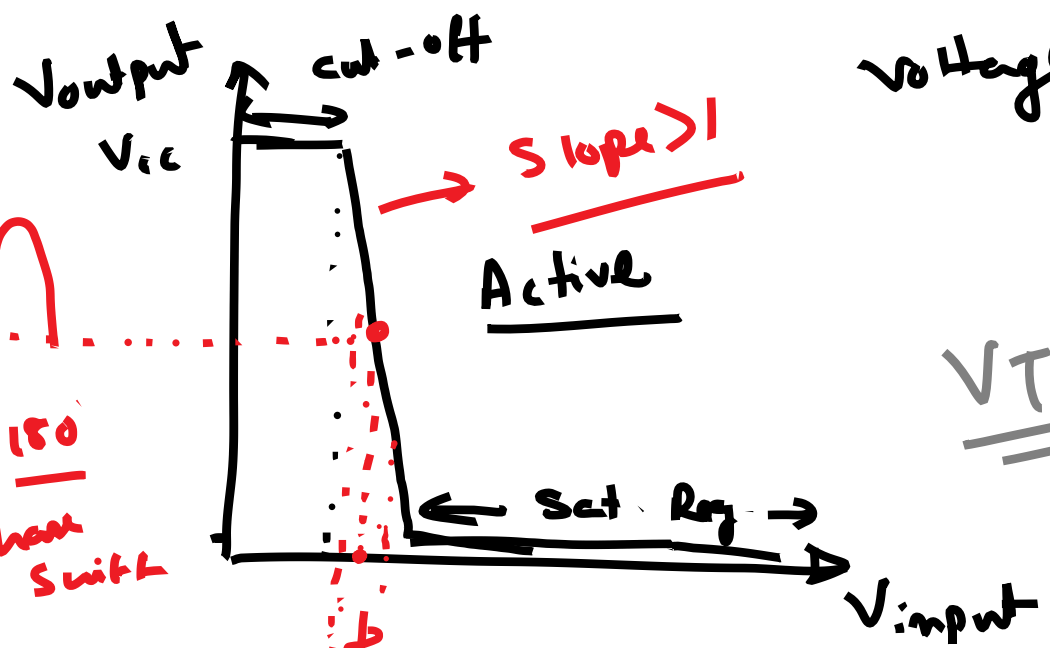

Small signal



Voltage Transfer Characteristics (VTC)

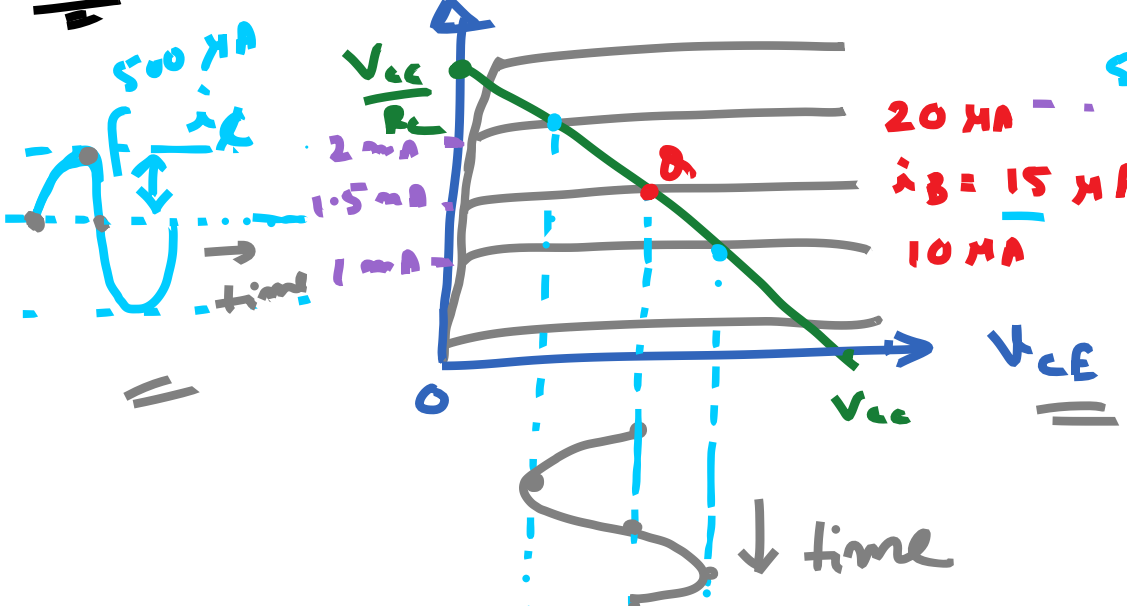


output ch.


i_b, i_c same phase

i/p and o/p 180° phase shift.

Basic BJT Amplifiers

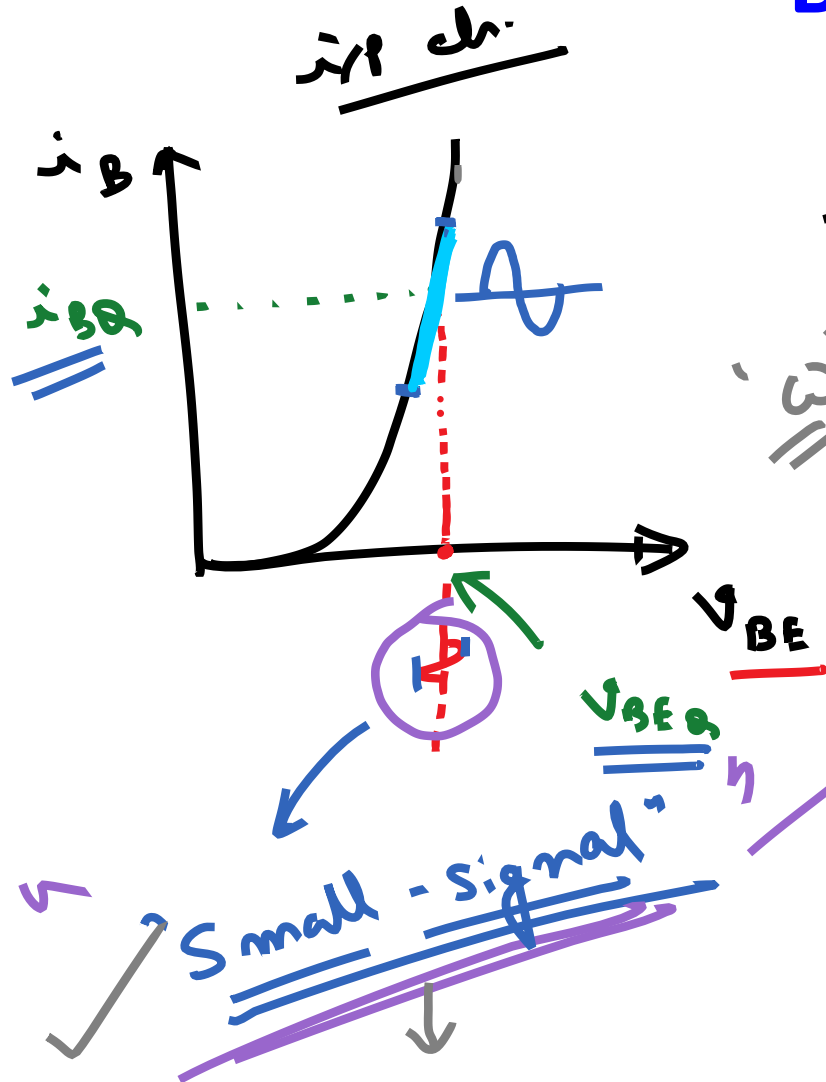
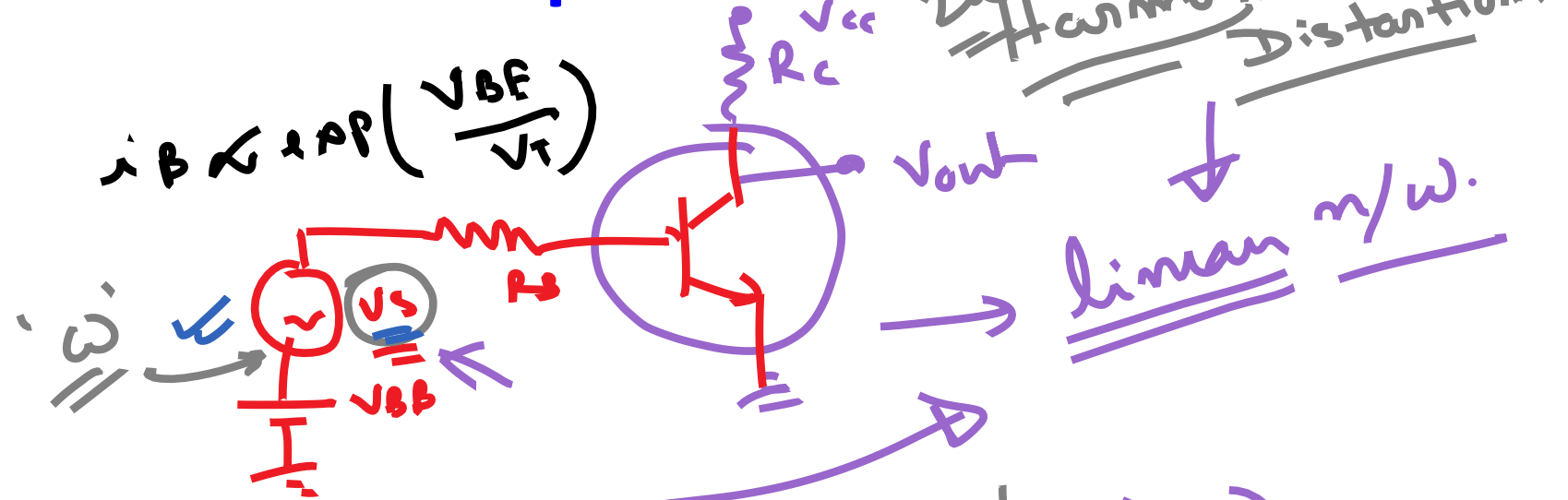
$$i_B \approx I_{BQ} \left(\frac{V_{BE}}{V_T} \right)$$



linear n/w.

i_B linearly related with V_{BE} (i/p)

i_c

$$V_{out} = V_{CE}$$


$i_B, i_c, V_{BE} \rightarrow$ total values (DC + AC)

$I_B, I_c, V_{BE} \rightarrow$ DC values


$i_b, i_c, V_{be} - V_{be} \rightarrow$ AC

Basic BJT Amplifiers

Small-signal equivalent circuit of BJT:

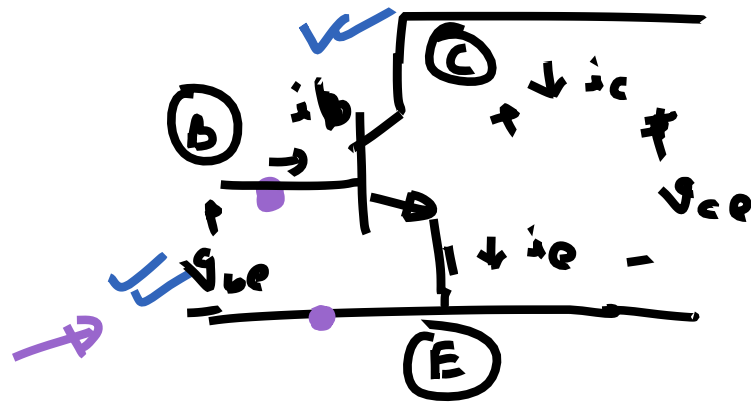
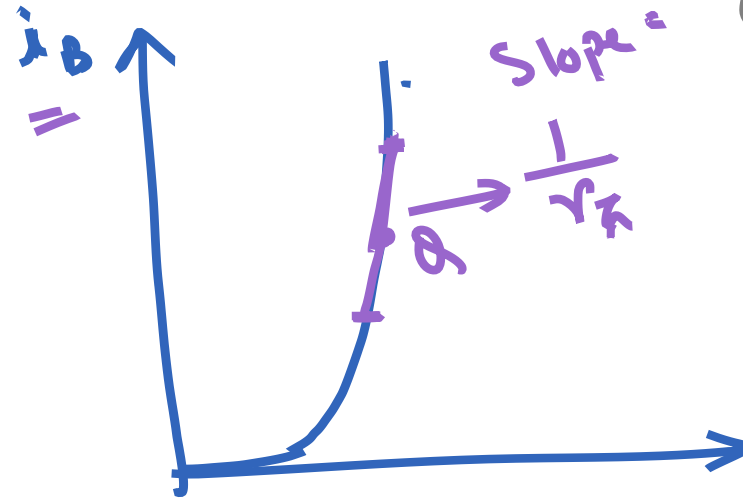
$$\begin{cases} i_C = I_S \exp\left(\frac{v_{BE}}{V_T}\right) \\ i_B = \frac{I_S}{\beta} \exp\left(\frac{v_{BE}}{V_T}\right) \end{cases}$$




$$\frac{1}{r_z} = \left. \frac{\partial i_B}{\partial v_{BE}} \right|_{Q\text{-point}}$$

$$= \left(\frac{I_S}{\beta V_T} \exp\left(\frac{v_{BE}}{V_T}\right) \right) = \frac{I_{BQ}}{V_T} = \frac{I_{CQ}}{\beta V_T}$$

$$r_z = \frac{\beta V_T}{I_{CQ}}$$

diffusion resistance / base-emitter r'/p resistance


Basic BJT Amplifiers

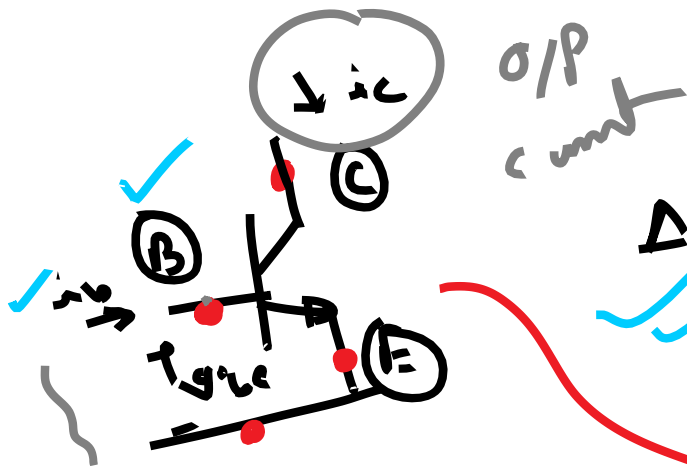

$$\Delta i_c = \left. \frac{\partial i_c}{\partial v_{BE}} \right|_{Q\text{-point}}$$

$$\Delta v_{BE}$$


g_m

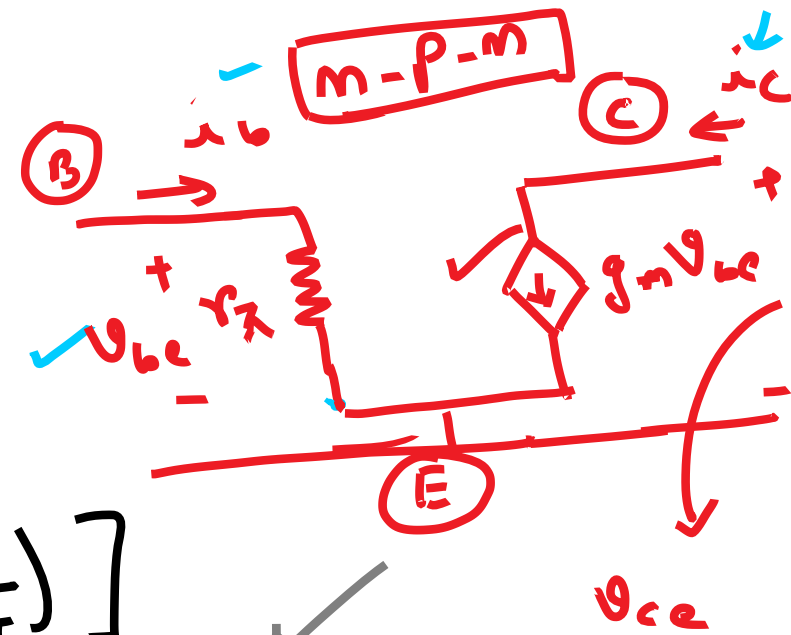

$$\left. \frac{\partial i_c}{\partial v_{BE}} \right|_{Q\text{-point}} = \frac{\partial}{\partial v_{BE}} \left[I_S \exp\left(\frac{v_{BE}}{V_T}\right) \right]$$

$$= \left(\frac{I_S}{V_T} \exp\left(\frac{v_{BE}}{V_T}\right) \right) = \frac{I_{CQ}}{V_T} = \underline{\underline{g_m}}$$

Trans - Conductance (g_m)

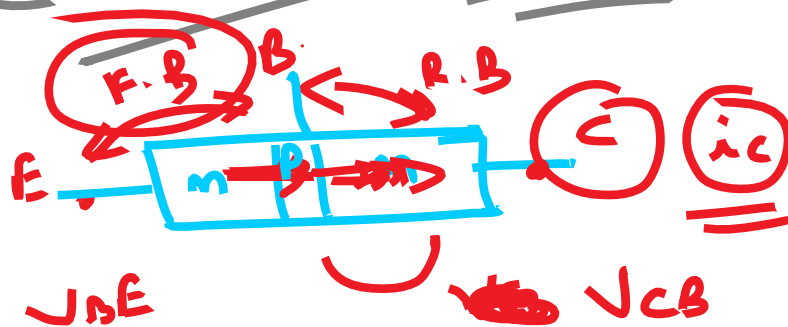



Basic BJT Amplifiers

Small-Signal

equivalent circuit of BJT

(AC)

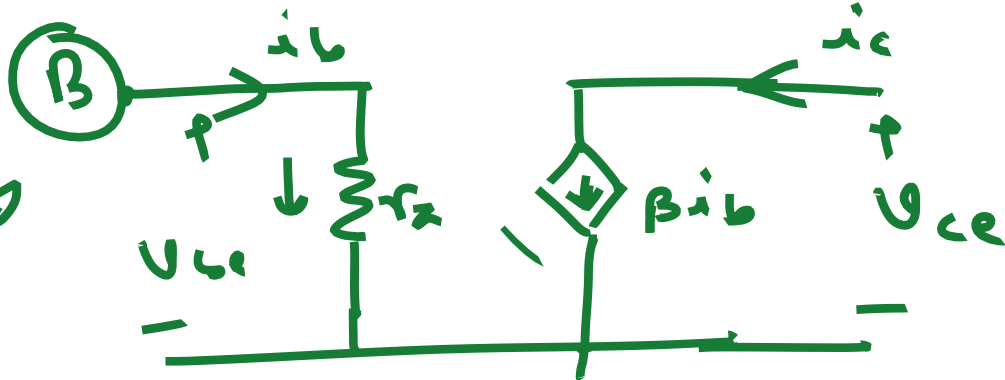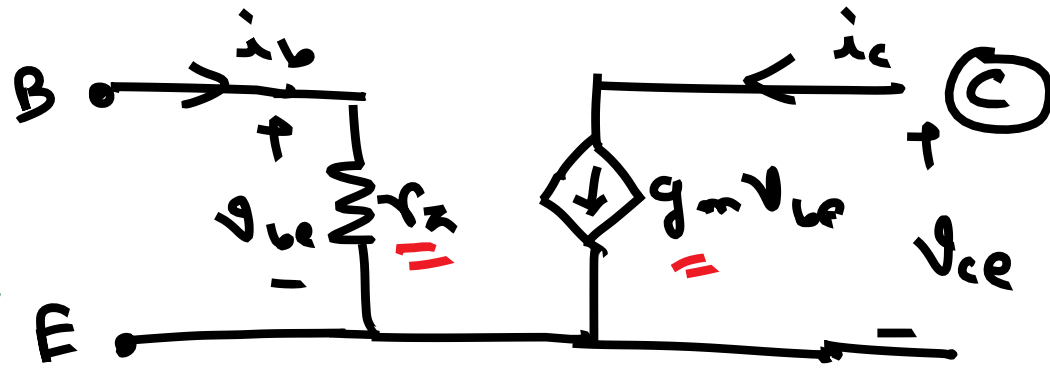Small-Signal hybrid- π eqn. circuit model.



n-p-n

$$\left\{ \begin{array}{l} r_{\pi} = \frac{\beta V_T}{I_{CQ}} \\ g_m = \frac{I_{CQ}}{V_T} \end{array} \right\} \begin{array}{l} \text{DC} \\ \text{biasing} \\ \text{point} \end{array}$$

$$\boxed{r_{\pi} \times g_m = \beta}$$