

Ans

Mid-Semester

Date: _____ FN/AN; Time: 2 hours; Full Marks: 60; Number of Students 255

Spring Semester, 2013-2014;

Department: E & ECE;

II year B. Tech.;

Subject no. EC 21008

Subject name: Analog Electronic Circuits

Instruction: Answer **ALL** questions and in the **same order** of the questions. Wherever it is necessary, you may use assumption(s) with reasonable justification.

Given: Saturation region drain current of an enhancement mode MOS transistor is,


$$|I_{DS}| = K \left(|V_{GS}| - |V_{th}| \right)^2 (1 + \lambda |V_{DS}|)$$

Q. 1. For all parts of this question refer to the adjacent circuit.

(a) Assuming the transistor is in active region of operation find the value of the quiescent current I_{CQ} of the transistor.

(b) Find the maximum value of the resistor R_C up to which the transistor remains in active region of operation.

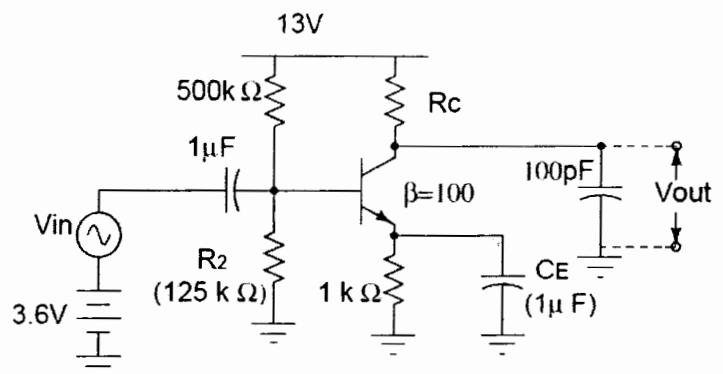(c) For R_C is equal to $4k\Omega$, find the value of the maximum possible output signal swing (without "significant distortion").



(d) Draw small signal equivalent circuit of the amplifier.

(e) For R_C is equal to $4k\Omega$, evaluate the following parameters and neatly sketch the frequency response of the amplifier:

(i) The voltage gain in mid-frequency range

(ii) The lower cut-off frequency

(iii) The upper cut-off frequency


(f) For R_C is equal to $4k\Omega$, if the capacitor CE is removed then what shall be the voltage gain in mid-frequency range and the lower cut-off frequency of the amplifier?

(g) For R_C is equal to $4k\Omega$, if the resistor R_2 is removed then what shall be the operating point (I_{CQ} and V_{CEQ}) of the transistor?

[3 + 3 + 3 + 3 + 9 + 6 + 3 = 30]

PLEASE TURN OVER


Q. 2. A common emitter amplifier with active load circuit is shown in the adjacent figure. Values of some parameters of the pMOS transistor are the following: Transconductance factor, $K = 2\text{mA/V}^2$; Threshold voltage, $|V_{Th}| = 3\text{ V}$; Channel length modulation factor, $\lambda = (1/70)\text{ V}^{-1}$. Values of the remaining parameters can be taken as that of ideal one. Similarly, for the n-p-n transistor, the Early voltage, $V_A = 50\text{V}$ and values of the remaining parameters can be taken as that of ideal one.

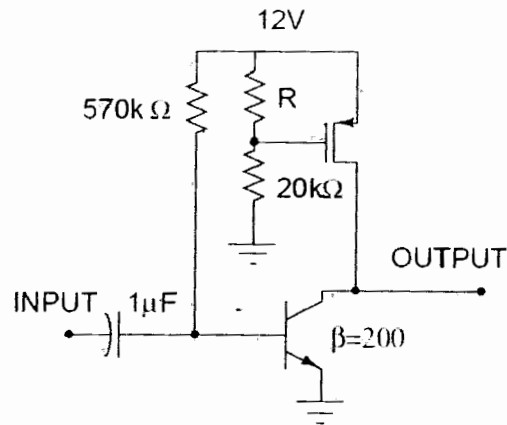

- Find the value of the resistor R so that $I_{CQ} = 2.02\text{ mA}$ and $V_{CEQ} = 5\text{V}$. Use this value of R for the subsequent parts of this question.
- Draw small signal equivalent circuit of the amplifier.
- Find the small signal gain of the amplifier.
- If you cascade two identical such amplifiers what will be the overall voltage gain

[3 + 3 + 3 + 6 = 15]

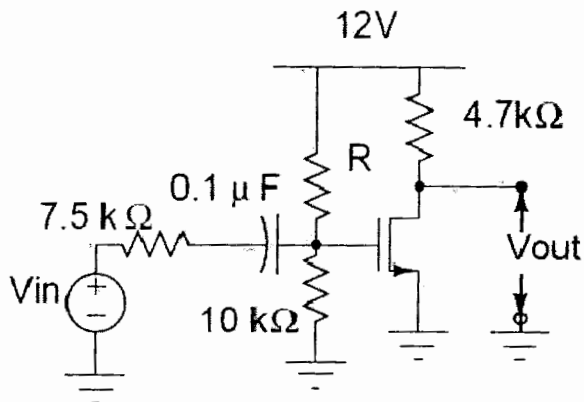Q. 3. A common source amplifier circuit is shown in the adjacent figure. Values of some parameters of the transistor are the following: Transconductance factor, $K = 1\text{mA/V}^2$; Threshold voltage, $V_{Th} = 2\text{ V}$; Channel length modulation factor, $\lambda = 0.01\text{ V}^{-1}$. Values of the remaining parameters can be taken as that of ideal one.



- Find the value of the resistor R such that $I_{DSQ} = 1\text{mA}$.
- With the value of R that is obtained in the part (a) of this question, find the small signal voltage gain of the amplifier in mid-frequency range.
- With the value of R that is obtained in the part (a) of this question, find the maximum output signal swing without having "significant distortion".
- With the value of R that is obtained in the part (a) of this question, find the lower cutoff frequency of the amplifier.
- With the value of R that is obtained in the part (a) of this question, for $V_{in} = 500 \sin((2000/3)t)\text{ mV}$, neatly sketch the output voltage V_{out} .

[3 + 3 + 3 + 3 + 3 = 15]