

FOR MORE EXCLUSIVE  
**(Civil, Mechanical, EEE, ECE)**  
**ENGINEERING & GENERAL STUDIES**  
(Competitive Exams)

TEXT BOOKS, IES GATE PSU's TANCET & GOVT EXAMS  
NOTES & ANNA UNIVERSITY STUDY MATERIALS

VISIT

**[www.EasyEngineering.net](http://www.EasyEngineering.net)**

**AN EXCLUSIVE WEBSITE FOR ENGINEERING STUDENTS &  
GRADUATES**



**\*\*Note:** Other Websites/Blogs Owners Please do not Copy (or) Republish this Materials, Students & Graduates if You Find the Same Materials with EasyEngineering.net *Watermarks or Logo*, Kindly report us to [easyengineeringnet@gmail.com](mailto:easyengineeringnet@gmail.com)



**KREATRYX**

**K** Notes



**ANALOG CIRCUITS**





## Contents

Manual for K-Notes.....	2
Diodes .....	3
Transistor Biasing.....	11
Transistor Amplifier .....	19
Feedback Amplifiers.....	25
Operational Amplifiers (OP-AMP) .....	29





## Manual for K-Notes

### Why K-Notes?

Towards the end of preparation, a student has lost the time to revise all the chapters from his / her class notes / standard text books. This is the reason why K-Notes is specifically intended for Quick Revision and should not be considered as comprehensive study material.

### What are K-Notes?

A 40 page or less notebook for each subject which contains all concepts covered in GATE Curriculum in a concise manner to aid a student in final stages of his/her preparation. It is highly useful for both the students as well as working professionals who are preparing for GATE as it comes handy while traveling long distances.

### When do I start using K-Notes?

It is highly recommended to use K-Notes in the last 2 months before GATE Exam (November end onwards).

### How do I use K-Notes?



Once you finish the entire K-Notes for a particular subject, you should practice the respective Subject Test / Mixed Question Bag containing questions from all the Chapters to make best use of it.



## Diodes

Representation:

A: Anode      K : Cathode

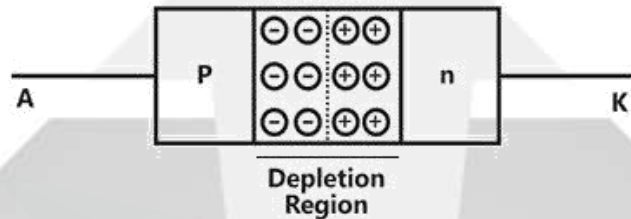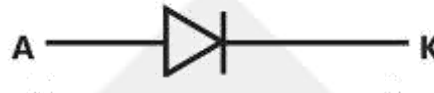

- The voltage at which the charged particles start crossing the junction is called as cut – in voltage or Threshold voltage.  
It is represented as  $V_{AK} = V_\gamma$ .
- When  $V_{AK} < V_\gamma$ , depletion region exists and no charge carriers cross the junction, therefore  $I_D = 0$
- When  $V_{AK} > V_\gamma$ , number of charged particles crossing the junction increases & the current through the diode increase, non – linearly or exponentially.
- Diode in the condition is said to be forward biased.

$$I_D = I_S \left[ e^{\frac{V_{AK}}{\eta V_T}} - 1 \right]$$

$I_S$  = reverse saturation current

$V_T$  = Thermal voltage =  $\frac{KT}{q}$

K = Boltzmann constant

T = Temp. in k

q = charge of one  $e^-$


$V_T = 26\text{mv}$  at room temperature

$\eta$  = intrinsic factor

- When  $V_{AK} < 0$ , diode is said to be in reverse biased condition & no majority carriers cross the depletion region, hence  $I_D = 0$




### Characteristics of Diode

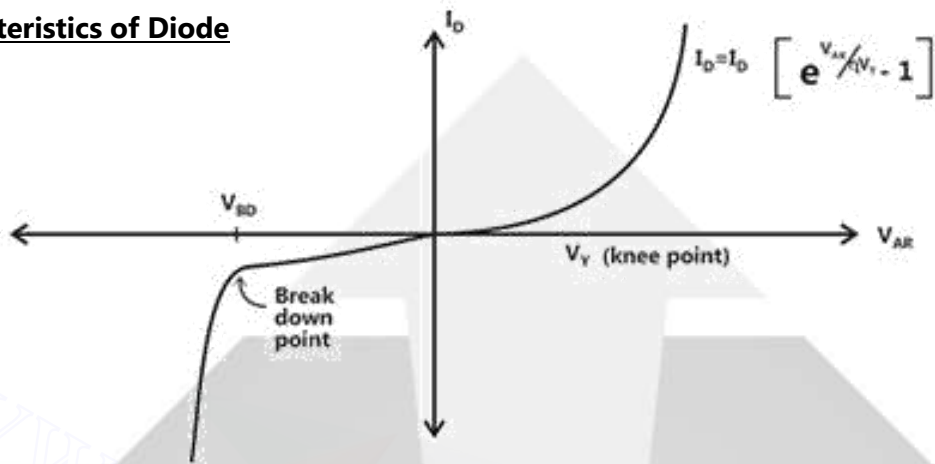


### Equivalent circuit of diode

#### Forward Bias

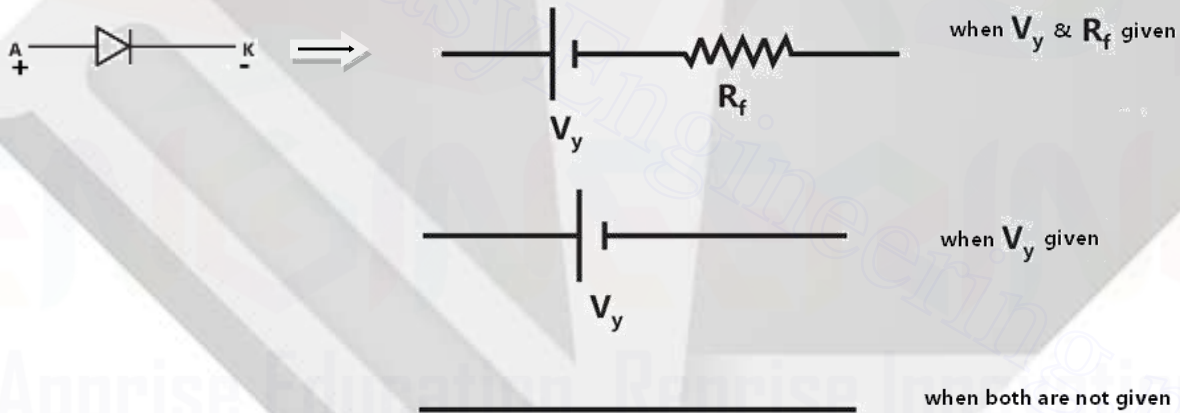

#### Reverse Bias

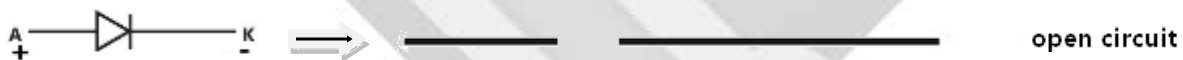

### Diode Resistance

#### 1) State or DC Resistance

$$R_{DC} = \frac{V_{AK}}{I_D}$$



## 2) Dynamic or AC Resistance

$$R_{AC} = \frac{dV_D}{dI_D} = \frac{\eta V_T}{I_D}$$



## Diode Applications

### Clippers

It is a transmission circuit which transmits a part of i/p voltage either above the reference voltage or below the reference voltage or b/w the two reference voltages.


#### • Series Clippers

##### i) Positive Clippers

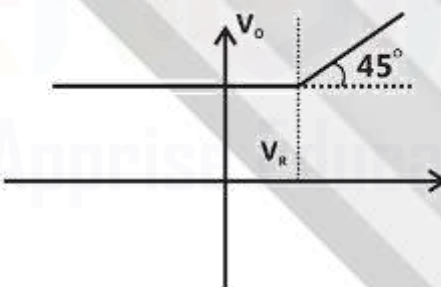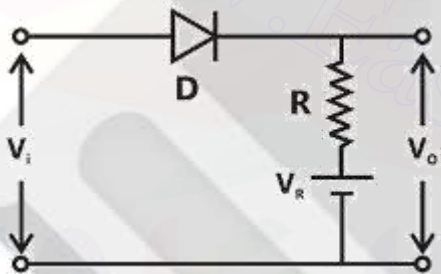


$$V_i = V_m \sin \omega t : \text{When } V_i < V_R \Rightarrow V_O = V_R$$
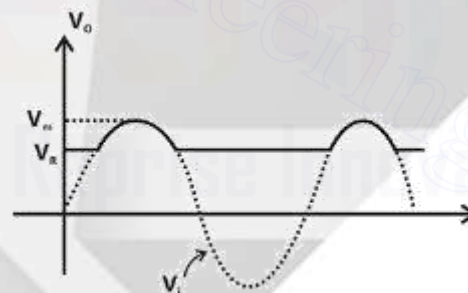
$$V_m > V_R \quad \text{When } V_i > V_R \Rightarrow V_O = V_i$$



##### ii) Negative Clipper

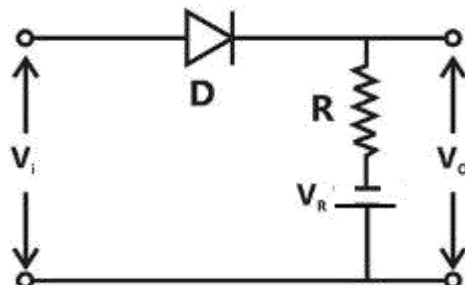



$$V_i = V_m \sin \omega t : \text{When } V_i < -V_R \Rightarrow V_O = -V_R$$

$$V_m > -V_R \quad \text{When } V_i > -V_R \Rightarrow V_O = V_i$$




## Analog Circuits

K Notes

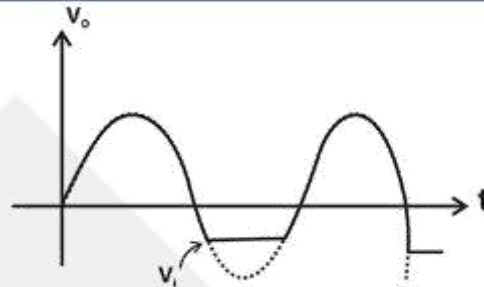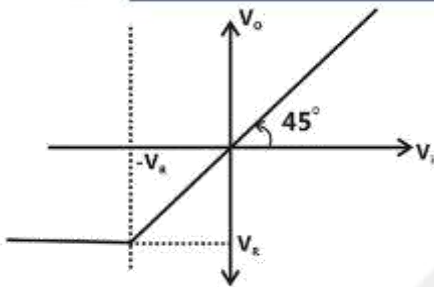

### • Shunt Clipper

#### i) Positive Clipper

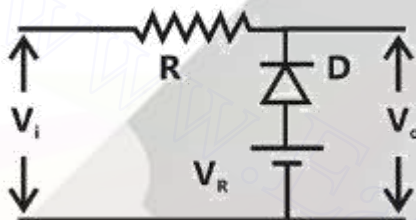


When  $V_i < V_R$ , D is ON

$$V_o = V_R$$

When  $V_i > V_R$ , D is OFF

$$V_o = V_i$$

#### ii) Negative Clipper

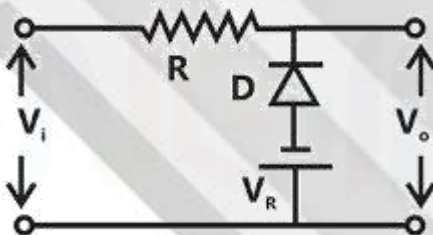


When  $V_i < -V_R$ , D is ON

$$V_o = -V_R$$

When  $V_i > -V_R$ , D is OFF

$$V_o = V_i$$

### • Two level Clipper

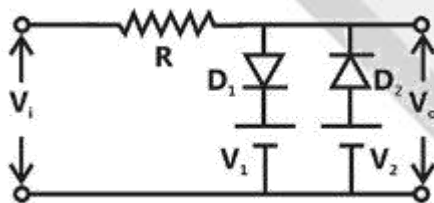

When  $V_i < V_2$ ,  $D_1$  is OFF &  $D_2$  is ON


$$V_o = V_2$$

When  $V_i \geq V_2$  &  $V_i < V_1$ ,  $D_2$  is OFF &  $D_1$  is OFF

$$V_o = V_i$$

When  $V_i > V_1$ ,  $D_2$  is OFF  $D_1$  is ON

$$V_o = V_1$$

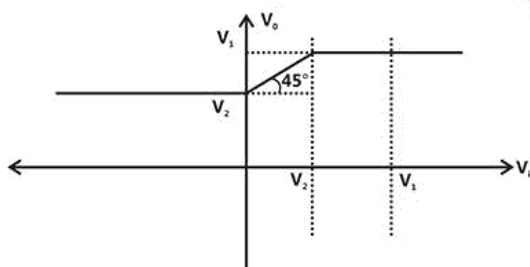







## CLAMPERS

These circuits are used to shift the signal either up words or down words.

- Negative Clampers**

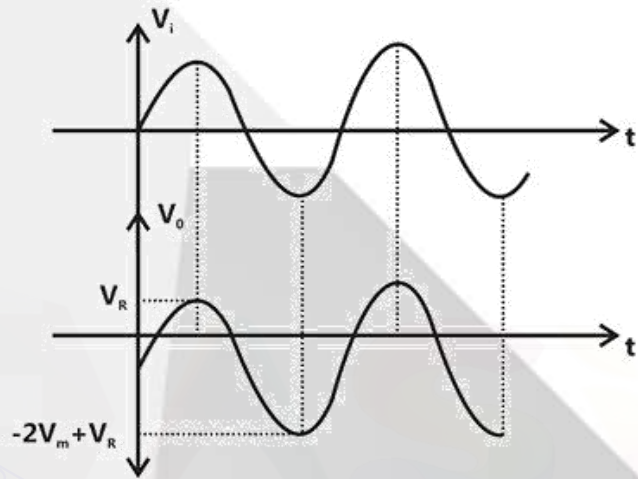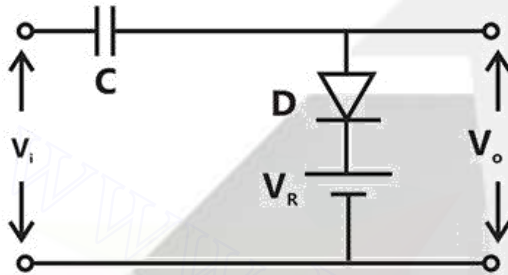

When  $V_R = 0$

+ve peak is shifted to 0


-ve peak is shifted to  $-2V_m$

When  $V_R \neq 0$

+ve peak is shifted to  $V_R$

-ve peak is shifted to  $-2V_m + V_R$

- Positive Clampers**

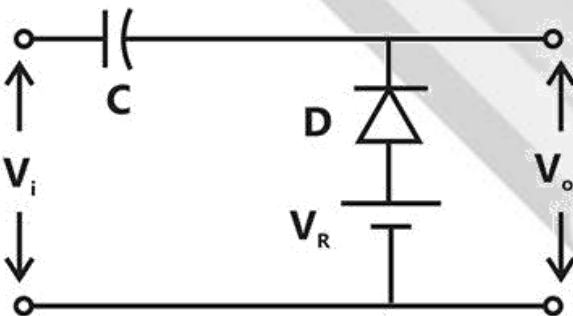



When  $V_R = 0$

-ve peak is shifted to 0

+ve peak is shifted to  $2V_m$

When  $V_R \neq 0$

-Ve peak is shifted to  $V_R$

+ve peak is shifted to  $2V_m + V_R$

### Rectifier


It converts AC signal into pulsating DC.

#### 1) Half wave rectifier

During positive half wave cycle

$$V_0 = V_m \sin \omega t \left[ \frac{R_L}{R_f + R_L} \right]$$

$R_f$  = diode resistance

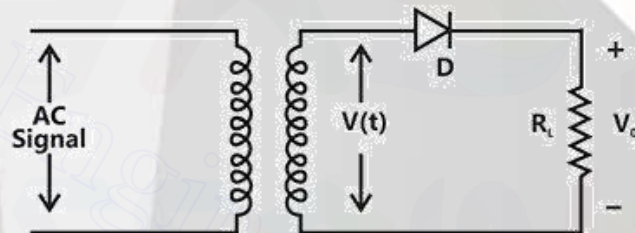

During negative half cycle

$$V_0 = 0$$

- $(V_0)_{avg} = \frac{V_m}{\pi}$
- $\eta = \frac{4}{\pi^2} \left( \frac{R_L}{R_f + R_L} \right) \times 100\%$
- $(V_0)_{RMS} = \frac{V_m}{2}$
- Form Factor =  $\frac{V_{RMS}}{V_{avg}} = \frac{\pi}{2}$
- Ripple factor =  $\sqrt{FF^2 - 1}$
- PIV =  $V_m$




### **Bridge full wave rectifier**

When +ve half wave cycle

$$V_o = V(t) \times \frac{R_L}{R_L + 2R_f}$$

When -ve half wave cycle

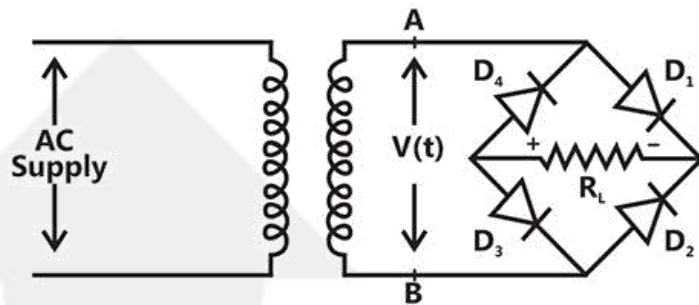
$$V_o = -V(t) \times \frac{R_L}{R_L + 2R_f}$$




- $(V_o)_{avg} = \frac{2V_m}{\pi}$
- $\eta = \frac{8}{\pi^2} \left( \frac{1}{1 + 2 \frac{R_f}{R_L}} \right) \times 100\%$
- $(V_o)_{RMS} = \frac{V_m}{\sqrt{2}}$
- $FF = \frac{\pi}{2\sqrt{2}}$
- $PIV = V_m$
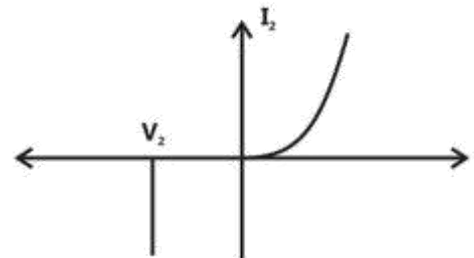
### **Zener Diode**


- A heavily doped a si diode which has sharp breakdown characteristics is called Zener Diode.
- When Zener Diode is forward biased, it acts as a normal PN junction diode.
- For an ideal zener diode, voltage across diode remains constant in breakdown region.
- If  $I_{z(min)}$  is not given, then consider  $I_{z(min)} = 0$



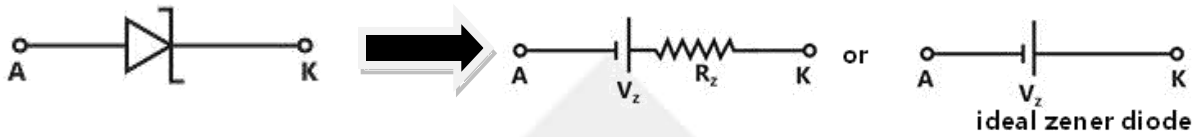
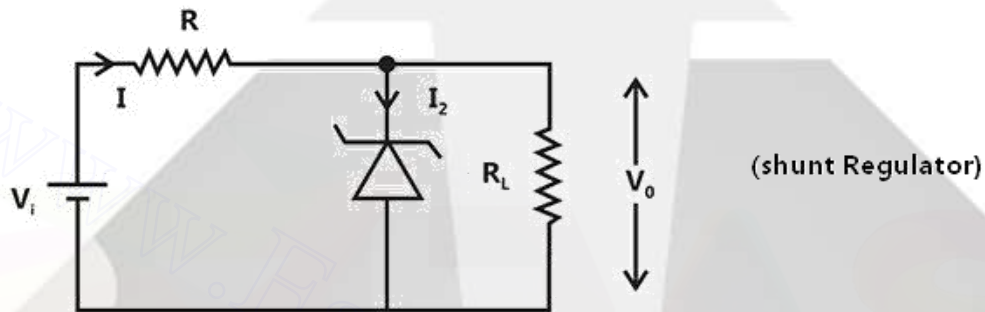
### Voltage Regulator

Regulators maintains constant output voltage irrespective of input voltage variation.



Zener must operate in breakdown region so  $V_i > V_z$

$$I = I_z + I_L$$

$$I_L = \frac{V_z}{R_L}$$

$$\therefore I_{\max} = I_{z(\max)} + I_L$$

$$I_{\min} = I_{z(\min)} + I_L$$

$$\therefore I_{z(\max)} = I_{(\max)} - I_L$$

$$I_{z(\min)} = I_{\min} - I_L$$






## Transistor Biasing


### Bipolar Junction Transistor

- Current conduction due to both e<sup>-</sup> & holes
- It is a current controlled current source.

#### NPN Transistor

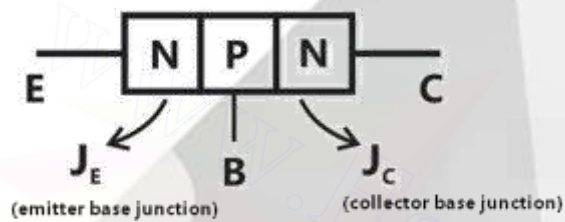

#### PNP Transistor

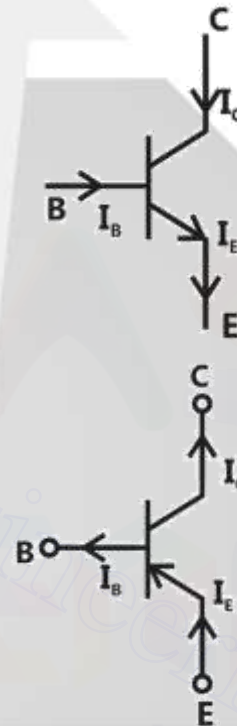

#### Region of Operation

Junctions	Region of operations	Applications
i) $J_E = RB$ $J_C = RB$	cut – off	Switch
ii) $J_E = FB$ $J_C = RB$	active	amplifier
iii) $J_E = FB$ $J_C = FB$	saturation	Switch
iv) $J_E = RB$ $J_C = FB$	reverse active	Attenuation



### Current gain ( $\alpha$ ) (common base)

$$I_C = I_{nc} + I_O$$

$I_{nc}$  : injected majority carrier current in collector

$$\alpha = \frac{I_{nc}}{I_E}$$

$$I_C = \frac{\alpha I_B + I_O}{(1-\alpha)} ; I_E = \frac{I_B}{(1-\alpha)} + \frac{1}{(1-\alpha)} I_O$$

### Current gain $\beta$ (common emitter)


$$I_C = \beta I_B + (1+\beta) I_O$$

$$\alpha = \frac{\beta}{1+\beta} ; \beta = \frac{\alpha}{(1-\alpha)}$$

- These relations are valid for active region of operations.

### Characteristics of BJT


- Common Base characteristics

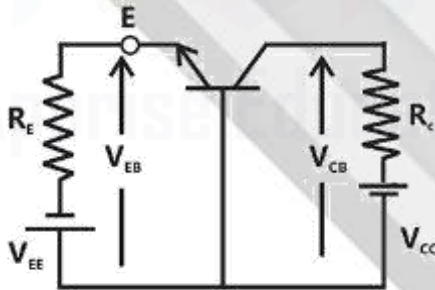

input =  $V_{BE}, I_E$   
output =  $V_{CB}, I_C$


Input characteristics

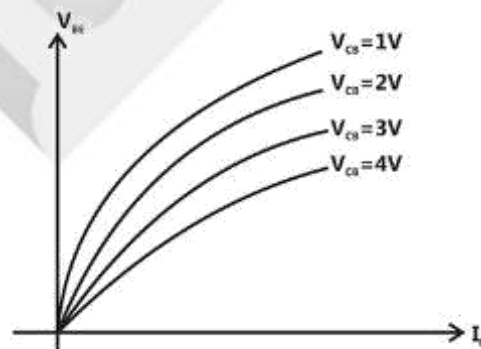$V_{BE}$  vs  $I_E$  when  $V_{CB} = \text{constant}$







### Output characteristics

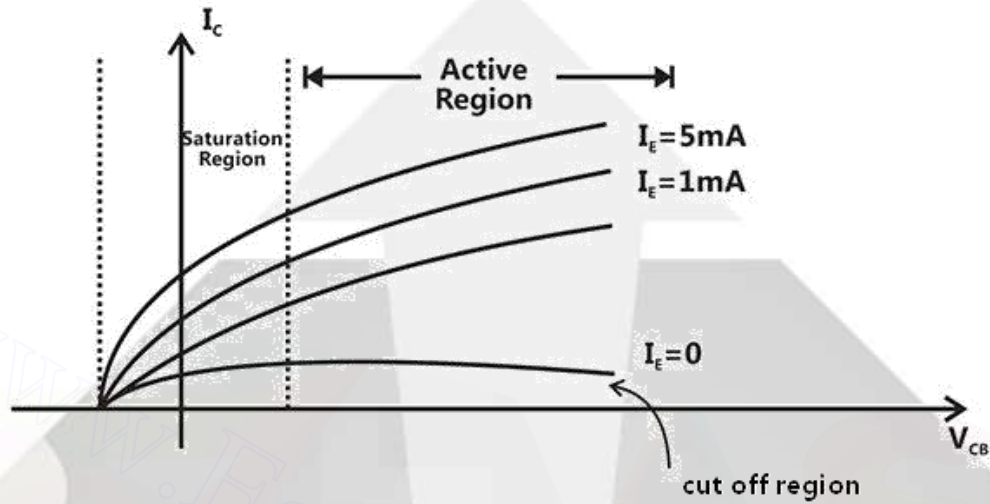

### Common emitter characteristics

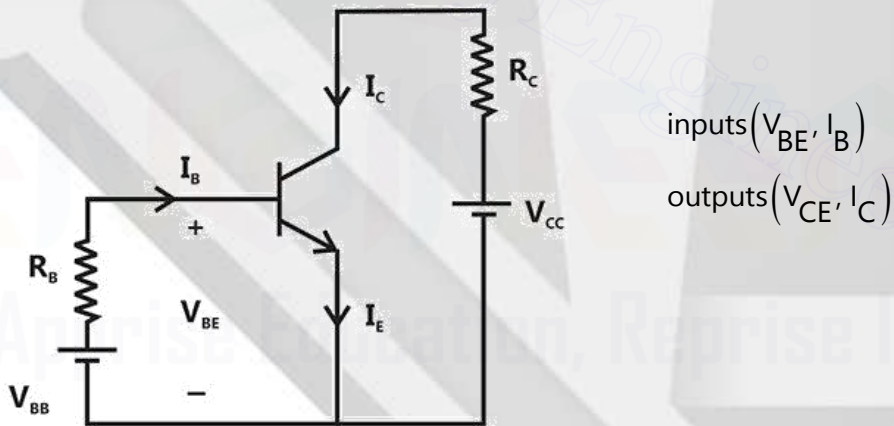


### Input characteristics

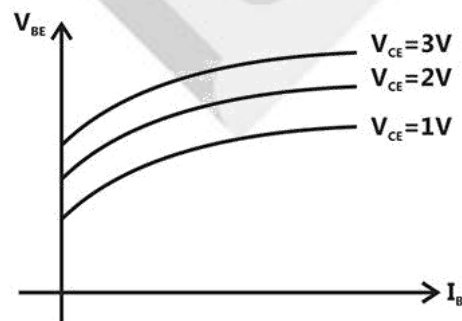



### Output characteristics

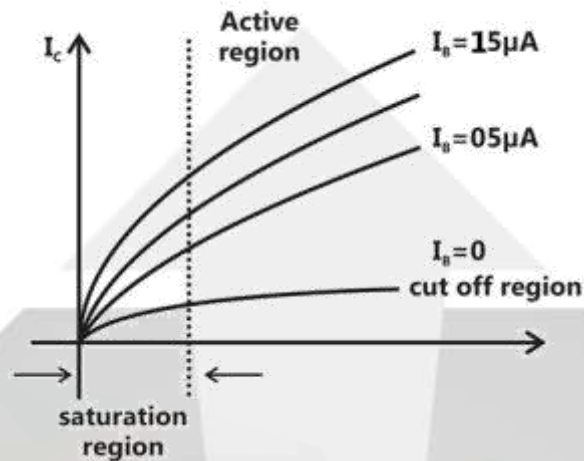

### Transistor Biasing

#### 1) Fixed Bias method

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

Assuming active region of operation

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - I_C R_C$$


#### Verification

- If  $V_{CE(sat)} < V_{CE} < V_{CC} \rightarrow$  Active Region  
If not ; then saturation region

- For saturation region ,  $V_{CE} = V_{CE(sat)}$

$$I_C = \frac{V_{CC} - V_{CE(sat)}}{R_C}$$

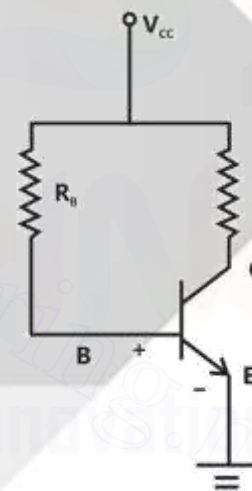- In saturation region ,  $I_B \geq \frac{I_C}{\beta_{min}}$







## 2) Feedback Resistor Bias Method

By KVL

$$V_{CC} - (I_C + I_B)R_C - I_B R_B - V_{BE} - I_E R_E = 0$$


$$V_{CC} - (I_C + I_B)R_C - I_B R_B - V_{BE} - (I_C + I_B)R_E = 0$$

Assuming active region

$$I_C = \beta I_B$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1 + \beta)(R_C + R_E)} ; I_C = \beta I_B$$
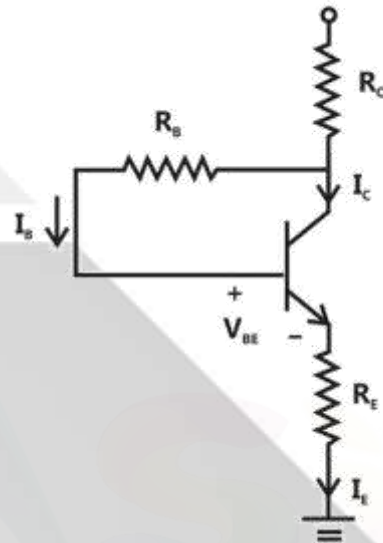
$$V_{CE} = V_{CC} - (I_C + I_B)(R_C + R_E)$$



## 3) Voltage divider bias or self-bias

By thevenin's theorem across  $R_2$

$$V_{TH} = V_{CC} \frac{R_2}{R_1 + R_2}$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$


Apply KVL

$$V_{TH} - V_{BE} = I_B R_{TH} + (I_B + I_C) R_E$$

Assuming active region  $I_C = \beta I_B$


$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta) R_E}$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

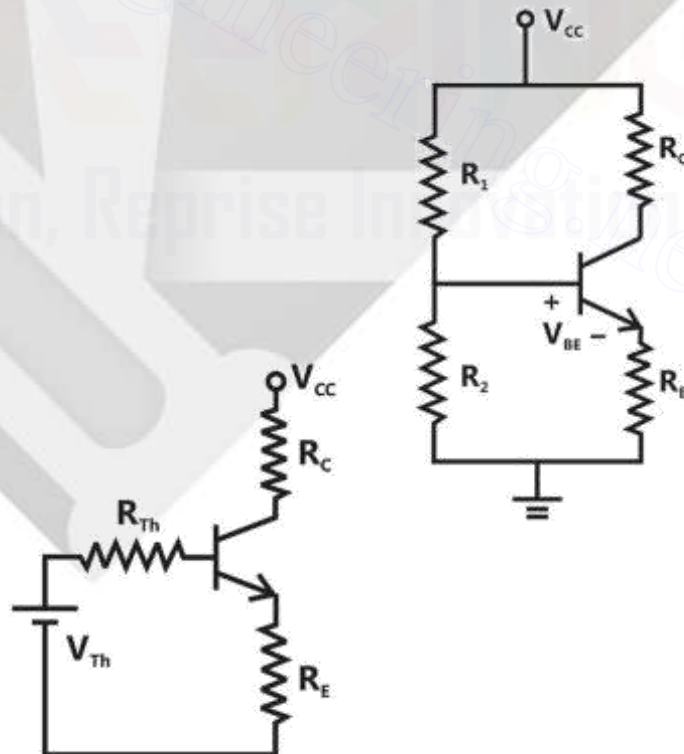

## FET Biasing

### JFET

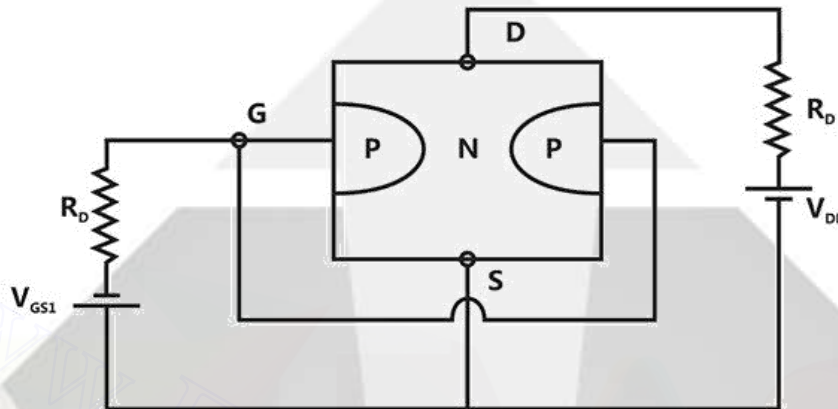

- When  $V_{GS}$  is negative, depletion layer is created between two P – region and that pinches the channel between drain & source.
- The voltage at which drain current is reduce to zero is called as pinch off voltage.
- Transfer – characteristics of JFET is inverted parabola

$$I_D = I_{DSS} \left[ 1 - \frac{V_{GS}}{V_{GS(OFF)}} \right]^2$$

When  $V_{GS} = 0$ ,  $I_D = I_{DSS}$

When  $V_{GS} = V_{GS(OFF)}$ ,  $I_D = 0$

Pinch of voltage,  $V_p = |V_{GS(OFF)}|$

- For a N – channel JFET, pinch off voltage is always positive

$$V_p > 0 \text{ \& } V_{GS} < 0$$



### JFET Parameters

#### 1) Drain Resistance

$$r_d = \frac{\Delta V_{DS}}{\Delta I_{DS}}$$

It is very high, of the order of  $M\Omega$ .

#### 2) Trans conductance

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}} = \frac{dI_D}{dV_{GS}}$$


$$I_D = I_{DSS} \left[ 1 - \frac{V_{GS}}{V_{GS(OFF)}} \right]^2$$

$$\frac{dI_D}{dV_{GS}} = g_m = \frac{-2I_{DSS}}{V_{GS(OFF)}} \left[ 1 - \frac{V_{GS}}{V_{GS(OFF)}} \right]$$

#### 3) Amplification factor

$$\mu = \frac{\Delta V_{DS}}{\Delta V_{GS}} = g_m r_d$$
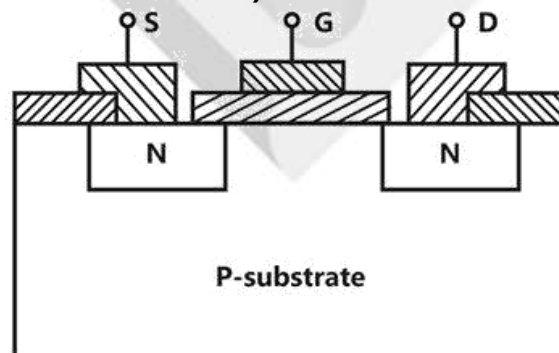
### MOSFET (Metal Oxide Semi-conductor FET)







### Enhancement Type MOSFET

- No physical channel between source & drain
- To induce a channel Gate – source voltage is applied.

### Depletion MOSFET

- Physical channel present between source & drain.

### Types of MOSFET

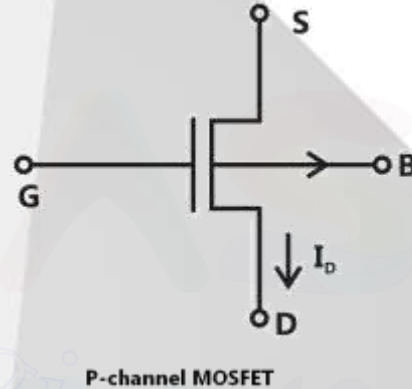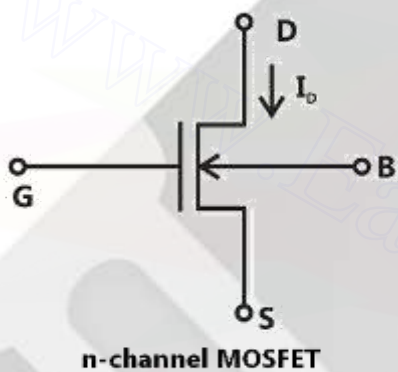

### Operating characteristics

#### 1. For n – channel MOSFET

- $I_D = 0$  for  $V_{GS} < V_T$  (cut – off region)

- $I_D = \mu_n C_{ox} \frac{W}{L} \left[ (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$  (linear region)

$$V_{GS} \geq V_T \text{ and } V_{DS} < (V_{GS} - V_T)$$

- $I_D = \mu_n C_{ox} \frac{W}{L} \frac{(V_{GS} - V_T)^2}{2}$  (saturation region)

$$V_{GS} \geq V_T \text{ and } V_{DS} \geq (V_{GS} - V_T)$$






## 2. For p – channel MOSFET

- $I_D = 0$  for  $V_{GS} > V_T$  (cut – off region)
- $I_D = \mu_n C_{ox} \frac{W}{L} \left[ (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$  (linear region)  
 $V_{GS} \leq V_T$  and  $V_{DS} > V_{GS} - V_T$
- $I_D = \mu_n C_{ox} \frac{W}{L} \frac{(V_{GS} - V_T)^2}{2}$  (saturation region)  
 $V_{GS} \leq V_T$  and  $V_{DS} \leq V_{GS} - V_T$

## Transistor Amplifier

### Small signal analysis for BJT

- h – parameter model of BJT

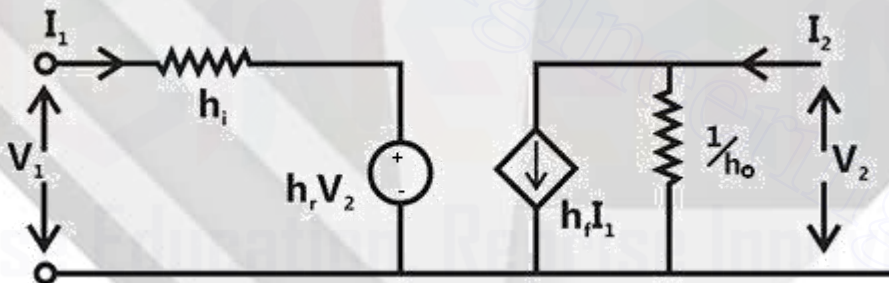


$$V_1 = h_i I_1 + h_r V_2$$

$$I_2 = h_f I_1 + h_o V_2$$

- current gain,  $A_I = -\frac{I_2}{I_1}$   

$$A_I = \frac{-h_f R_L}{1 + h_o R_L}$$

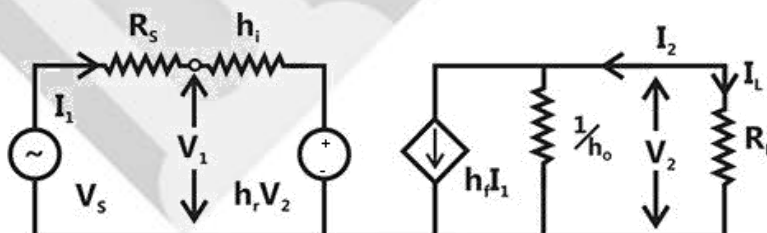


- Input Impedance,  $Z_i = \frac{V_1}{I_1} = h_i + h_r A_I R_L$




- Voltage gain,  $A_V = \frac{A_I R_L}{Z_i}$
- Output impedance,  $Z_o = \frac{1}{\left( h_o - \frac{h_f h_r}{h_i + R_s} \right)}$

### Common Emitter (CE) Amplifier

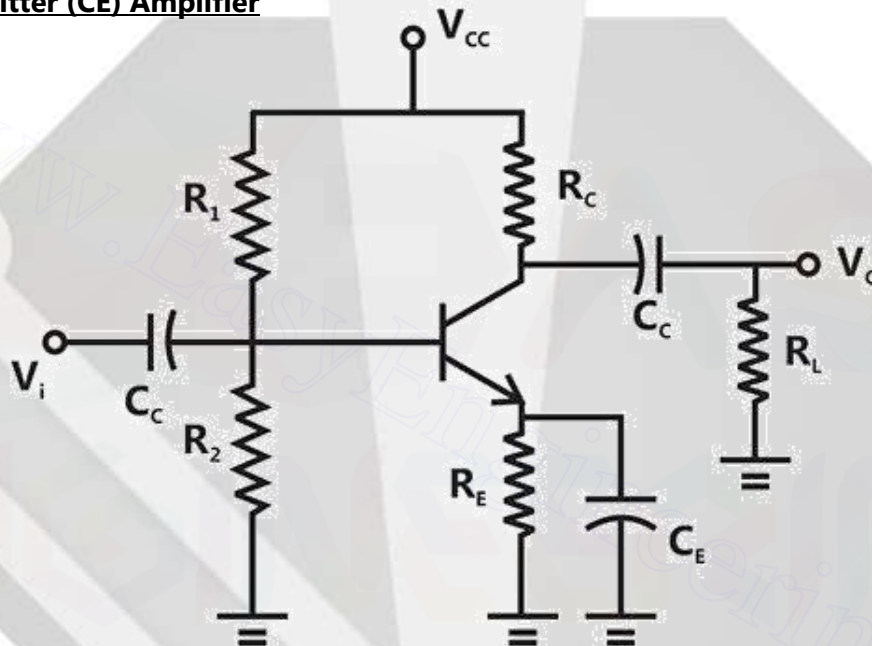


### Small signal model

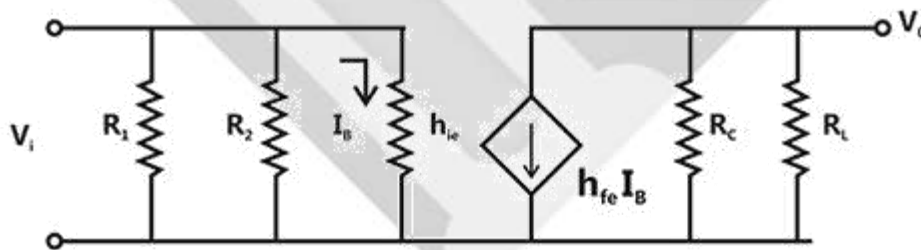

$$\text{Voltage gain } A_V = \frac{V_o}{V_i} = \frac{-h_{fe}}{h_{ie}} (R_c \parallel R_L)$$



### High frequency Analysis of BST

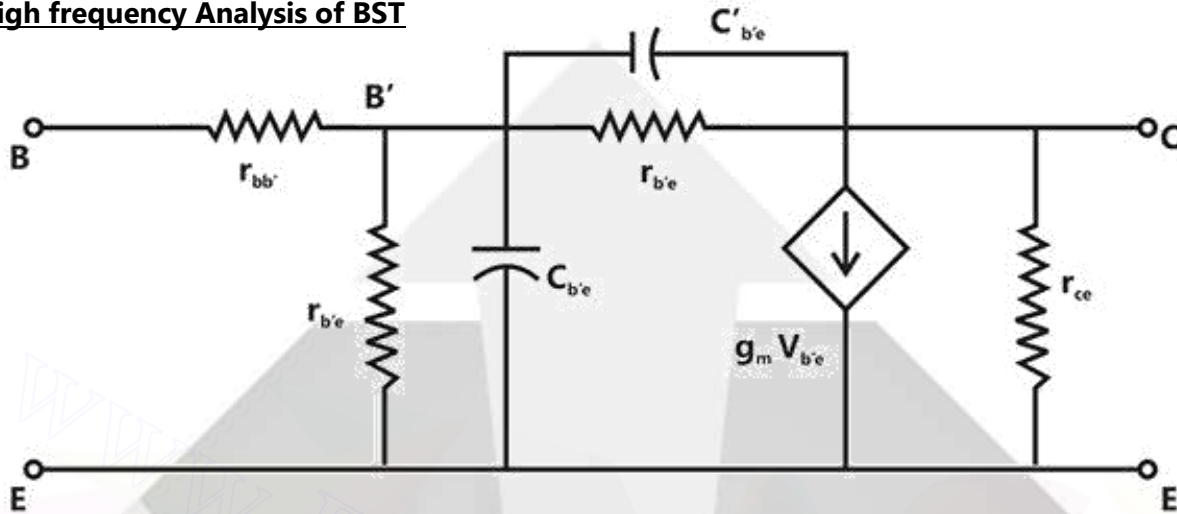

$r_{bb'}$  = base spreading resistance.

$r_{b'e}$  = input resistance.

$r_{b'c}$  = feedback resistance.

$r_{ce}$  = output resistance.

$C_{b'e}$  = diffusion capacitance.

$C_{b'c}$  = Transition capacitance.

$g_m$  = Transconductance.

### Hybrid $\pi$ - parameters


$$1) \quad g_m = \frac{(I_C)_Q}{V_T} \quad ; \quad V_T = \frac{KT}{q},$$

$I_{CQ}$  = dc bias point collector current.


$$2) \quad r_{b'e} = \frac{h_{fe}}{g_m}$$




### High Frequency Model

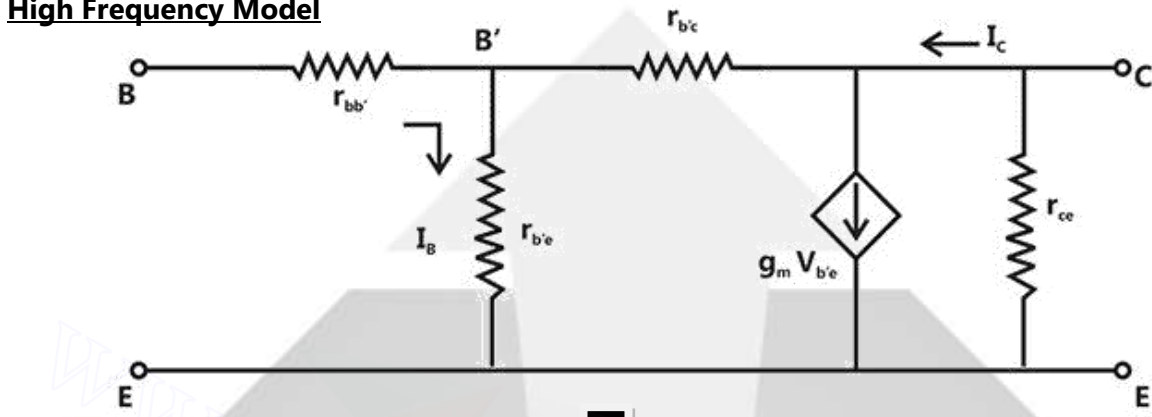

$r_{b'c}$  = open circuited.

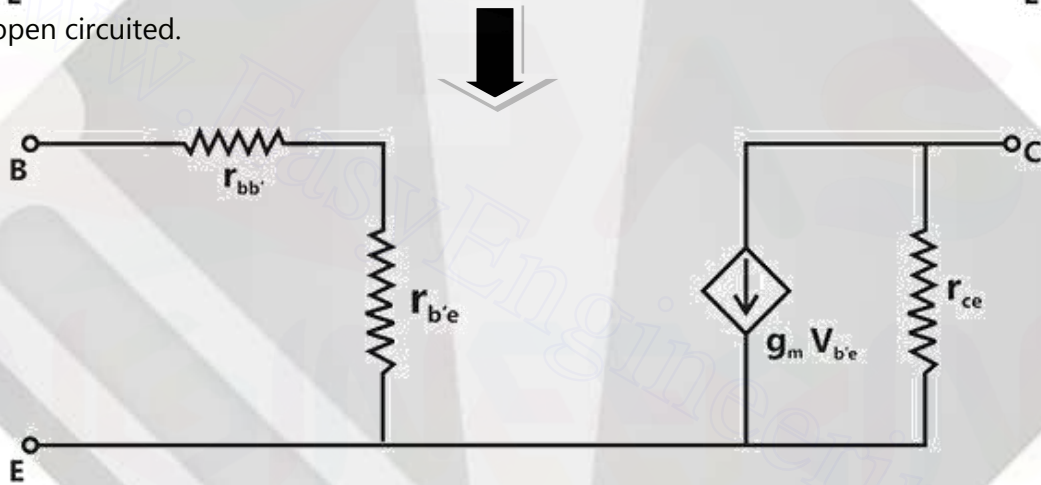



### Low Frequency Model

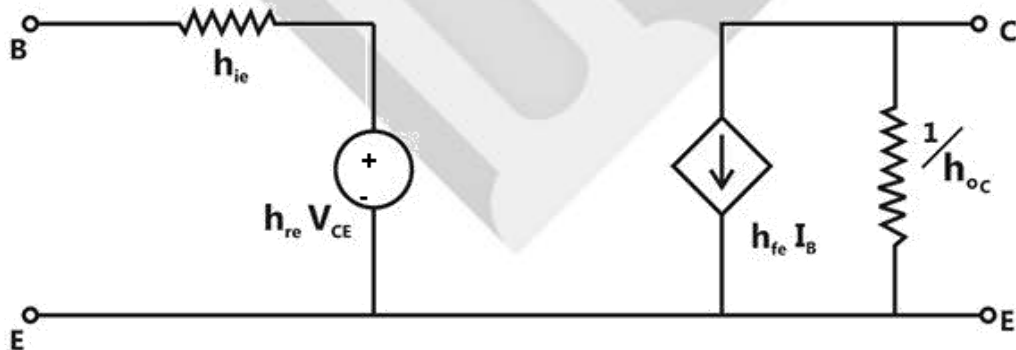






### Voltage gain as frequency

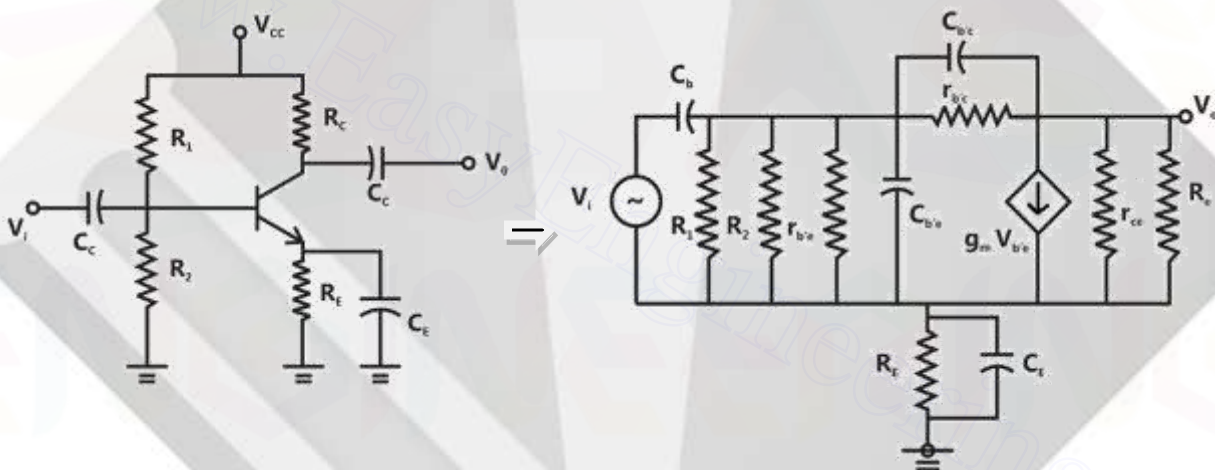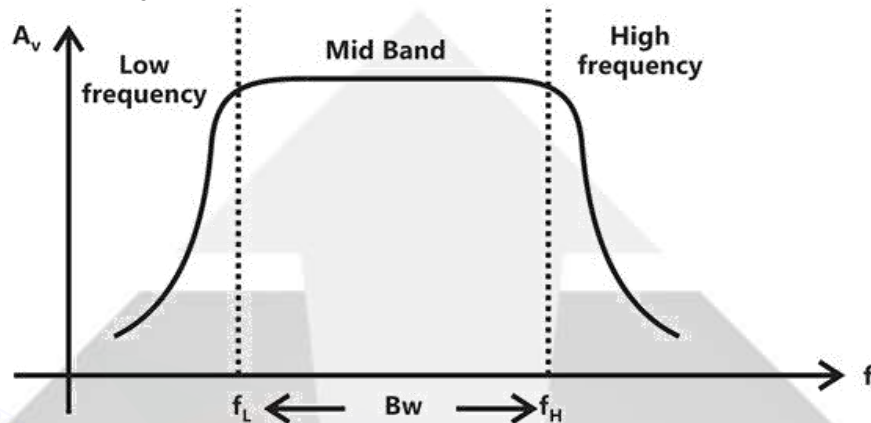
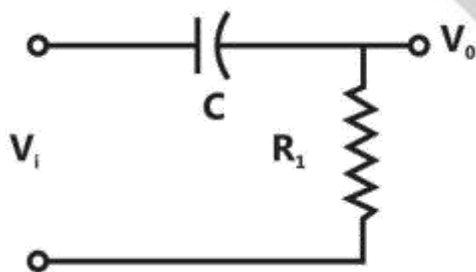
### Low Frequency Range

- External capacitor  $C_E$  and  $C_C$  are short circuited.
- Internal capacitor  $C_{b'c}$  and  $C_{b'e}$  are open circuited.
- Circuit becomes like.



= acts as high pass filter.



### High frequency range

- External capacitors  $C_b, C_c$  and  $C_E$  are short circuited.
- $C_{b'c}$  is open circuited.
- Equivalent circuit behaves as a low pass filter with cut-off frequency  $f_L$ .

### Mid – band range

- All internal and external capacitance are neglected, so gain is independent of frequency.

### FET Small Signal parameters

Trans conductance,  $g_m = \frac{\partial I_D}{\partial V_{GS}}$


In non – saturation region

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L} \cdot V_{DS}$$

In saturation region


$$g_{ms} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)$$

### Small Signal equivalent circuit

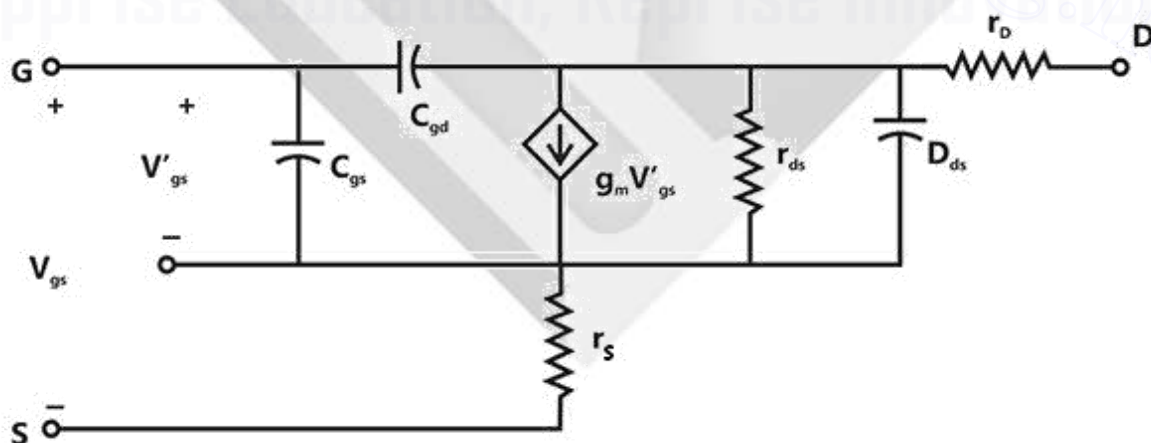




For low frequency

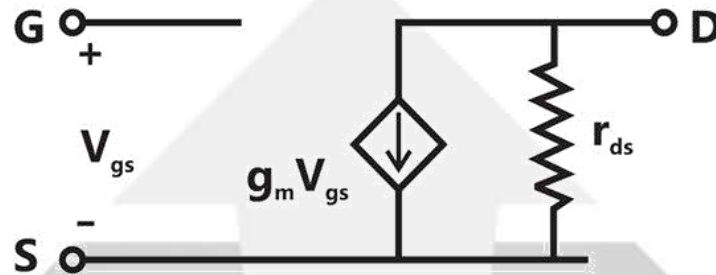

For high frequency

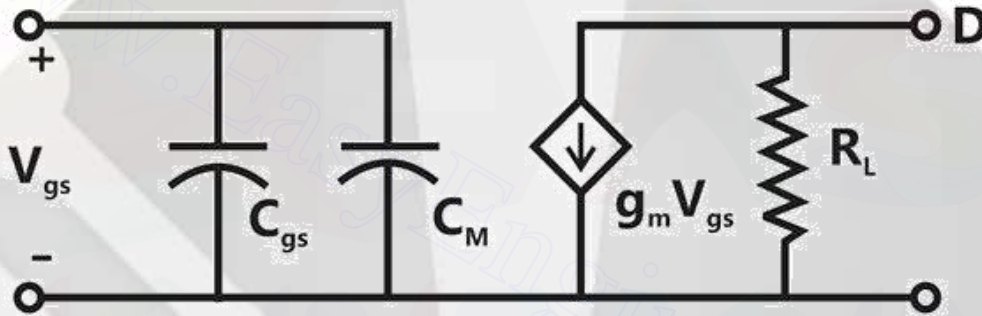

## Feedback Amplifiers

Ideal Amplifier

$$Z_{in} = \infty$$


$$Z_o = 0$$

Positive feedback :  $V_i = V_s + V_f$

Negative Feedback :  $V_i = V_s - V_f$

For negative feedback,  $\frac{V_o}{V_s} = \frac{A}{1 + A\beta}$

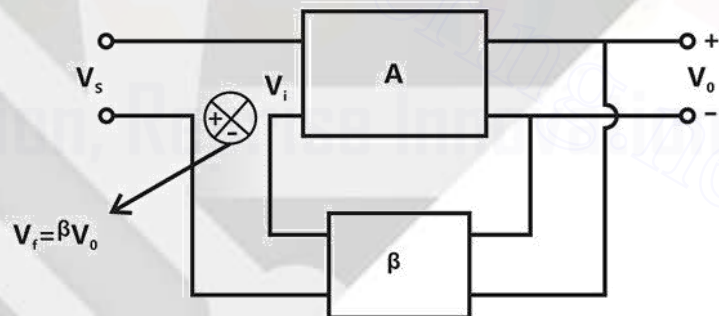For positive feedback,  $\frac{V_o}{V_s} = \frac{A}{1 - A\beta}$



- Positive feedback is used for unstable system like oscillators.



## Effects of Negative Feedback

### i) Sensitivity

$$\text{Without feedback} = \frac{\delta A}{A}$$

$$\text{With feedback} = \frac{\delta A_f}{A_f}$$

$$\frac{\delta A_f}{A_f} = \frac{1}{(1 + A\beta)} \frac{\delta A}{A}$$

### ii) Input Impedance

$$\text{Without feedback} = Z_i$$

$$\text{With feedback} = Z_{if}$$

$$Z_{if} = Z_i (1 + A\beta)$$

### iii) Output impedance

$$\text{Without feedback} = Z_o$$

$$\text{With feedback} = Z_{of}$$

$$Z_{of} = Z_o / (1 + A\beta)$$

- Negative feedback also leads to increase in band width


## Topologies of Negative feedback

Output	Input
Voltage	Series
Voltage	Shunt
Current	Series
Current	Shunt



### 1) Voltage Series Topologies

$$V_f = \beta V_o$$

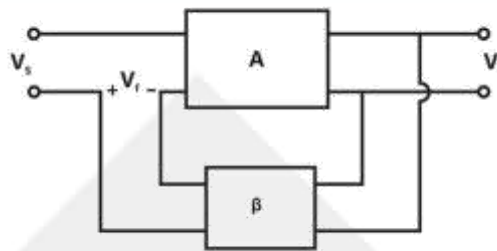


It is called as series shunt feedback or voltage - voltage feedback.

In this case, input impedance increases & output impedance decreases.

### 2) Voltage shunt topologies

$$I_f = \beta V_o$$

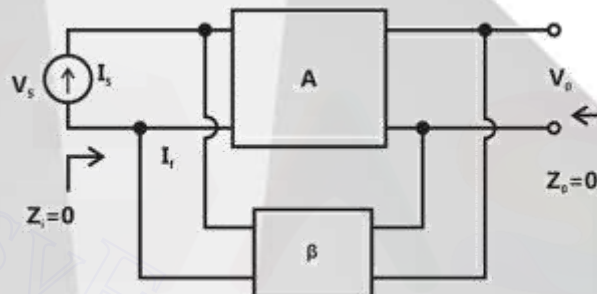

$\beta$  = Trans conductance

It is called as shunt-shunt or voltage current feedback.

### 3) Current series Topologies

$$V_f = \beta I_o$$


$\beta$  = resistance



It is called as shunt – shunt or voltage current feedback.

### 4) Current shunt Topologies

$$I_f = \beta I_o$$

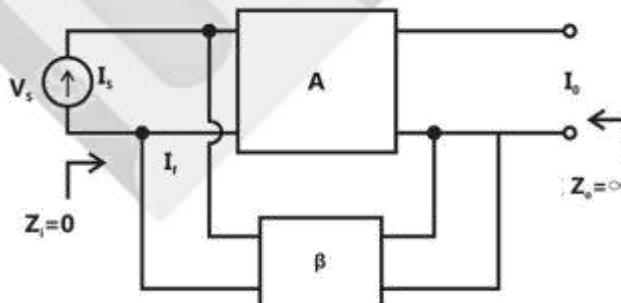


It is also called as shunt – series or current – current feedback.






### Circuit Topologies


#### 1) Voltage series

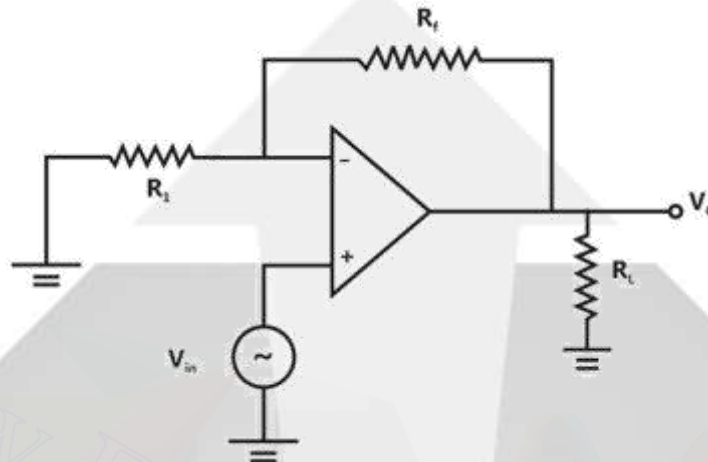

#### 2) Voltage shunt

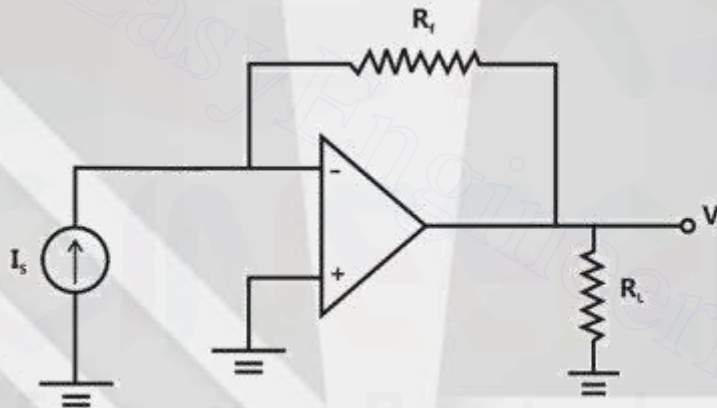


#### 3) Current – series

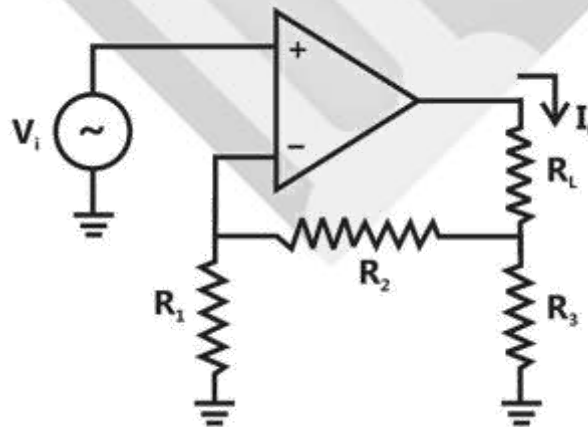




#### 4) Current – shunt

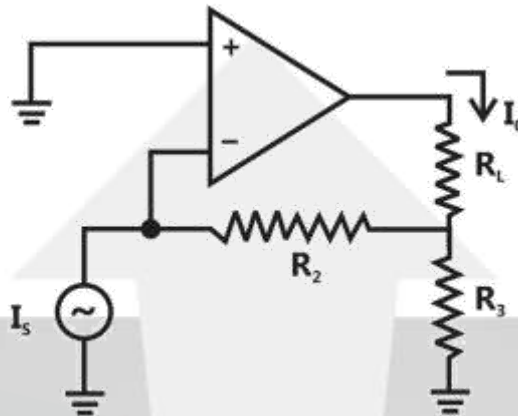

### Operational Amplifiers (OP-AMP)

+ → Non – inverting terminal

- → inverting terminal

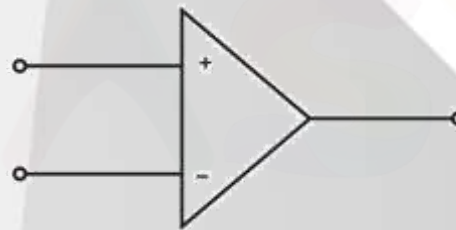

#### Parameters of OP-AMP

##### 1) Input offset voltage

Voltage applied between input terminals of OP – AMP to null or zero the output.

##### 2) Input offset current

Difference between current into inverting and non – inverting terminals of OP – AMP.

##### 3) Input Bias Current

Average of current entering the input terminals of OP – AMP.

##### 4) Common mode Rejection Ratio (CMRR)

Defined as ratio of differential voltage gain  $A_d$  to common mode gain  $(A_{cm})$ .

$$CMRR = \frac{A_d}{A_{cm}}$$

5) Slew Rate

Maximum rate of change of output voltage per unit time under large signal conditions.


$$SR = \left. \frac{dV_o}{dt} \right|_{\max} \quad V/\mu s$$

**Concept of Virtual ground**


In an OP – AMP with negative feedback, the potential at non – inserting terminals is same as the potential at inverting terminal.

**Applications of OP –AMP**1) Inverting Amplifier


$$V_o = -\frac{R_f}{R_1} V_{in}$$

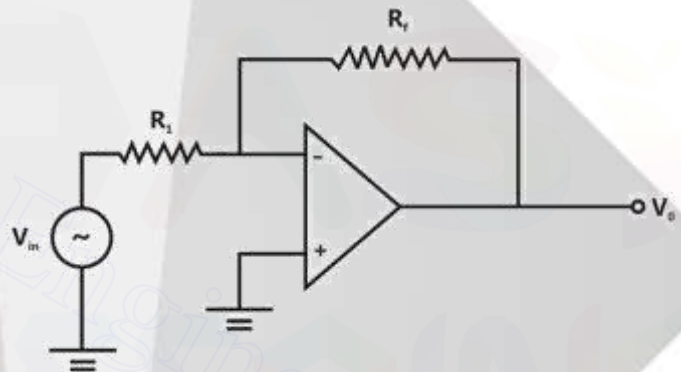2) Inverting Summer

$$V_o = -R_f \left( \frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} \right)$$

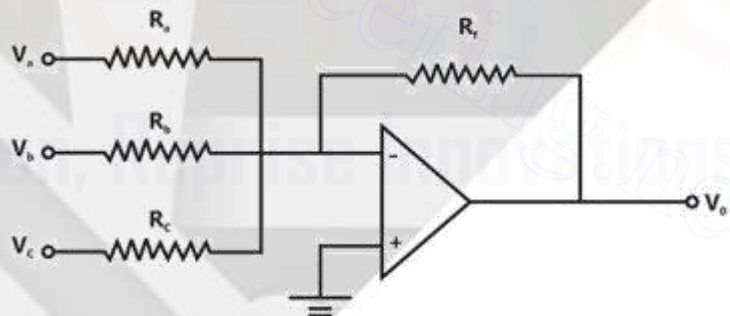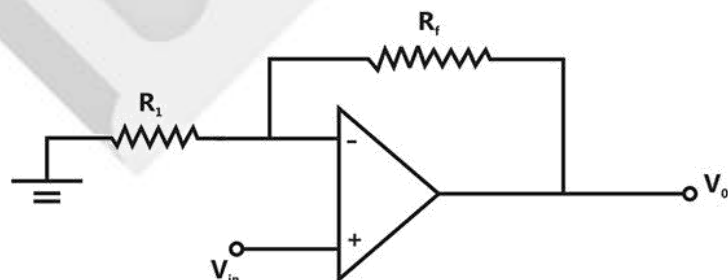3) Non – inverting Amplifier

$$V_o = \left( 1 + \frac{R_f}{R_1} \right) V_{in}$$






#### 4) Non – inverting summer

If  $R_a = R_b = R_c = R$

$$V_1 = \frac{V_a \left(\frac{R}{2}\right)}{R + \frac{R}{2}} + \frac{V_b \left(\frac{R}{2}\right)}{R + \frac{R}{2}} + \frac{V_c \left(\frac{R}{2}\right)}{R + \frac{R}{2}}$$

$$V_1 = \frac{(V_a + V_b + V_c)}{3}$$
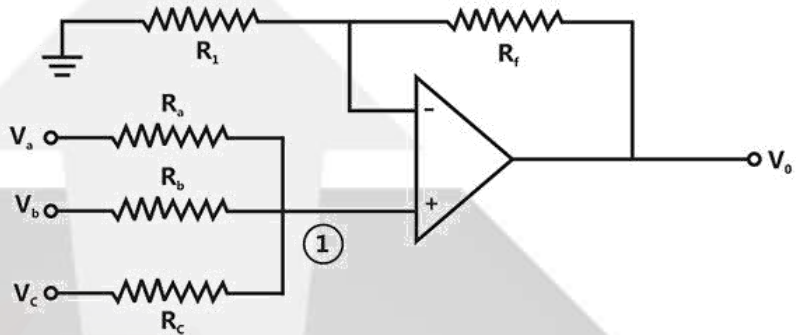
$$V_o = \left(1 + \frac{R_f}{R_1}\right) \left(\frac{V_a + V_b + V_c}{3}\right)$$




#### 5) Differential Amplifier

By Super position

$$V_{ob} = \left(1 + \frac{R_f}{R_1}\right) \left(\frac{R_3}{R_2 + R_3}\right) V_b$$


$$V_{oa} = \frac{-R_f}{R_1} V_a$$

$$V_o = V_{oa} + V_{ob}$$

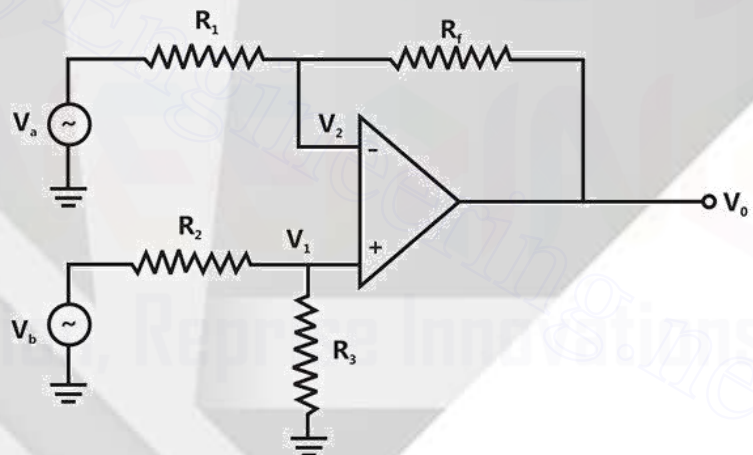

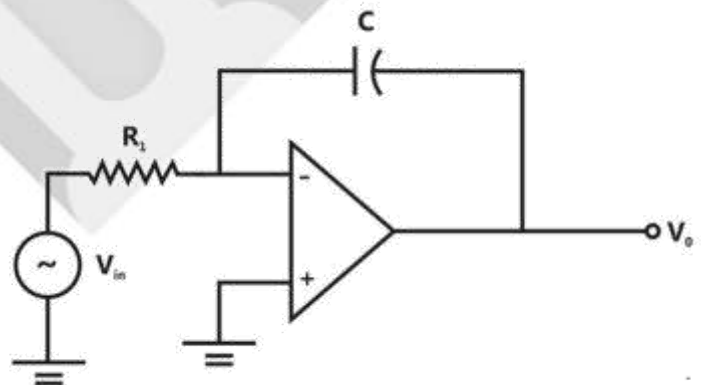
#### 6) Integrator

$$V_o = \frac{-1}{RC} \int_0^t V_{in} dt$$





 7) Differentiator


$$V_o = -RC \frac{dV_{in}}{dt}$$

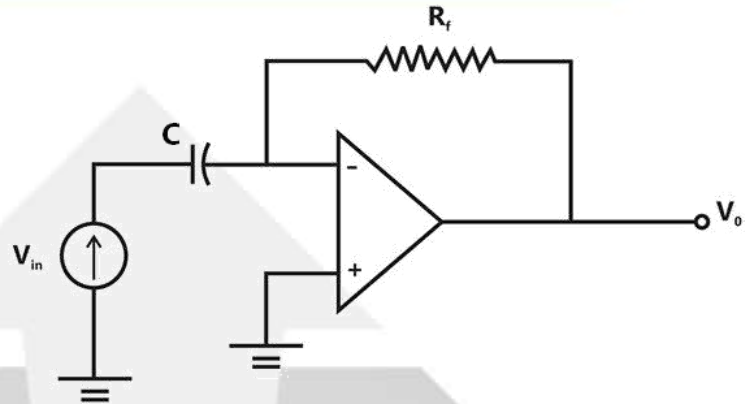
 8) Voltage to current converter

$$I_L = \frac{V_{in}}{R}$$

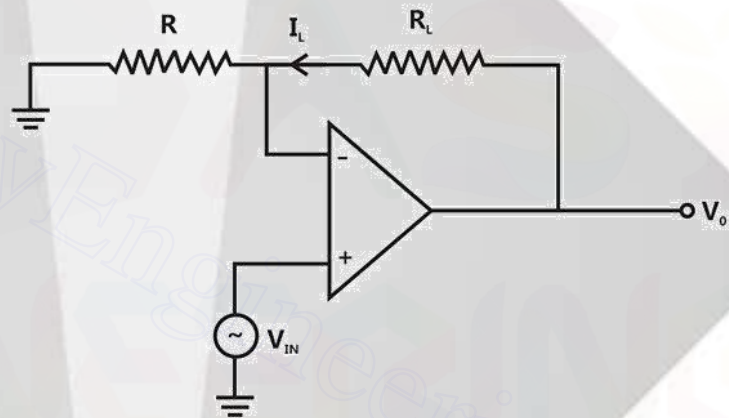
 9) Current to voltage Converter

$$V_{out} = -R_p I_{IN}$$

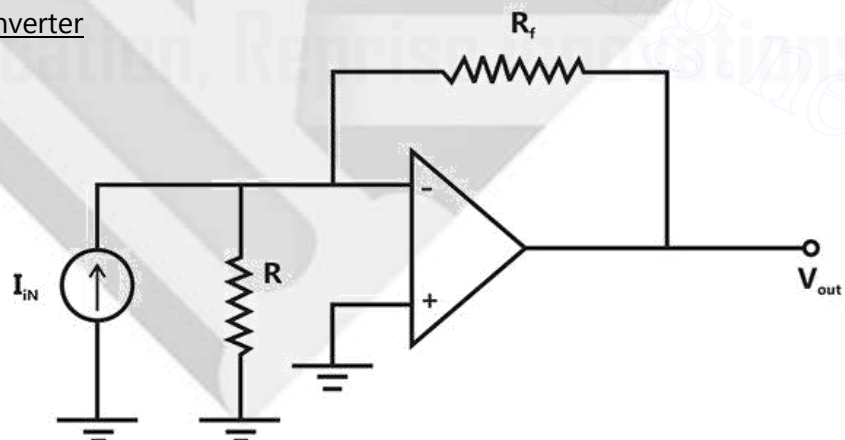





 10) Butter – worth Low Pass Filter

$$V_o = \left( 1 + \frac{R_f}{R_1} \right) \frac{V_{in}}{(1 + j2\pi fRC)}$$

$$\frac{V_o}{V_{in}} = \frac{A_f}{1 + j \left( \frac{f}{f_H} \right)}$$

$$A_f = \left( 1 + \frac{R_f}{R_1} \right) ; f_H = \frac{1}{2\pi RC}$$

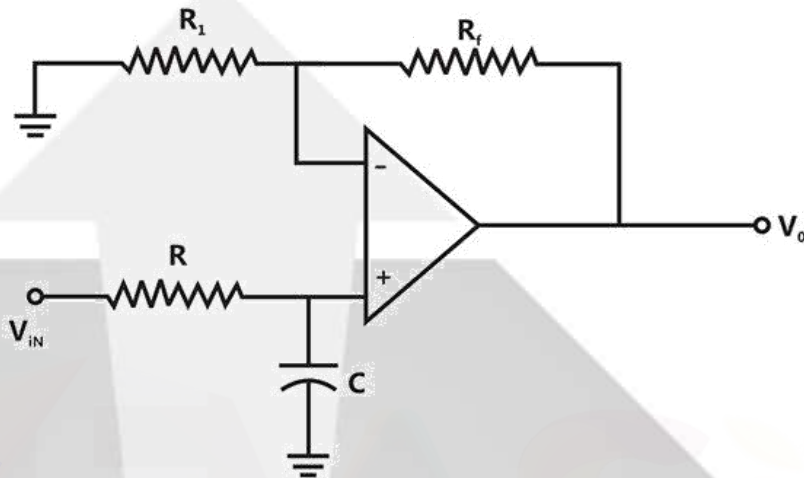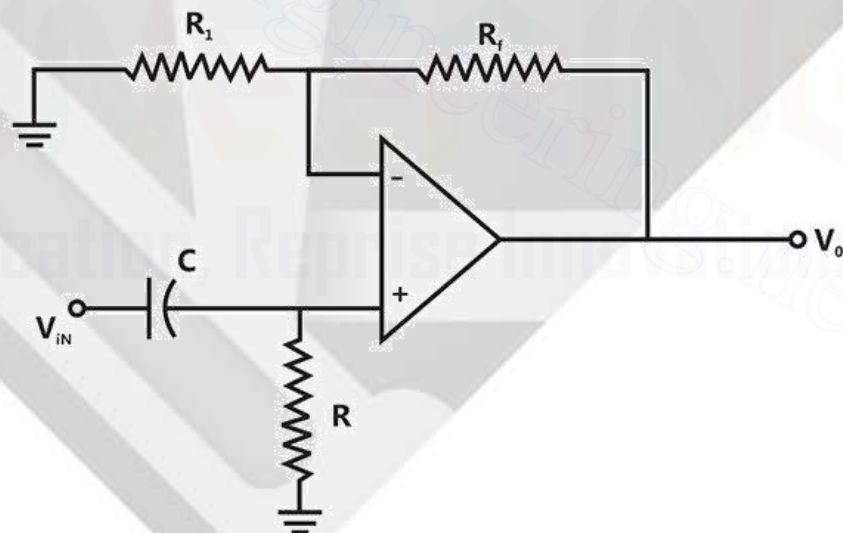

 11) Butter – worth High Pass Filter

$$\frac{V_o}{V_{in}} = \left( 1 + \frac{R_f}{R_1} \right) \left( \frac{j2\pi fRc}{1 + j2\pi fRC} \right)$$

$$= A_f \left[ \frac{j \left( \frac{f}{f_L} \right)}{1 + j \left( \frac{f}{f_L} \right)} \right]$$

$$A_f = 1 + \frac{R_f}{R_1}$$

$$f_L = \frac{1}{2\pi RC}$$






### 12) Active Half – wave rectifier

In this circuit, diode voltage drop between


input & output is not  $V_D$  but rather  $\frac{V_D}{A}$ ,

where  $A$  = open loop gain of OP – AMP.



$$\therefore V_{in} \approx V_o$$

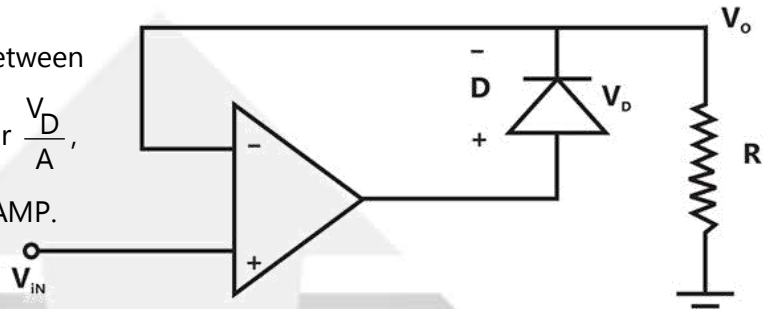

### 13) Active Full – wave Rectifier

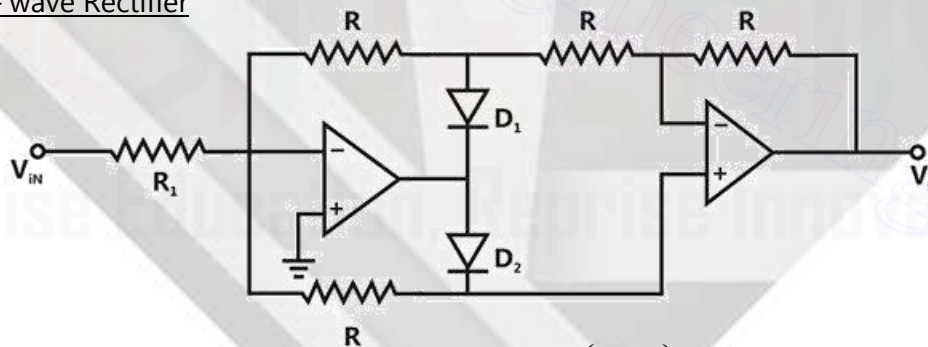

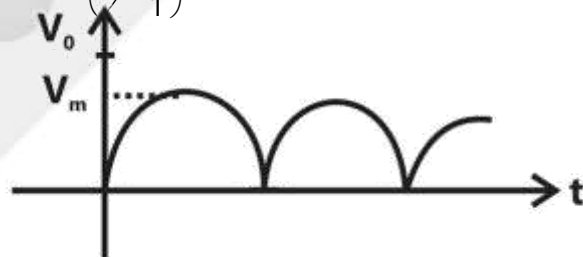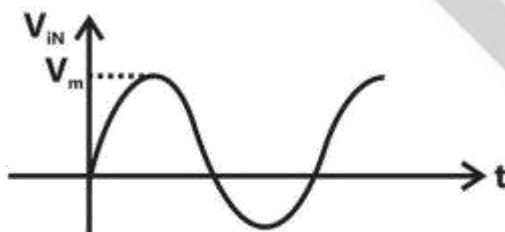This circuit provides full wave rectification with a gain of  $\left(\frac{R}{R_1}\right)$



$$V'_m = \frac{R}{R_1} V_m$$





#### 14) Active Clipper

$V_{IN} < V_R$ , Diode conducts and  $V_O = V_R$

And when  $V_{IN} > V_R$  Diode is OFF



$\therefore V_O = V_{IN}$





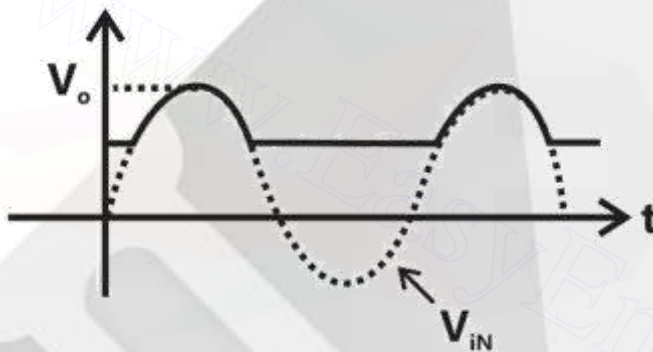
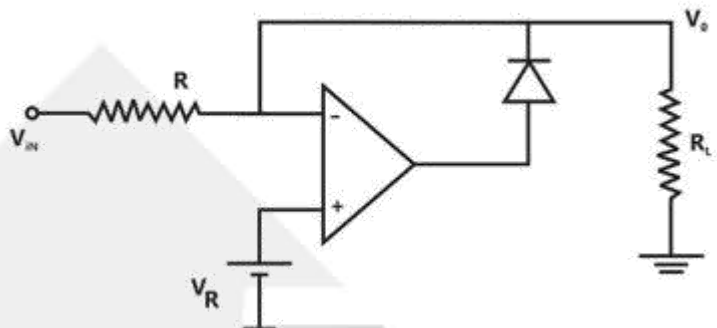


#### 15) Active Clamper

$V_O = V_{IN} + V_p$

$V_p$  = peak value of  $V_{IN}$

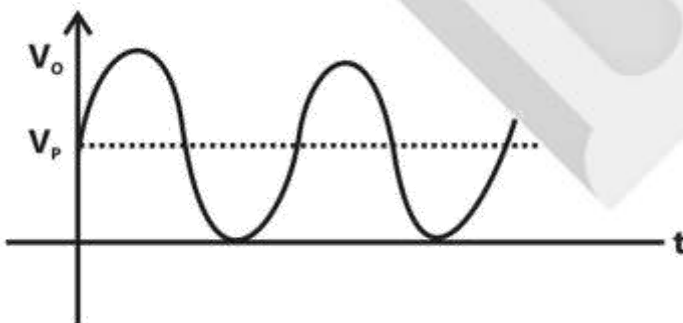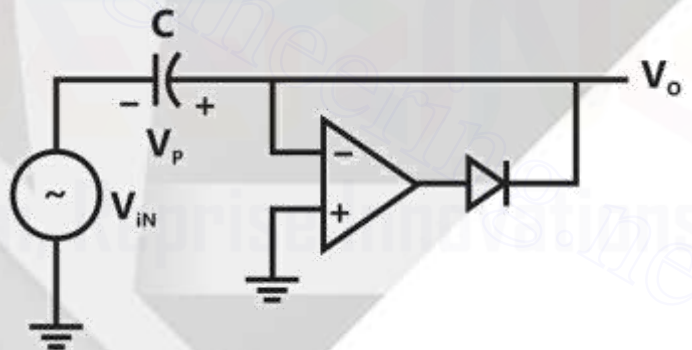


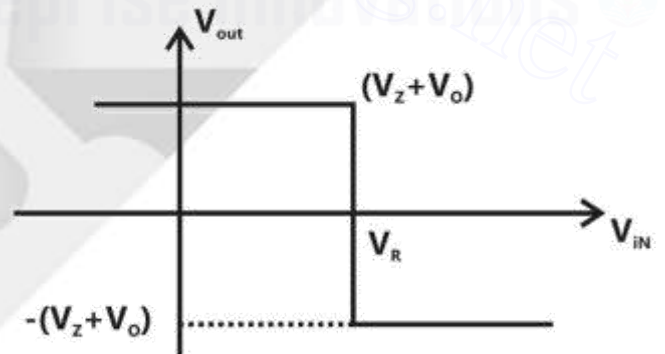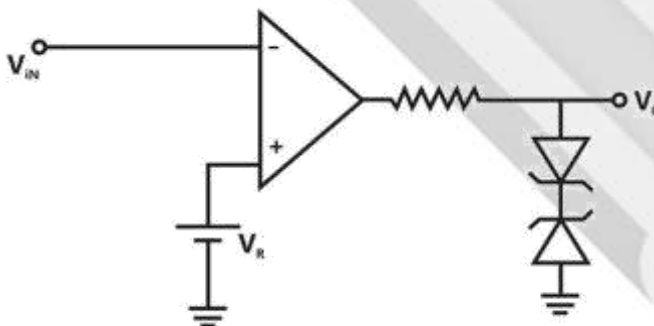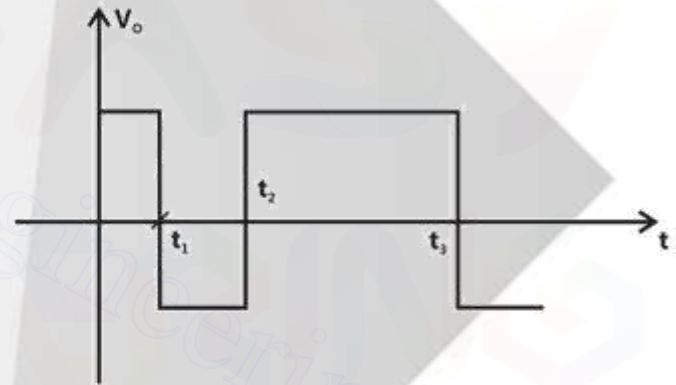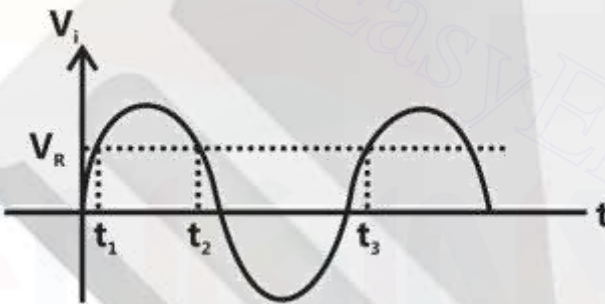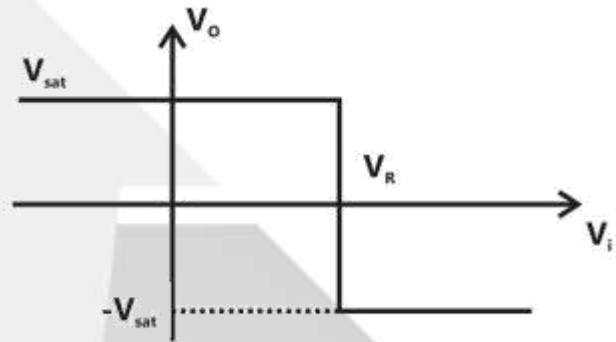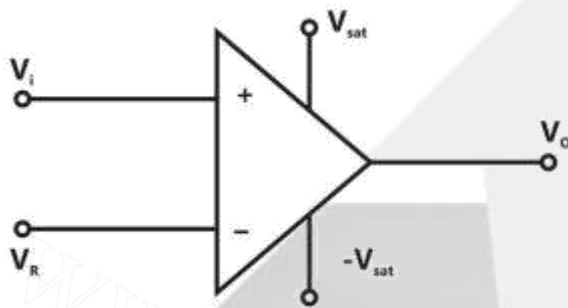
 16) Comparators




## 17) Schmitt Trigger

### Inverting Schmitt Trigger

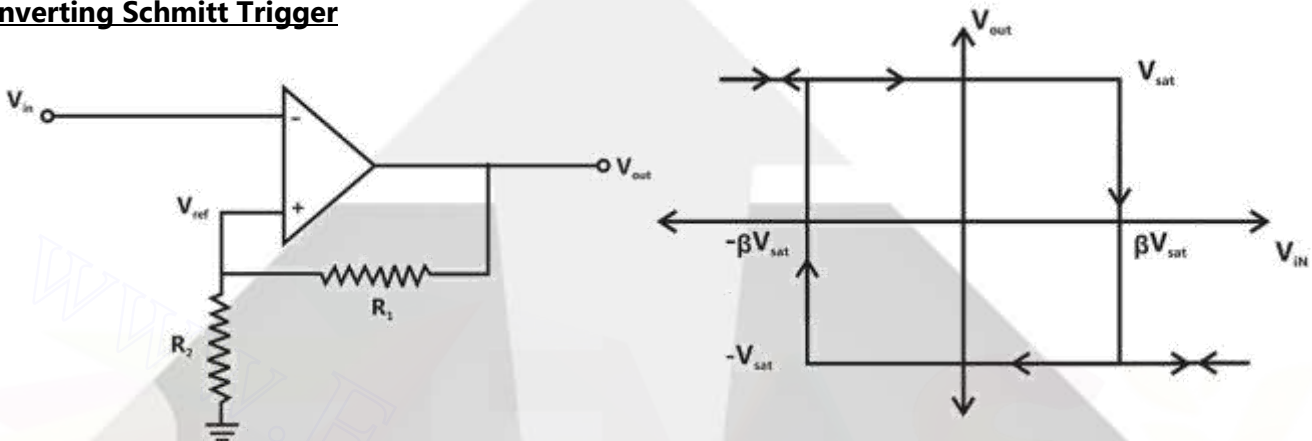


- When output is  $+V_{sat}$ , then  $V_{ref} = \beta V_{sat}$
- When output is  $-V_{sat}$ , then  $V_{ref} = -\beta V_{sat}$

$$\text{When } \beta = \frac{R_2}{R_1 + R_2}$$

- Upper triggering point (utp) =  $\beta V_{sat}$   
Lower triggering point (Ltp) =  $-\beta V_{sat}$
- Hysteresis voltage =  $UTP - LTP = 2\beta V_{sat}$

$$UTP = \beta V_{sat} + \frac{R_1}{R_1 + R_2} V_R$$

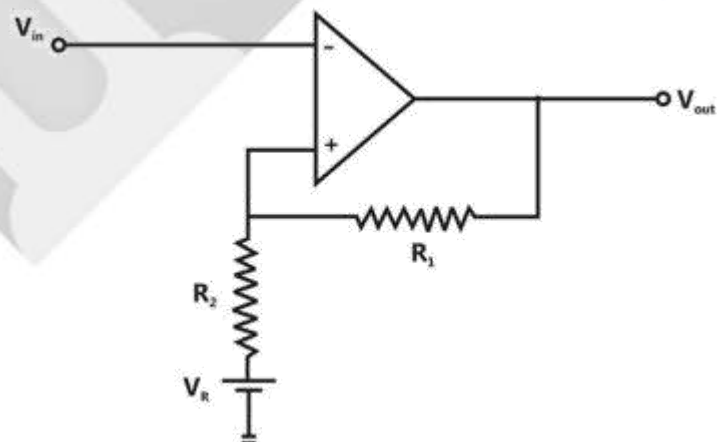
$$LTP = -\beta V_{sat} + \frac{R_1}{R_1 + R_2} V_R$$









### Non – Inverting Schmitt Trigger

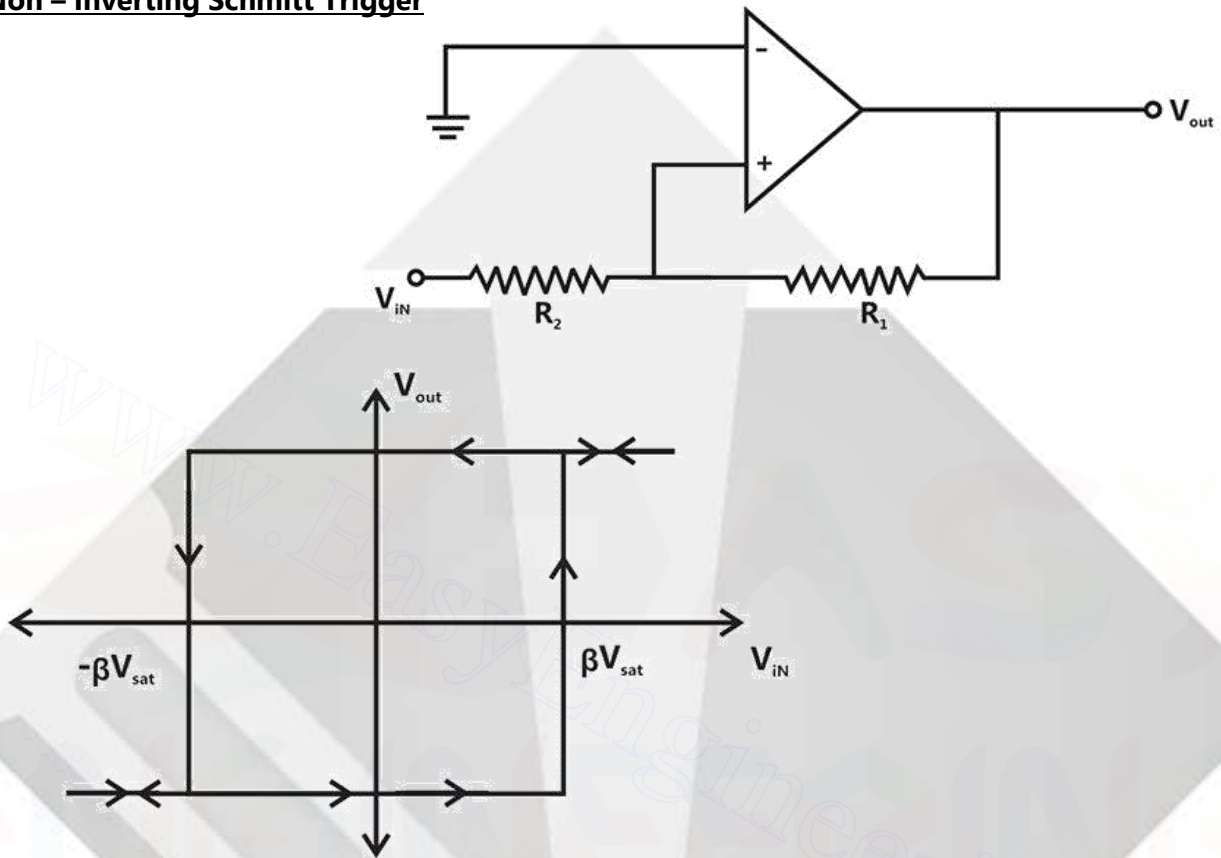

- Upper trigger Point (UTP) =  $\frac{R_2}{R_1} V_{sat}$ , Lower triggering point (LTP) =  $-\frac{R_2}{R_1} V_{sat}$ ,  $\beta = \frac{R_2}{R_1}$
- Hysteric voltage =  $UTP - LTP = 2\beta V_{sat}$

### 18) Relaxation Oscillator

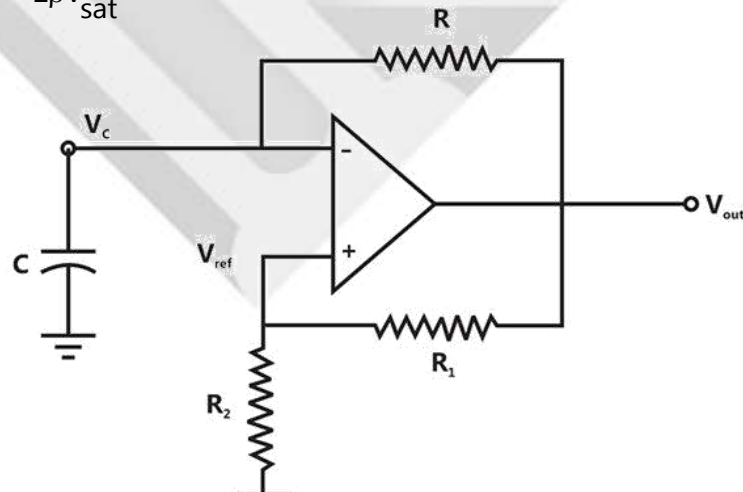

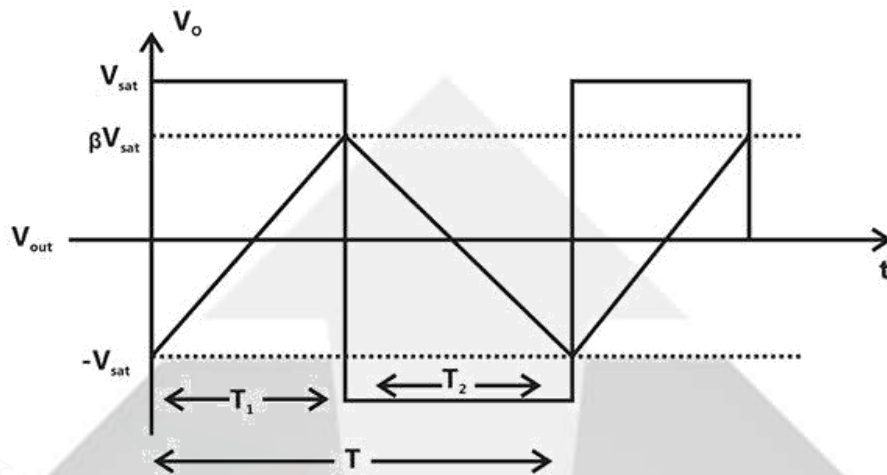


$$\beta = \left( \frac{R_2}{R_1 + R_2} \right)$$

$$T = 2RC \ln \left( \frac{1 + \beta}{1 - \beta} \right)$$

$$f = \frac{1}{T} = \frac{1}{2RC \ln \left( \frac{1 + \beta}{1 - \beta} \right)}$$

### 555 Timer


#### Pin Diagram

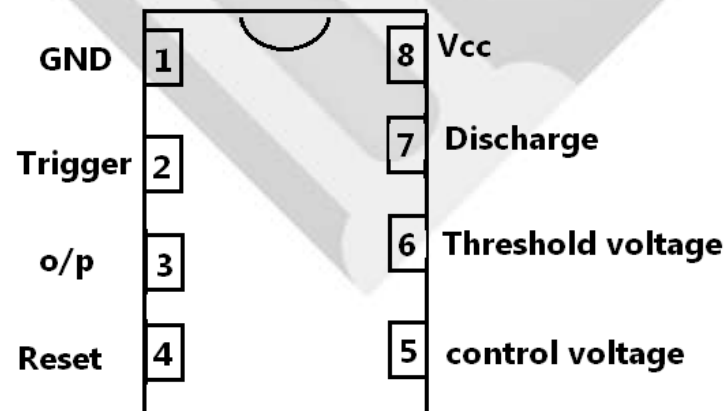



- Bistable multi vibrator acts as a FF.
- Monostable Multi vibrator produces pulse output.
- Bistable Multi vibrator acts as free running oscillator.

### A stable Multi vibrator

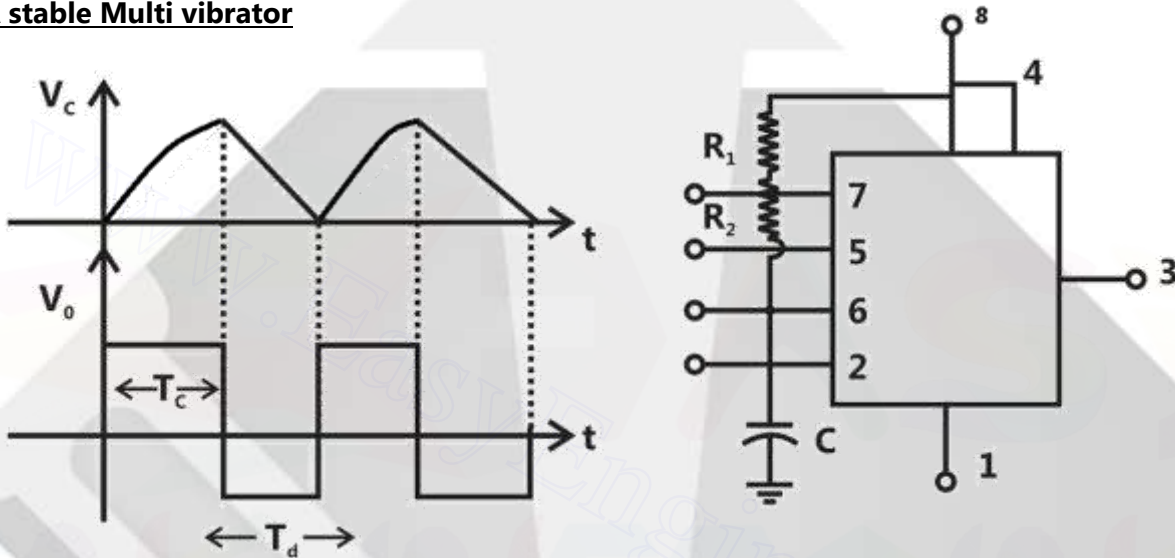

$$T_c = 0.69(R_1 + R_2)C$$

$$T_d = 0.69R_2C$$

$$T = T_c + T_d = 0.69(R_1 + 2R_2)C$$

$$f = \frac{1}{T} = \frac{1}{0.69(R_1 + 2R_2)C}$$

## connect with us



[facebook.com/kreatryx](https://facebook.com/kreatryx)



[twitter.com/kreatryx](https://twitter.com/kreatryx)



[plus.google.com/kreatryx](https://plus.google.com/kreatryx)



[youtube.com/kreatryx](https://youtube.com/kreatryx)



[linkedin.com/kreatryx](https://linkedin.com/kreatryx)

---

**info@kreatryx.com**

**kreatryx.thegateguru@gmail.com**

**+91 7406144144**

**+91 9819373645**

**0120-4326333**

**Address - SE 617, Shastri Nagar, Ghaziabad, U.P (201002)**

**www.kreatryx.com**