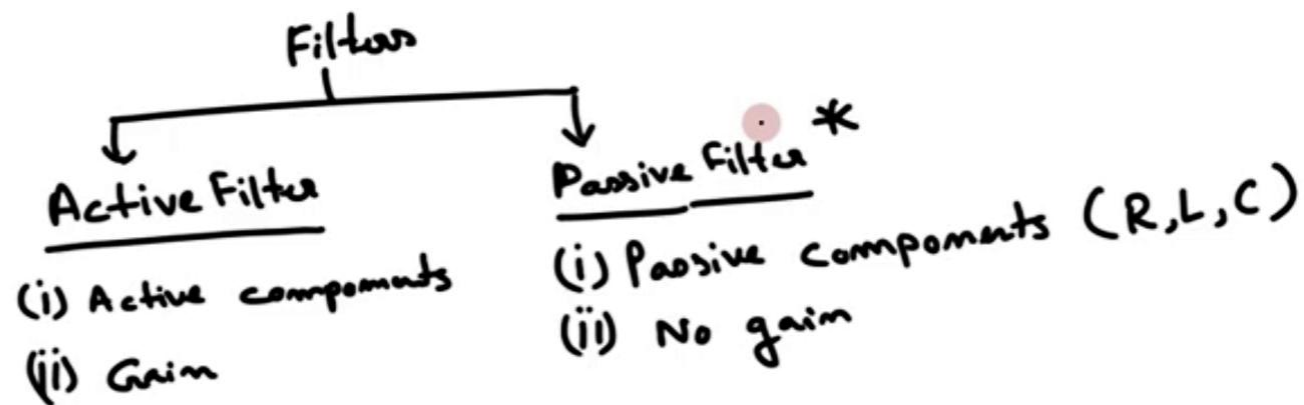



# Passive Filters



# Passive Filters

## Passive Filter


(i) Low pass filter (LPF)

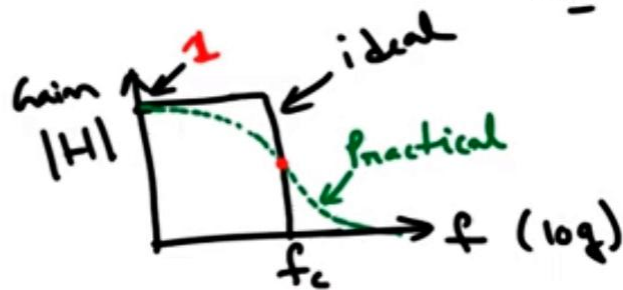


$$\text{Gain} = \frac{v_{out}}{v_{in}}$$

$$H = \frac{v_{out}}{v_{in}}$$

(ii) High Pass filter (HPF)

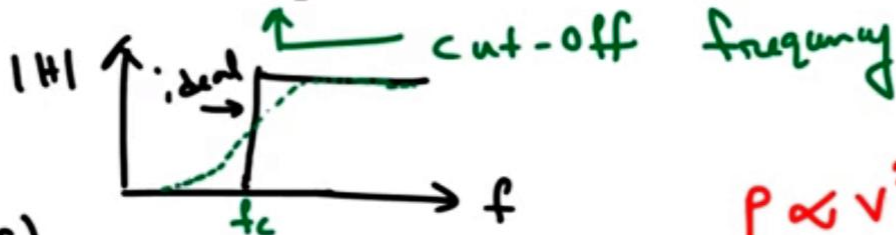

(iii) Band pass filter (BPF)

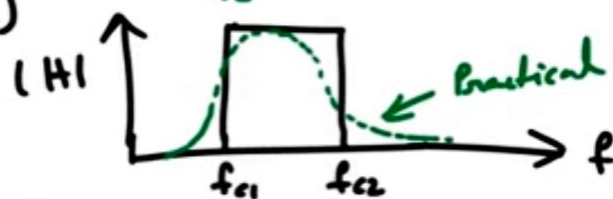

(iv) Band-Stop Filter (BSF)  
Band-Reject ~



$$P \propto V^2$$


$$V_{out} = \frac{1}{\sqrt{2}} V_{in}$$

$$|H| = \frac{1}{\sqrt{2}}$$

' $f_c$ '

# Passive Filters

## Low Pass Filter (LPF)

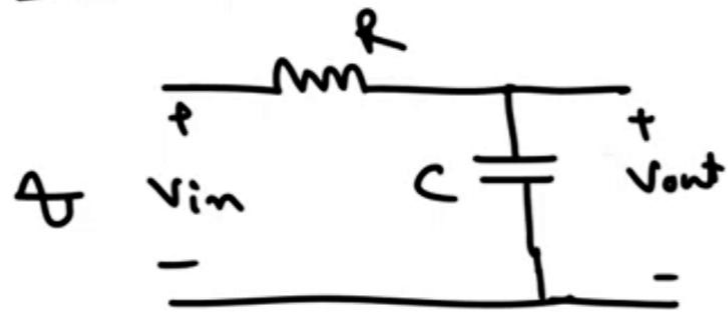

$$\omega_c = \frac{1}{RC} \quad \checkmark$$
$$|H(\omega)| = \frac{1}{\sqrt{2}} \rightarrow \text{Cut-off}$$
$$\omega_c = \text{cut-off freq.} = \frac{1}{RC}$$


$$V_{out} = \frac{Z_C}{R + Z_C} V_{in} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} V_{in}$$

$$= \frac{1}{1 + j\omega RC} V_{in}$$

$$H = \frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega RC}$$

$$|H| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} \quad \checkmark$$

$$\omega = 2\pi f$$

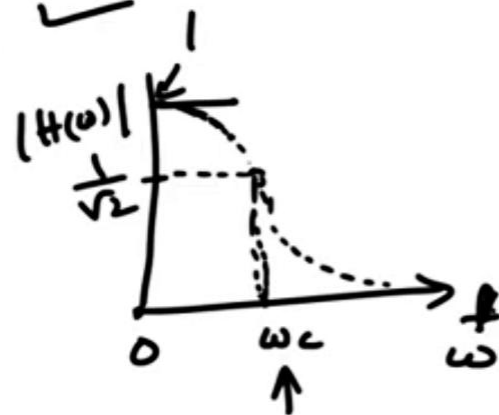

# Passive Filters

$$\uparrow \left| \frac{V_{out}}{V_{in}} \right|$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$$10 \log \left( \frac{P_{out}}{P_{in}} \right) = 10 \log \left( \frac{V_{out}^2}{V_{in}^2} \right)$$

$$= 20 \log \left( \frac{V_{out}}{V_{in}} \right)$$

(dB)  $\rightarrow$   $20 \log \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$

$\downarrow$   
??

$$\omega = \omega_c = \frac{1}{RC}$$


$\uparrow$   
Cut-off  
Freq.

=

$$20 \log \frac{1}{\sqrt{1+1}}$$

$$\longleftrightarrow = \underline{\underline{-3 \text{ dB}} \text{ } \underline{\underline{freq.}}}$$

$H(\omega)$   
dB  $\uparrow$

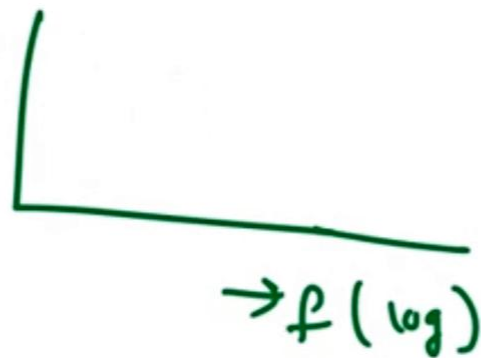

# Passive Filters


$V_o$  Phase??

$$|H(\omega)|_{dB} = 20 \log \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

at  $\omega=0$ ,  $|H(\omega)|_{dB} = 0$

$\omega_c = 1/RC$

$\omega = \omega_c$ ,  $|H(\omega)|_{dB} = -3 \text{ dB}$

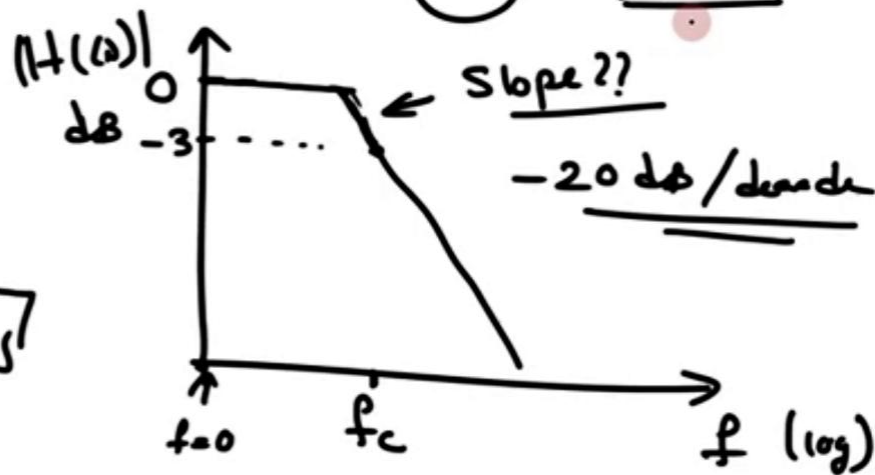

$|H(\omega)|_{dB} = 20 \log \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_c})^2}}$

Slope = -20 dB/decade

$\omega = 10\omega_c$   
decade

$$\begin{aligned} |H(\omega)|_{dB} &= 20 \log \frac{1}{\sqrt{1 + (\frac{10}{1})^2}} \\ &= 20 \log(\frac{1}{10}) = -20 \text{ dB} \end{aligned}$$

# Passive Filters

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

$$\Phi = -\tan^{-1}(\omega RC)$$




phase  
 $\Phi = -\tan^{-1}(\omega RC)$

$$\omega = 0, \Phi = 0$$


$$\omega = \omega_c = \frac{1}{RC}, \Phi = -\frac{\pi}{4}$$

$$\omega \rightarrow \infty, \Phi = -\frac{\pi}{2}$$



( $\Phi$ )

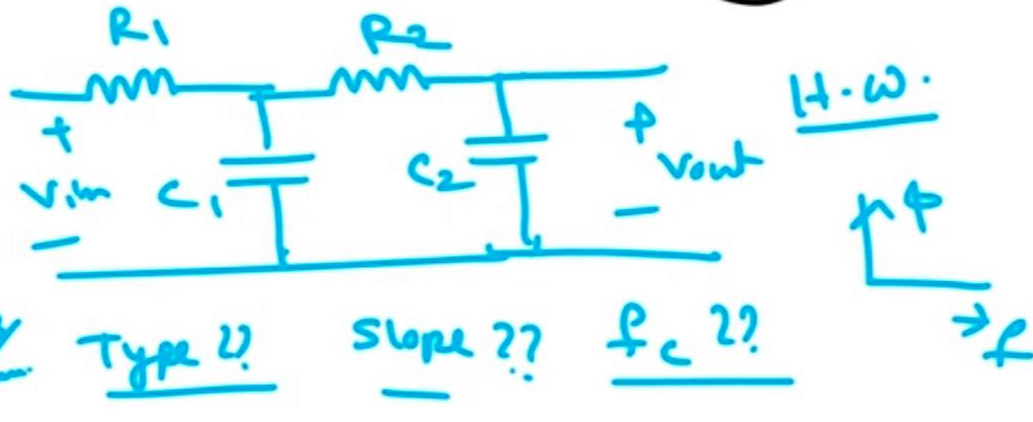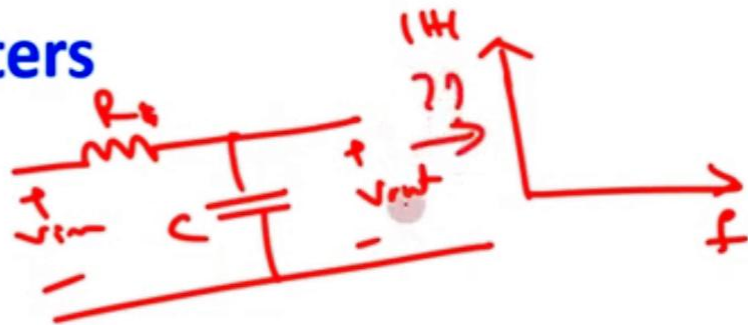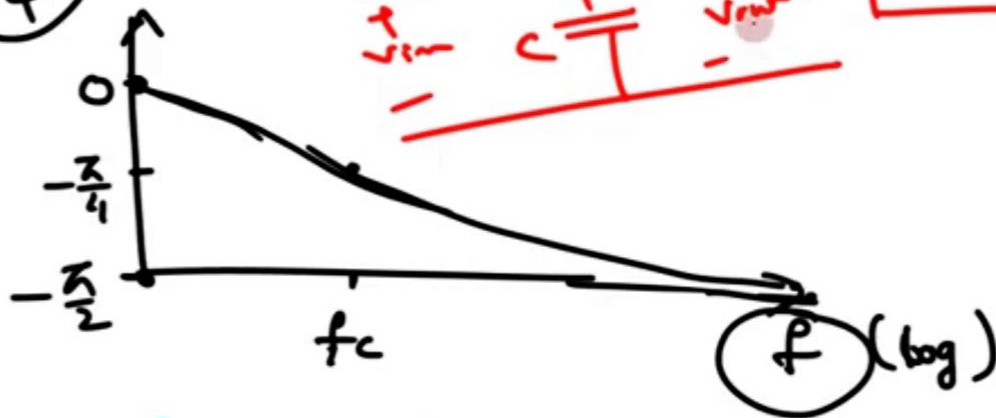


# Passive Filters

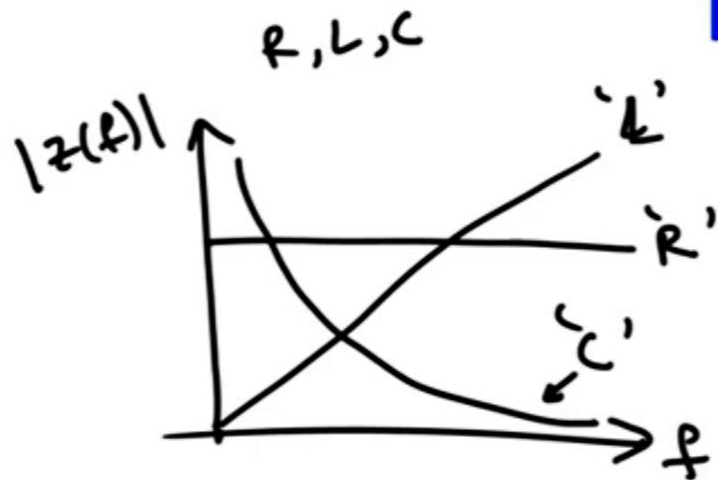
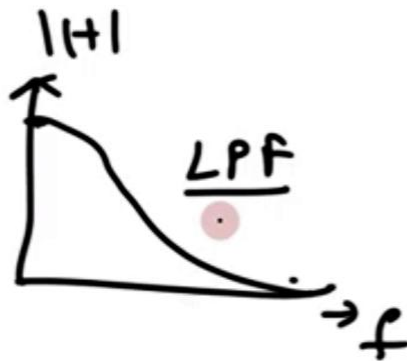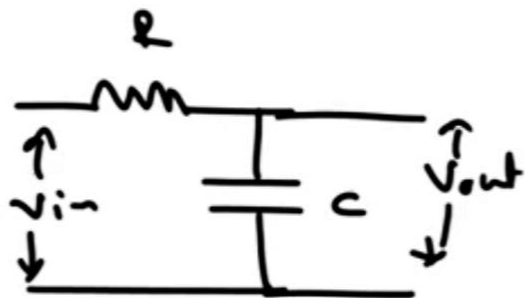
$$X_L = j\omega L$$
$$X_C = \frac{1}{j\omega C}$$




## Passive Filters

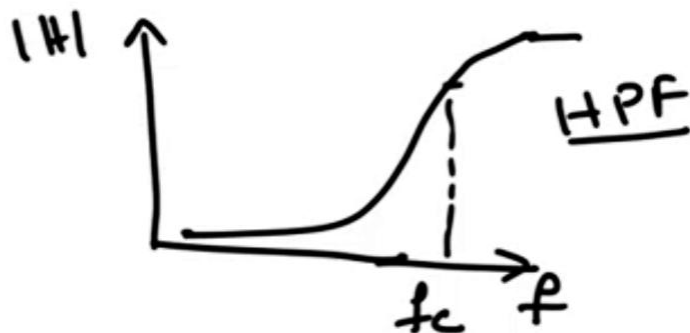

$$\frac{V_{out}}{V_{in}} = \frac{R}{R + \frac{1}{j\omega C}}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{Rj\omega C}{Rj\omega C + 1} = \frac{R\omega C}{\sqrt{1 + R^2\omega^2 C^2}}$$




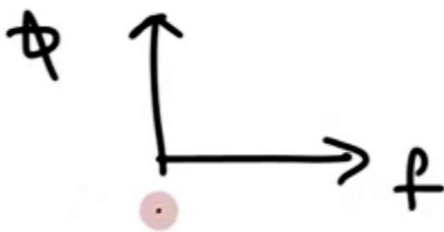


$$\omega = \frac{1}{RC}, \quad \left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{2}}$$

$\uparrow$   
 $\omega_c$




# Passive Filters

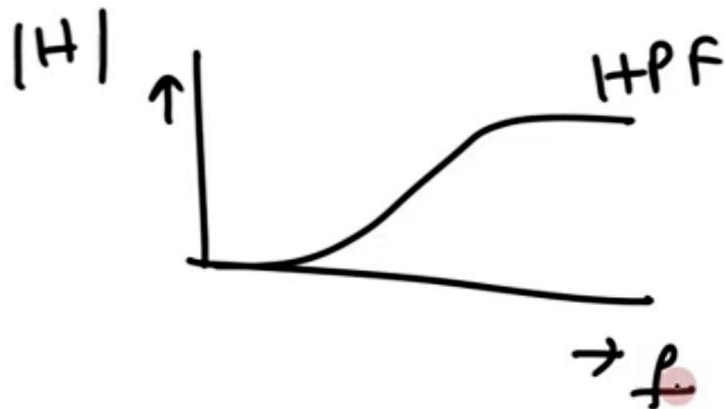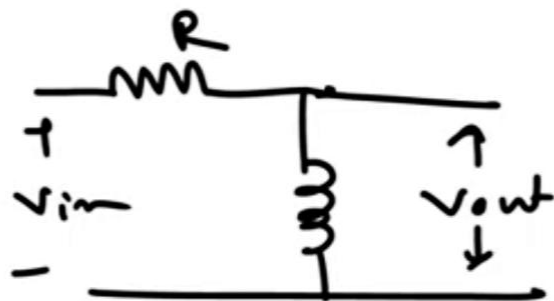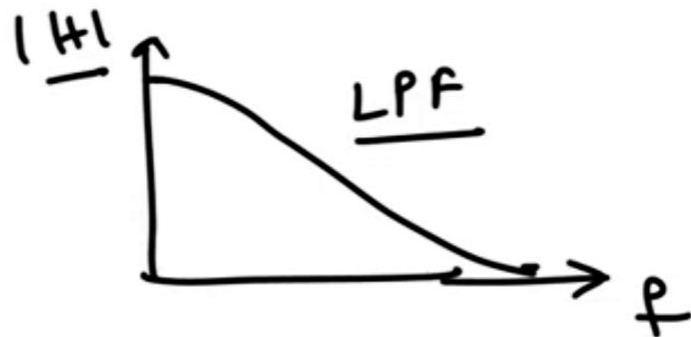
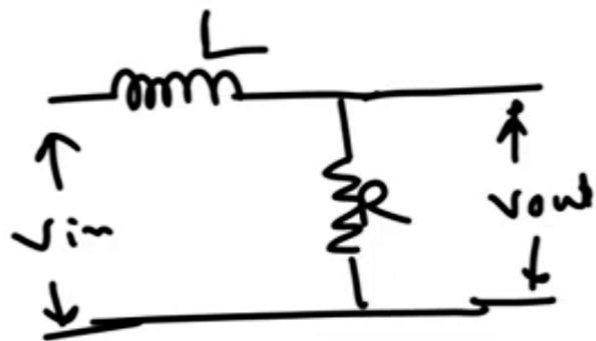


# Passive Filters

R-L-C

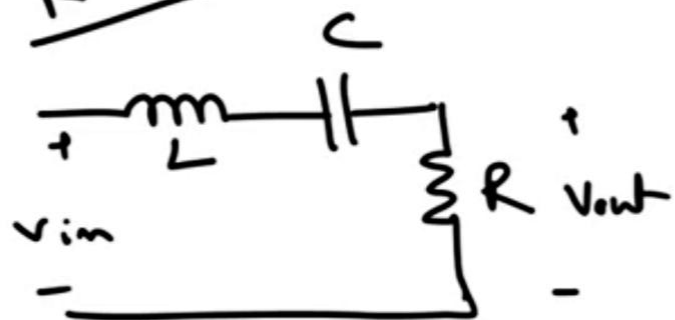


$|H(\omega)|$

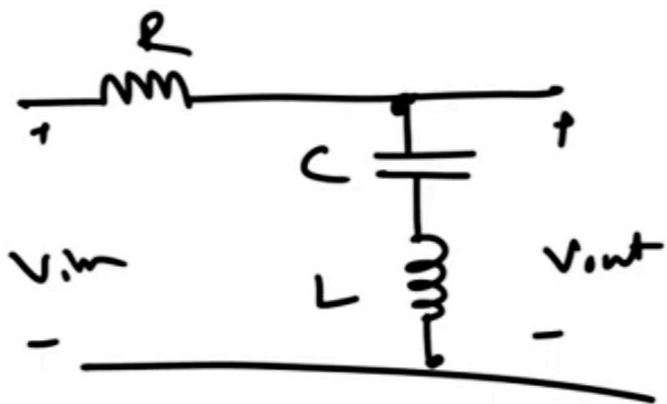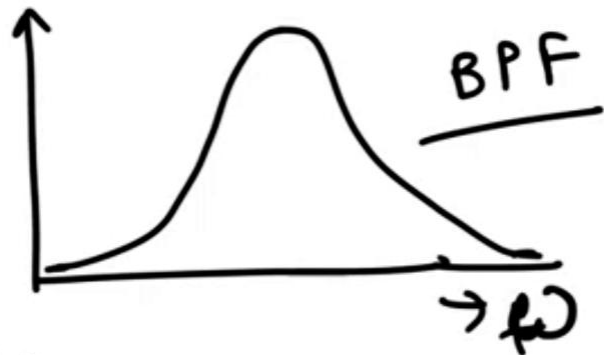

$|H(\omega)|$



## Passive Filters

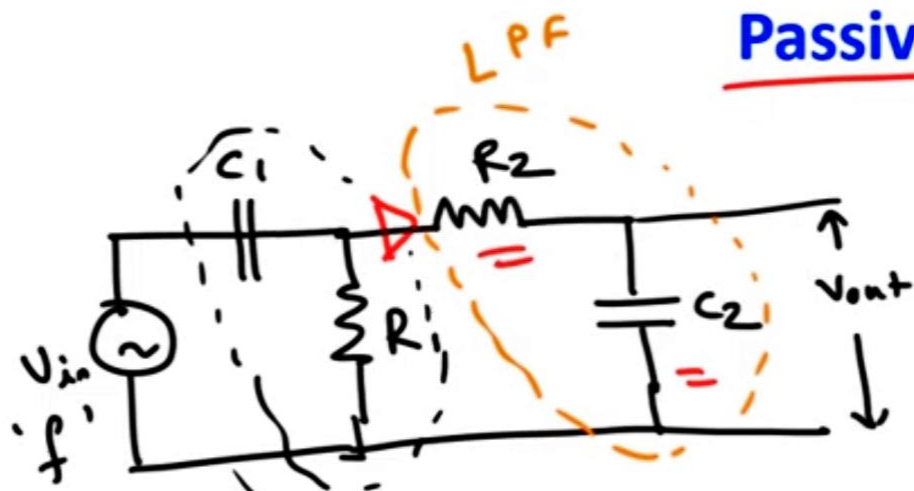

LPF  $\rightarrow f_{c2}$   
HPF  $\rightarrow f_{c1}$  }  $f_{c2} > f_{c1}$

