



Electromagnetic Engineering (EC21006)

Mid Semester Examination

Department of Electronics and Electrical Communication Engineering

Full Marks : 60

Time – 2 hrs

Answer all questions. The marks for the individual questions are indicated on the right.

1. The permittivity, permeability and conductivity of a medium are given by : $\epsilon = 1.2 \times 10^{-10} \text{ F/m}$, $\mu = 3 \times 10^{-5} \text{ H/m}$ and $\sigma = 0$ respectively. The medium is excited with a magnetic field $\vec{H} = 2 \cos(10^{10}t - \beta x) \hat{a}_z \text{ A/m}$. Obtain the field components \vec{B} , \vec{D} and \vec{E} and the value of β . (10)


2. The relative permittivity and conductivity of a medium are given by : $\epsilon_r = 1$ and $\sigma = 0$ respectively. If the magnetic field in the medium is $\vec{H} = 4 \sin(10^6t - 0.01z) \hat{a}_y \text{ A/m}$, determine the electric field and the relative permeability μ_r of the medium. (10)

3. A voltage source $v(t) = 10 \cos(\omega t)$ is connected across a parallel plate capacitor filled with polystyrene ($\epsilon = 2.56\epsilon_0$, $\sigma = 3.7 \times 10^{-4} \text{ S/m}$) between the plates. Assuming a plate separation of 2 cm with no field fringing, determine the maximum values of the conduction and displacement current densities within the polystyrene at the frequencies 1 MHz and 100 MHz. Comment on the results. (10)

4. The electric field \vec{E} in a nonmagnetic medium is given by $\vec{E} = 4 \sin(2\pi \times 10^7t - 0.866y - 0.5z) \hat{a}_x \text{ V/m}$. Compute the following :
 (a) The relative permittivity ϵ_r and the intrinsic impedance η of the medium. (b) The time average power flow. (c) The total power crossing 100 cm^2 of the plane $2x + y = 5$. (15)

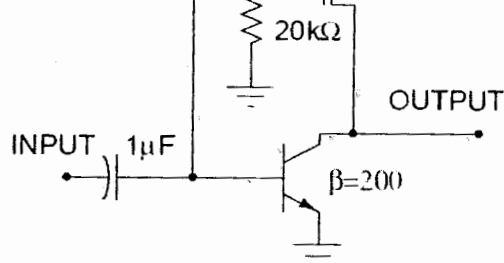5. Derive and explain the power conservation theorem for instantaneous electromagnetic fields. (15)


factor, $\lambda = (1/70) \text{ V}^{-1}$. Values of the remaining parameters can be taken as that of ideal one. Similarly, for the n-p-n transistor, the Early voltage, $V_A = 50\text{V}$ and values of the remaining parameters can be taken as that of ideal one.



- Find the value of the resistor R so that $I_{CQ} = 2.02 \text{ mA}$ and $V_{CEQ} = 5\text{V}$. Use this value of R for the subsequent parts of this question.
- Draw small signal equivalent circuit of the amplifier.
- Find the small signal gain of the amplifier.
- If you cascade two identical such amplifiers what will be the overall voltage gain

[3 + 3 + 3 + 6 = 15]

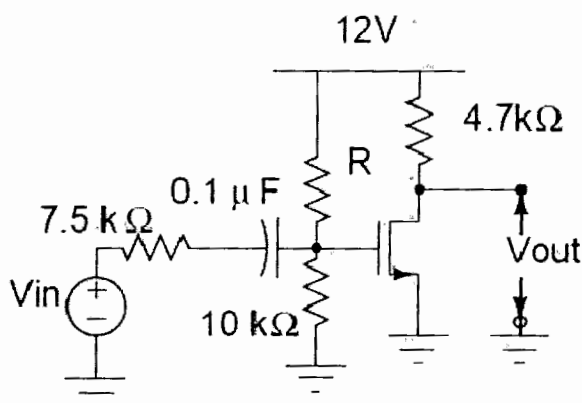Q. 3. A common source amplifier circuit is shown in the adjacent figure. Values of some parameters of the transistor are the following: Transconductance factor, $K = 1\text{mA/V}^2$; Threshold voltage, $V_{Th} = 2 \text{ V}$; Channel length modulation factor, $\lambda = 0.01 \text{ V}^{-1}$. Values of the remaining parameters can be taken as that of ideal one.



- Find the value of the resistor R such that $I_{DSQ} = 1\text{mA}$.
- With the value of R that is obtained in the part (a) of this question, find the small signal voltage gain of the amplifier in mid-frequency range.
- With the value of R that is obtained in the part (a) of this question, find the maximum output signal swing without having "significant distortion".
- With the value of R that is obtained in the part (a) of this question, find the lower cutoff frequency of the amplifier.
- With the value of R that is obtained in the part (a) of this question, for $V_{in} = 500 \sin((2000/3)t) \text{ mV}$, neatly sketch the output voltage V_{out} .

[3 + 3 + 3 + 3 + 3 = 15]