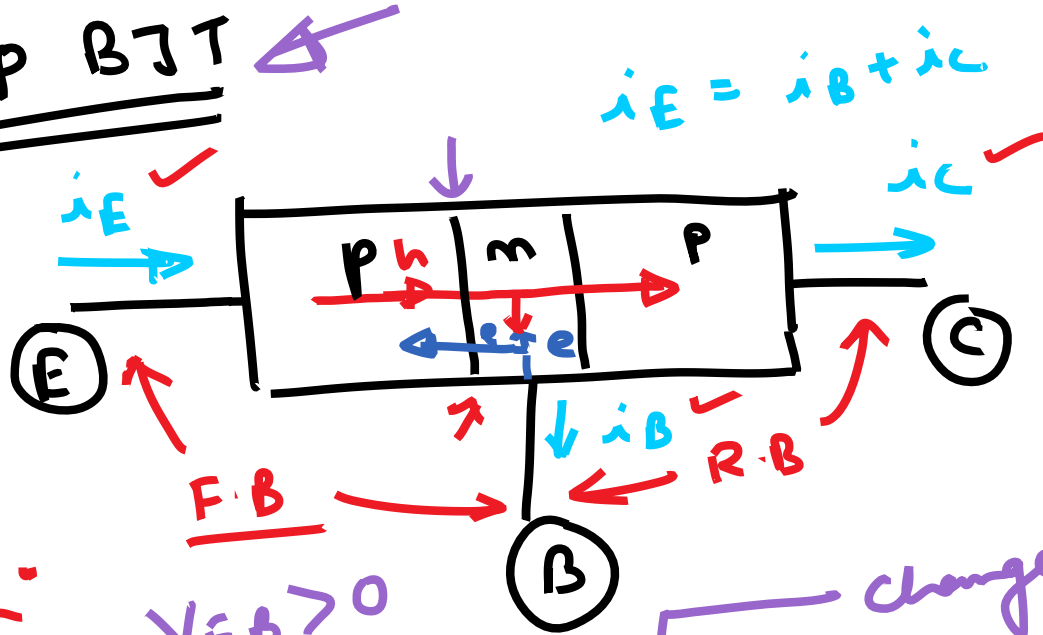



Bipolar Junction Transistor (BJT)

Last class
n-p-n BJT

p-n-p BJT


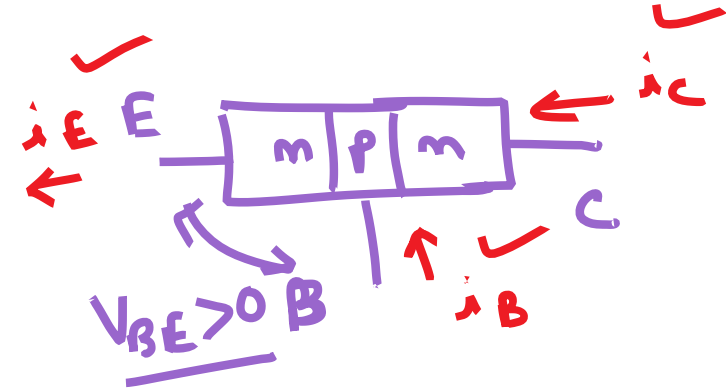
$$i_E = I_{E0} \exp\left(\frac{V_{EB}}{V_T}\right)$$



change in con. of BJT

$$i_C \propto \exp\left(\frac{V_{EB}}{V_T}\right)$$

$$i_C = I_S \exp\left(\frac{V_{EB}}{V_T}\right)$$

Bipolar Junction Transistor (BJT)

* Important Relations: (npn & pnp)

$$\checkmark i_E = i_C + i_B \rightarrow i_E = (1 + \beta) i_B$$

$$\checkmark i_C = \beta i_B \rightarrow \text{Active region}$$

$$\checkmark i_C = \alpha i_E \rightarrow i_C = \frac{\beta}{1 + \beta} i_E$$


$$\checkmark \beta = \frac{\alpha}{1 - \alpha}$$

$$\checkmark \alpha = \frac{\beta}{1 + \beta}$$

Bipolar Junction Transistor (BJT)


Configurations

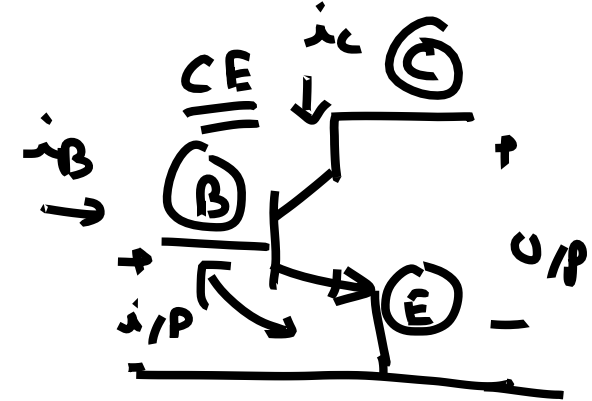- (i) Common Emitter (CE) ✓
- (ii) Common Base (CB) ✓
- (iii) Common Collector (CC) ✓




Characteristics:

(i) input characteristics

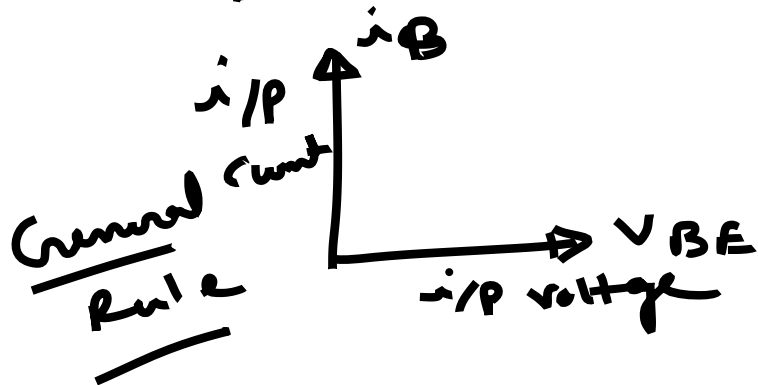


(ii) o/p characteristics

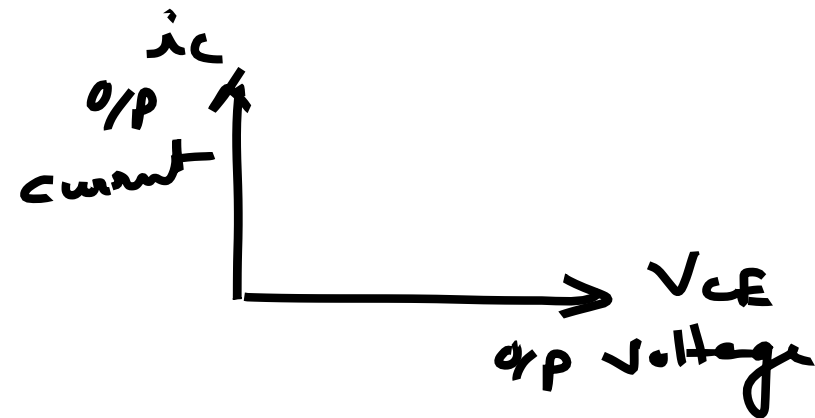



Bipolar Junction Transistor (BJT)

Common Emitter Configuration (CE)

Input characteristics

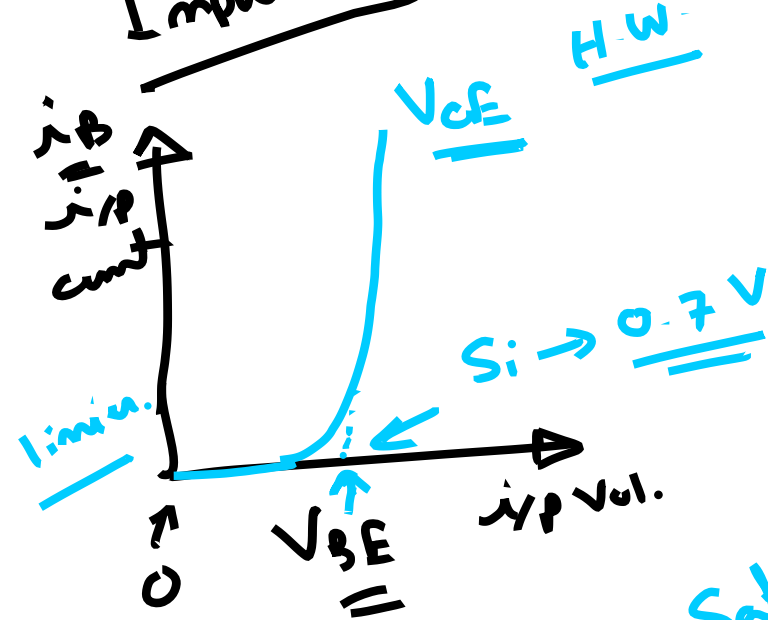


Output characteristics

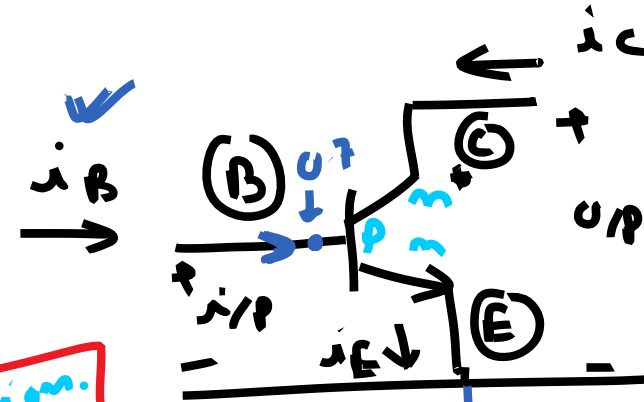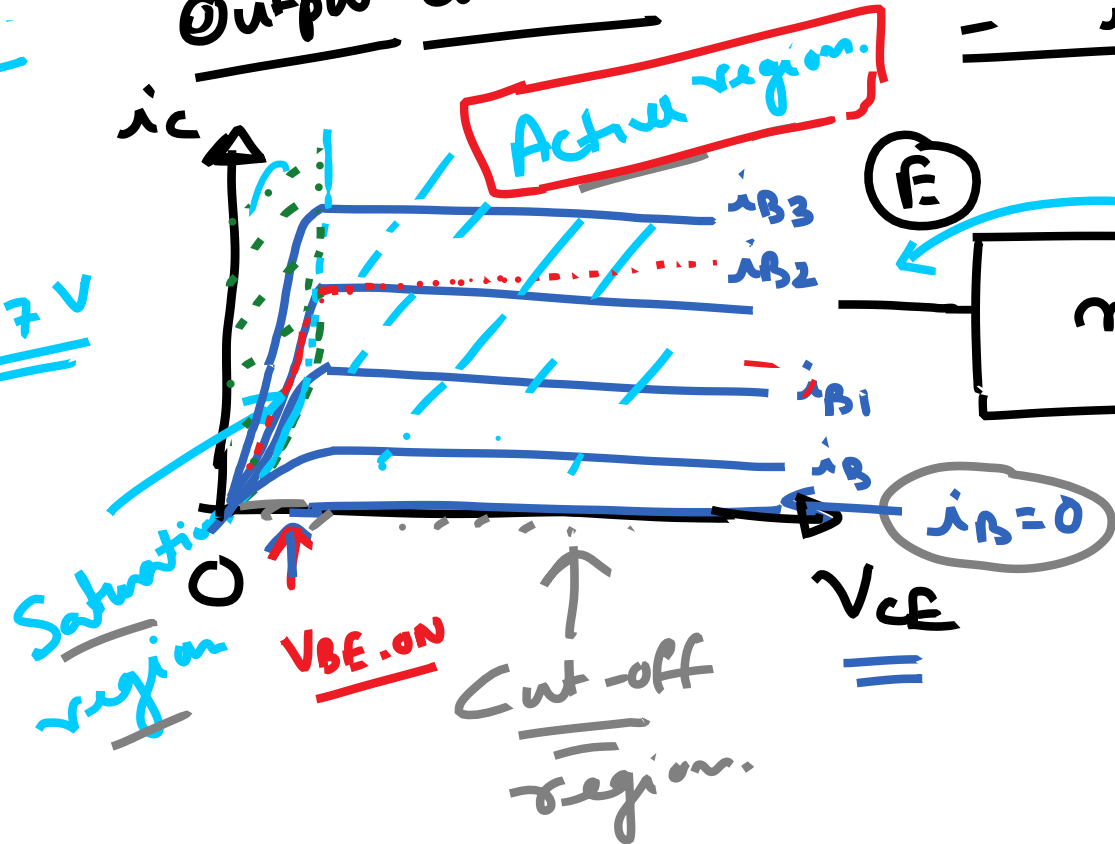

$$I_C = \beta I_B$$

Active region

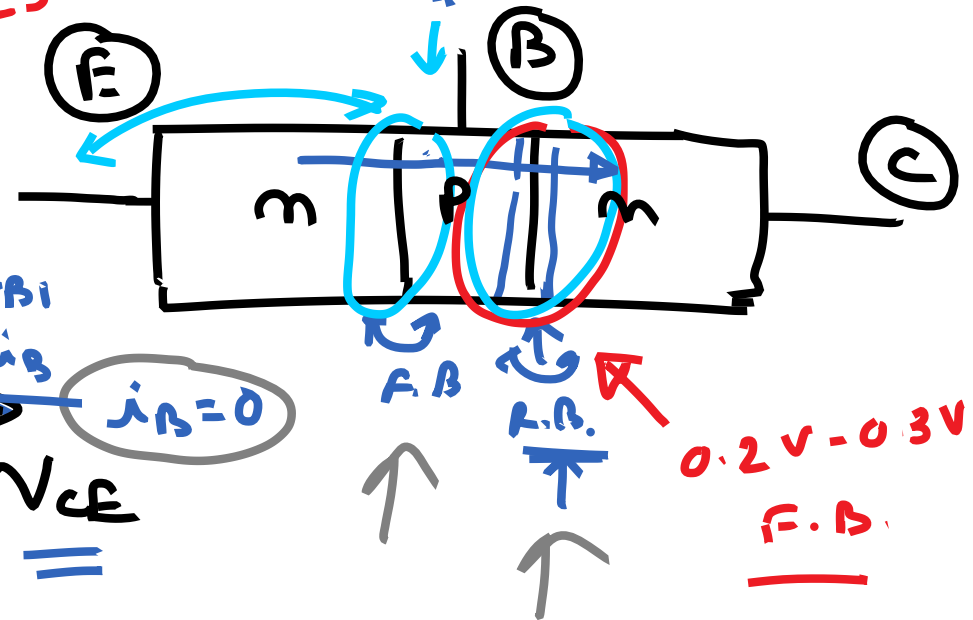

$$0.2V - 0.3V$$

F.B.


Bipolar Junction Transistor (BJT)

$$i_c = I_s \exp\left(\frac{V_{BE}}{V_T}\right)$$


$$i_c = I_s \exp\left(\frac{V_{BE}}{V_T}\right) \left(1 + \frac{V_{CE}}{V_A}\right)$$

Early voltage

V_{CE} dP.
characteristic

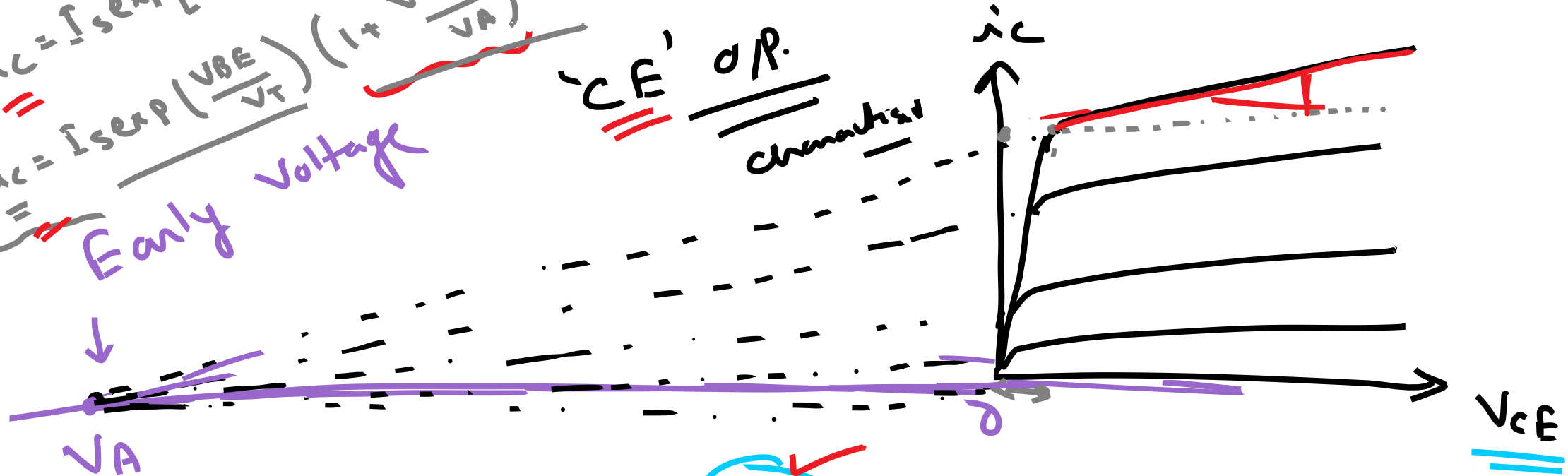

$\propto \frac{d n}{d n} \uparrow$

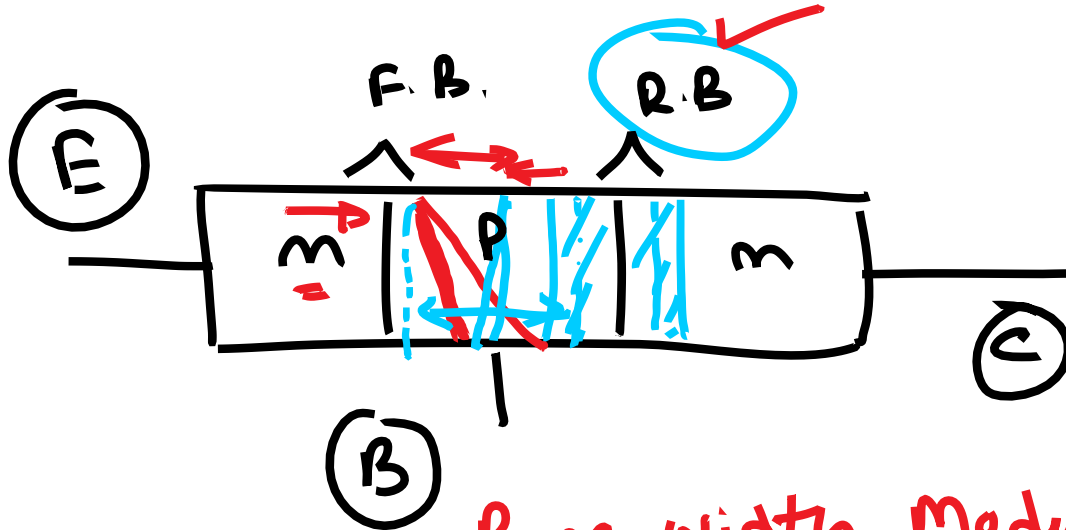

Base width modulation

Early Effect
"J.M. Early"


Bipolar Junction Transistor (BJT)

$$i_c = I_s \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A} \right]$$

Early voltage $r_o = \frac{\partial V_{CE}}{\partial i_c}$

magnitude

$$\left. \frac{\partial i_c}{\partial V_{CE}} \right|_{V_{BE} = \text{const.}} = \frac{1}{r_o} = I_s \exp\left(\frac{V_{BE}}{V_T}\right) \frac{1}{V_A} = \frac{I_c}{V_A}$$

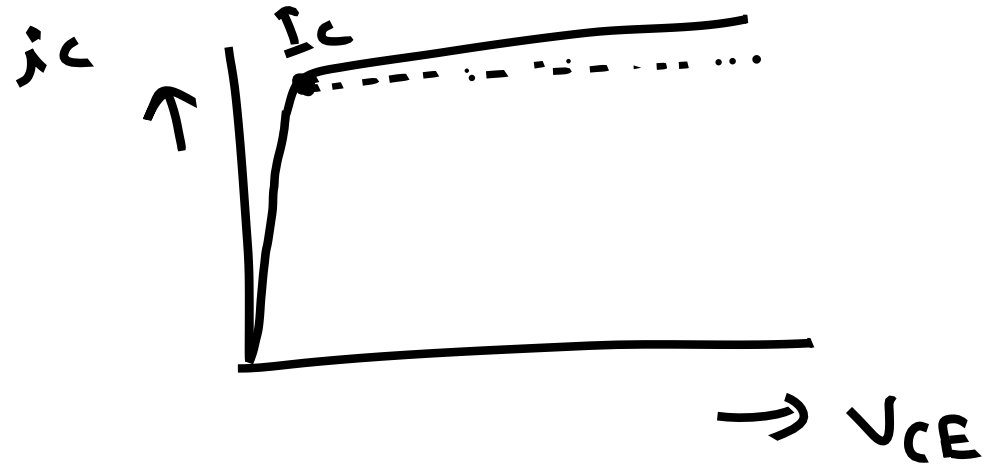


$r_o = \frac{V_A}{I_c}$

I_c is the DC current.

Bipolar Junction Transistor (BJT)

Common-Base (CB)



Input ch.

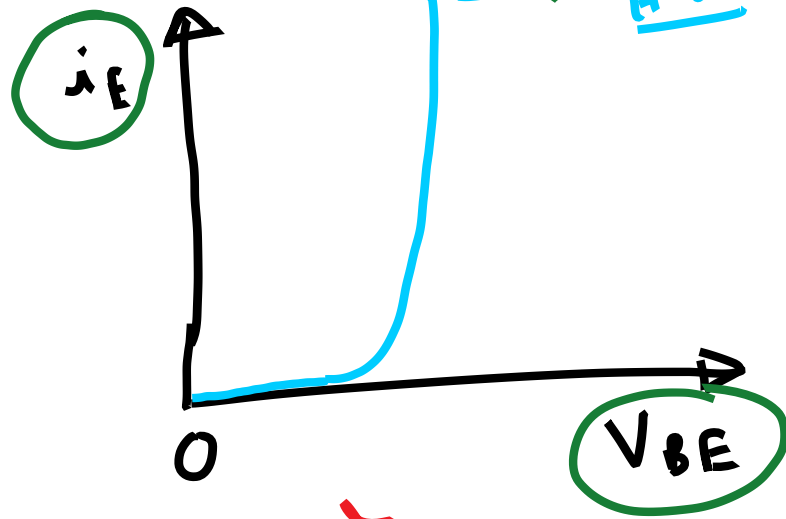

Non-ideal effect


$$i_C \approx \beta i_B$$

Output ch.

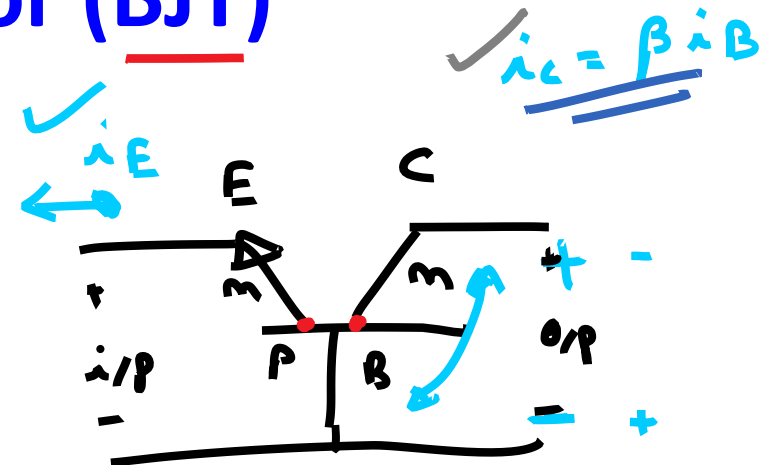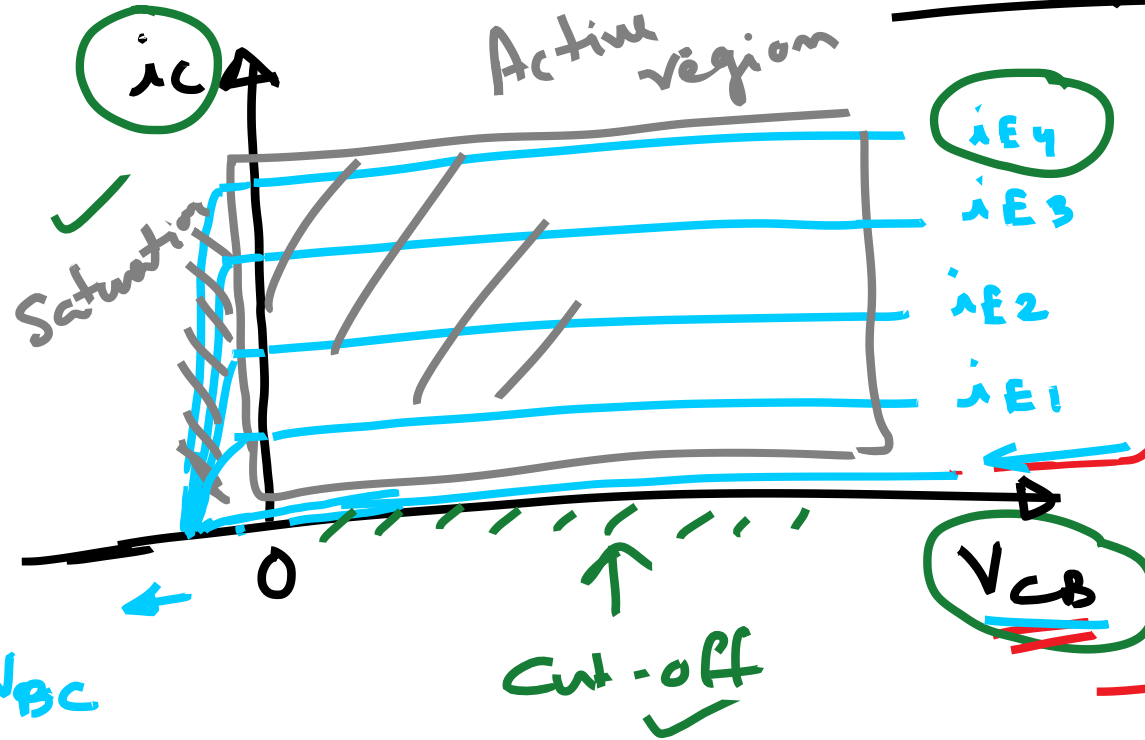

Breakdown voltage

Bipolar Junction Transistor (BJT)

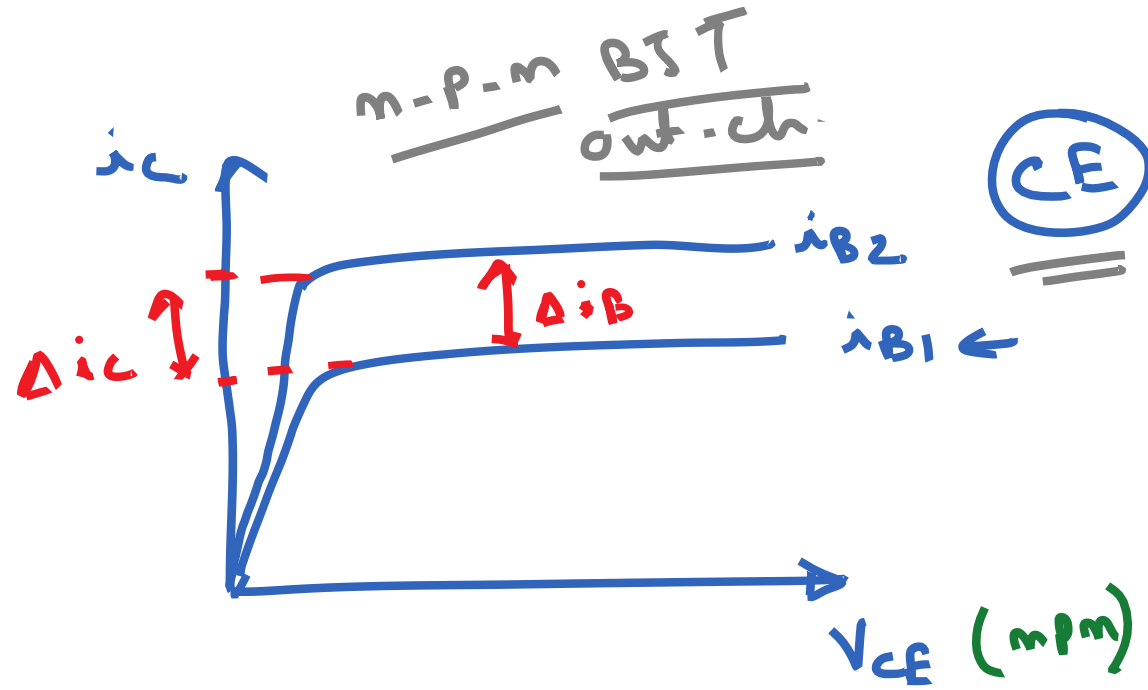

$$\beta_{ac} = \frac{\Delta i_c}{\Delta i_B}$$

$$\beta \approx \beta_{ac}$$

V_{EC} (pnp)

p-m-p BJT ??

'CB' - p-m-p BJT.

