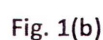
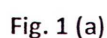


Subject name: **Analog Electronic Circuits**

For n-MOS and p-MOS enhancement transistors, the trans-conductance factor,  $K = 1\text{mA/V}^2$ ,  $|V_{th}| = 2\text{V}$ ,  $\lambda = 0.01\text{V}^{-1}$   
 $V_{dd} = 12\text{V}$ .

 $[6 + 2 + 2]$ 

OR

Referring to figure 1.b, assume bias currents in all stages to be 1mA.  $V_B$  is a DC bias voltage. For all MOSFETs,  $C_{gs} = 10\text{pF}$ ,  $C_{gd} = 2\text{pF}$ ,  $C_{db} = C_{sb} = 0$ .

- Identify the feedback topology and find the value of the feedback factor.
- Find the small signal loop gain ( $A\beta$ ).
- Find the two dominant poles in the circuit.
- Ignoring any other poles and zeros apart from those found in part (c), determine the phase margin. Justify any approximation taken.

[1+3+3+3]

Q.2. The transfer function of the differential amplifier in the circuit shown in Fig. 2.a is given by,

$$A(s) = \frac{A(0)}{\left(1 + \frac{s}{100}\right)}$$

Assume that the input resistance and the output resistance of the amplifier are respectively very high and very small.

(a) For the switch "SW" connected to the terminal "A",

- derive the expression of the transfer function of the complete system (i.e.,  $\frac{v_{out}}{v_s}$ ).

(ii) For  $R_1 = 1\text{k}\Omega$ ,  $R_2 = 10\text{k}\Omega$  and  $C_1 = C_2 = 100\text{nF}$ , neatly sketch the Bode' plots of the transfer function.

(b) For  $R_1 = 1\text{k}\Omega$  and  $R_2 = 10\text{k}\Omega$  and  $C_1 = C_2 = 100\text{nF}$ , what should be the value of low frequency gain of the differential amplifier (i.e.  $A(0)$ ) so that, by connecting the switch "SW" to the terminal "B" the circuit satisfy the Barkhausen criterion of oscillation?

(c) On satisfying the Barkhausen criterion of oscillation as stated in the part (b) of this question, calculate the frequency of oscillation.

[3+2+3+2]

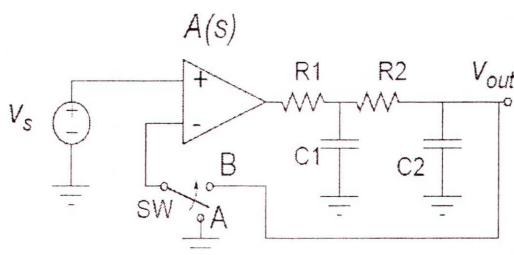


Fig. 2(a)

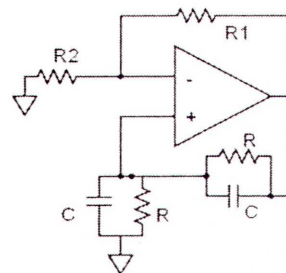


Fig. 2(b)

OR

Referring to figure.2b,

- Find the expression for loop gain for the oscillator circuit given in fig. 2b.
- Find the minimum required value of  $R_1/R_2$  for sustained oscillations and the frequency of oscillation.

- (c) Show that the loop transfer function for the given oscillator circuit has a band-pass response. Find the approximate expression for higher and lower 3dB cutoff frequency of the loop transfer-function.

[4+2+4]

Q. 3 Referring to figure 3(a), Given:  $V_{DD} = 12V$ ,  $I_{BIAS} = 1mA$ ,  $R = 5 \text{ Meg}\Omega$ ,  $C1 = 100 \text{ pF}$ ,  $C2 = 100 \text{ nF}$ .

- (a) Find the range of the input d.c. voltage,  $V_{IN\_DC}$  over which all the transistors remain in saturation region of operation. For the subsequent parts of this question, use the mid-value of its range.
- (b) Assuming the value of capacitor  $C3$  is "very high", find the values of low frequency gain and two poles of the transfer function (from " $V_{in}$ " to output signal across the capacitor  $C2$ ) of the amplifier.
- (c) For  $C3 = 20 \mu F$ , find the modified transfer function of the amplifier.
- (d) Find the value of maximum signal swing at the output node (i.e. voltage across  $C2$ ).

[2+5+2+1]

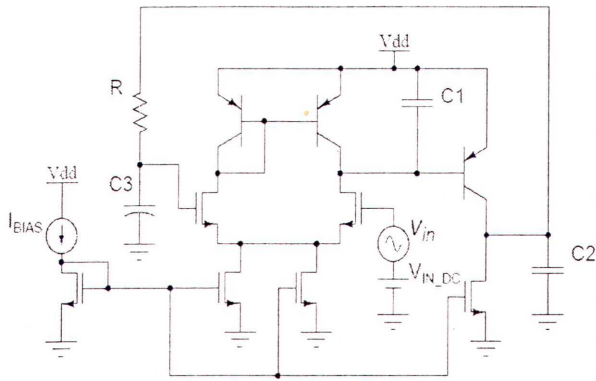


Fig 3 (a)

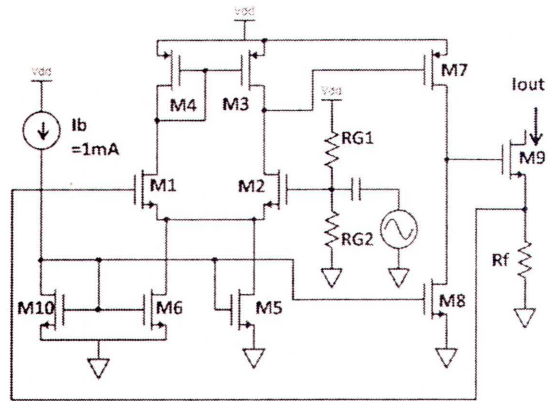


Fig. 3(b)

OR

Referring to Fig 3(b), assume  $R_B$  and  $C_c$  to be large;

- (a) For  $RG1 = RG2 = 100k\Omega$ , and  $R_f = 5k\Omega$ , find the DC voltage at the gate of  $M9$ .
- (b) Find the DC voltage at the gate of  $M7$  for the given bias condition.
- (c) Find the maximum symmetric swing available at the output for the condition in part (a).
- (d) Find the loop gain.

[2.5x4]

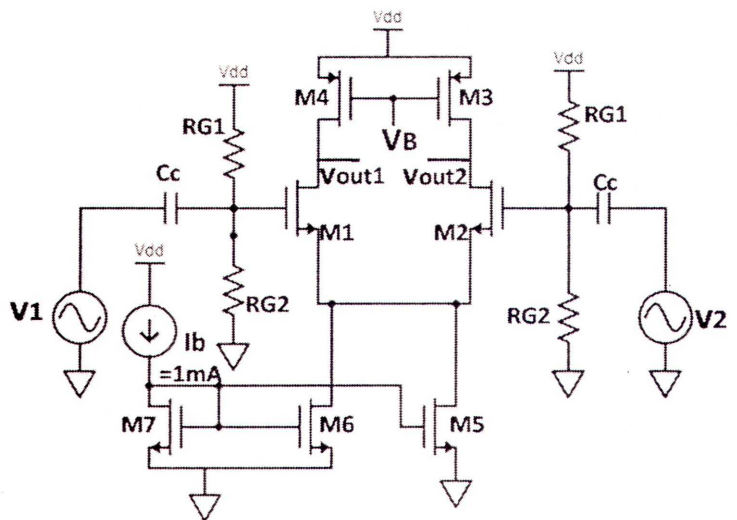


Fig. 4

Q.4 Referring to figure 4:

- (a) Assuming all transistors in saturation and ignoring channel length modulation, find the value of DC voltage  $V_B$ , for the given bias condition. Use this value of  $V_B$  in subsequent parts of this question.
- (b) For  $RG1/RG2 = 5/7$ , find the maximum symmetric swing at the output.
- (c) Find the small signal differential and common-mode gain and hence their ratio (called CMRR).
- (d) For  $V_1 = 90 \times 10^{-3} \sin(\omega t)$  and  $V_2 = 105 \times 10^{-3} \sin(\omega t)$  find the expressions for  $V_{out1}$  and  $V_{out2}$ .

[2.5 x 4]

Q.5 In a negative feedback system, transfer function of the forward amplifier is,

$$A(s) = \frac{10000}{\left(1 + \frac{s}{10^4}\right) \left(1 + \frac{s}{\sqrt{3} \times 10^6}\right) \left(1 + \frac{s}{\sqrt{3} \times 10^8}\right)}$$

- (a) For a feedback factor of 0.1:
- neatly Sketch the **Bode' plots** of the loop gain (with clear indication of poles),
  - neatly Sketch the **Bode' plots** of the feedback system gain (with clear indication of poles),
  - find the value of **unity gain frequency** and calculate the **phase margin** of the feedback system,
  - find the value of **the frequency** at which total phase shift of the loop gain becomes  $0^\circ$  and calculate the **gain margin** of the feedback system.

- (b) For a feedback factor of  $\sqrt{3}/10$ , neatly draw the **Nyquist diagram** of the feedback system and comment about its stability

[5 x 2]

OR

For the circuit given in figure 5, M1, M2, M3 and M4 constitute a cascade amplifier. Assume,  $C_{gs} = 10\text{pF}$ ,  $C_{gd} = 2\text{pF}$ ,  $C_{sb} = C_{db} = 0$  for all transistors.

- Find the DC bias voltage at the gates of M3 and M2
- Using the result in (a), find the maximum allowed swing at the output node, and also the desired DC bias point for  $V_{out}$  that can achieve maximum symmetric swing.
- Find the small signal gain  $V_{out}/V_{in}$ .
- Find the high frequency poles at the output node and at the drain of M1.

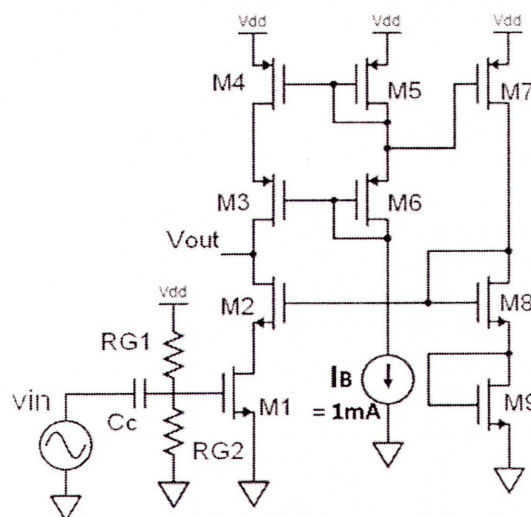


Fig. 5

[2 + 2 + 3 + 3]