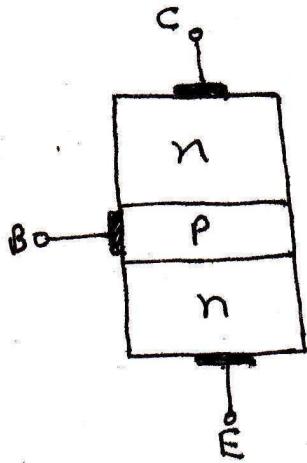



PHYSICS OF BIPOLAR TRANSISTORS

* A bipolar transistor consists of three doped regions forming a sandwich:-

- ① Emitter → emits charge carriers
- ② Base → controls the ~~near~~ number of charge carriers making the journey.
- ③ Collector → collects the charge carriers.




structure

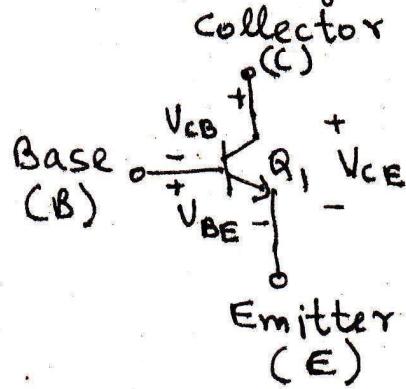

Symbol

- * Two pn-junctions
 - between base-emitter
 - between base-collector.
- * The device is not symmetric with respect to emitter and collector.
- * The dimensions and doping levels of emitter and collector are quite different.
- * EMITTER AND COLLECTOR CANNOT BE INTERCHANGED.
- * Proper operation of the device require that base be a thin region, e.g. about $100\text{ }\mu\text{m}$ in modern integrated circuits.

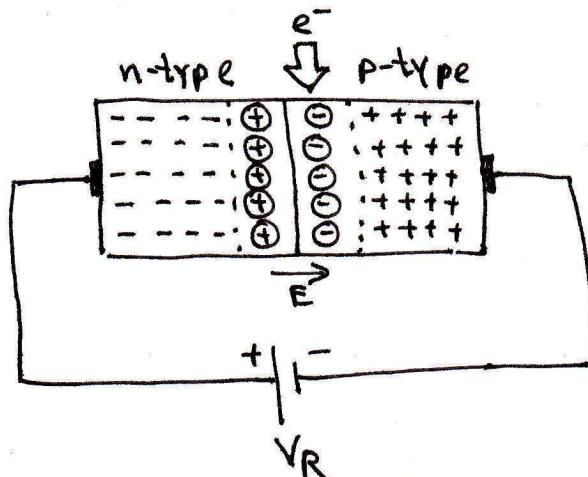Injection of electrons into depletion region:-




Lets inject an electron into the depletion region in a reverse biased pn-junction.


It serves as minority carrier in p-type and is rapidly swept away into n-side by the electric field.

- * Ability of the reverse-biased pn-junction to efficiently "collect" externally-injected electrons/holes proves essential to the operation of bipolar transistors.

OPERATION OF BIPOLAR TRANSISTOR IN ACTIVE MODE:-

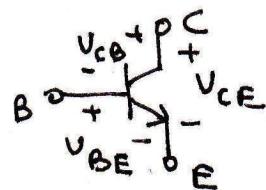- * In this mode the transistor acts a current source between collector and emitter.
- * The above current is controlled by the voltage between base and emitter.
- * For a bipolar transistor the terminal voltages V_{BE} , V_{BC} , and V_{CE} , which can assume positive and negative values, there are 2^3 possible cases.
- * One ~~out of~~ of these combinations is useful.



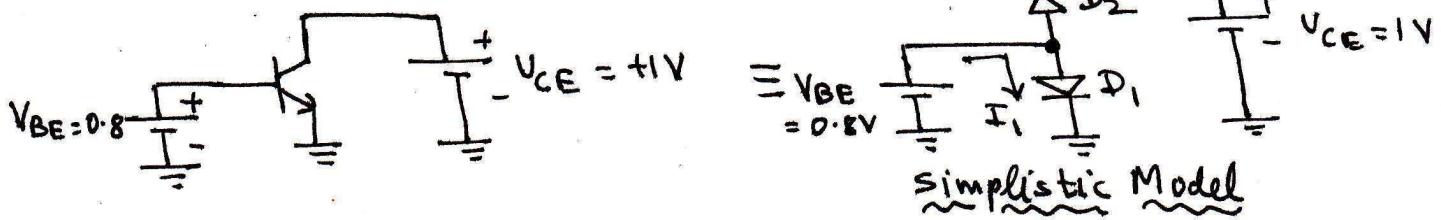



Circuit Condition :- $V_{BE} > 0$

$$V_{CE} > 0$$

$$\text{and } V_{BC} < 0$$

- * The simplistic model assumes that D_2 should not carry any current and hence there cannot be any voltage to current conversion.


MOTION OF CARRIERS IN SLOW MOTION :-

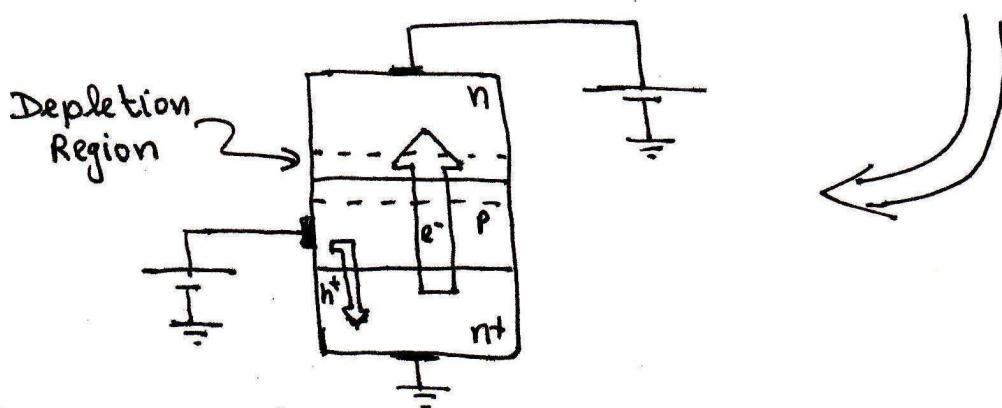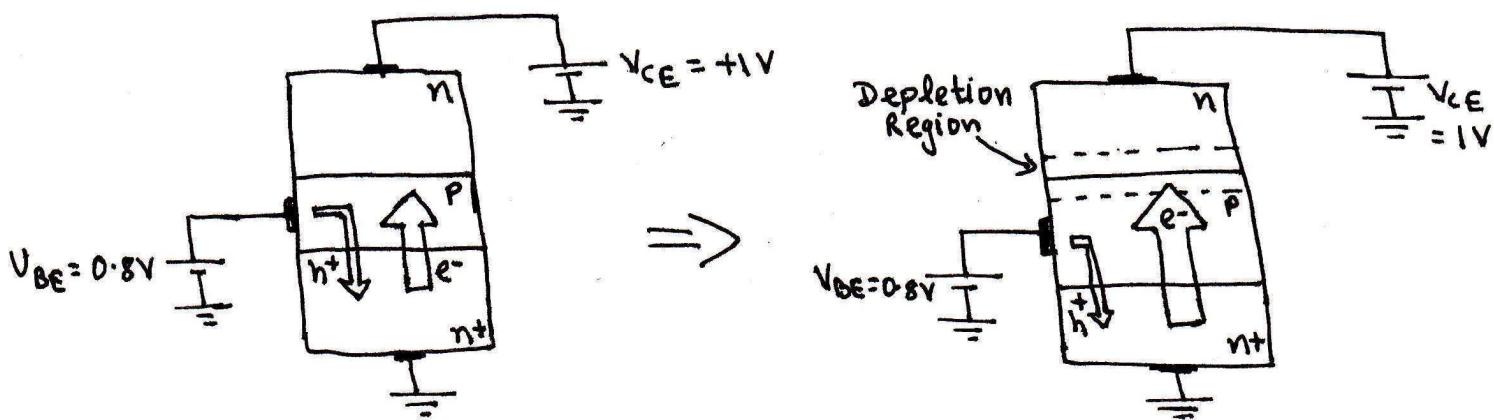


* Emitter is heavily doped.

* Base is thin.

Illustration of Current flow:-

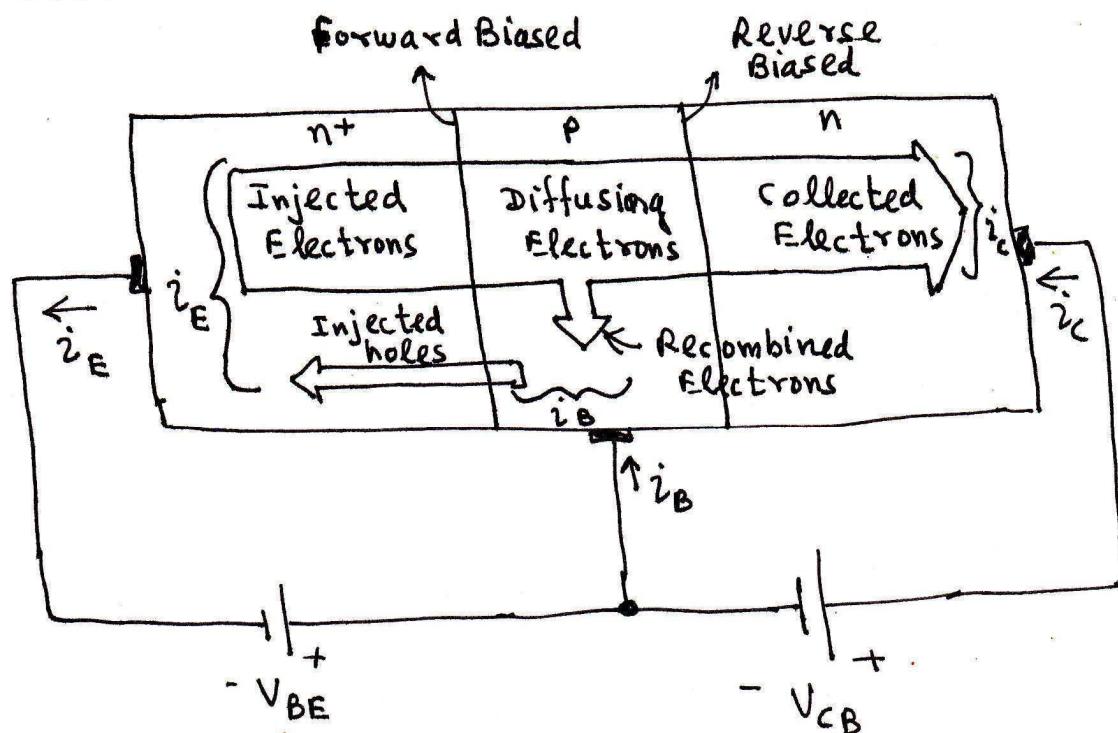

Minority Carrier Concentration Profile:-

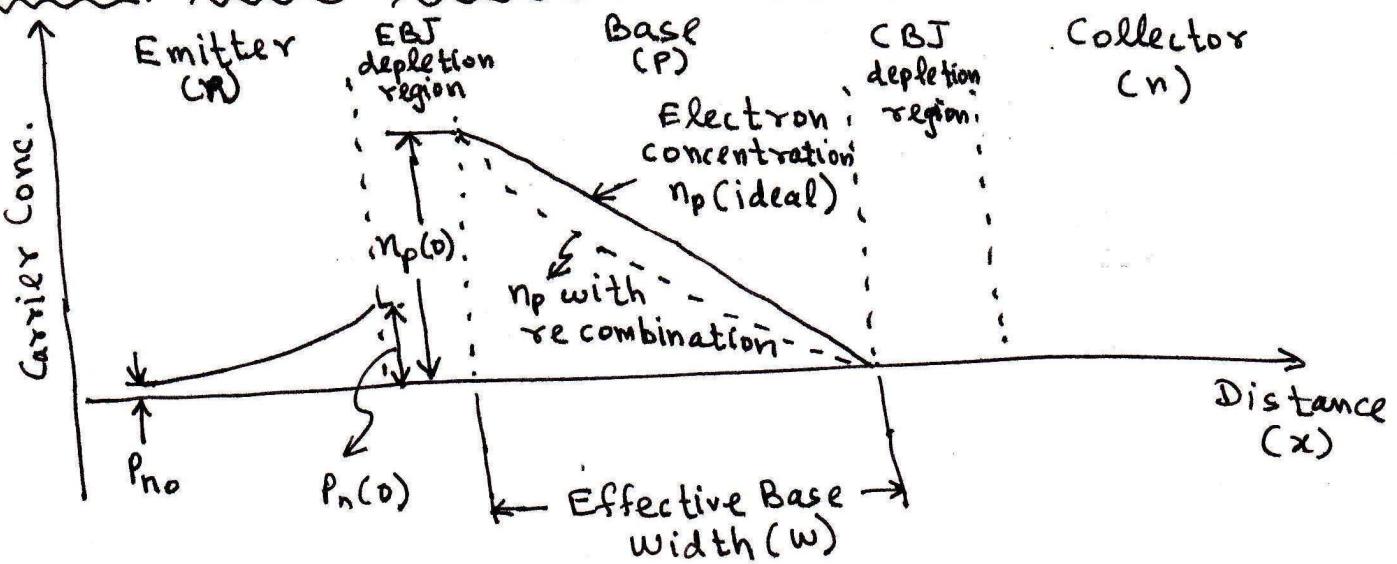

* Since base is very thin
 \Rightarrow carrier concentration will be almost a straight line.

* Why is the concentration "0" at CBJ, depletion region?

→ Since any electron reaching there is swept away by the electric field in depletion region the concentration falls to "0".

* What about recombination of electrons & holes in the base region?

→ Due to recombination the profile deviates from straight line ~~and becomes~~ slightly. We can ignore this while deriving the current.

* In a forward biased p-n junction the concentration,

$$n_p(0) = n_{p0} e^{\frac{V_{BE}}{V_T}}$$

where, n_{p0} = thermal equilibrium value of minority-carrier concentration.

V_T = thermal voltage $\approx 25 \text{ mV}$.

V_{BE} = forward biased base emitter voltage.

* The diffusion current in base region is,

$$I_n = A_E q D_n \frac{d n_p(x)}{dx}$$

$$\Rightarrow I_n = A_E q D_n \left(-\frac{n_p(0)}{w} \right)$$

where, A_E = cross-sectional area of BE junction.

$$q = 1.6 \times 10^{-19} \text{ C}$$

D_n = electron diffusivity in base.

w = effective base width.

* The electrons diffusing through base get collected by the collector thus giving collector current as,

$$i_c = I_n$$

$$\Rightarrow i_c = I_s e^{\frac{V_{BE}}{V_T}}$$

where, I_s = saturation current = $A_E q D_n \frac{n_{p0}}{W}$.

Now, $n_{p0} = \frac{n_i^2}{N_A}$, where n_i = intrinsic carrier concentration and N_A = doping concentration in base.

Thus,

$$I_s = \frac{A_E q D_n n_i^2}{N_A W}$$

* Is & i_c dependent on V_{CB} ??

NO.

→ So what do we have?

→ A current source between collector & emitter.

* What about the base current?

It has two components:-

- ① Due to holes injected from base region to emitter. This is given by,

$$i_{B1} = \frac{A_E q D_p n_i^2}{N_D L_p} e^{\frac{V_{BE}}{V_T}}$$

where, L_p = diffusion length (related to minority carrier lifetime).

D_p = hole diffusivity.

N_D = doping concentration in emitter.

- ② Due to holes that have to be supplied by external circuit in order to replace holes lost from the base through recombination.

$$i_{B2} = \frac{Q_n}{\tau_b}$$

where, τ_b = average time for minority electron to recombine with majority hole in the base.

Q_n = minority carrier charge stored in the base.

$$\Rightarrow Q_n = A_E q \times \frac{1}{2} n_p(0) W \dots \text{[Area of triangle].}$$

$$\Rightarrow Q_n = \frac{A_E q W n_i^2}{2 N_A} e^{V_{BE}/V_T} \dots \because n_p(0) = n_{p0} e^{V_{BE}/V_T}$$

or, $n_p(0) = \frac{n_i^2}{N_A} e^{V_{BE}/V_T}$

Thus, $i_{B2} = \frac{1}{2} \frac{A_E q W n_i^2}{\gamma_b N_A} e^{V_{BE}/V_T}$

Hence, total base current is,

$$i_B = i_{B1} + i_{B2}$$

$$\Rightarrow i_B = I_s \left[\frac{D_p}{D_N} \frac{N_A}{N_D} \frac{W}{L_p} + \frac{1}{2} \frac{W^2}{D_n \gamma_b} \right] e^{V_{BE}/V_T}$$

We know,

$$i_c = I_s e^{V_{BE}/V_T}$$

Thus, $i_B = \frac{i_c}{\beta}$

$$\text{where, } \beta = \frac{1}{\left(\frac{D_p}{D_N} \frac{N_A}{N_D} \frac{W}{L_p} + \frac{1}{2} \frac{W^2}{D_n \gamma_b} \right)}$$

* β is typically around 50 to 200.

* β is called common-emitter current gain.

→ What is β in a MOS??

* For high β :-

→ Base should be thin (W)

→ Emitter should be heavily doped than base i.e.
 $N_D \gg N_A$.

Emitter Current :- Since current entering a transistor must leave it, we have,

$$i_E = i_C + i_B$$

$$\Rightarrow i_E = (\beta + 1) i_B.$$

$$\Rightarrow i_E = \frac{\beta + 1}{\beta} i_C.$$

Sometimes i_C is expressed in terms of i_E leading to the following,


$$i_C = \frac{\beta}{\beta + 1} i_E$$

$$\text{or, } i_C = \alpha i_E \dots \text{where, } \alpha = \frac{\beta}{\beta + 1}.$$


* α = Common Base Current Gain.

LARGE SIGNAL EQUIVALENT CIRCUIT MODEL

(i) Voltage-Controlled-Current Source :-

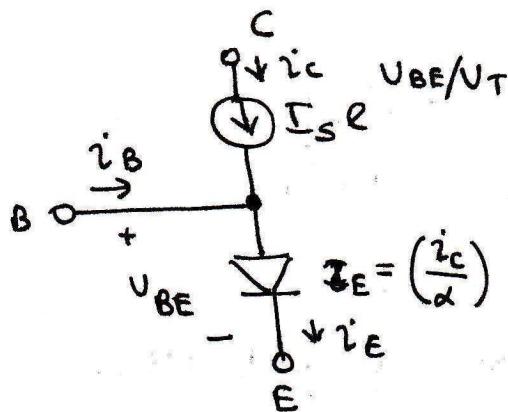

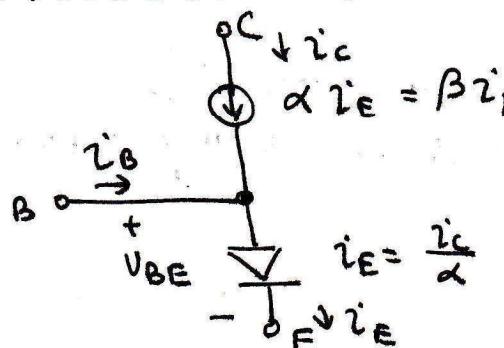(ii) Current-Controlled Current Source :-




BJT MODES OF OPERATION :-

<u>MODE</u>	<u>E B J</u>	<u>C B J</u>
① Cutoff	Reverse	Reverse
② Active	Forward	Reverse
③ Reverse Active	Reverse	Forward
④ Saturation	Forward	Forward

- * The " α " and " β " derived earlier is for active mode also sometimes called "forward active" mode to distinguish it from "reverse active" mode.
- * " α_F " & " β_F " are for "forward active" mode.
- * " α_R " & " β_R " are for "reverse active" mode.

NOTE:- Since BJT is rarely used in reverse active mode, whenever we use " α " & " β " we mean " α_F " and " β_F ".


STRUCTURE OF ACTUAL TRANSISTOR :-

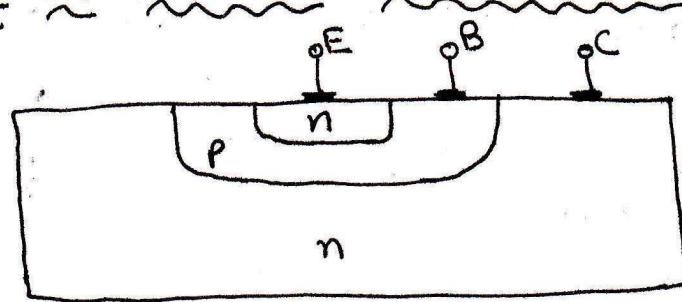

- * CBJ has a much larger area than EBJ.
- * If the roles of collector and emitter are reversed then we say the transistor is in "reverse active" mode.
- * So in reverse active mode we should have " α_R " and " β_R ".

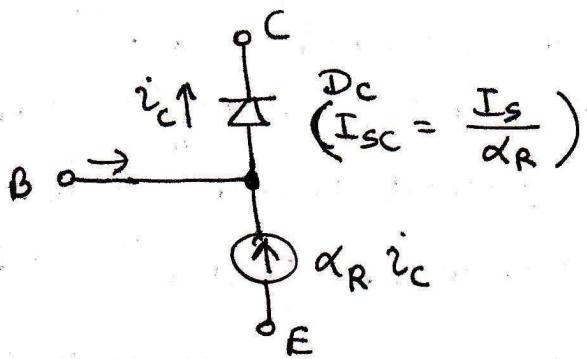- (10)
- * Typically " α_R " is in the range 0.01 to 0.5 and " β_R " is in the range 0.01 to 1.
 - * " α_R " and " β_R " are few orders of magnitude lower than " α_F " and " β_F ".

LARGE SIGNAL MODEL FOR NPN TRANSISTOR IN REVERSE ACTIVE MODE :-




NOTE :-


SATURATION IN BJT \equiv TRIODE IN MOS

ACTIVE IN BJT \equiv SATURATION IN MOS



PNP TRANSISTOR :-

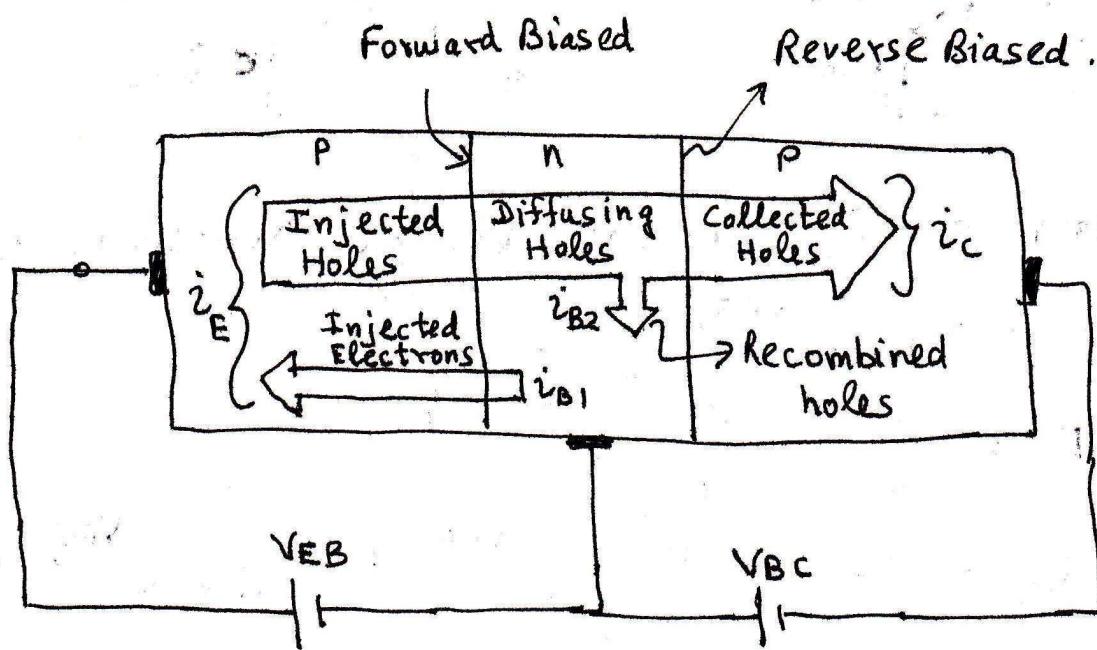


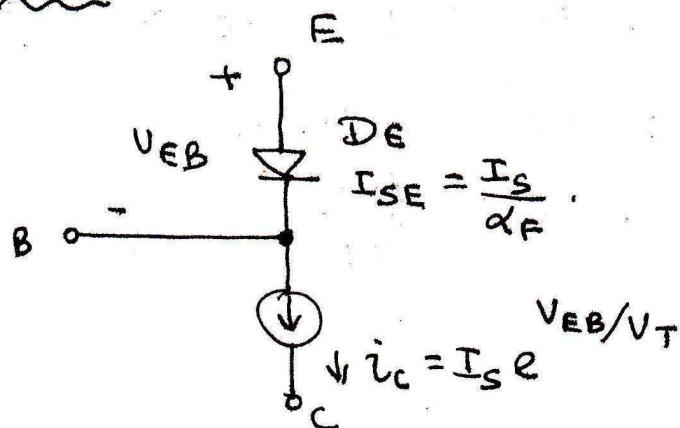
Large Signal Model for PNP transistor in Forward Active Mode :-



TRANSISTOR SYMBOL :-

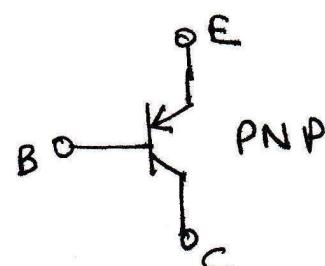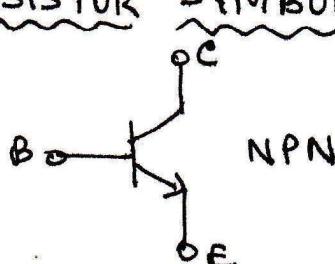

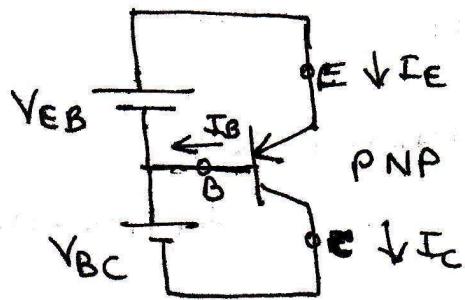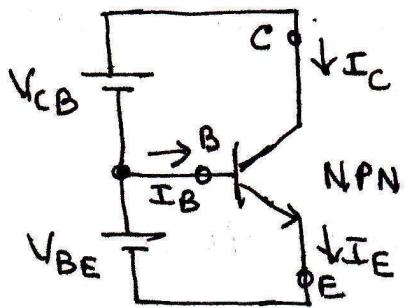Voltage Polarities And Current Flow in Transistors biased in active mode:-



SUMMARY OF BJT Current Voltage Relationship IN ACTIVE MODE :-

$$\textcircled{1} \quad I_c = I_s e^{V_{BE}/V_T}$$

$$\textcircled{2} \quad I_B = \frac{I_c}{\beta} = \left(\frac{I_s}{\beta} \right) e^{V_{BE}/V_T}$$

$$\textcircled{3} \quad I_E = \frac{I_c}{\alpha} = \left(\frac{I_s}{\alpha} \right) e^{V_{BE}/V_T} = I_{SE} e^{V_{BE}/V_T}$$


For PNP, replace V_{BE} with V_{EB}

$$\textcircled{4} \quad I_c = \alpha I_E, \quad I_B = (1-\alpha) I_E = \frac{I_E}{\beta+1}$$

$$\textcircled{5} \quad I_c = \beta I_B, \quad I_E = (\beta+1) I_B$$

$$\textcircled{6} \quad \beta = \frac{\alpha}{1-\alpha}, \quad \alpha = \frac{\beta}{\beta+1}$$


COMMON BASE TRANSISTOR CHARACTERISTICS:-

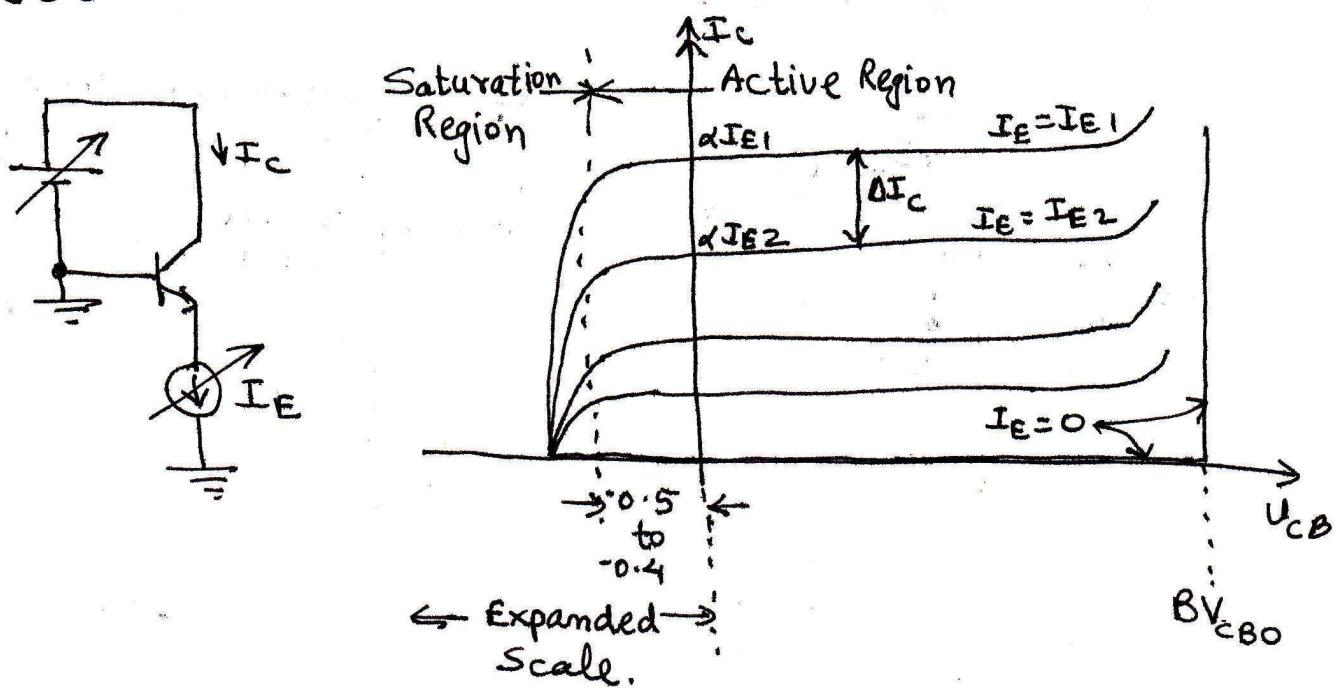

- * The curves intersect x-axis at αI_E , where I_E is constant emitter current, and α is "large signal" α .
- * An "incremental" or "small signal" α is given by,

$$\alpha_{\text{small-signal}} = \frac{\Delta I_C}{\Delta I_E}.$$

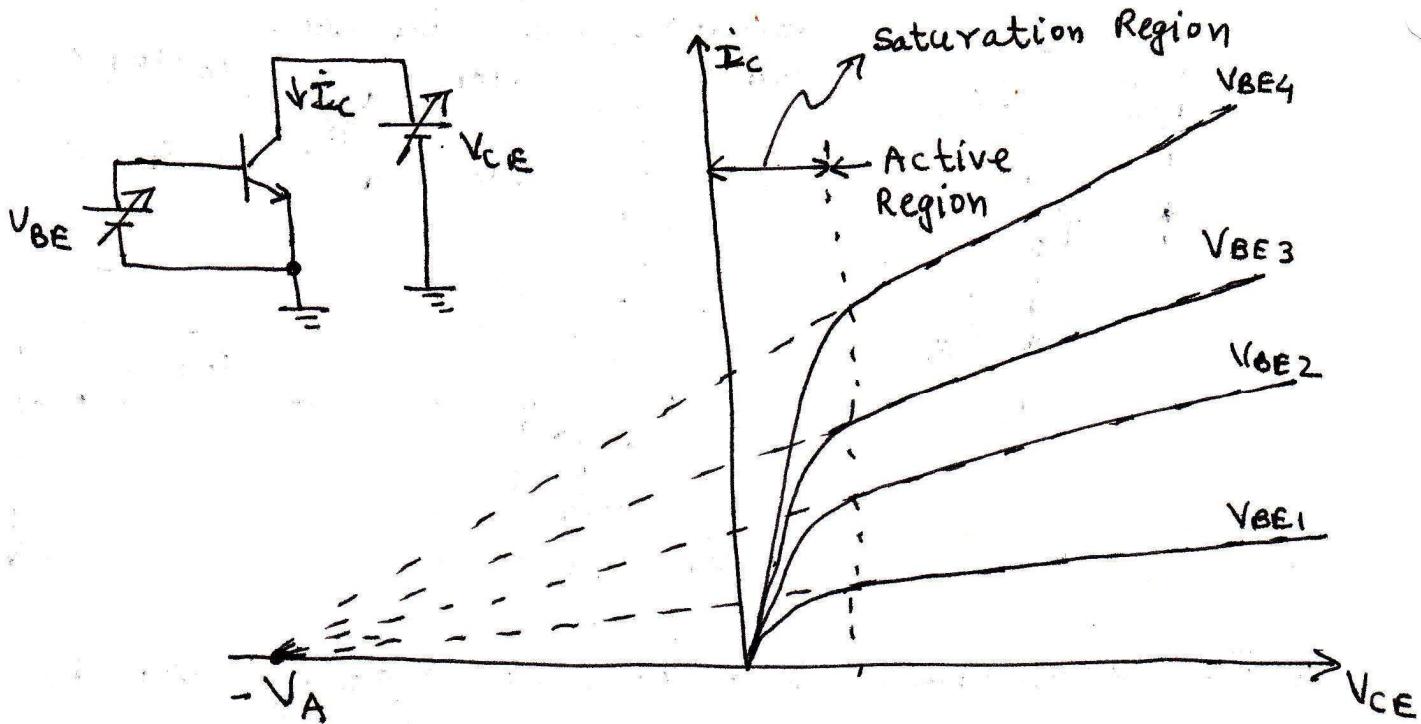DEPENDENCE OF I_c ON COLLECTOR VOLTAGE - EARLY EFFECT:-



For a particular V_{BE} we have,

$$I_c = A_E q D_n \frac{n_{p0}}{w} e^{\frac{V_{BE}/V_T}{}}$$

$$\text{or, } I_c = A_E q D_n \underbrace{\frac{n_i^2}{N_A w}}_{I_S} e^{\frac{V_{BE}/V_T}{}}$$

* We see, $I_s \propto \frac{1}{w} \Rightarrow$ if w reduces I_s increases.

* What defines w ? i.e. ~~is~~ effective base width?

* Increasing V_{CE} for particular V_{BE} , is going to increase CBJ depletion width $\Rightarrow w$ reduces.

* If w reduces I_s increases $\Rightarrow I_c$ increases.

* ~~Discovered by~~ Discovered by J.M. Early \Rightarrow found extrapolated characteristics all meet at one point called EARLY VOLTAGE.

- * The linear dependence of I_c on V_{CE} can be accounted by assuming I_s doesn't change but adding additional factor $(1 + \frac{V_{CE}}{V_A})$ to I_c as shown below:-

$$I_c = I_s e^{\frac{V_{BE}/V_T}{1 + \frac{V_{CE}}{V_A}}}$$

- * Since, I_c changes with V_{CE} there has to be a resistance associated with it and it is called the output resistance " r_o ".


$$r_o = \left[\left(\frac{\partial I_c}{\partial V_{CE}} \right)_{V_{BE} = \text{constant}} \right]^{-1}$$

$$\Rightarrow r_o = \frac{V_A}{I_c}$$


~~Typically $V_{CE} > V_A$, thus,~~

where, $I_c = I_s e^{\frac{V_{BE}/V_T}{1 + \frac{V_{CE}}{V_A}}}$ is the current with "Early Effect" neglected.

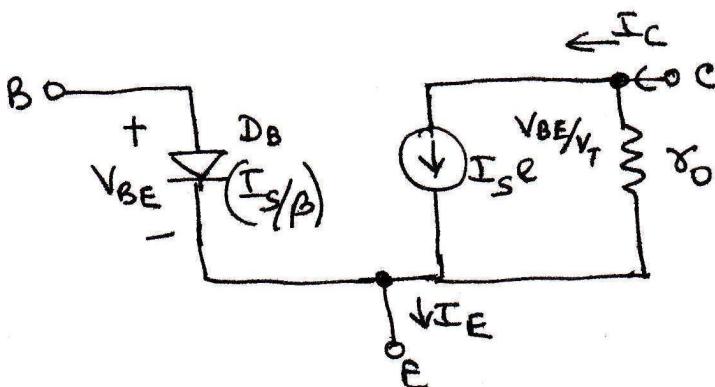- * LARGE SIGNAL MODEL WITH EARLY EFFECT:-





VCCS Model

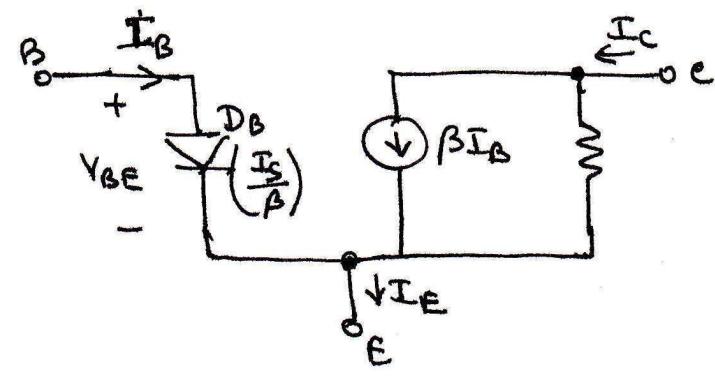

CCCS Model

COMMON Emitter Characteristics :-

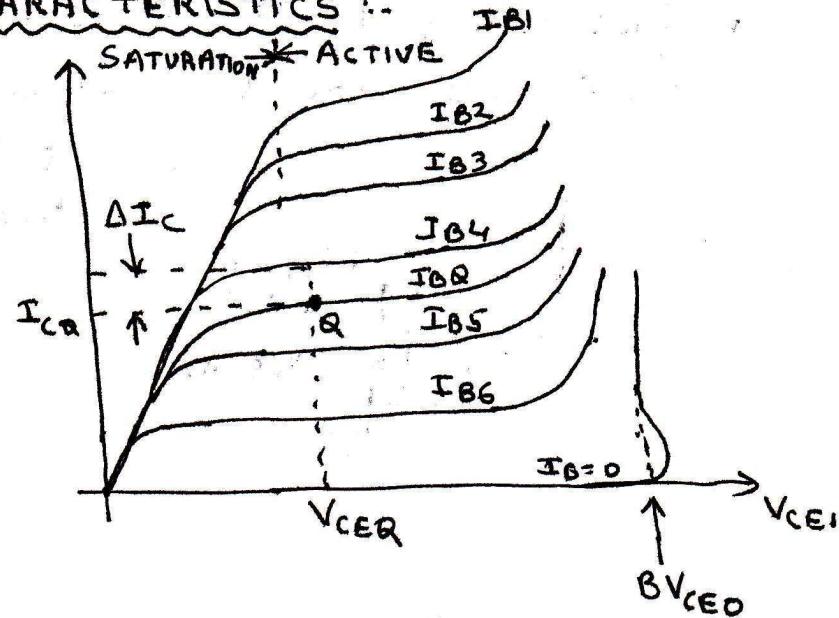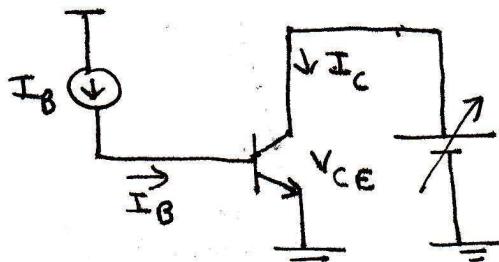

- * Common emitter current gain is simply called β (to be more precise β_F).

- * At the operating point,

$$\beta_{dc} \equiv \frac{I_{ca}}{I_{BQ}}$$

This is called large signal or dc β .



- * Incremental or ac β is given by,

$$\beta_{ac} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE} = \text{constant}}$$

- * β_{ac} and β_{dc} differ in magnitude by approx. 10 to 20%.

- * For this course, β_{ac} and β_{dc} will not be differentiated i.e. we won't make a distinction between the two.

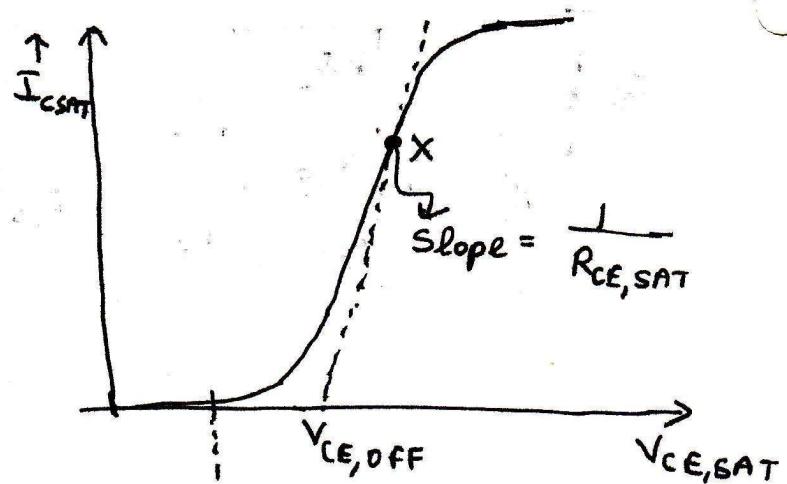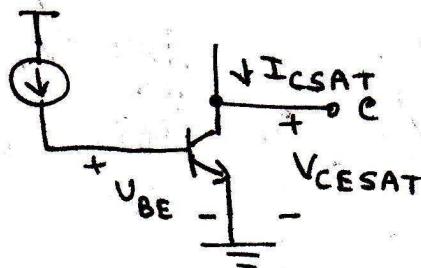
* Just like a MOSFET in triode region a saturated BJT acts like a resistor.



$$R_{CE,SAT} = \left. \frac{\partial V_{CE}}{\partial I_c} \right|_{I_B = \text{some value}, I_c = I_{CSAT}}$$

$$V_T \ln \left(\frac{1}{\alpha_F} \right)$$

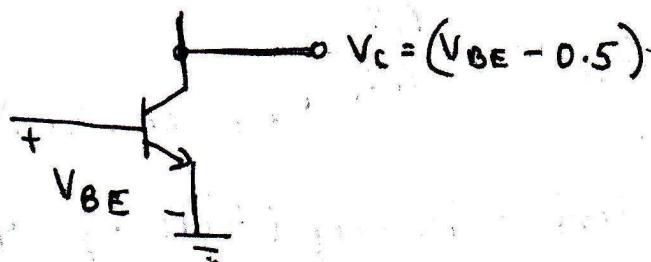* Note that Base-Collector junction get forward biased and carries substantial current when base is greater than collector by 0.5 Volts atleast.



$$\Rightarrow V_{CE,SAT} \approx 0.2V$$

SMALL SIGNAL OPERATION AND MODELS :-

Convention :- $v_{BE} = V_{BE} + v_{be}$

$$v_{CE} = V_{CE} + v_{ce}$$


$$i_c = I_c + i_e$$

$$i_B = I_B + i_b$$

$$i_E = I_E + i_e$$

Conceptual circuit to arrive at small signal model :-

At DC (i.e. no ac signal applied).

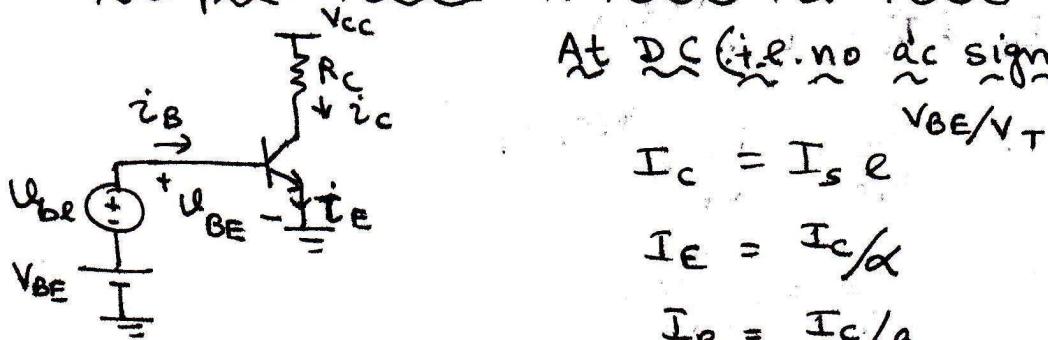

$$I_c = I_s e^{\frac{V_{BE}}{V_T}}$$

$$I_E = I_c / \alpha$$

$$I_B = I_c / \beta$$

$$V_C = V_{CE} = V_{CC} - I_c R_C$$

With ac signal :-

$$v_{BE} = V_{BE} + v_{be}$$

$$\Rightarrow i_c = I_c + i_e$$

$$\Rightarrow i_c = I_s e^{(V_{BE} + v_{be}) / V_T}$$

$$\Rightarrow i_c = I_s e^{\frac{V_{BE}}{V_T}} e^{\frac{v_{be}}{V_T}}$$

$$\Rightarrow i_c = I_c e^{\frac{v_{be}}{V_T}}$$

$$\Rightarrow i_c = I_c \left(1 + \frac{v_{be}}{V_T} \right) \dots \text{[By Taylor series expansion with } \frac{v_{be}}{V_T} \ll 1 \text{]}$$

Thus,

$$i_c = I_c + \frac{I_c}{V_T} u_{be}$$

$$\Rightarrow \text{small signal, } i_c = \frac{I_c}{V_T} u_{be}$$

$$\Rightarrow \text{Transconductance, } g_m = \frac{I_c}{V_T}.$$

* Can you prove that, $g_m = \left. \frac{\partial i_c}{\partial V_{BE}} \right|_{i_c = I_c}$?

Now, $\cancel{I_c} = I_s e^{V_{BE}/V_T}$

$$\Rightarrow \frac{\partial i_c}{\partial V_{BE}} = \frac{I_s}{V_T} e^{V_{BE}/V_T}$$

$$\Rightarrow \frac{\partial i_c}{\partial V_{BE}} = \frac{I_c}{V_T}.$$

* Unlike MOSFET where there is no gate current at DC, we have a base current in BJT at DC.

* Now,

$$i_B = I_B + i_b$$

$$\Rightarrow i_B = \frac{I_c}{\beta} + \frac{I_c}{\beta V_T} u_{be}$$

Thus,

$$i_b = \frac{g_m}{\beta} u_{be}$$

$$\Rightarrow \frac{u_{be}}{i_b} = \frac{\beta}{g_m} = r_\pi = \text{small signal input resistance between base and emitter.}$$

Thus, small signal model of BJT is as follows:-

