

End-Semester

Date: April 2016 ;
Spring Semester, 2015-2016;
Subject no. **EC 21008**

Time: 3 hours;
Full Marks: 50;
Department: E & ECE;
Subject name: **Analog Electronic Circuits**

Number of Students **245**
II year B. Tech.

Instruction: Answer **ALL** questions and in the **same order** of the questions. Wherever it is necessary, you may use assumption(s) with reasonable justification.

Common Information: Unless otherwise it is specified in question, use the following values of different device parameters:

For n-p-n transistor, $V_{BE(on)} \approx 0.6$ V, $V_{CE(sat)} \approx 0.3$ V, $\beta_F = 100$, $V_A = 100$ V

For p-n-p transistor, $V_{EB(on)} \approx 0.6$ V, $V_{EC(sat)} \approx 0.3$ V, $\beta_F = 100$, $V_A = 100$ V

For n-MOS and p-MOS enhancement transistors, the trans-conductance factor, $K = 1\text{mA/V}^2$, $|V_{th}| = 1$ V, $\lambda = 0.01\text{ V}^{-1}$

Q.1. For the circuit given in Fig.1.a,

- Find d.c. operating point of the transistor.
 - Find the values of trans-impedance and input impedance of the amplifier in mid-frequency range when the switch SW is closed.
 - Find the values of transconductance and voltage gain amplifier in mid-frequency range when the switch is open
- [2 +4+4]

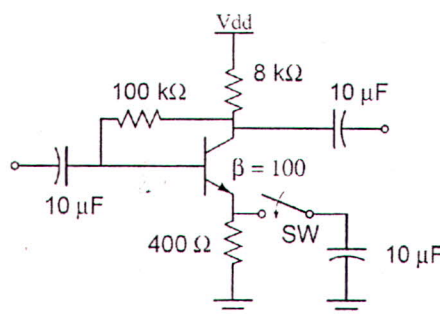


Fig. 1.a

OR

For the circuit given in Fig.1.b,

- Find the d.c. operating point of all the transistors, (ii) Find the small signal voltage gain, input impedance and output impedance in mid-frequency range,
 - Find the output voltage v_{out} in terms of the input voltage v_s .
- [Given: $R_{G1} = 10\text{ k}\Omega$, $R_{G2} = 20\text{ k}\Omega$, $R_D = 10\text{ k}\Omega$, $R_L = 1\text{ k}\Omega$, $R_S = 1\text{ k}\Omega$, $C_1 = C_2 = C_3 = 1\text{ }\mu\text{F}$, $I_{ref} = 0.15\text{ mA}$, $V_{dd} = 10\text{ V}$, For d.c. condition, you may approximate $(1 + \lambda|V_{DS}|) \approx 1$]

[2 +6+2]

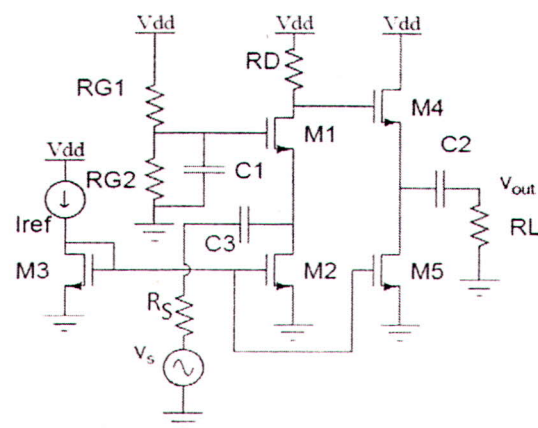


Fig. 1.b

Q.2. Circuit diagram of a feedback system is shown in Fig. 2.a. The input signal $V_s = 0.2 \sin(\omega t)$ Volts.

- Find the **output voltage** V_o when the switch **SW1** is closed but the switch **SW2** is open.
 - Find the **feedback voltage** V_f and the **output voltage** V_o when both the switched **SW1** and **SW2** are open.
 - Find the **output voltage** V_o when the switch **SW1** is open but the switch **SW2** is closed.
- [4+4+2]

P.T.O.

(1)

P.M.

PRADIP MANDAL
MRIGANK SHARAD

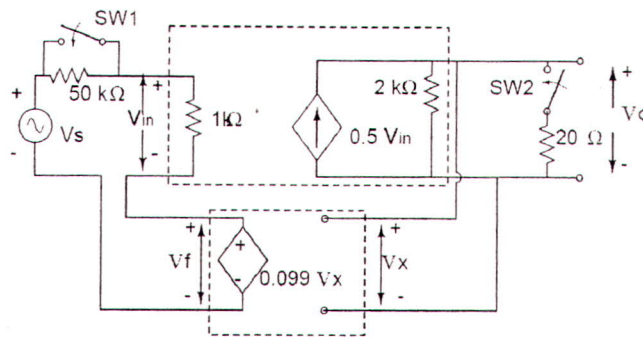


Fig. 2.a

OR

Q.2. The circuit in fig.2.b acts like a trans-impedance amplifier. The first stage has the input device M1, which is biased with a DC current of $100\mu\text{A}$. The input terminal faces a relatively large capacitor C_{in} . The input source provides a pulsed current waveform with $I_{ON} = 25\mu\text{A}$ and $I_{OFF} = 0$. M1 has been sized up to minimize the input resistance of the first stage and to keep the pole corresponding to node A at sufficiently high frequency. A Common-Source amplifier with M6 as the input device, constitutes the 2nd stage. The W/L ratio of all the transistors are marked in the figure ($L = 1\mu\text{m}$ for all devices). For transistors use $\mu_n C_{ox} = \mu_p C_{ox} = 5 \text{ mA/V}^2$, $\lambda = 0$, $V_{tn} = |V_{tp}| = 2\text{V}$, $C_{gs} = 5\text{pF}/\mu\text{m}^2$, $C_{gd} = 2\text{pF}/\mu\text{m}^2$, $C_{db} = C_{sb} \sim 0$. $V_{dd} = 10\text{V}$.

- Ignoring small signal swing at nodes A and B, for a DC bias current of $100\mu\text{A}$ in M1, find the minimum gate voltages V_{g1} and V_{g2} , to keep M1, M2 in saturation. Hence, determine the ratio $R_{g1}:R_{g2}:R_{g3}$.
- Considering the case of $i_{in} = I_{ON}$, find the VSG drop for M3. Using this information, and for the values of V_{g1} and V_{g2} determined above, find the minimum V_{dd} needed to keep all transistors in the first stage in saturation.
- Find the high frequency poles at nodes A, B and C.
- Find the value of R_d such that the pole at node D is equal to the lowest of the three poles calculated in part (c).

[3+2+3+2]

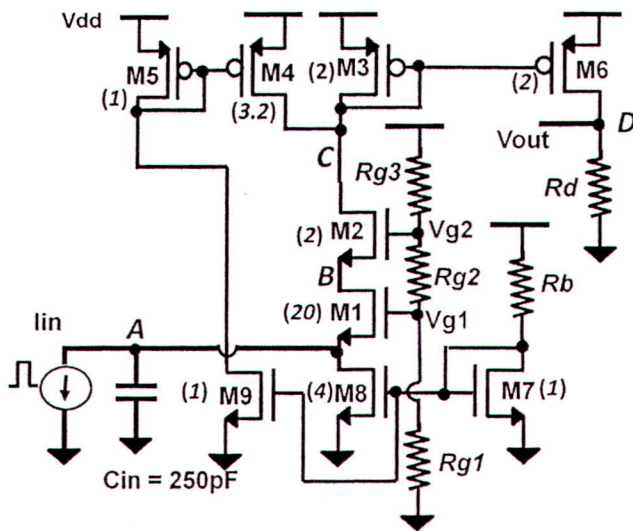


Fig. 1.b

Q.3. The circuit given in fig. 3.a depicts a differential amplifier with resistive load followed by a differential amplifier with current mirror load. For transistors use $\mu_n C_{ox} = 5 \text{ mA/V}^2$, $|V_A| = 50\text{V}$, $V_{tn} = |V_{tp}| = 2\text{V}$. The W/L ratio of all the transistors are marked in the figure ($L = 1\mu\text{m}$ for all devices). Bias current in both stages has been set to 1mA . $R_{d1} = R_{d2} = 10\text{k}\Omega$.

Find the expressions for V_{o+} , V_{o-} and V_{out} when

(2)

P.M

- (i) $V_{in+} = V_{in-} = 5 + 0.01 \sin(\omega t)$ V, hence, report the common mode gain of the 1st and the 2nd stage and hence for the overall circuit.

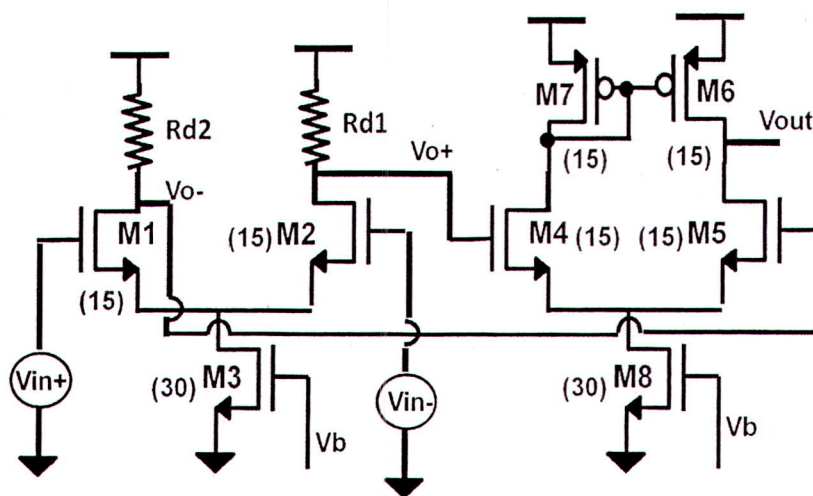


Fig. 3.a

- (ii) $V_{in+} = V_{in-} = 5 + 0.01 \sin(\omega t)$ V, $R_{d1} = 10.05$ k Ω , $R_{d2} = 10.0$ k Ω , report the overall common-mode gain. Justify any approximation. [3+7]

OR of Q.3

A fully differential amplifier circuit is shown in Fig. 3.b.

- (i) Find the values of differential mode gain and common mode gain of the amplifier for 0V input quiescent voltage (i.e. $V_{IN1Q} = V_{IN2Q} = 0$ V).
(ii) For input signals $V_{in1} = -2.2$ V and $V_{in2} = -2.2 + 0.02 \sin(2000\pi t)$ V, find the output voltages of the amplifier. (4+6)

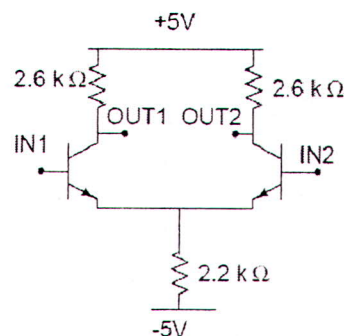


Fig 3.b

Q4. For the differential amplifier in Fig. 4, assume that the devices in the two branches are well matched.

- (i) Find the value of R_o so that in d.c. condition (with suitable input common mode level) $I_{SD1} = 2$ mA. Use this value of R_o for the subsequent parts.
(ii) Calculate the input common mode range over which all the transistors remain in saturation region of operation.
(iii) Draw small signal equivalent circuits of the amplifier for differential mode of operation, derive the expression of differential mode gain and find its value.
(iv) Draw small signal equivalent circuits of the amplifier for common mode of operation derive the expression of common mode gain and find its value.

[Given: $V_{DD} = 10$ V]

[2+2+3+3]

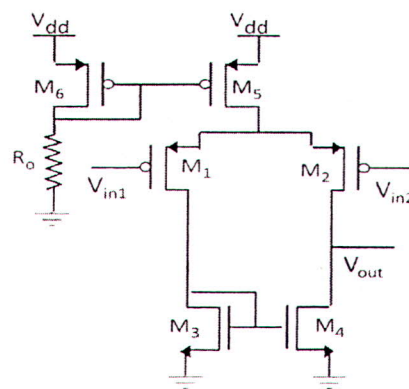


Fig. 4

$$A(s) = \frac{200}{\left(1 + \frac{s}{10^3}\right)\left(1 + \frac{s}{\sqrt{3} \times 10^7}\right)} \text{ and } B(s) = \frac{0.5}{\left(1 + \frac{s}{\sqrt{3} \times 10^5}\right)} \text{ respectively}$$

OR

[illegible]

- (i) Identify the feedback topology and find the feedback factor β .
- (ii) Find the open loop gain, input resistance and output resistance of the open-loop amplifier, considering the loading effect of the feedback network.
- (iii) For the open-loop amplifier (considering the loading effect of the feedback network), find the values of the dominant and the first non-dominant high frequency poles.
- (iv) Assuming only the dominant and first non-dominant pole to be significant, (assuming 2-pole system), find the phase margin for the loop transfer function $A\beta$.

(4)

P.D