


BJT (npn)

BJT (pnp)

N-MOS


P-MOS

(1)

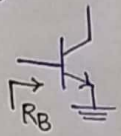


$$R_B = r_{\pi}$$

(1)

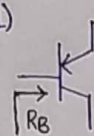


$$R_B = r_{\pi}$$

(1)

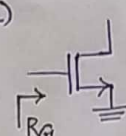


$$R_G = \infty$$

(1)

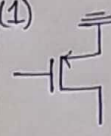


$$R_G = \infty$$

(2)

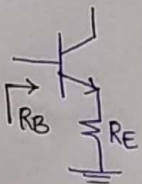


$$R_B = r_{\pi} + (\beta + 1)R_E$$

(2)

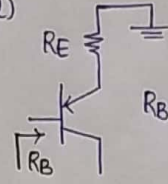


$$R_B = r_{\pi} + (\beta + 1)R_E$$

(2)

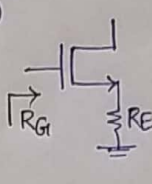


$$R_G = \infty$$

(2)

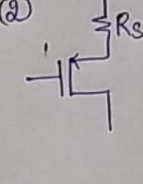


$$R_G = \infty$$

(3)

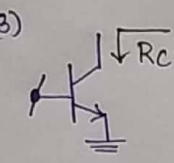


$$R_C = r_o$$

(3)

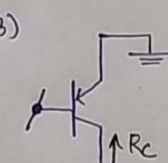


$$R_C = r_o$$

(3)

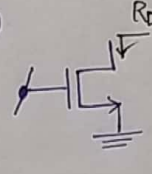


$$R_D = r_o$$

(3)

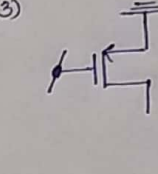


$$R_D = r_o$$

(4)

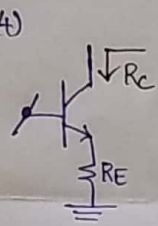


$$R_C = g_m r_o (R_E \parallel r_{\pi}) + r_o + R_E \parallel r_{\pi}$$

(4)

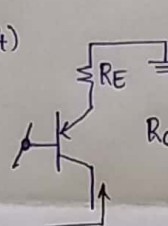


$$R_C = g_m r_o (R_E \parallel r_{\pi}) + r_o + R_E \parallel r_{\pi}$$

(4)

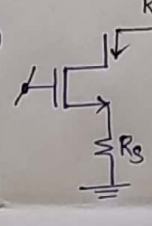


$$R_D = g_m r_o R_S + R_S + r_o$$

(4)

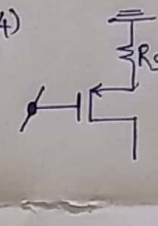


$$R_D = g_m r_o R_S + R_S + r_o$$

(5)

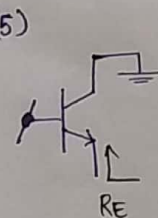


$$R_E = \frac{1}{g_m} \parallel r_o \parallel r_{\pi}$$

(5)

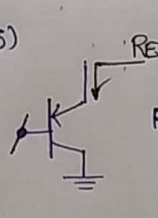


$$R_E = \frac{1}{g_m} \parallel r_o \parallel r_{\pi}$$

(5)

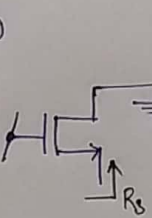


$$R_S = \frac{1}{g_m} \parallel r_o$$

(5)

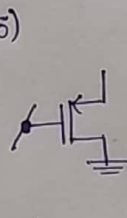


$$R_S = \frac{1}{g_m} \parallel r_o$$

(6)

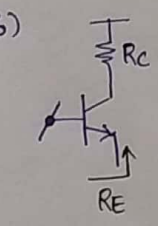


$$R_E = \frac{R_C + r_o}{1 + g_m r_o} \parallel r_{\pi}$$

(6)

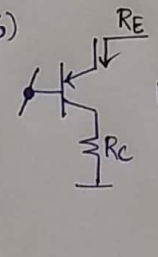


$$R_E = \frac{R_C + r_o}{1 + g_m r_o} \parallel r_{\pi}$$

(6)

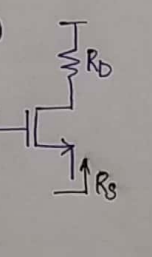


$$R_S = \frac{r_o + R_D}{1 + g_m r_o}$$

(6)

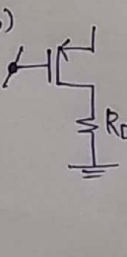


$$R_S = \frac{r_o + R_D}{1 + g_m r_o}$$

(7)

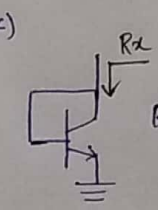


$$R_L = r_{\pi} \parallel r_o \parallel \frac{1}{g_m}$$

(7)

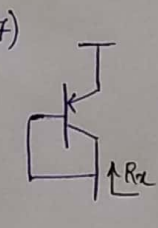


$$R_L = r_{\pi} \parallel r_o \parallel \frac{1}{g_m}$$

(7)

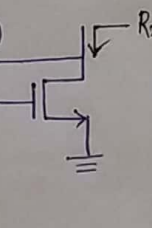


$$R_L = r_o \parallel \frac{1}{g_m}$$

(7)

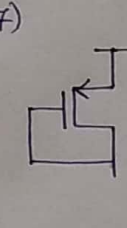


$$R_L = r_o \parallel \frac{1}{g_m}$$

BJT (npn)

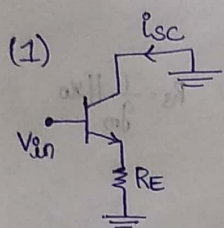


$$G_m = \frac{g_m \alpha_o \alpha_c - R_E}{R_E (\alpha_o + \alpha_c) + \alpha_o \alpha_c (1 + g_m R_E)}$$

BJT (npn)

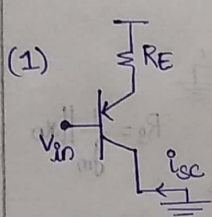


$$G_m = \frac{g_m \alpha_o \alpha_c - R_E}{R_E (\alpha_o + \alpha_c) + \alpha_o \alpha_c (1 + g_m R_E)}$$

N-MOS

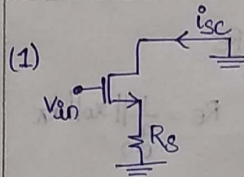


$$G_m = \frac{g_m}{1 + g_m R_S + \frac{R_S}{\alpha_o}}$$


P-MOS

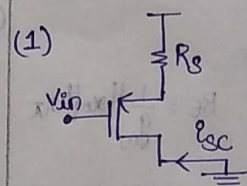

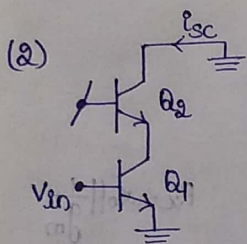
$$G_m = \frac{g_m}{1 + g_m R_S + \frac{R_S}{\alpha_o}}$$



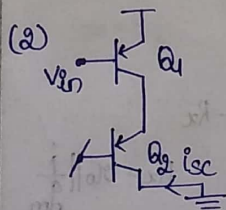
$$G_m = \frac{g_{m1} \alpha_{o1}}{\alpha_{o1} + \frac{\alpha_{o2}}{1 + g_{m2} \alpha_{o2}} + \frac{\alpha_{o1} \alpha_{o2}}{(1 + g_{m2} \alpha_{o2}) \alpha_{o2}}}$$


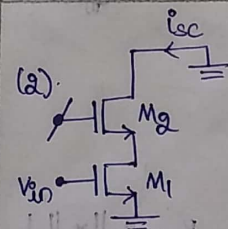
$$G_m = \frac{g_{m1} \alpha_{o1}}{\alpha_{o1} + \frac{\alpha_{o2}}{1 + g_{m2} \alpha_{o2}} + \frac{\alpha_{o1} \alpha_{o2}}{(1 + g_{m2} \alpha_{o2}) \alpha_{o2}}}$$



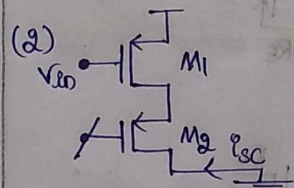
$$G_m = \frac{g_{m1} \alpha_{o1}}{\alpha_{o1} + \frac{\alpha_{o2}}{1 + g_{m2} \alpha_{o2}}}$$



$$G_m = \frac{g_{m1} \alpha_{o1}}{\alpha_{o1} + \frac{\alpha_{o2}}{1 + g_{m2} \alpha_{o2}}}$$

Voltage amplifier : A_v

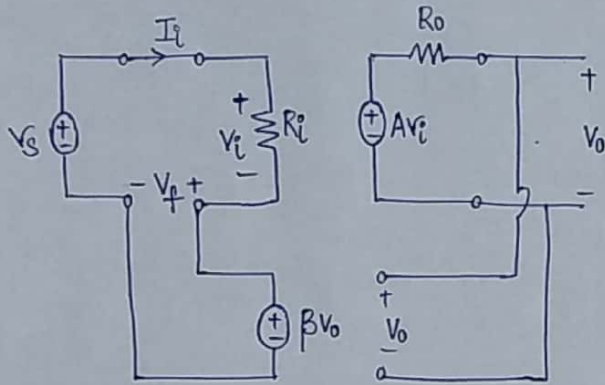


$$R_{if} = R_i (1 + A\beta) ; R_{of} = \frac{R_o}{1 + A\beta} ;$$

$$A_f = \frac{A}{1 + \beta A}$$

Series - Shunt feedback

Voltage - Voltage feedback
(sense) (return)

Current amplifier : A_i

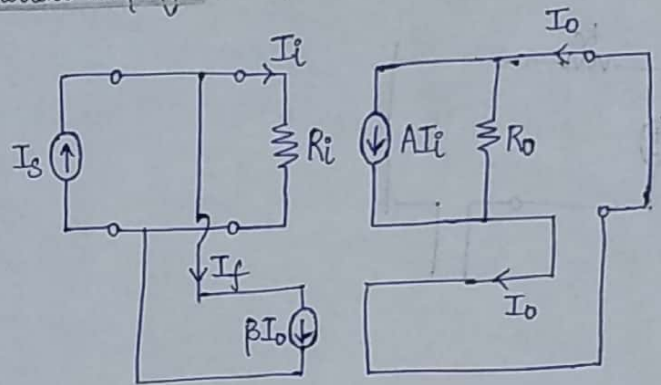


$$R_{if} = \frac{R_i}{1 + A\beta} ; R_{of} = R_o (1 + A\beta) ;$$

$$A_f = \frac{A}{1 + \beta A}$$

Shunt - Series feedback

Current - Current feedback
(sense) (return)

Transconductance amplifier : G_{m}

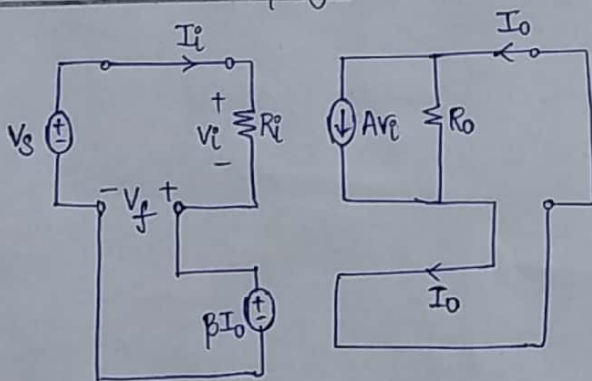


$$R_{if} = R_i (1 + A\beta) ; R_{of} = R_o (1 + A\beta) ;$$

$$A_f = \frac{A}{1 + A\beta}$$

Series - Series feedback

Current - Voltage feedback
(sense) (return)

Transresistance amplifier : R_m

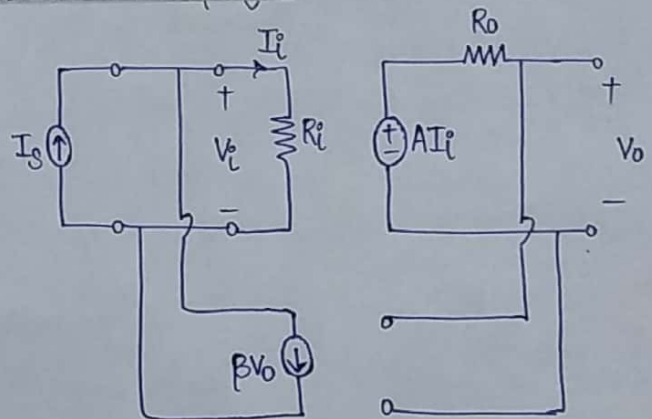


$$R_{if} = \frac{R_i}{1 + A\beta} ; R_{of} = \frac{R_o}{1 + A\beta} ; A_f = \frac{A}{1 + A\beta}$$

Shunt - Shunt feedback

Voltage - Current feedback
(sense) (return)


Feedback Factor (β)

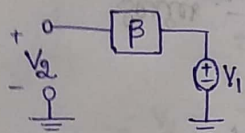

$$\beta = \frac{V_2}{V_1}$$

Series - Shunt


Voltage - Voltage

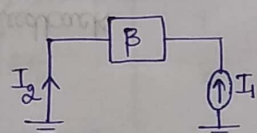

$$\beta = \frac{I_2}{I_1}$$

Shunt - Series


Current - Current

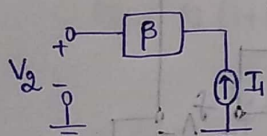

$$\beta = \frac{V_2}{I_1}$$

Series - Series

Current - Voltage

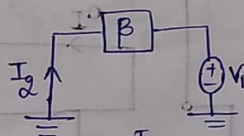


$$\beta = \frac{I_2}{V_1}$$

Shunt - Shunt


Voltage - Current

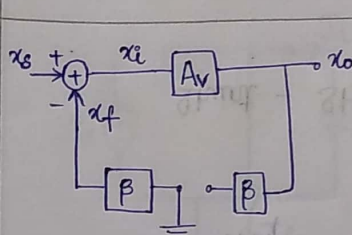Connections of Sense duplicate and Return duplicate




Series - Shunt

Voltage - Voltage

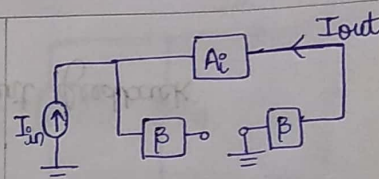


Shunt - Series

Current - Current

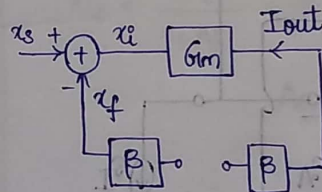

Series - Series

Current - Voltage

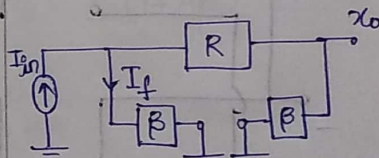


Shunt - Shunt


Voltage - Current

BJT & MOS

① NPN :

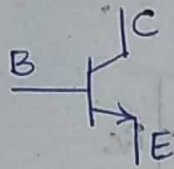


PNP :

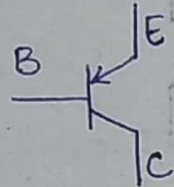


①

NMOS :

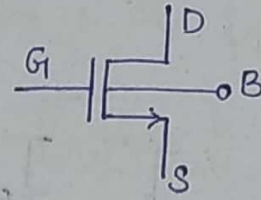

PMOS :

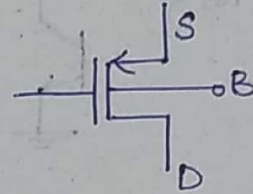

②

$$I_C = I_S \cdot e^{\frac{V_{BE}}{V_T}} \cdot \left(1 + \frac{V_{CE}}{V_A}\right)$$

②

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left(2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2 \right)$$

—— triode

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

—— saturation

③

$$g_m = \frac{I_C}{V_T}$$

③

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$$

$$r_o = \frac{V_A}{I_C}$$


$$r_o = \frac{1}{\lambda I_D}$$

$$\beta = \frac{\beta}{g_m}$$


$$\beta = \frac{I_C}{I_B}$$

Biasing Schemes :


BJT :

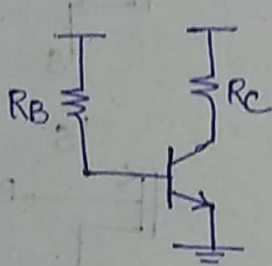


simple biasing

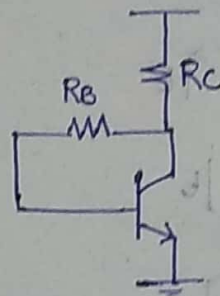

self biasing

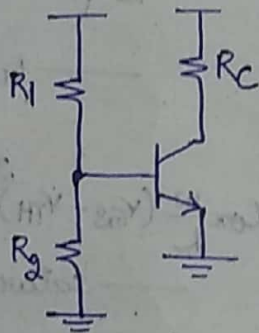


resistive divider biasing

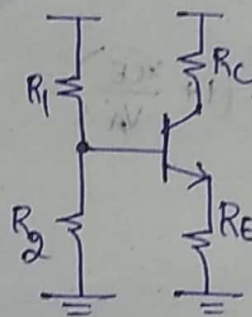


emitter degeneration biasing


MOS :

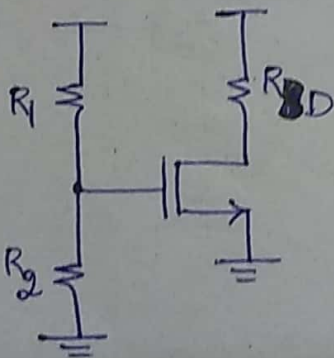

resistive divider biasing

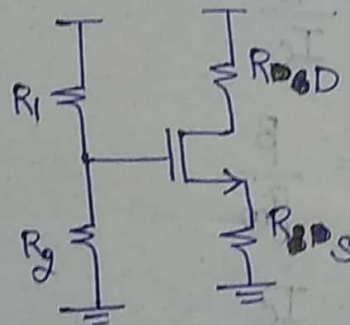


source degeneration biasing

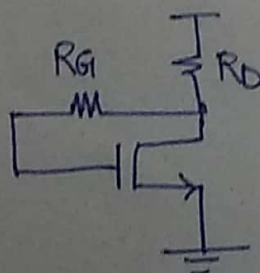

self biasing

Common Emitter :


(a) Resistive Load :

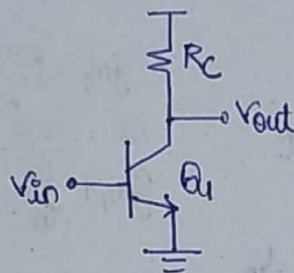


$$g_{m1} ; R_c ; \beta \alpha_1$$

$$-g_{m1} R_c$$

(b) Diode Connected load :

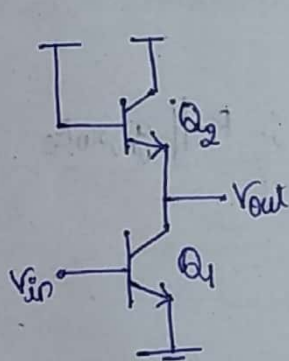

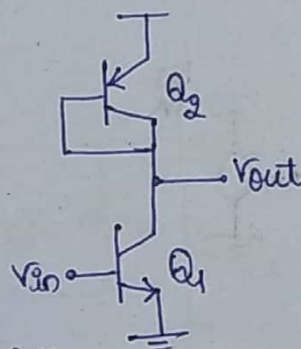
$$g_{m1} ; \frac{1}{g_{m2}} ; \beta \alpha_1$$



$$-\frac{g_{m1}}{g_{m2}}$$


(c) Current Source Load :

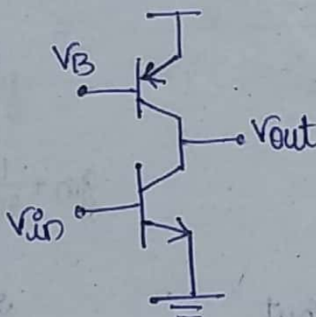

$$g_{m1} ; \alpha_{01} \parallel \alpha_{02} ; \beta \alpha_1$$

$$-g_{m1} (\alpha_{01} \parallel \alpha_{02})$$


(d) Emitter Degenerated :

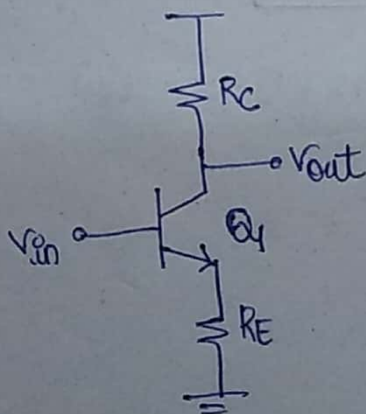

$$\frac{g_{m1}}{1 + g_{m1} R_E} ; \cong R_c ; \beta \alpha_1 + (\beta + 1) R_E$$

$$-\frac{R_c}{R_E}$$

Common base :

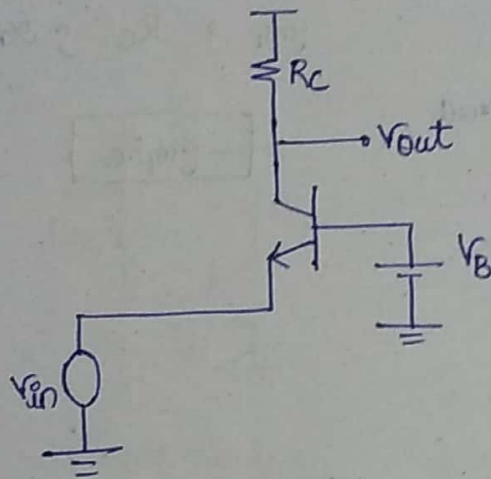


$$g_{m1} ; R_C || \omega_o ; \frac{R_C + \omega_o}{1 + g_{m1} \omega_o} || \omega_o$$

$$g_{m1} + \frac{1}{\omega_o}$$

$$+ (g_{m1} + \frac{1}{\omega_o}) (R_C || \omega_o)$$


if

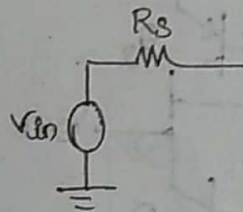

$$\frac{g_{m1}}{1 + g_{m1} R_S} ; R_C || g_{m1} \omega_o R_S$$

Common collector :

Emitter Follower

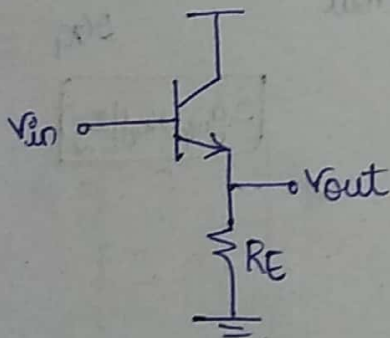

$$g_{m1} + \frac{1}{\omega_o} ; R_E || \omega_o || \frac{1}{g_{m1}} || \omega_o ;$$

$$\omega_o + (\beta + 1) R_E$$

$$g_{m1} \frac{R_E}{1 + g_{m1} R_E}$$

BJT

* CB : $C_u = \frac{C_{u0}}{\left(1 + \frac{V_{CB}}{V_0}\right)^m}$


* Base-diffusion cap.

$$C_{de} = \tau_F \frac{I_C}{V_T}$$

* EB : $C_{je} \approx 2C_{je0}$
— bias of 0V

$$C_\pi = C_{je} + C_{de}$$

* C_{cs} - collector substrate cap.

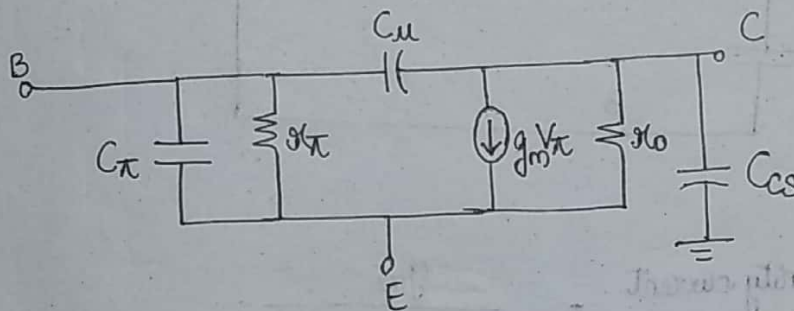

f_T : unity current gain frequency $= \frac{g_m}{2\pi(C_\pi + C_\mu)}$

MOS

* $C_{gs} = C_{gd} = \frac{1}{2} \omega L C_{ox} + \omega C_{ov}$ } Triode

$C_{gs} = \frac{2}{3} \omega L C_{ox} + \omega C_{ov}$
 $C_{gd} \approx 0 + \omega C_{ov}$ } Saturation


$C_{gs} = C_{gd} \approx 0 + \omega C_{ov}$ } Cut off

ωC_{ov} — overlap capacitance.

* C_{sb} and C_{db} - (RB) depletion cap.


$$C_{sb} = \frac{C_{sbo}}{\sqrt{1 + \frac{V_{sb}}{V_0}}}$$
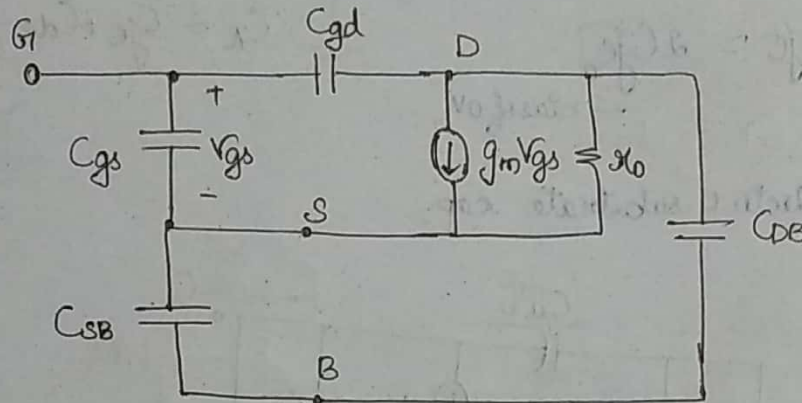
$$C_{db} = \frac{C_{dbo}}{\sqrt{1 + \frac{V_{db}}{V_0}}}$$



f_T : unity current gain frequency = $\frac{g_m}{2\pi(C_{gs} + C_{gd})}$

Miller Theorem:

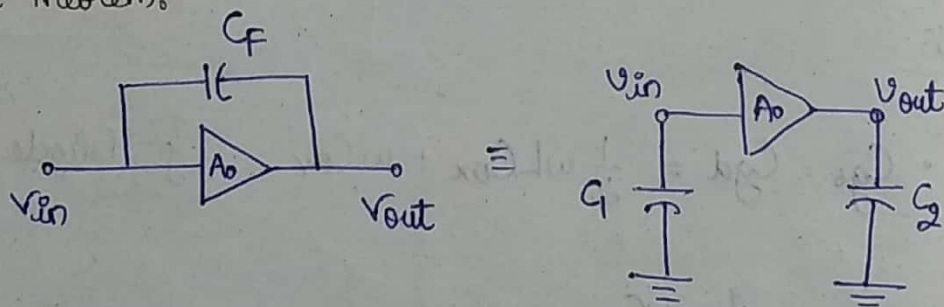

$$C_1 = C_F(1 - A_o)$$

$$C_2 = C_F(1 - \frac{1}{A_o})$$