

BipolarPhysics

Thursday, January 14, 2021 9:02 AM




BipolarPhysics

PHYSICS OF BIPOLAR TRANSISTORS

* A bipolar transistor consists of three doped regions forming a sandwich:-

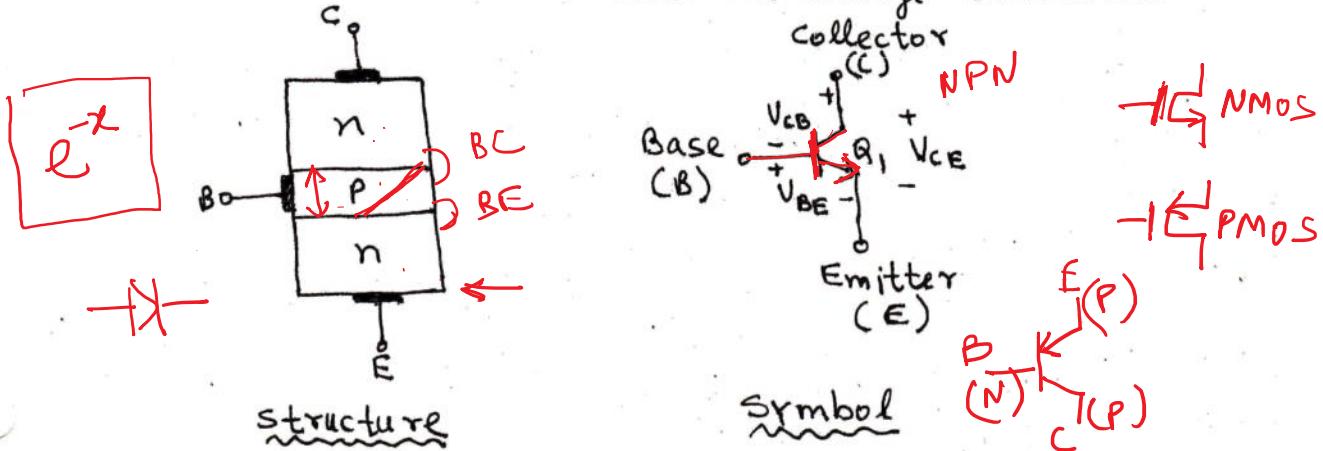- Source \leftarrow ① Emitter. \rightarrow emits charge carriers
 Gate \leftarrow ② Base \rightarrow controls the number of charge carriers making the journey.
 Drain \leftarrow ③ Collector \rightarrow collects the charge carriers.



* Two pn-junctions

\rightarrow between base-emitter

\rightarrow between base-collector.


* The device is not symmetric with respect to emitter and collector.

* The dimensions and doping levels of emitter and collector are quite different.

* EMITTER AND COLLECTOR CANNOT BE INTERCHANGED.

* Proper operation of the device require that base be a thin region, e.g. about 100 Å in modern integrated circuits.

(2)

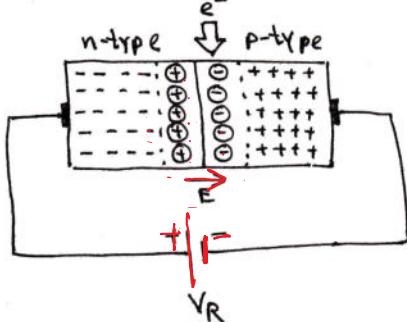Injection of electrons into depletion region:-


Lets inject an electron into the depletion region in a reverse biased pn-junction.

It serves as minority carrier in p-type and is rapidly swept away into n-side by the electric field.

- * Ability of the reverse-biased pn-junction to efficiently "collect" externally-injected electrons / holes proves essential to the operation of bipolar transistors.

OPERATION OF BIPOLAR TRANSISTOR IN ACTIVE MODE:-

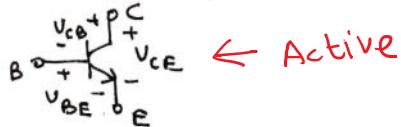- * In this mode the transistor acts a current source between collector and emitter.
- * The above current is controlled by the voltage between base and emitter.
- * For a bipolar transistor the terminal voltages V_{BE} , V_{BC} , and V_{CE} , which can assume positive and negative values, there are 2^3 possible cases.
- * One ~~kind~~ of these combinations is useful.




BJT MOS
Active → Saturation
Saturation → Linear.
Cut-off → Cut-off.

Page 3

Thursday, January 14, 2021 9:03 AM

(3)

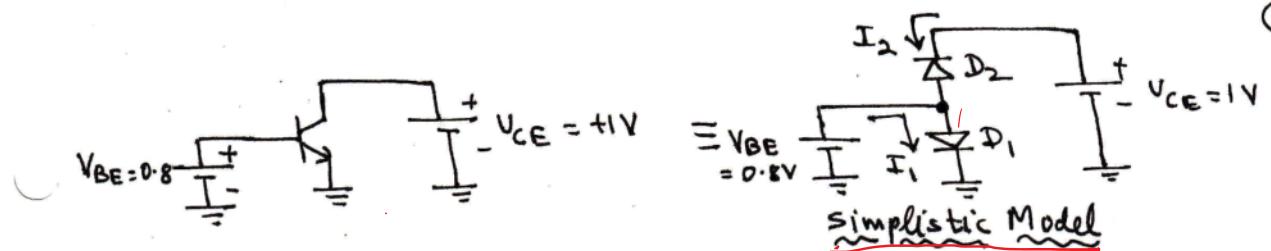


Circuit Condition :- $V_{BE} > 0$

$V_{CE} > 0$

and $V_{BC} < 0$

* The simplistic model assumes that D_2 should not carry any current and hence there cannot be any voltage to current conversion.



MOTION OF CARRIERS IN SLOW MOTION :-

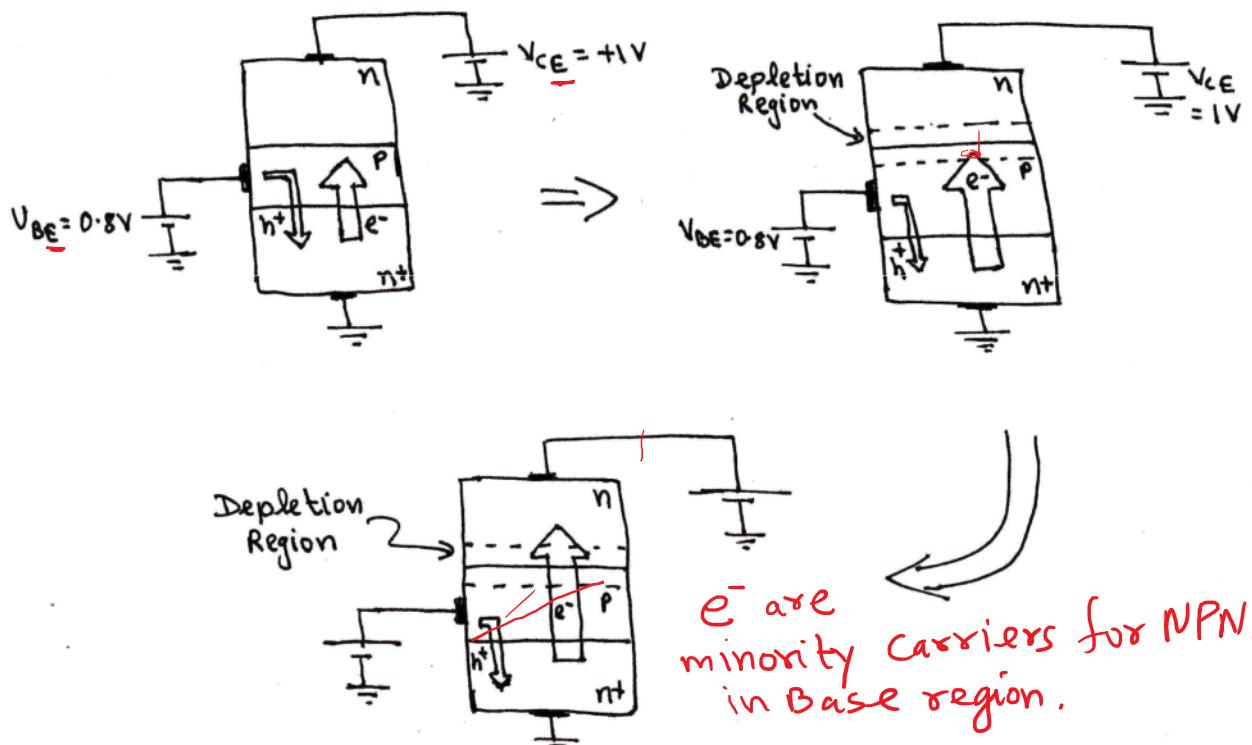

* Emitter is heavily doped.

* Base is thin.

(4)

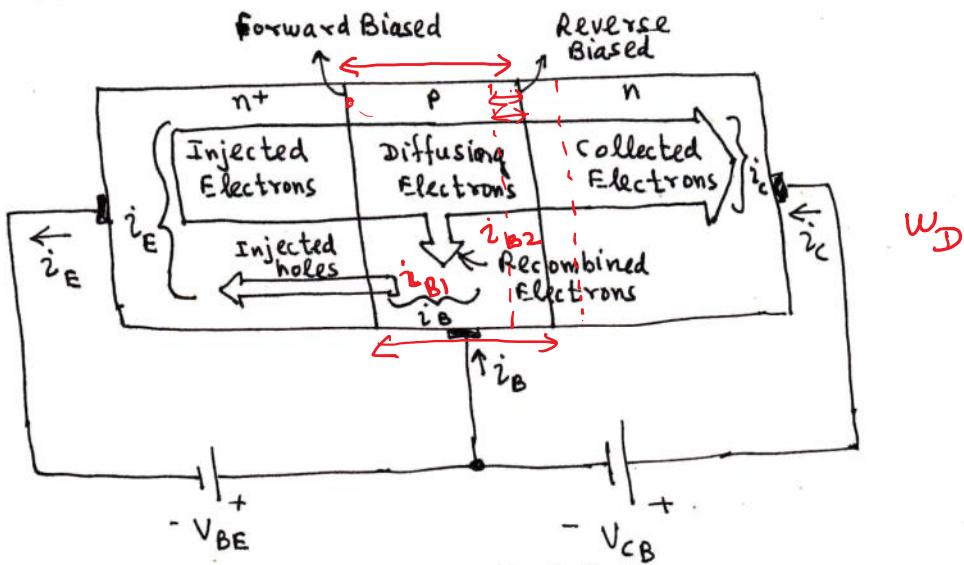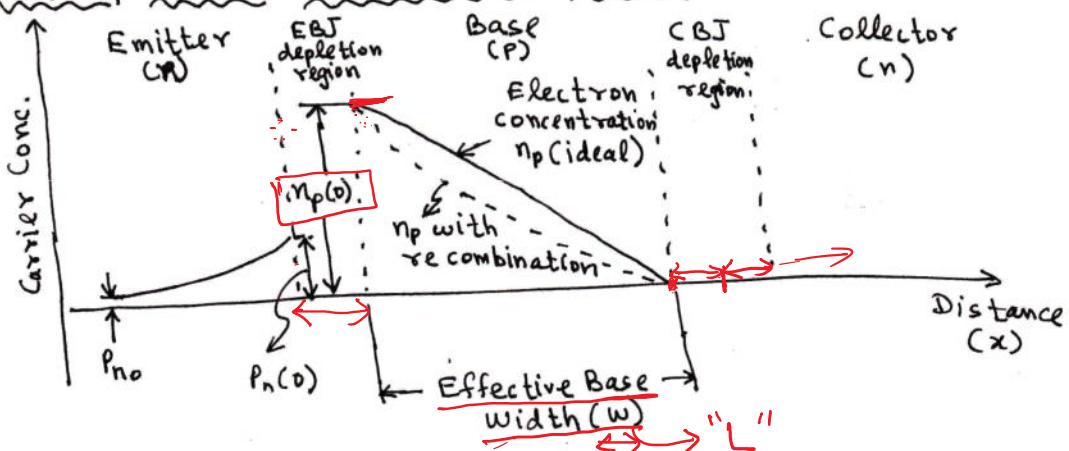Illustration of Current flow:-Minority Carrier Concentration Profile:-

* Since base is very thin
 \Rightarrow carrier concentration will be almost a straight line.

(5)

- * Why is the concentration "0" at CBJ, depletion region?
→ Since any electron reaching there is swept away by the electric field in depletion region the concentration falls to "0".

- * What about recombination of electrons & holes in the base region?
→ Due to recombination the profile deviates from straight line ~~and becomes~~ slightly. We can ignore this while deriving the current.

- * In a forward biased p-n junction the concentration,
- $$n_p(0) = n_{p0} e^{V_{BE}/V_T}$$

where, n_{p0} = thermal equilibrium value of minority-carrier concentration.

V_T = thermal voltage $\approx 25\text{mV}$. or 26mV

V_{BE} = forward biased base emitter voltage.

- * The diffusion current in base region is,

$$I_n = A_E q D_n \frac{d n_p(x)}{dx}$$

$$\Rightarrow I_n = A_E q D_n \left(-\frac{n_p(0)}{w} \right)$$

where, A_E = cross-sectional area of BE junction.


$$q = 1.6 \times 10^{-19} \text{ C}$$


D_n = electron diffusivity in base.

w = effective base width.


- * The electrons diffusing through base get collected by the collector thus giving collector current as,
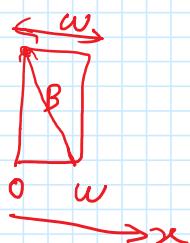
$$i_c = I_n. \leftarrow \text{collector current}$$



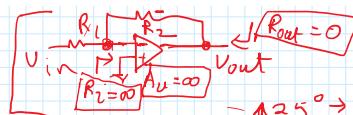

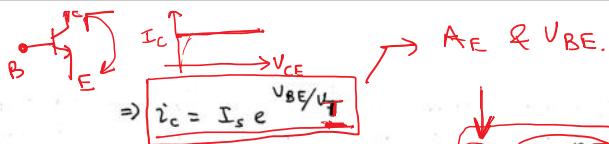$\rightarrow 25^\circ \rightarrow 60\text{dB}$
 $\rightarrow 25^\circ \rightarrow 50\text{dB}$



where, $I_S = \text{saturation current} = A_E q D_n n_i^2 / N_A W$, where $n_i = \text{intrinsic carrier concentration}$ and $N_A = \text{doping concentration in base}$.

$$\text{Thus, } I_S = \frac{A_E q D_n n_i^2}{N_A W}.$$

* I_S is i_c dependent on V_{CE} ?? \Rightarrow not dependent on CE-Voltage
NO.

\rightarrow So what do we have?

\rightarrow A current source between collector & emitter.

* What about the base current?

It has two components:-

① Due to holes injected from base region to emitter. This is given by,

$$i_{B1} = \frac{A_E q D_p n_i^2}{N_D L_p} e^{V_{BE}/U_T}$$

where, $L_p = \text{diffusion length}$ (related to minority carrier lifetime).

$D_p = \text{hole diffusivity}$.

$N_D = \text{doping concentration in emitter}$.

② Due to holes that have to be supplied by external circuit in order to replace holes lost from the base through recombination.

$$i_{B2} = \frac{q n}{\tau_b}$$

where, $\tau_b = \text{average time for minority electron to recombine with majority hole in the base}$.

⑥ $I_D = \frac{L}{2} \mu n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$


$\Rightarrow W, L, V_{GS}, V_{TH}$



BC junction

\rightarrow NPN electrons get injected

\rightarrow PNP holes get injected

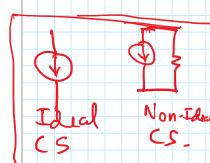

(7)

Q_n = minority carrier charge stored in the base.

$$\Rightarrow Q_n = A_E q \times \frac{1}{2} n_p(0) W \dots \text{[Area of triangle].}$$

$$\Rightarrow Q_n = \frac{A_E q W n_i^2}{2 N_A} e^{V_{BE}/V_T} \dots \because n_p(0) = n_{p0} e^{V_{BE}/V_T}$$

or, $n_p(0) = \frac{n_i^2}{N_A} e^{V_{BE}/V_T}$

Thus, $i_{B2} = \frac{1}{2} \frac{A_E q W n_i^2}{\gamma_b N_A} e^{V_{BE}/V_T}$

Hence, total base current is,

$$i_B = i_{B1} + i_{B2}$$

$$\Rightarrow i_B = I_S \left[\frac{D_p}{D_N} \frac{N_A}{N_D} \frac{W}{L_p} + \frac{1}{2} \frac{W^2}{D_N \gamma_b} \right] e^{V_{BE}/V_T}$$

We know,

$$i_c = I_S e^{V_{BE}/V_T}$$

50 to 200

Thus, $i_B = \frac{i_c}{\beta}$

$$\text{where, } \beta = \frac{1}{\left(\frac{D_p}{D_N} \frac{N_A}{N_D} \frac{W}{L_p} + \frac{1}{2} \frac{W^2}{D_N \gamma_b} \right)}$$

* β is typically around 50 to 200.


* β is called common-emitter current gain.

→ What is β in a MOS??


* For high β :-

→ Base should be thin (w)

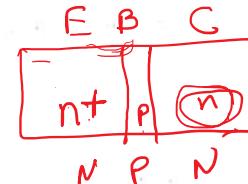→ Emitter should be heavily doped than base i.e. $N_D \gg N_A$.



$N_D, C < N_D, E$

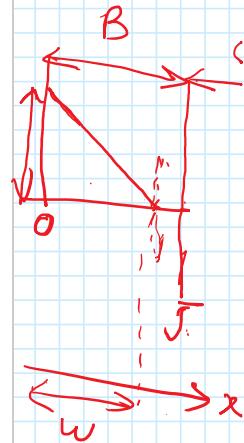


(8)

Emitter Current :- Since current entering a transistor must leave it, we have,

$$i_E = i_C + i_B$$

$$\Rightarrow i_E = (\beta + 1) i_B$$
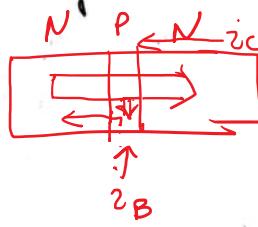
$$\Rightarrow i_E = \frac{\beta + 1}{\beta} i_C$$



Sometimes i_C is expressed in terms of i_E leading to the following,

$$i_C = \frac{\beta}{\beta + 1} i_E$$

$\beta \rightarrow C E$ current gain.


$$\text{or, } i_C = \alpha i_E \dots \text{where, } \alpha = \frac{\beta}{\beta + 1} \approx 1 \text{ if } \beta \text{ is large.}$$

* α = Common Base Current Gain.



LARGE SIGNAL EQUIVALENT CIRCUIT MODEL

exact expression of I-V. unfin transistor burns out.

(i) Voltage-Controlled-Current Source :-

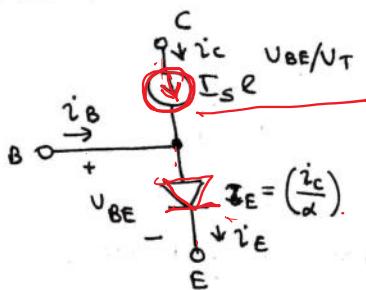

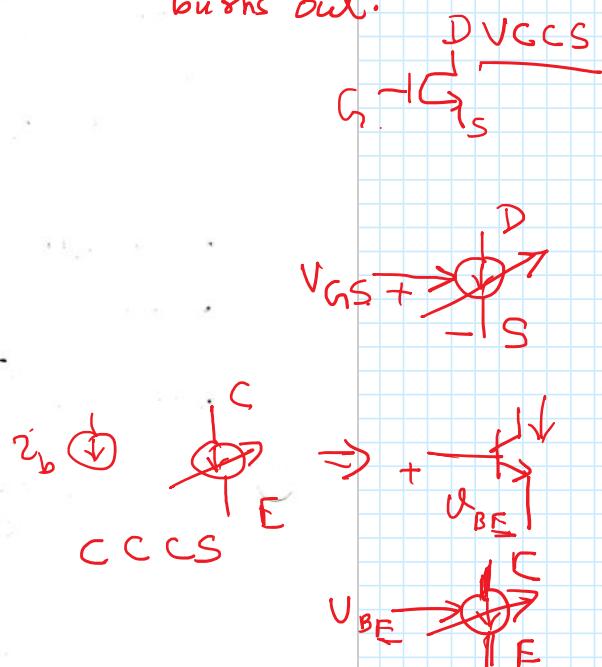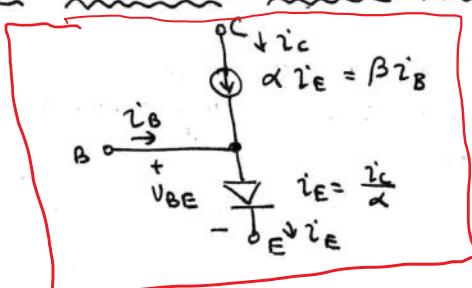
(ii) Current-Controlled Current Source :-



BJT MODES OF OPERATION :-

MODE	E BJ
① Cutoff	Reverse
② Active	Forward
③ Reverse Active	Reverse
④ Saturation	Forward

C BJ
Reverse
Reverse
Forward
Forward

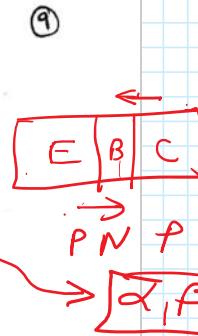

$$\left. \begin{array}{l} \alpha_F, \beta_F \\ \alpha_R, \beta_R \end{array} \right\}$$


* The " α " and " β " derived earlier is for active mode also sometimes called "forward active" mode to distinguish it from "reverse active" mode.

* " α_F " & " β_F " are for "forward active" mode.

* " α_R " & " β_R " are for "reverse active" mode.

* If subscript is not given and α & β are given to you $\Rightarrow \alpha = \alpha_F$ & $\beta = \beta_F$
 NOTE:- Since BJT is rarely used in reverse active mode, whenever we use " α " & " β " we mean " α_F " and " β_F ".

STRUCTURE OF ACTUAL TRANSISTOR :-

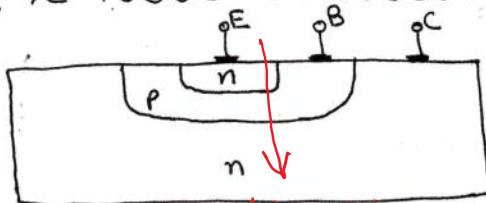

Top View

* C BJ has a much larger area than E BJ.

* If the roles of collector and emitter are reversed then we say the transistor is in "reverse active" mode.


* So in reverse active mode we should have " α_R " and " β_R ".

(10)

- * Typically " α_R " is in the range 0.01 to 0.5 and " β_R " is in the range 0.01 to 1.
- * " α_R " and " β_R " are few orders of magnitude lower than " α_F " and " β_F ".

1 order lower $\Rightarrow \frac{1}{10}$ 2 order lower $\Rightarrow \frac{1}{100}$ 1 order higher $\Rightarrow 10$ 2 orders higher $\Rightarrow 100$

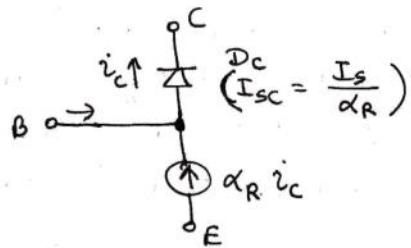
LARGE SIGNAL MODEL FOR NPN TRANSISTOR IN REVERSE ACTIVE MODE :-



* Which one is E & C?





* In case of MOS if 3 terminals only given the S & D are defined and therefore not interchangeable.

(13)

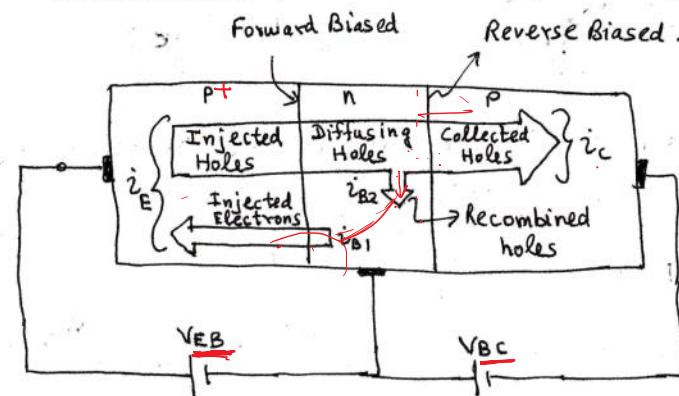NOTE :-SATURATION IN BJT \equiv TRIODE IN MOSACTIVE IN BJT \equiv SATURATION IN MOSPNP TRANSISTOR :-

NMOS $\rightarrow V_{GS}, V_{DS}, V_{GD}, V_T$ is positive
PMOS $\rightarrow V_{SG}, V_{SD}, V_{DG}, V_T$ is negative.

NPN $\rightarrow V_{BE}, V_{CE}, V_{CB}$
PNP $\rightarrow \underline{V_{EB}}, \underline{V_{EC}}, \underline{V_{BC}}$.

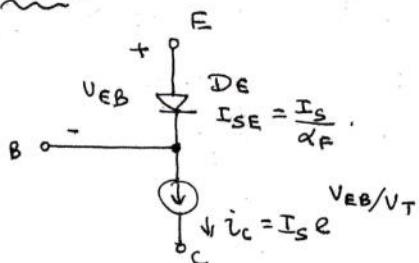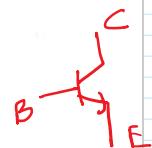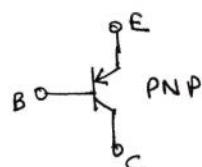
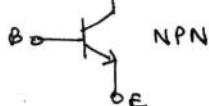
Large Signal Model for PNP transistor in Forward Active Mode :-TRANSISTOR SYMBOL :-

Page 12

Thursday, January 14, 2021 9:03 AM

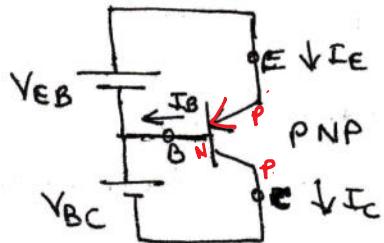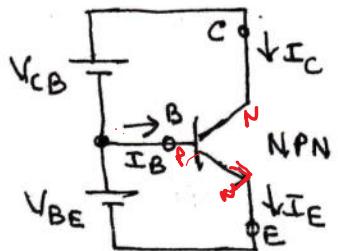(14)

Voltage Polarities And Current Flow in Transistors biased in active mode:-



SUMMARY OF BJT Current Voltage Relationship IN ACTIVE MODE :-

$$\textcircled{1} \quad I_C = I_S e^{\frac{V_{BE}}{V_T}}$$

$$\textcircled{2} \quad I_B = \frac{I_C}{\beta} = \left(\frac{I_S}{\beta} \right) e^{\frac{V_{BE}}{V_T}}$$

$$\textcircled{3} \quad I_E = \frac{I_C}{\alpha} = \left(\frac{I_S}{\alpha} \right) e^{\frac{V_{BE}}{V_T}} = I_{SE} e^{\frac{V_{BE}}{V_T}}$$

For PNP, replace V_{BE} with V_{EB}

$$I_E = I_C + I_B$$

$$\textcircled{4} \quad I_C = \alpha I_E, \quad I_B = (1-\alpha) I_E = \frac{I_E}{\beta+1}$$


$$\textcircled{5} \quad I_C = \beta I_B, \quad I_E = (\beta+1) I_B$$

$$\textcircled{6} \quad \beta = \frac{\alpha}{1-\alpha}, \quad \alpha = \frac{\beta}{\beta+1}$$

$$I_S = I_D + I_A$$

$$\Rightarrow I_S = I_D$$

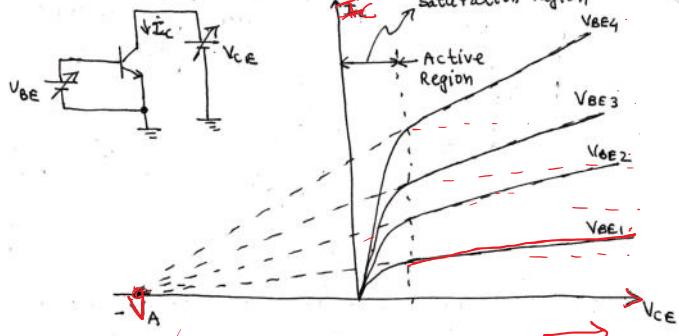DEPENDENCE OF I_c ON COLLECTOR VOLTAGE - EARLY EFFECT:-



For a particular V_{BE} we have,

$$I_c = A_E q D_n \frac{n_{p0}}{W} e^{\frac{V_{BE}/V_T}{W}}$$

$$\text{or, } I_c = A_E q D_n \frac{n_i^2}{N_A W} e^{\frac{V_{BE}/V_T}{W}}$$


I_s

- * We see, $I_s \propto \frac{1}{W} \Rightarrow$ if W reduces, I_s increases.
- * What defines W ? i.e. effective base width?
- * Increasing V_{CE} for particular V_{BE} , is going to increase CBT depletion width $\Rightarrow W$ reduces.
- * If W reduces I_s increases $\Rightarrow I_c$ increases.
- * Discovered by J.M. Early \Rightarrow found extrapolated characteristics all meet at one point called EARLY VOLTAGE.


(14)

Base width gets modulated


$\Rightarrow I_c$ increases

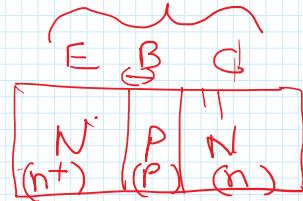

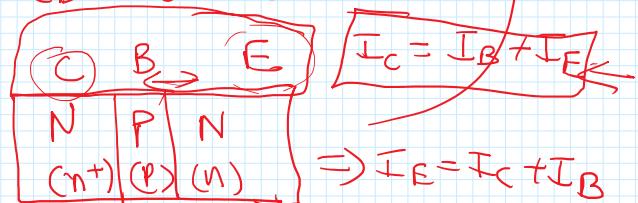EB \rightarrow forward biased
CB \rightarrow reverse biased.



$$I_c =$$

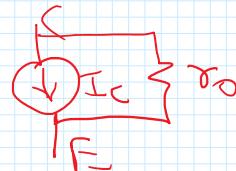

Page 15

Thursday, January 14, 2021 9:03 AM

(17)

- * The linear dependence of I_c on V_{CE} can be accounted by assuming I_s doesn't change but adding additional factor $(1 + \frac{V_{CE}}{V_A})$ to I_c as shown below:-

$$I_c = I_s e^{\frac{V_{BE}}{V_T}} \left(1 + \frac{V_{CE}}{V_A}\right) \Rightarrow I_D = \frac{1}{2} \mu_n C_o x W L (V_{GS} - V_{TH}) (1 + \gamma V_{DS})$$

- * Since, I_c changes with V_{CE} there has to be a resistance associated with it and it is called the output resistance " r_o ".

Unified approach to
ckt analysis for
analyzing both MOS & BJT

$$r_o = \left[\left(\frac{\partial I_c}{\partial V_{CE}} \right)_{V_{BE} = \text{constant}} \right]^{-1}$$

$$\Rightarrow r_o = \frac{V_A}{I_c} \quad \Rightarrow r_o = \frac{1}{\gamma I_D} \Rightarrow A = \frac{1}{V_A}$$



Typically $V_{CE} \gg V_A$, thus,


without channel length modulation.

where, $I_c = I_s e^{\frac{V_{BE}}{V_T}}$ is the current with "Early Effect" neglected.

$$I_C = 0 \\ I_B \neq 0$$

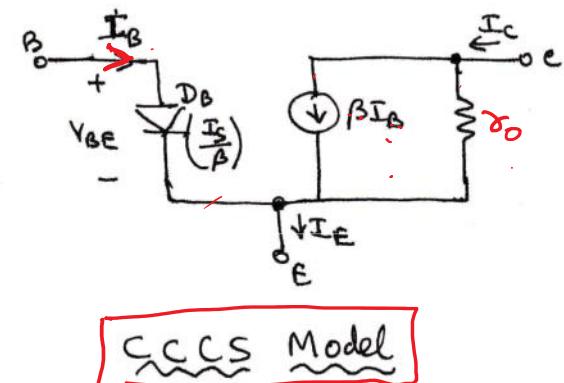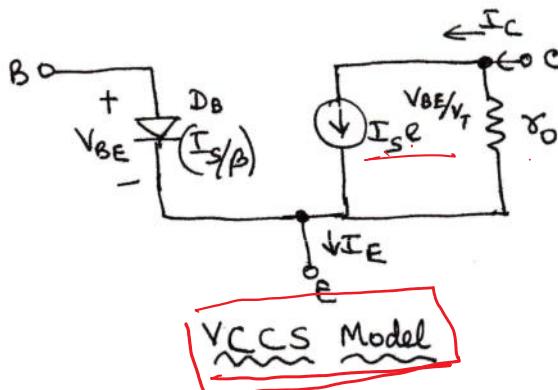- * LARGE SIGNAL MODEL WITH EARLY EFFECT:-



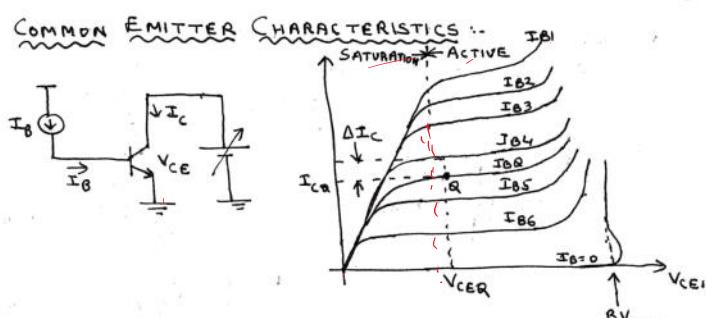

* Common emitter current gain is simply called β (to be more precise β_p). β_C

* At the operating point,

$$\beta_{DC} = \frac{I_{C1}}{I_{B1}}$$

This is called large signal or dc β .

* Incremental or ac β is given by,

$$\beta_{AC} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE} = \text{constant}}$$

* β_{AC} and β_{DC} differ in magnitude by approx. 10 to 20%.


* For this course, β_{AC} and β_{DC} will not be differentiated i.e. we won't make a distinction between the two.

$$\beta_{DC}$$

$$\beta_{AC}$$

$$\frac{I_C}{I_B}$$

$$\left. \frac{I_C + \Delta I_C}{I_B + \Delta I_B} \right|_{V_{CE} = \text{constant}} \Rightarrow \beta_{AC} = \frac{\Delta I_C}{\Delta I_B}$$

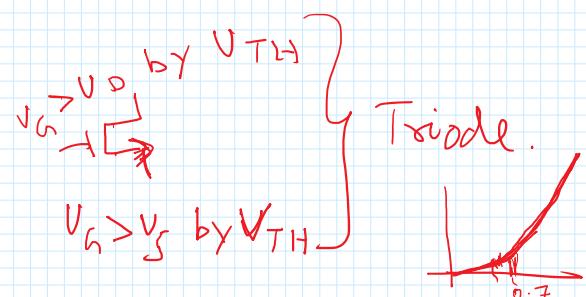

$$V_B = V_E + 0.7 \Rightarrow V_B = 0.7$$

Cut-in voltage of diode.



$$\beta_{AC} = \beta_{DC}$$

for this

course.

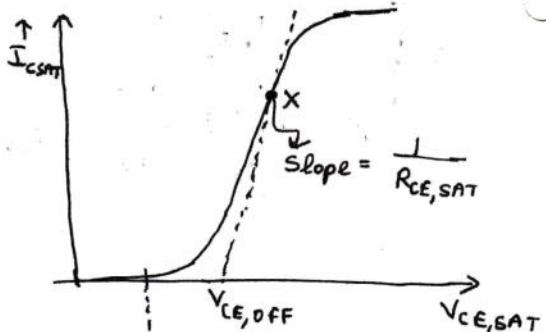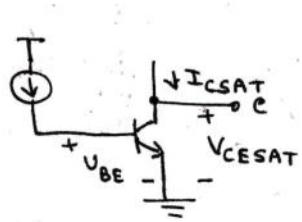
(19)

- * Just like a MOSFET in triode region a saturated BJT acts like a resistor.



$$R_{CE,SAT} = \left. \frac{\partial V_{CE}}{\partial I_C} \right|_{I_B = \text{some value}, I_C = I_{CSAT}}$$

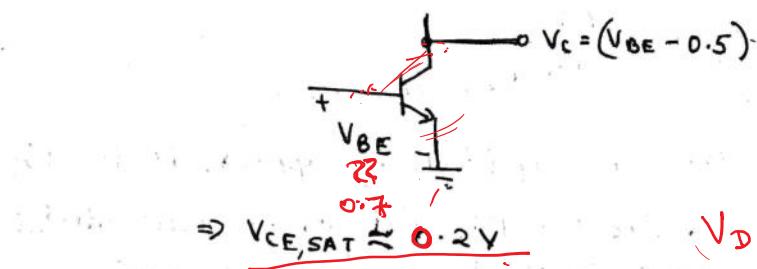- * Note that Base-Collector junction get forward biased and carries substantial current when base is greater than collector by 0.5 Volts atleast.



$$V_{DSAT} = (V_{GS} - V_{TH}) \quad \text{for long channel}$$

SMALL SIGNAL OPERATION AND MODELS :-

(20)

Convention :- $\underline{V}_{BE} = V_{BE} + \underline{v}_{be}$

$$\rightarrow \underline{V}_{CE} = V_{CE} + \underline{v}_{ce}$$


$$\rightarrow \underline{i}_C = I_C + \underline{i}_c$$

$$\rightarrow \underline{i}_B = I_B + \underline{i}_b = 0 \text{ in case of MOS.}$$

$$\rightarrow \underline{i}_E = I_E + \underline{i}_e$$

Conceptual circuit to arrive at small signal model :-

At DC (i.e. no ac signal applied).

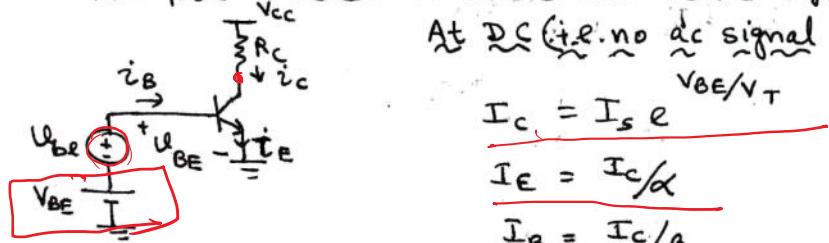

$$I_C = I_s e^{\frac{V_{BE}}{V_T}}$$

$$I_E = I_C / \alpha$$

$$I_B = I_C / \beta$$

$$V_C = V_{CE} = V_{CC} - I_C R_C$$

With ac signal :-

$$\underline{V}_{BE} = V_{BE} + \underline{v}_{be}$$

$$\Rightarrow i_C = I_C + \underline{i}_c$$

$$\Rightarrow i_C = I_s e^{\frac{(V_{BE} + \underline{v}_{be})}{V_T}}$$

$$\Rightarrow i_C = \frac{I_s e^{\frac{V_{BE}}{V_T}}}{I_s e^{\frac{\underline{v}_{be}}{V_T}}} e^{\frac{\underline{v}_{be}}{V_T}}$$

$$\Rightarrow i_C = I_C e^{\frac{\underline{v}_{be}}{V_T}}$$

$$\Rightarrow i_C = I_C \left(1 + \frac{\underline{v}_{be}}{V_T} \right) \dots \text{[By Taylor series expansion with } \frac{\underline{v}_{be}}{V_T} \ll 1 \text{]}$$

$$\boxed{\underline{v}_{be} \ll V_T}$$

$V_{GS} < 2V_{OV}$

$$i_c = I_c \left(1 + \frac{u_{be}}{V_T} \right) \quad (a)$$

Thus,

$$\underline{i_c} = \underline{I_c} + \left[\frac{I_c}{V_T} u_{be} \right]$$

$$\Rightarrow \text{small signal, } i_c = \left[\frac{I_c}{V_T} u_{be} \right]$$

$$\Rightarrow \boxed{\text{Transconductance, } g_m = \frac{I_c}{V_T}}$$

$$* \text{ Can you prove that, } g_m = \left. \frac{\partial i_c}{\partial u_{be}} \right|_{i_c = I_c}$$

$$\text{Now, } \underline{I_c} = I_s e^{\frac{u_{be}}{V_T}}$$

$$\Rightarrow \frac{\partial \underline{i_c}}{\partial u_{be}} = \frac{I_s}{V_T} e^{\frac{u_{be}}{V_T}}$$

$$\Rightarrow \boxed{\frac{\partial i_c}{\partial u_{be}} = \frac{I_c}{V_T}}$$

$$I_c = I_s e^{\frac{u_{be}}{V_T}}$$

$$\Rightarrow \frac{\partial I_c}{\partial u_{be}} = \frac{I_s}{V_T} e^{\frac{u_{be}}{V_T}}$$

$$= \frac{I_c}{V_T}$$

* Unlike MOSFET where there is no gate current at DC, we have a base current in BJT at DC.

* Now,

$$i_B = I_B + i_b$$


$$\Rightarrow i_B = \frac{I_c}{\beta} + \frac{I_c}{\beta V_T} u_{be}$$

$$\text{Thus, } i_b = \frac{g_m}{\beta} u_{be}$$

$$\Rightarrow \frac{u_{be}}{i_b} = \frac{\beta}{g_m} = r_\pi = \text{small signal input resistance between base and emitter.}$$


Thus, small signal model of BJT is as follows:-

(22)

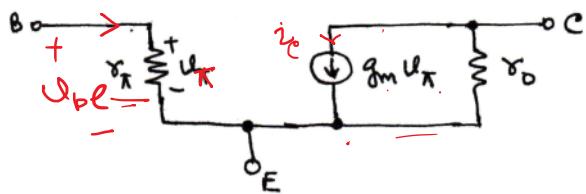

BJT Amp.

Counterpart
in MOS -

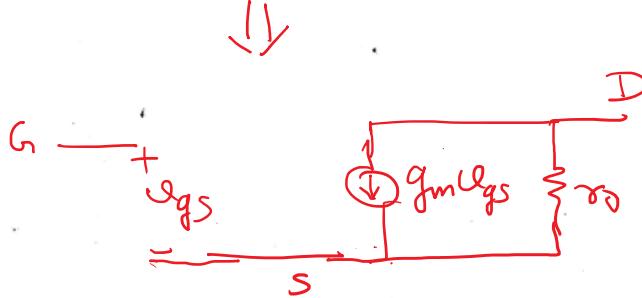


edge of saturation in MOS \rightarrow pinch-off happens @ drain end $\Rightarrow (V_{DS} = V_{GS} - V_{TH})$
 $V_{D,SAT}$

edge of active in BJT $\rightarrow V_{CE} = 0.2 V.$
 $V_{CE,SAT}$


OBTAINING GAIN OF A TWO PORT NETWORK (A_{v2}):-



Trust But Verify

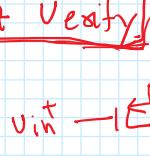

SUCCESSFUL FAILURE

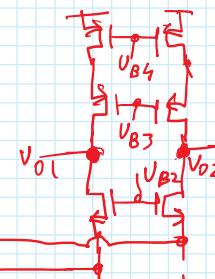

$$\frac{V_{O2} - V_{O1}}{V_{in^+} - V_{in^-}}$$

$$A_{v2} = \text{Voltage Gain} = G_m R_{out}$$

$$G_m = \text{Short Circuit Current Gain} = \text{Effective } G_m$$

$$R_{out} = \text{O/p resistance} = \text{Effective } R_{out}$$

$G_m \Rightarrow$ 1. AC short @ O/P, 2. apply V_{in} @ I/P, and obtain the short circuit current (I_{sc})

$$G_m = \frac{I_{sc}}{V_{in}}$$

(Solve for current flowing through v_x and cell that is v_x)


$$\Rightarrow R_{out} = \frac{v_x}{i_x}$$

$R_{out} \Rightarrow$ i) Apply test voltage (v_x) at O/P

$$R_{out} = \frac{v_x}{i_x}$$

- ii) Remove all independent voltage sources by shorting them out.
- iii) Remove all independent current sources by opening them.
- iv) Leave all dependent voltage & current sources as they are.


AC Short what is it??

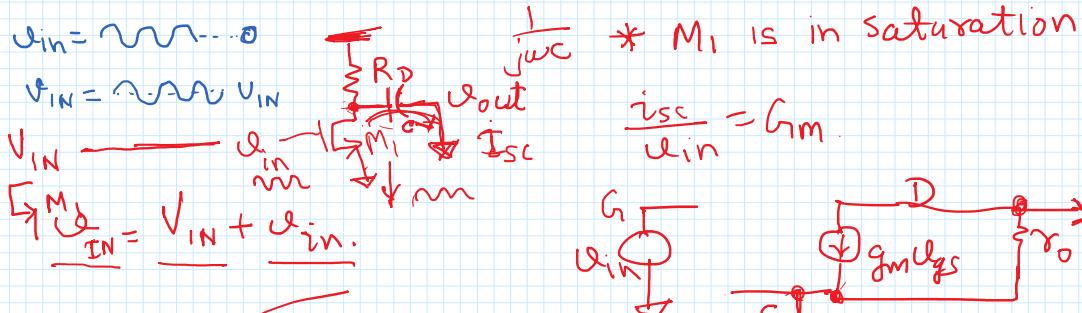

* DC Ground
* AC Ground
* Virtual Ground

* M_1 is in saturation


$$\frac{i_{sc}}{v_{in}} = G_m$$

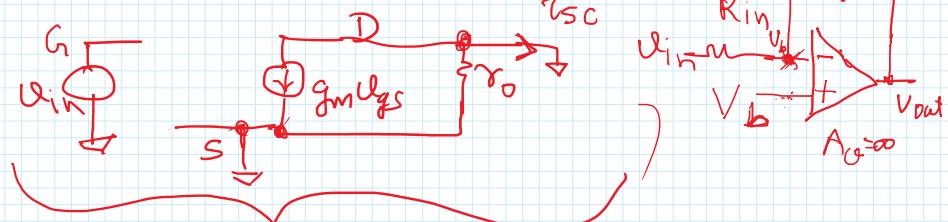

* DC Ground is absolute ground

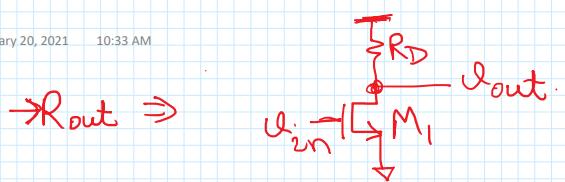* AC Ground is any node that does not have a change in voltage






* Find gain

* Find i/p impedance

* Find o/p impedance

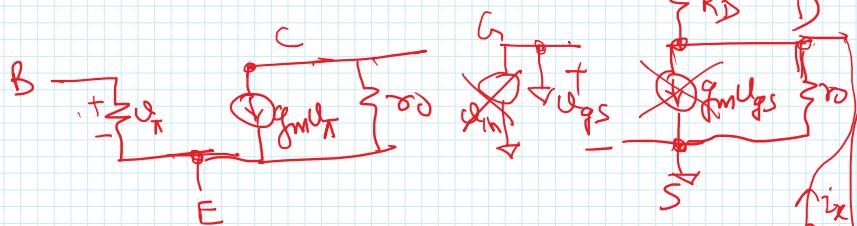The circuit is biased & the operating point is set properly.



$$\frac{U_T}{i_x} = (\tau_0 \parallel R_D)$$



	BJT	MOS
①	Active(Forward)	saturation
②	I_C	I_D
③	$\frac{I_C}{V_{CE}}$	V_{GS} & V_{DS}
④	$\frac{I_C}{V_T}$	(V_{SD}) & (V_{GD})
⑤	$\tau_0 = \frac{V_A}{I_C}$	$g_m = \mu_n C_o x \frac{w}{L} (V_{GS} - \frac{V_T}{2})$
		$\tau_0 = \frac{1}{\lambda I_D}$

* Simple ckt's using small signal model.


* For complex ckt's use above results

& find out A_v, R_{in}, R_{out} w/o small signal model.

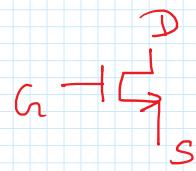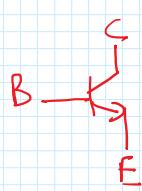
* Resistance looking into various terminals of BJT & MOS:-



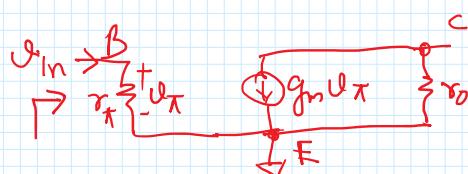- (i) Resistance looking into B/G with E/S grounded :-
 * We do not care where C/D is connected.




$$R_B = r_T$$

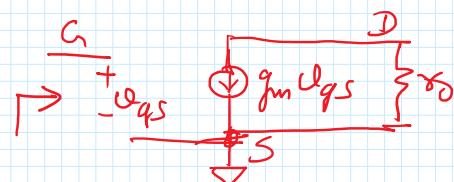

$$R_B = \infty$$

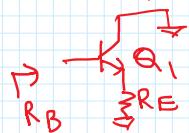- (ii) Resistance looking into B/G with E/S connected to a resistor; ~~v_A = 0~~





* Let C/D be connected to AC ground.



* Let Q_1/M_1 be ideal transistor.
 $v_A = 0$ ~~$\beta = 0$~~

If BJT is not ideal $\Rightarrow V_A \neq 0$ then, $R_B = r_T + (R_E \| r_o) [1 + \beta]$

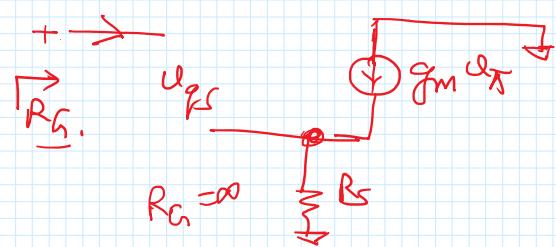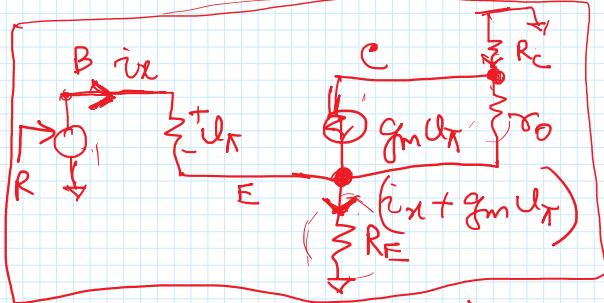

$$U_T = U_X - (i_x + g_m U_T) R_E.$$

$$\Rightarrow U_T (1 + g_m R_E) = U_X - i_x R_E.$$

$$\Rightarrow i_x r_T (1 + g_m R_E) = U_X - i_x R_E$$

$$\Rightarrow i_x \left[r_T + g_m R_E r_T + R_E \right] = U_X.$$

$$\Rightarrow \frac{U_X}{i_x} = r_T + R_E (1 + g_m r_T) \Rightarrow R_B = r_T + R_E (1 + \beta)$$

* r_o of BJT is of 10's of kΩ.

$r_o \gg R_E$.




$$\Rightarrow (r_o || R_E) \approx R_E$$

Typically,
 $R_E < 1 \text{ k}\Omega$
of the order
100-2 to 500Ω.


* Prove that in presence of $R_C \Rightarrow R_B \approx r_T + R_E (1 + \beta)$. β

* Resistance looking into collector/Drain:-

Case 1 :- E/S is grounded.

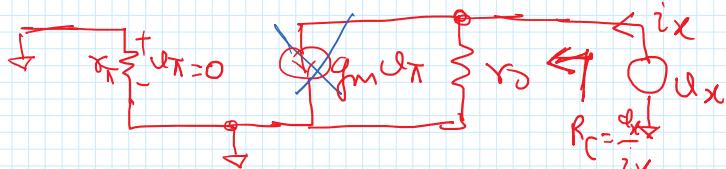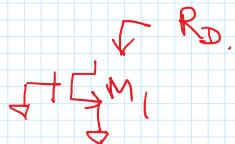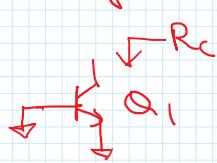

$$R_C = \frac{u_x}{i_x} = r_0$$

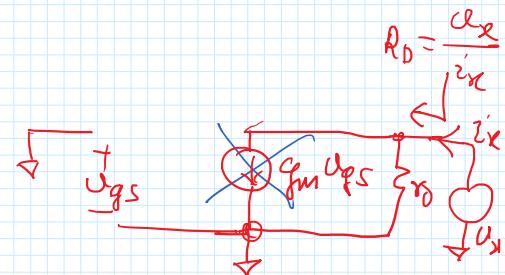


$$R_D = \frac{u_x}{i_x} = r_0$$

If Q_1/M_1 is ideal $\Rightarrow R_C = \infty$ and $R_D = \infty$.

Case 2 :-
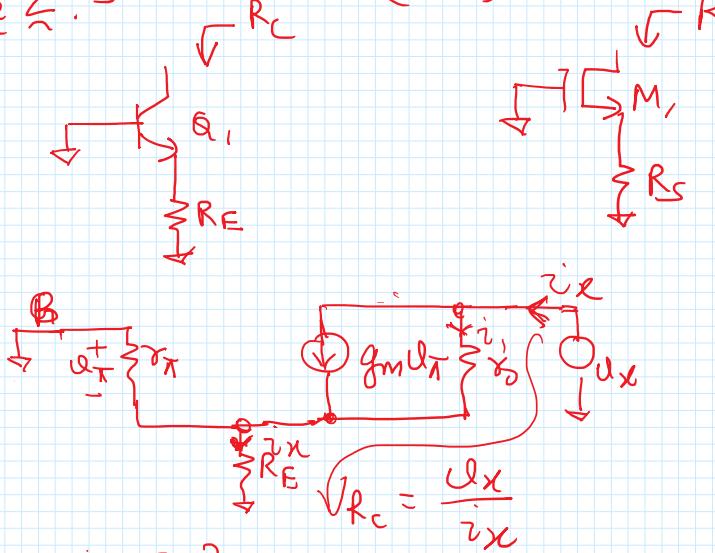
$$i_1 \tau_o + i_x (R_E \parallel r_A) = U_N \Rightarrow \frac{U_N}{i_x} = (R_E \parallel r_A) + (1 + g_m (R_E \parallel r_A)) \tau_o$$




* What is R_C ?

$$\mathcal{L}_x = -i_x (R_E \parallel r_A)$$

$$i_1 = g_m i_x (R_E \parallel r_A) + i_x$$





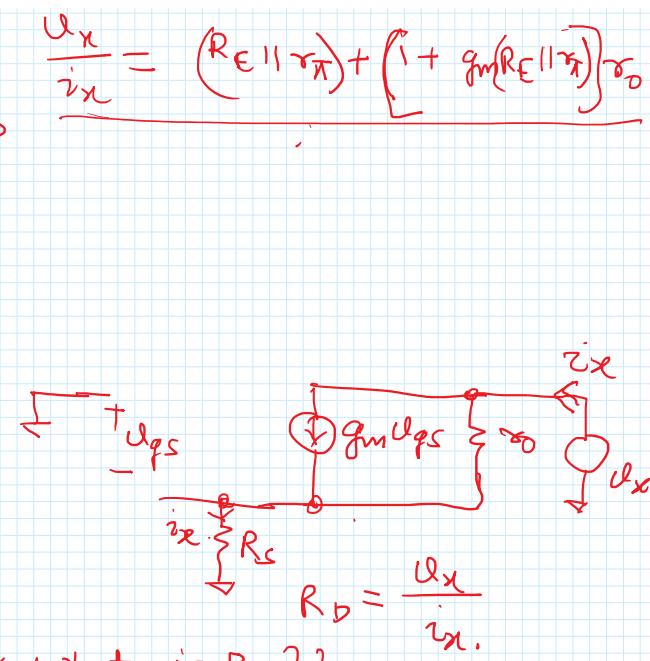
$$\Rightarrow i_1 = [g_m (R_E \parallel r_A) + 1] i_x$$



* What is R_D ??



$$R_D = \tau_o + g_m \tau_o R_S \approx g_m \tau_o R_S$$
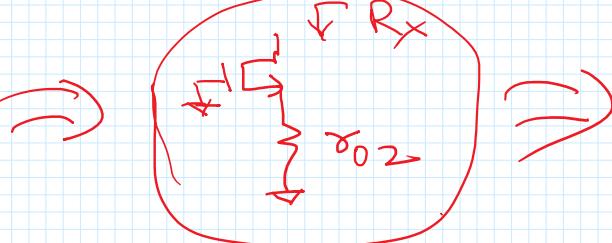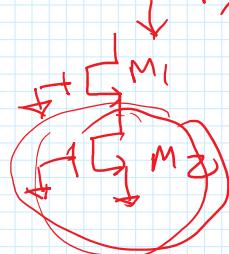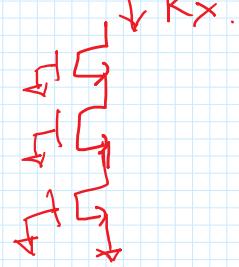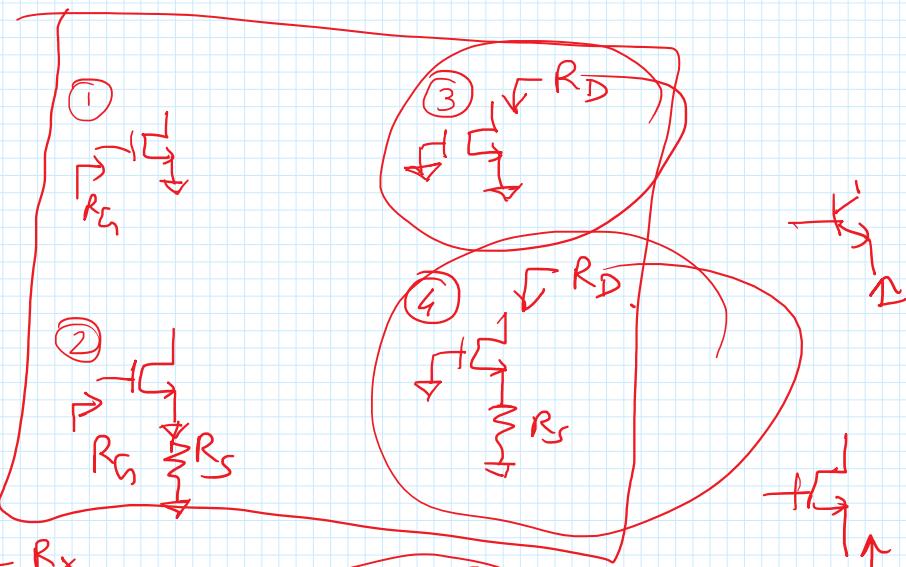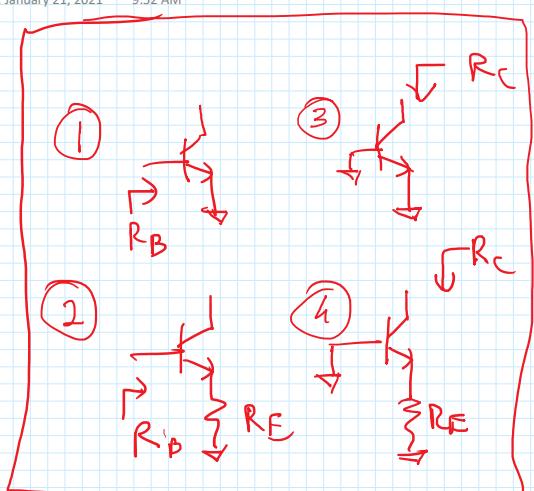
$$\frac{U_x}{i_x} = R_S + (1 + g_m R_S) \tau_o$$




Resistance Looking into E/S :-

(i)

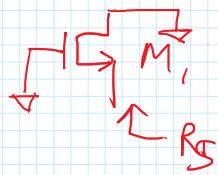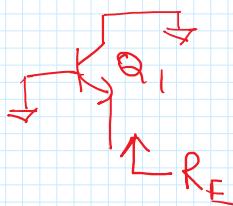
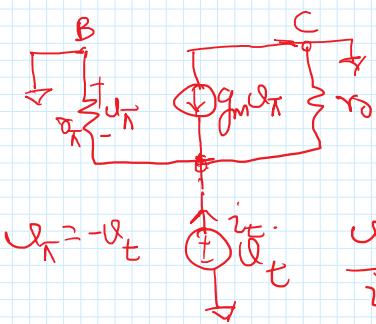
$$R_E = \left(\frac{1}{g_m} \parallel r_\pi \parallel r_o \right) \quad R_S = \left(g_{fm} \parallel r_o \right) \approx \frac{1}{g_m}$$





Typically $r_o = 1k\Omega$ to $1M\Omega$,
 $r_\pi = 10's$ of $k\Omega$.

$$\frac{1}{g_m} = (10 \text{ to } 100) \Omega$$

$$\frac{u_t}{u_i} = \left(\frac{1}{g_m} \parallel r_\pi \parallel r_o \right) \approx \frac{1}{g_m}$$

(ii)

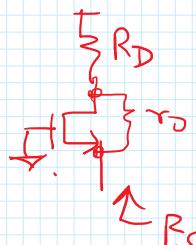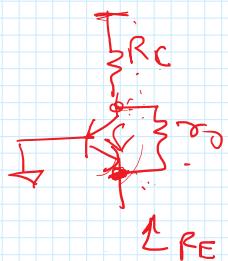


$$\frac{\beta_{AC}}{\beta_{DC}} \approx \beta_{DC}$$

$$\beta =$$

$$g_m = \frac{I_C}{V_T}$$

$$\boxed{\frac{1}{R_s} g_m = \beta}$$

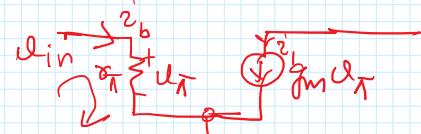 \Rightarrow 

$$u_{in} = u_T$$

$$i_b = g_m u_T$$

$$i_b = \beta i_b' = \beta \frac{u_{in}}{u_T}$$

$$\Rightarrow i_b = g_m u_T = \beta \frac{u_{in}}{u_T}$$

* Solve for R_E & R_S ??

* Make appropriate approx..

$$\sin \theta \approx \theta ? \text{ if } \theta \text{ is small? ?}$$

$$\sin 1^\circ = 1^\circ \Rightarrow$$

$$A_{v_o} = g_m \underbrace{R_{out}}$$

Def'n of ideal transistor $\Rightarrow V_A = \infty$ for BJT, $\lambda = 0$ for MOS.

BJT

MOS

① Looking into Base.

(i)
(ii)

Approx. for ideal transistor.

② Looking into collector

(i)
(ii)

* Ideal tran. approx.

③ Looking into emitter

(i)
(ii)

* Ideal tran. approx.

③ Looking into Gate

Approx. for ideal transistor.

② Looking into Drain.

(i)
(ii)

* Ideal tran. approx.


③ Looking into source.

(i)
(ii)

* Ideal tran. approx.

2-Port NW $\Rightarrow A_{\omega} = G_m R_{out}$

* Solving for effective G_m :

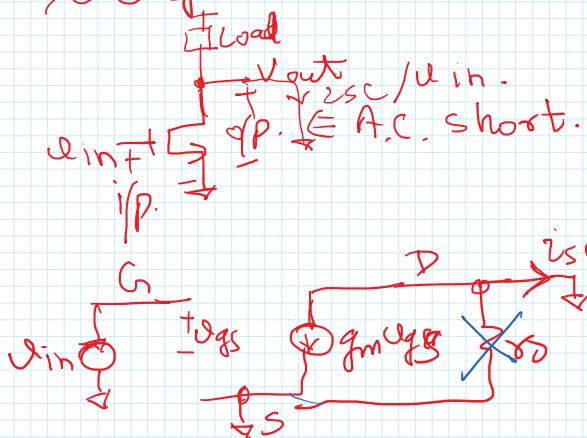

* Find o/p node.

* Put an a.c. short @ o/p.

* ~~Draw~~ Draw small signal model.


* Find i_{sc}/u_{in} .

$$\therefore G_m = \frac{i_{sc}}{u_{in}} = g_m.$$


$$i_{in} \rightarrow i_{sc} \Rightarrow G_m = \frac{i_{sc}}{u_{in}} = g_m.$$

$$i_{in} \rightarrow i_{sc} \quad G_m = \frac{i_{sc}}{u_{in}}$$

$$A_{\omega} = G_m R_{out}.$$

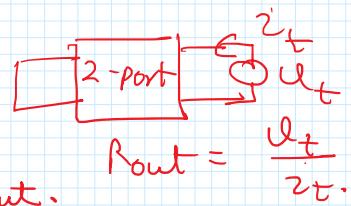


$$R_{out} = \frac{u_{in}}{i_{out}}$$

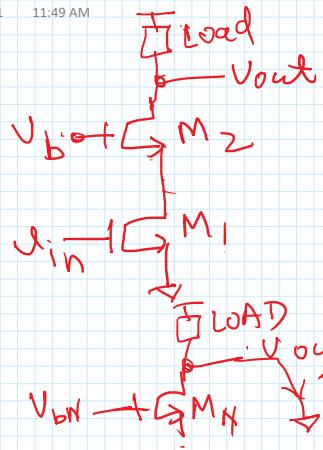


* \$V_b\$ is bias voltage \Rightarrow A.C. ground.

* Let, \$M_1\$ be an ideal transistor.

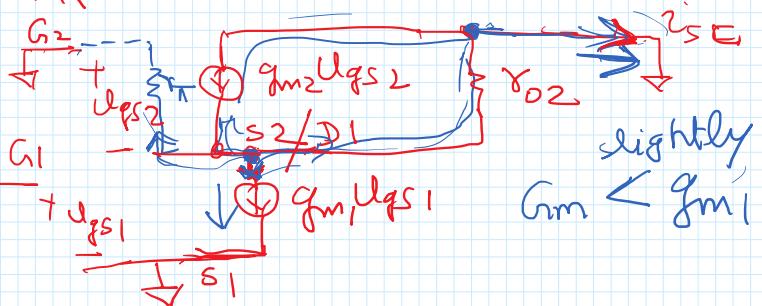


$$i_{sc} = g_{m1} u_{gs1} = g_{m1} u_{in}$$

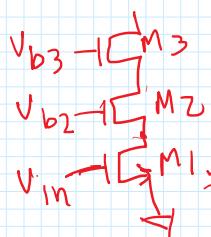
$$\Rightarrow \frac{i_{sc}}{u_{in}} = g_{m1}$$



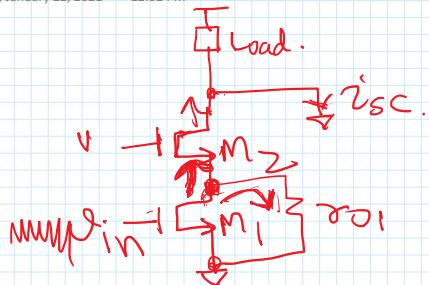* If \$M_1\$ is ideal what is \$g_m = g_{m1}\$



If M_1 is not ideal??

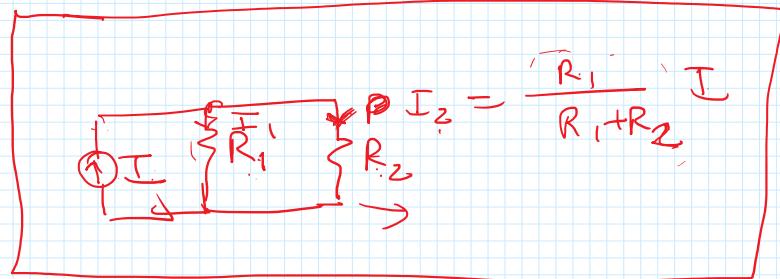

$$I = g_{m1} v_{in}$$


$$G_m \approx g_{m1}$$

$$i_{SC} = \frac{r_o}{r_o + R_2} g_{m1} v_{in} = \frac{r_o}{r_o + \left(\frac{1}{g_{m2}} \| r_{o2} \right)} g_{m1} v_{in}$$


↓
resistance looking into ~~the~~ source of M_2 when
drain of M_2 is grounded.

$$G_m = \frac{i_{SC}}{v_{in}} = \frac{r_{o1}}{r_{o1} + \left(\frac{1}{g_{m2}} \| r_{o2} \right)} g_{m1}$$

MOSFET \Rightarrow BJT case is your job.

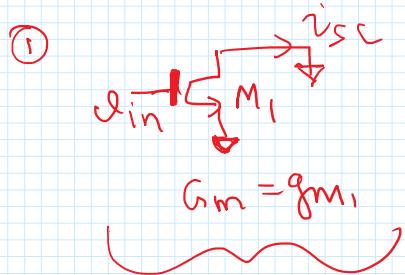


$$G_m = g_{m1}$$

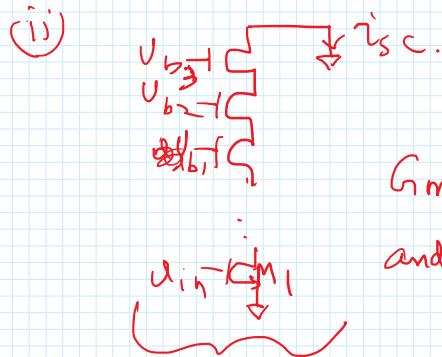


$$G_m \approx g_{m1} \text{ if } \lambda \neq 0.$$
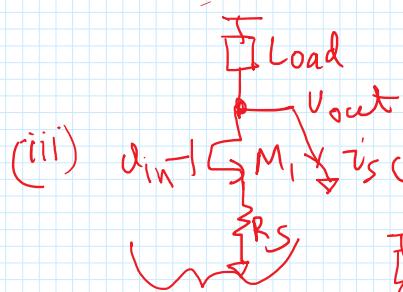
$$\text{and, } G_m = g_{m1} \text{ if } \lambda = 0.$$



$$G_m \approx \frac{g_{m1}}{1 + g_{m1} R_S}$$

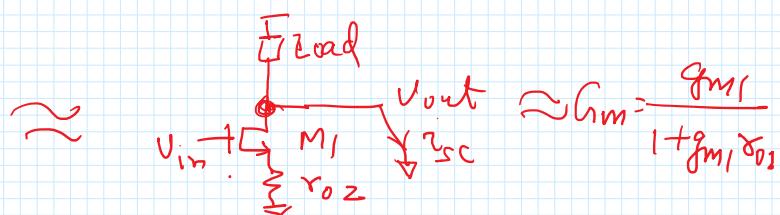R_S can bleed transistor in saturation. $v_{in} \rightarrow M_1 \rightarrow M_2 \rightarrow v_{out}$



$$\approx G_m = \frac{g_{m1}}{1 + g_{m1} \gamma_{D2}}$$

$$|A_{\text{eff}}| = G_m R_{\text{out}}$$


↑ effective

effective o/p resistance

(i) Transistor is ideal $\Rightarrow V_A = \infty$ for BJT
 $\lambda = 0$ for MOSFET

(ii) Transistor is real

Example 1 :-

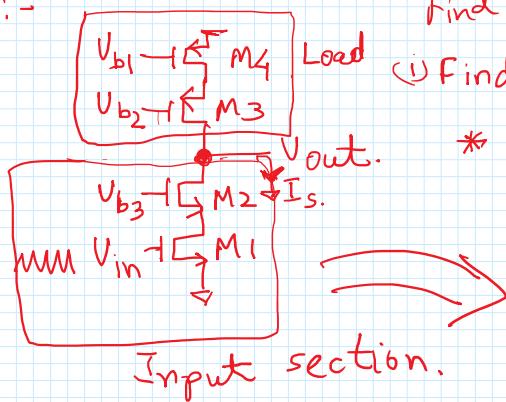


Find the voltage gain, $\lambda \neq 0$.

(i) Find effective G_m :

* We do not care what is in the load.

$$\frac{V_{b3} - V_{in}}{V_{in}} \xrightarrow{M_2} I_{sc} \Rightarrow G_m \approx g_{m1}$$

(ii) How to find R_{out} ??

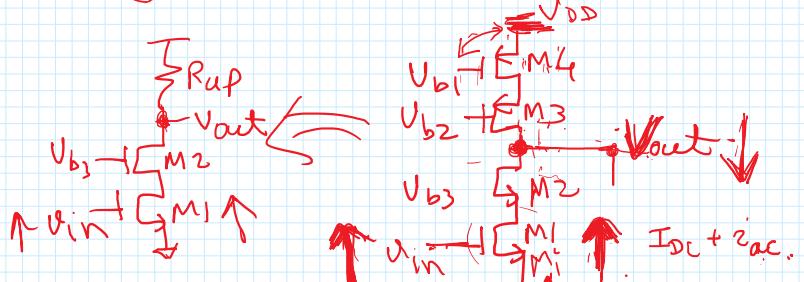


$$v_{out} = V_{DD} - i_{M1} * R_{up}$$

$$\frac{i_x}{i_{up}} = R_{up}$$

$$\Rightarrow R_{out} = R_{up} || R_{DN}$$

$$\frac{i_x}{i_{DN}} = R_{DN}$$

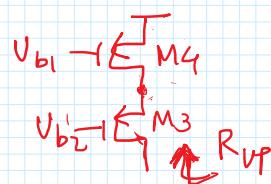
$$A_{v_o} \approx -g_{m1} \cdot \left(g_{m3} r_{o3} r_{o4} \right) / \left(g_{m2} r_{o2} r_{o1} \right)$$



$$R_{out} = \frac{i_x}{i_x}$$



$$\sum r_{o4}$$
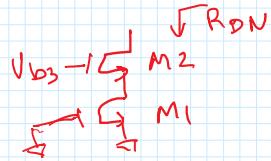
$$\approx R_{up} \approx g_{m3} r_{o3} r_{o4}$$




$$\rightsquigarrow$$

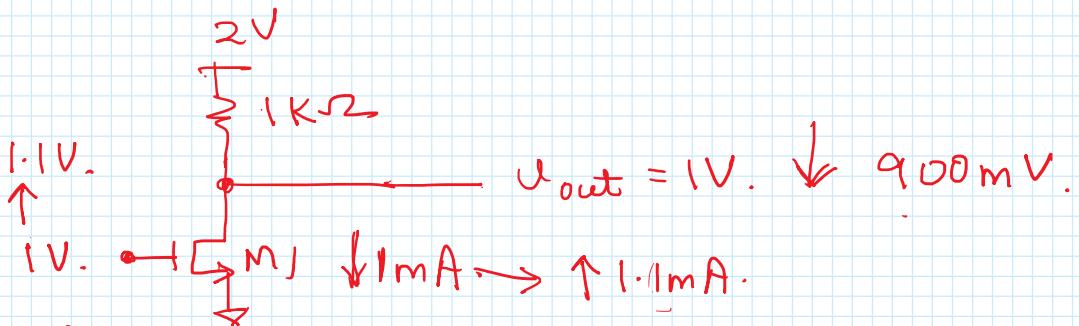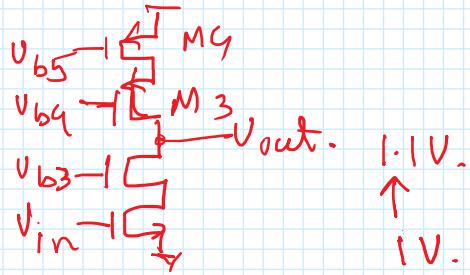
$$R_{out} = \left(g_{m3} r_{o3} r_{o4} \right) / \left(g_{m2} r_{o2} r_{o1} \right)$$


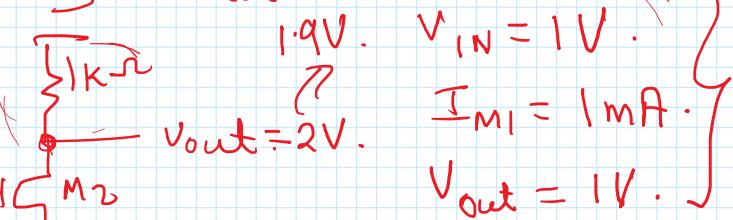
$$3\text{ V} \cdot \Delta V_{out} \approx 100\text{ mV}$$



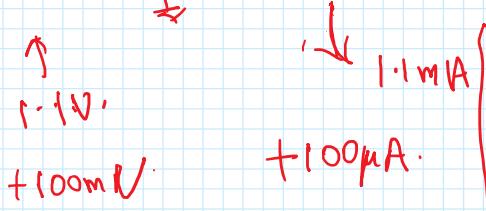
$$V_{IN} \rightarrow M_1 \quad I_1 = 1\text{ mA}$$




$$V_{IN}^{\text{new}} = 1.1\text{ V.}$$

$$I_{M1}^{\text{new}} = 1\text{ mA}$$
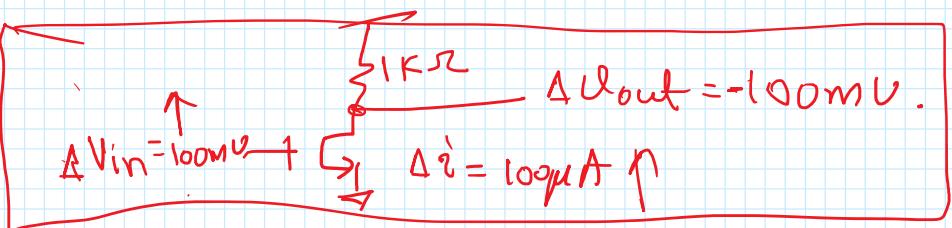
$$V_{out}^{\text{new}} = 900\text{ mV.}$$



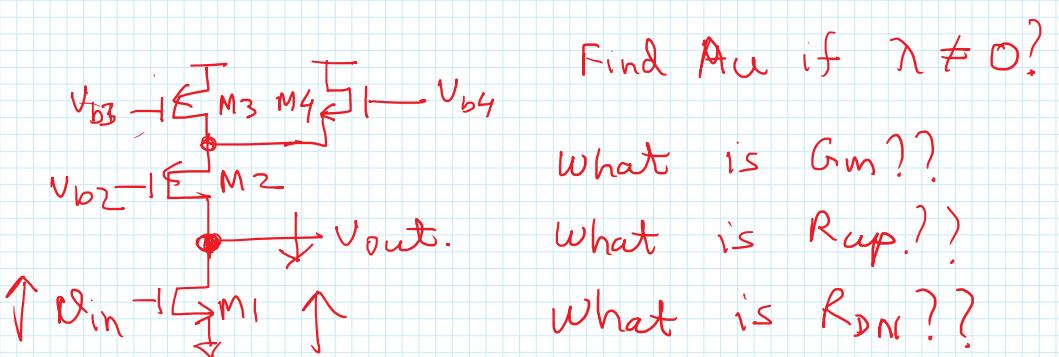


$$G_m = g_{m1}.$$


$$R_{DN} = r_{o1}.$$

$$R_{up} \cong g_{m2} r_{o2} \left(r_{o3} || r_{o4} || \frac{1}{g_{m4}} \right)$$

$$R_{out} = \left\{ r_{o1} || \left[g_{m2} r_{o2} \left(r_{o3} || r_{o4} || \frac{1}{g_{m4}} \right) \right] \right\}$$

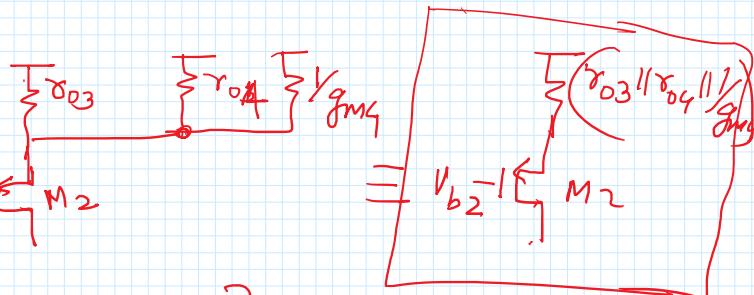

$$R = 0$$

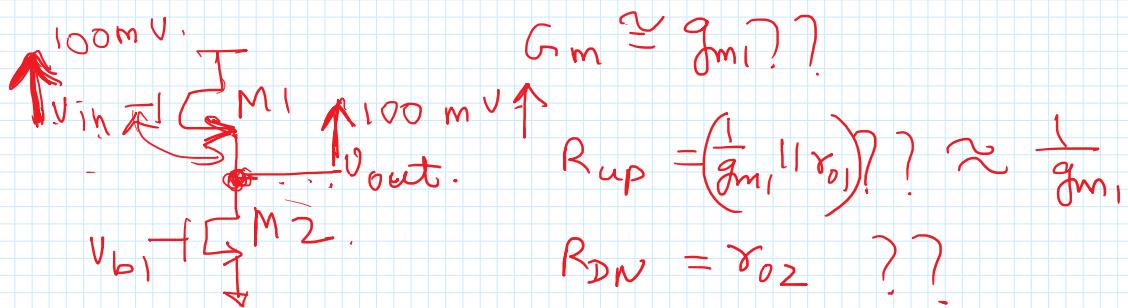

$$A_v = + g_{m1} \cdot \left(\frac{1}{g_{m1}} \parallel r_{o2} \right) \approx 1$$

Source Follower
Emitter Follower.

$$100 \parallel 1000 \\ \approx 990$$