
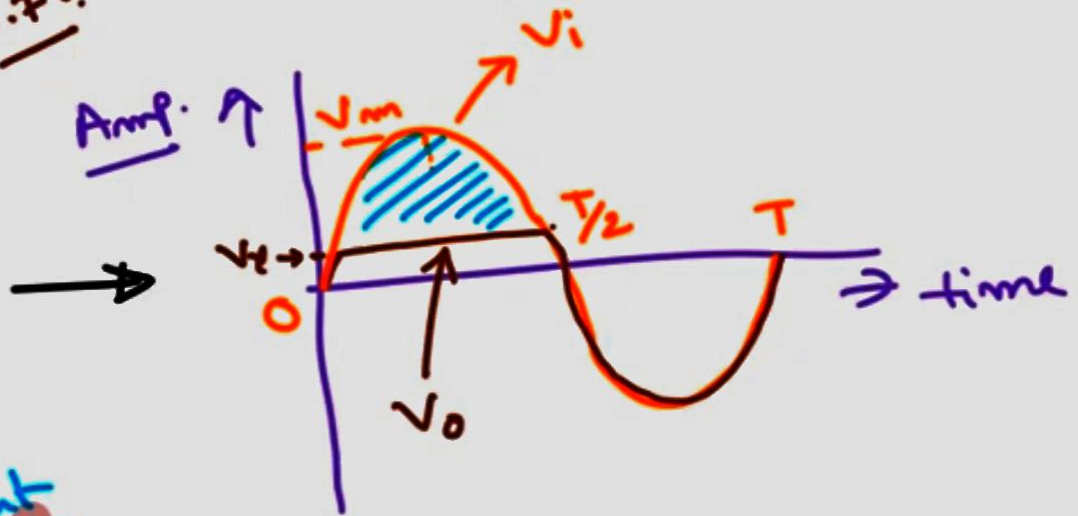






# Clipper Circuits

Clipper circuits are used to eliminate some portion of a signal above or below a specified level.



→ limiter circuits.

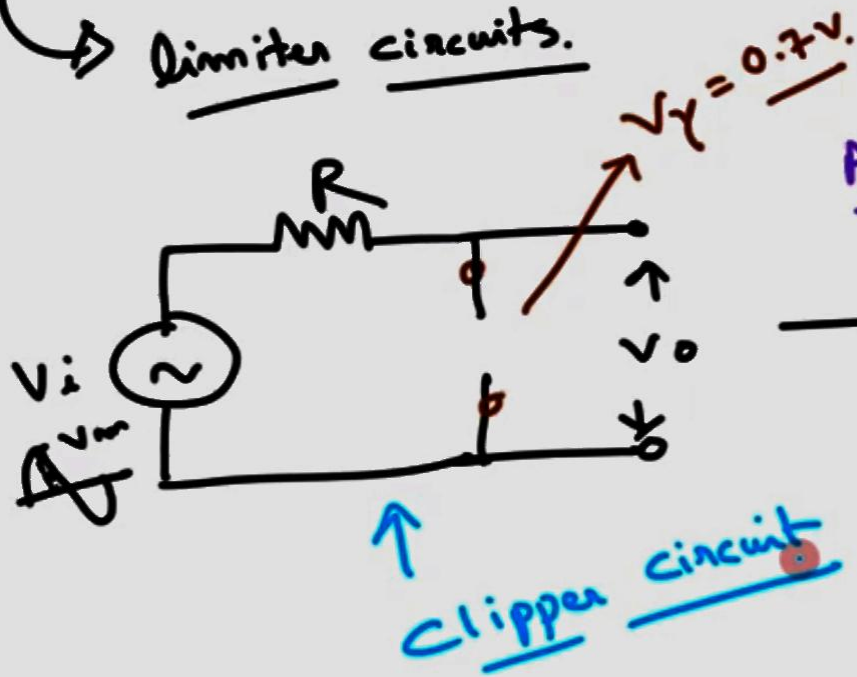

# Clipper Circuits

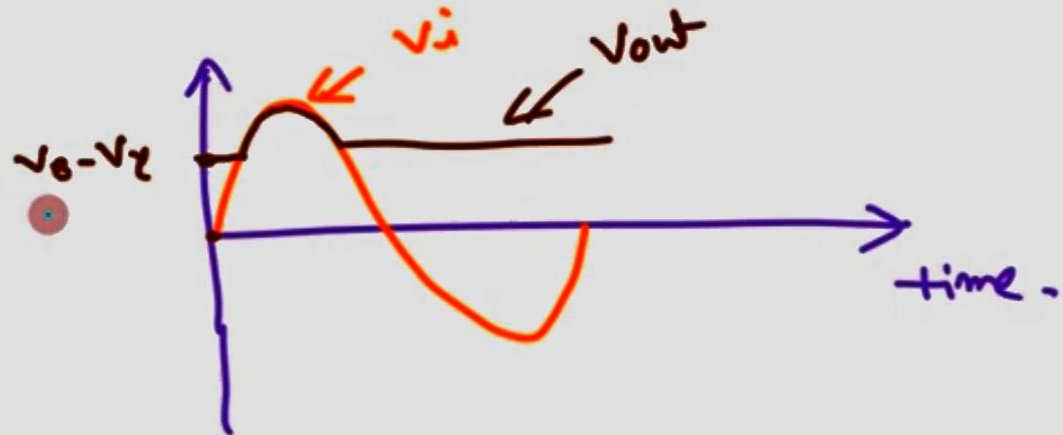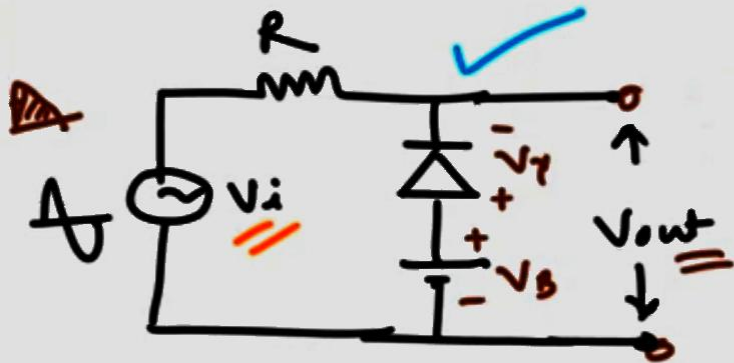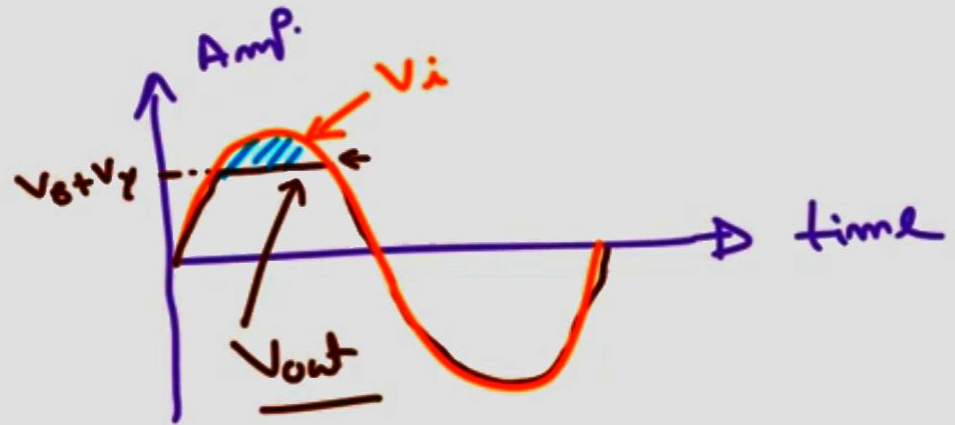
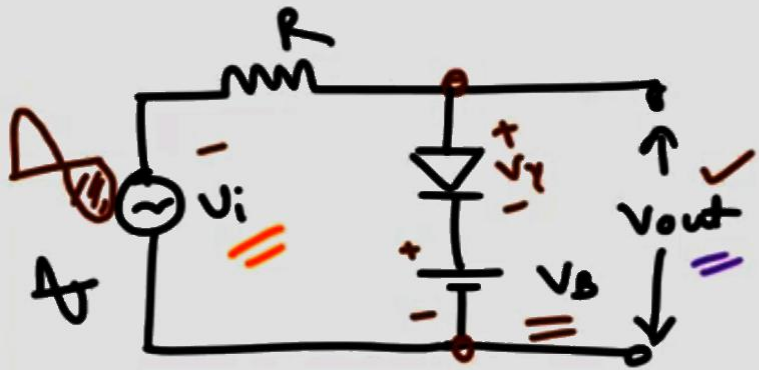


# Clipper Circuits

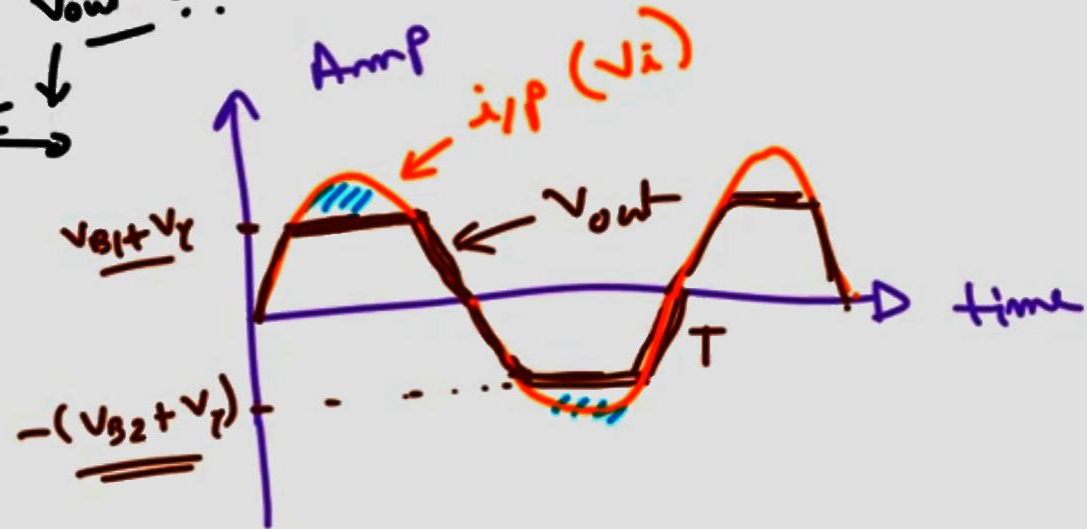
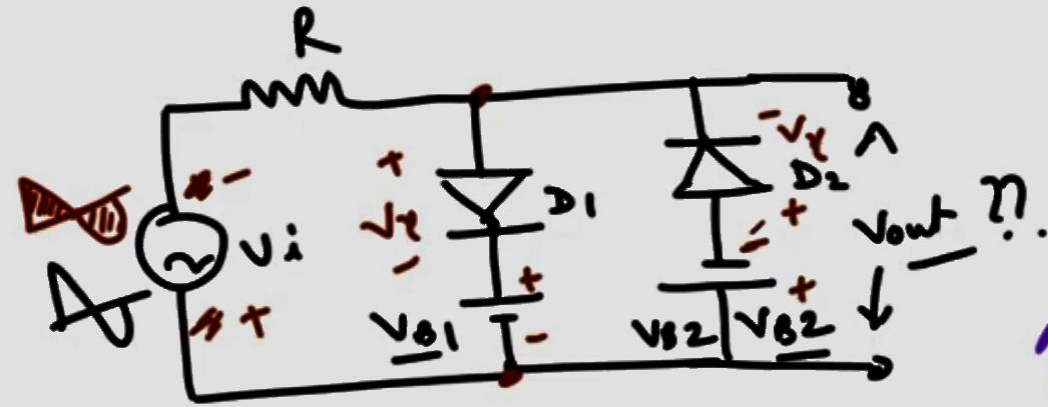

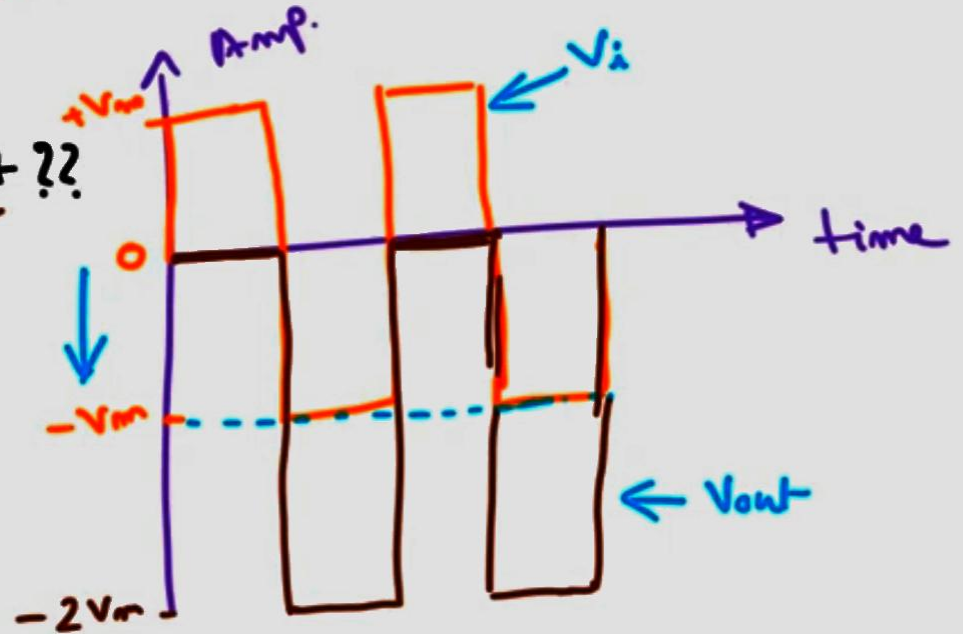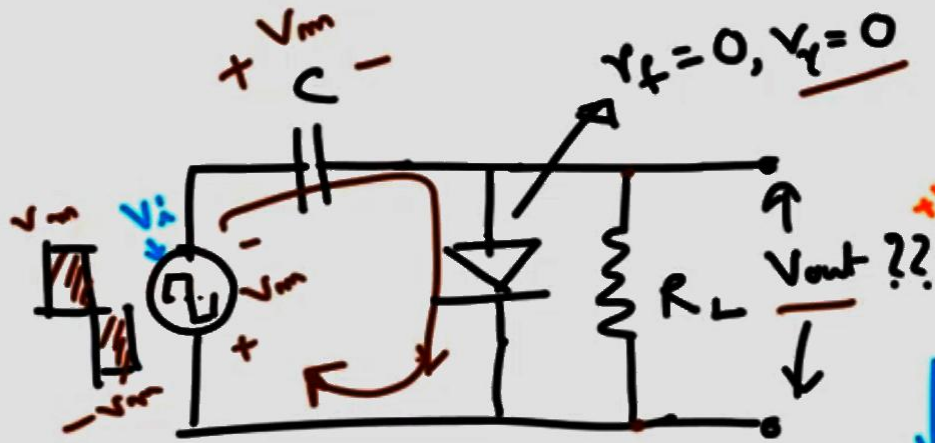
# ✓ Clamper Circuits

→ Shifts the entire signal by a DC level.



# Clamper Circuits

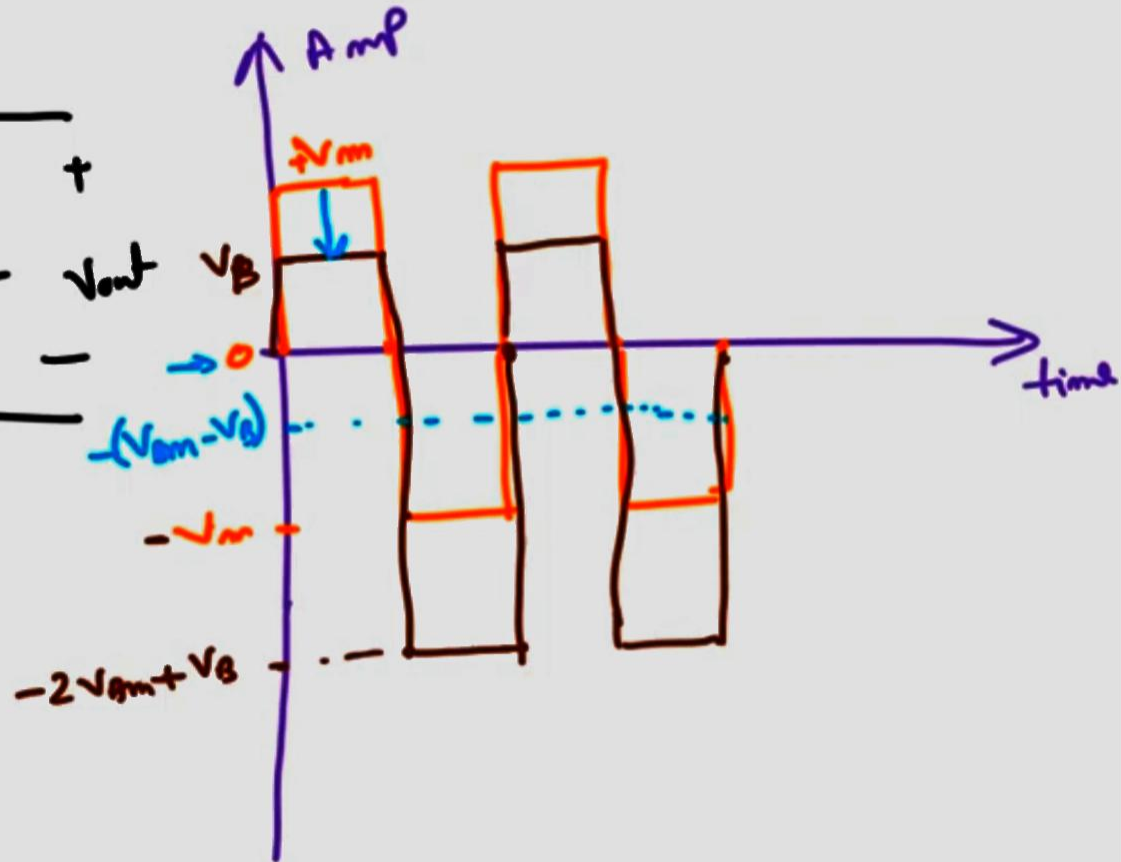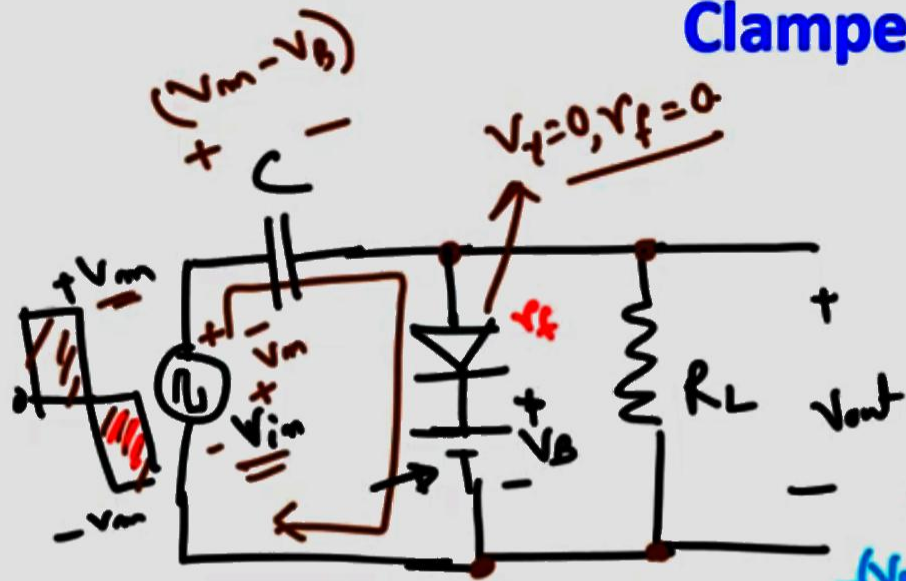

$$\begin{aligned}
 & -V_m - V_m + V_B \\
 & = -2V_m + V_B
 \end{aligned}$$

$$R_L > V_f$$

$$\begin{aligned}
 \tau_{charging} &= V_f C \\
 &= \tau_{discharging} = R_L C
 \end{aligned}$$



# Clamper Circuits

