

E

INDIAN INSTITUTE OF TECHNOLOGY KHARAGPUR
Department of Electronics and Electrical Communication Engineering

End Spring Semester Examination 2013
Subject name: Electromagnetic Engineering
Subject No: EC21006

Full Marks : 120
Time: 3Hrs

Answer all the questions
All questions carry equal marks.

1. (a) For a lossless medium for which the characteristic impedance $\eta = 60\pi$, relative permeability $\mu_r = 1$ and the magnetic field $\vec{H} = -0.1 \cos(\omega t - z) \hat{a}_x + 0.5 \sin(\omega t - z) \hat{a}_y$ A/m, calculate the relative permittivity ϵ_r , ω , and the electric field \vec{E} . [12]
- (b) Given the electric flux density $\vec{D} = (2y^2 + z) \hat{a}_x + 4xy \hat{a}_y + x \hat{a}_z$ C/m², find
 - (i) The volume charge density at the point (-1, 0, 3).
 - (ii) The flux through the cube defined by $0 \leq x \leq 1, 0 \leq y \leq 1, 0 \leq z \leq 1$.
 - (iii) The total charge enclosed by the cube. [8]
2. (a) For the circuit shown below in Fig. 1, the load $Z_L = 200 + j100 \Omega$ is to be matched to a 40Ω line using a lossless transmission line of characteristic impedance Z_1 and length l . Find l and Z_1 . [12]


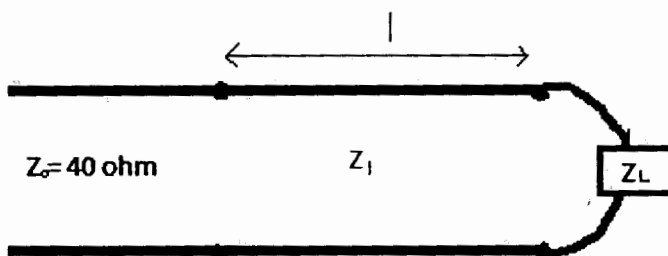


Fig. 1

(b) Find the input impedance Z_{in} of the following circuit :

[8]

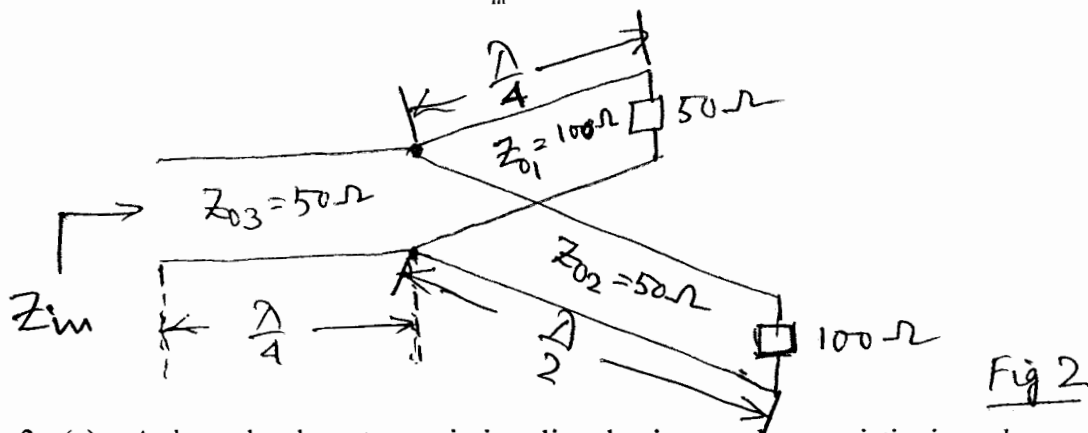

3. (a) A long lossless transmission line having a characteristic impedance of 50Ω and terminated with a matched load is fed from a generator of internal resistance 1Ω and open circuit voltage $V_g = 0.5 \cos(\pi \times 10^8 t)$ volts. The velocity of propagation on the line is 1.25×10^8 m/s. For the above configuration, find
- Input impedance seen by the generator. [4]
 - The voltage and current at the transmission line input. [4]
 - The instantaneous voltage and current at an arbitrary location 'x' along the line from the transmission line input. [4]
- (b) The characteristic impedance of a uniform transmission line is 2040Ω at a frequency of 800 Hz, with a propagation constant of $0.0054 \angle 87.9^\circ$ /m. Determine the per unit resistance, conductance, inductance and capacitance of the line. [8]
4. A long lossless line with characteristic impedance $Z_0 = 50 \Omega$ and operating at 1 GHz is terminated by a load impedance of $75 + j100 \Omega$. Assuming the speed of propagation on the line to be $c = 3 \times 10^8$ m/s, find
- The reflection coefficient at the load. [2]
 - The reflection coefficient at a distance of 20 m from the load. [5]
 - The input impedance at 20 m from the load. [5]
 - The standing wave ratio on the line. [2]
 - The locations of the first voltage minimum and the first voltage maximum from the load. [6]

5. An antenna operates at a wavelength of 2 m and is designed with an impedance of 75Ω . However, because of mistakes in design, the antenna is badly mismatched. The measured impedance after installation is $15 + j60\Omega$. The antenna is connected to a 75Ω line as shown in Fig. 3. Calculate

- (a) The required shorted stub and its location on the line to match the antenna to the line, assuming the line and the stub to have the same characteristic impedance. [15]
- (b) The shortest lengths of open circuit stub that will accomplish the same purpose as the short circuit stub in (a). [5]

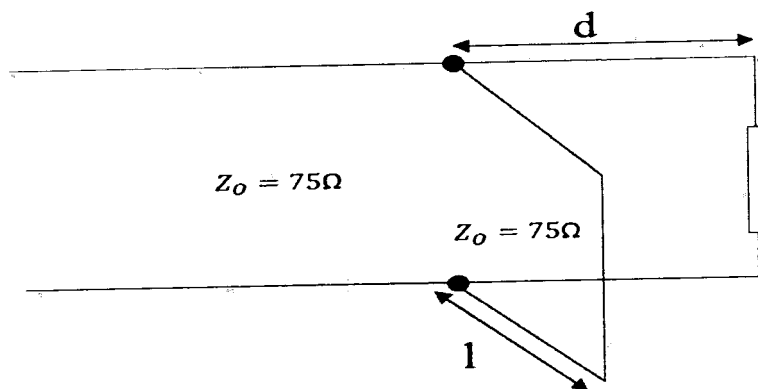


Fig. 3

6. (a) For the circuit configuration shown in the figure below (Fig. 4), find the location of the transformer (distance d in the figure) and the characteristic impedance of the transformer Z_t , with $Z_L = 50 + j50$, assuming the characteristic impedance of quarter-wavelength transformer to be real. [14]

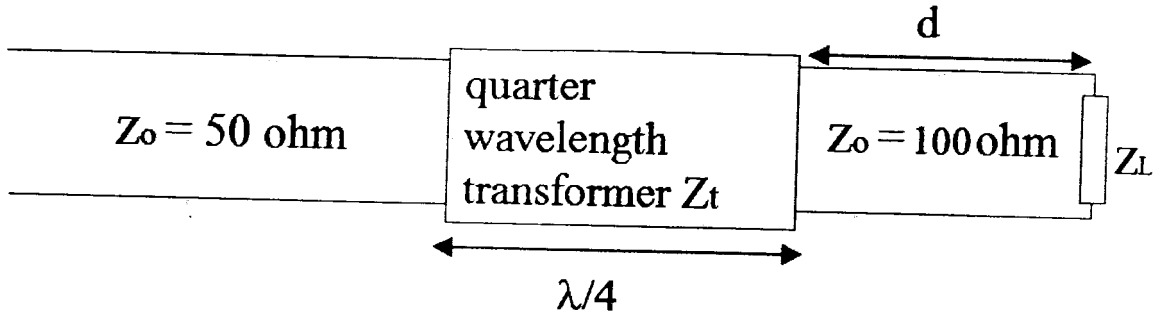


Fig. 4

- b) For the given transmission line parameters $R = 1.675 \text{ } \Omega/\text{m}$, $L = 0.592 \text{ } \mu\text{H}/\text{m}$, $C = 75 \text{ pF}/\text{m}$ and $G = 2.12 \times 10^{-4} \text{ mho}/\text{m}$, find the following at frequency 1 GHz :
- Propagation constant.
 - Phase velocity.
 - Characteristic impedance.

[2x3=6]

The Complete Smith Chart

Black Magic Design

