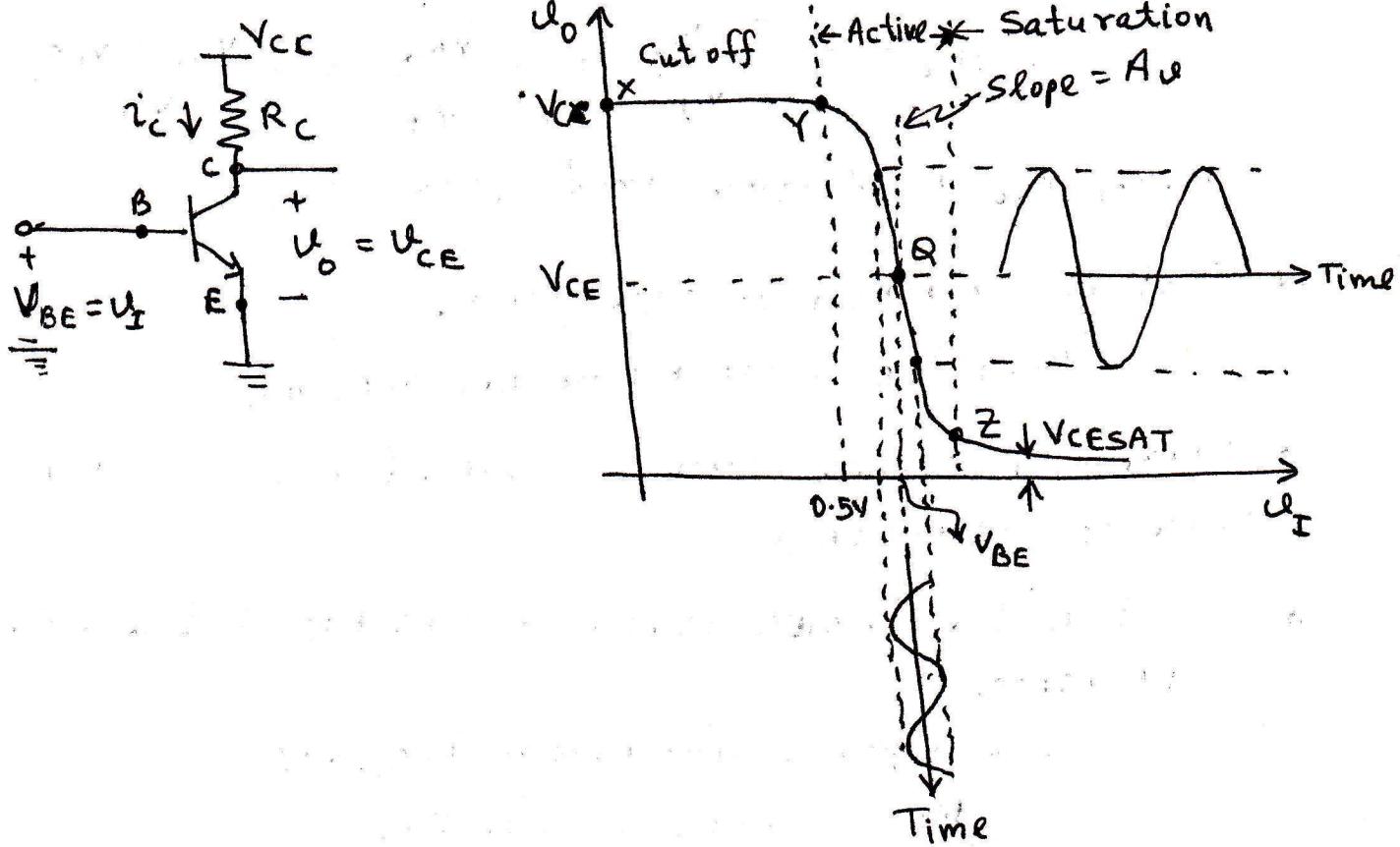


BIPOLAR AMPLIFIERS

COMMON Emitter Large Signal Characteristic



Here, $v_o = V_{CC} - I_C R_C$.

In active mode,

$$v_o = V_{CC} - R_C I_S e^{V_{BE}/V_T}$$

In saturation region, $v_{CE} = V_{CESAT}$ (which is around 0.2 to 0.3V)

$$I_{C,SAT} = \frac{V_{CC} - V_{CESAT}}{R_C}$$

* Amplifier gain is defined in Active region.

$$A_v = \left. \frac{\partial v_o}{\partial v_I} \right|_{v_I = v_{BE}}$$

$$\Rightarrow A_v = \left. \frac{\partial [V_{CC} - R_C I_S e^{V_{BE}/V_T}]}{\partial v_I} \right|_{v_I = v_{BE}}$$

(2)

$$\Rightarrow A_u = -\frac{1}{V_T} I_s R^{\frac{V_{BE}/V_T}{R}} \cdot R_C$$

$$\Rightarrow A_u = -\frac{I_C R_C}{V_T} = -\frac{V_{RC}}{V_T} = -\frac{V_{CC} - V_{CE}}{V_T}$$

where, V_{RC} is voltage drop across R_C .

* What is maximum voltage gain?

→ When V_{CE} is minimum i.e. $V_{CE,SAT}$.

* Maximum voltage gain is obtained when BJT is at edge of saturation.

* What is the repercussion of biasing at the edge of saturation?

→ Can you swing below $V_{CE,SAT}$?

No. \Rightarrow signal is clipped.

* Theoretical maximum gain is,


$$A_{u,max} \approx -\frac{V_{CC}}{V_T}$$

* How is this different from MOSFET?

→ Does the designer have control over the gain in BJT?

→ How about in MOSFET?

Example:-

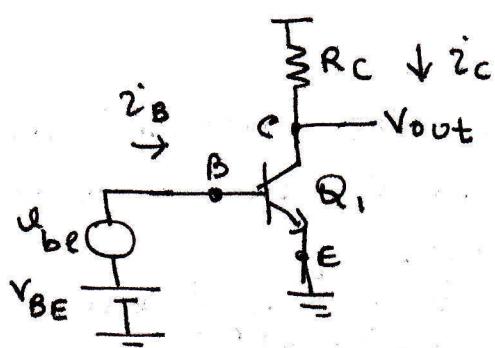

$$I_S = 10^{-15} \text{ A}$$

$$R_C = 6.8 \text{ k}\Omega$$

$$V_{CC} = 10 \text{ V}$$

(i) What is V_{BE} if $V_{CE} = 3.2 \text{ V}$?

$$I_C = \frac{V_{CC} - V_{CE}}{R_C} = \frac{10 - 3.2}{6.8 \times 10^3} = 1 \text{ mA.}$$

$$\Rightarrow V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 690.8 \text{ mV.}$$

(ii) What is the voltage gain? If $u_{be} = 5 \times 10^{-3} \sin(2\pi ft)$ what is u_{out} ?

$$A_u = -\frac{V_{CC} - V_{CE}}{V_T} = -\frac{10 - 3.2}{0.025} = -272 \text{ V/V.}$$

Thus,

$$u_{out} = -5 \times 10^{-3} \times 272 \sin(2\pi ft)$$

$$\Rightarrow u_{out} = -1.36 \sin(2\pi ft).$$

(iii) What value of u_{BE} drives Q_1 into saturation? Assume $V_{CE,SAT} = 0.3 \text{ V}$.

$$\text{At saturation, } I_C = \frac{10 - 0.3}{6.8 \times 10^3} = 1.617 \text{ mA.}$$

$$\text{New, } V_{BE} = V_T \ln\left(\frac{1.617 \times 10^{-3}}{1 \times 10^{-15}}\right) = 702.8 \text{ mV.}$$

$$\Rightarrow \Delta V_{BE} = 702.8 - 690.8 = 12 \text{ mV.}$$

(iv) What value of V_{BE} drives Q_1 into ~~cutoff~~ 1% of cut off (i.e. $V_o = 0.99 V_{CC}$).


$$I_C = \frac{V_{CC} - 0.99 V_{CC}}{6800} = 14.7 \mu\text{A.}$$

$$\Rightarrow V_{BE} = V_T \ln\left(\frac{14.7 \times 10^{-6}}{1 \times 10^{-15}}\right) = 585.3 \text{ mV.}$$

$$\Rightarrow \Delta V_{BE} = -105.5 \text{ mV.}$$

BIASING SCHEMES FOR BJT :-


① FIXED V_{BE} :-

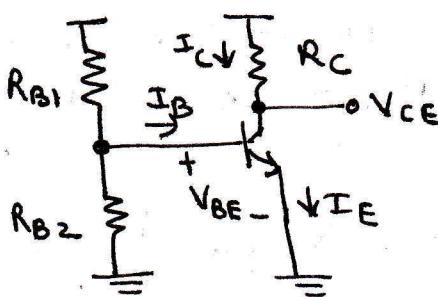

- * Sharp $I_C - V_{BE}$ characteristic results in drastic changes in bias point.
- * Similar to constant V_{GS} biasing for MOSFET.

Not very useful



② FIXED I_B :-

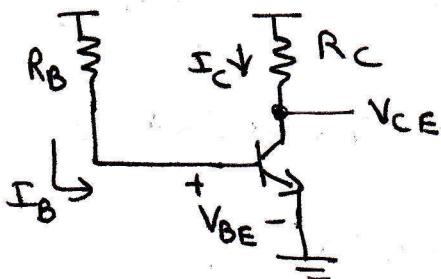

- * Changes in β can cause drastic changes in bias point.

Not very useful.

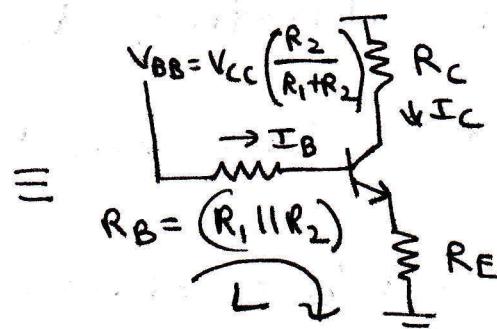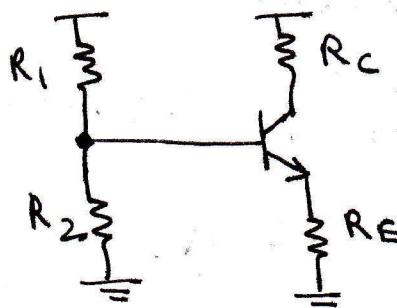③ BIASING USING RESISTOR DIVIDER & EMITTER DEGENERATION



Writing KVL in loop "L" we get,


$$V_{BB} = I_B R_B + I_E R_E + V_{BE}$$

$$\Rightarrow I_E = \frac{V_{BB} - V_{BE}}{R_E + R_B(\beta + 1)}$$

* If $V_{BB} \gg V_{BE} + R_E \Rightarrow \frac{R_B}{\beta + 1} \rightarrow$

I_E is insensitive to transistor parameter variation (Robust biasing)

*

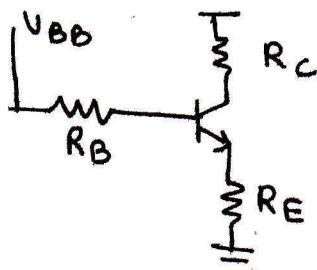

How large can V_{BB} be?

→ Larger the value of $V_{BB} \Rightarrow$ sum of voltage drop across R_C and V_{CB} .

→ We want large voltage drop across R_C for higher gain and large signal swing before transistor cut-off.

→ We also want V_{CB} (or V_{CE}) to be large for larger swing before transistor enters saturation.

⇒ Conflicting requirement. (Your calibre comes into picture).

* No tool is yet good enough for designing automatically.

* ANALOG DESIGN IS ART.


TYPICAL RULE OF THUMB:-

$$V_{BB} \approx \frac{1}{3} V_{CC}$$

$$V_{CB} \approx \frac{1}{3} V_{CC}$$


$$\text{and } I_C R_C \approx \frac{1}{3} V_{CC}.$$

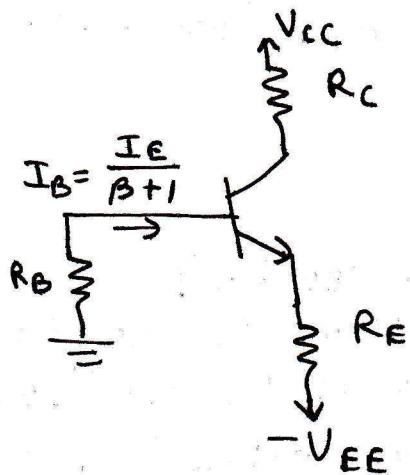TWO-Power Supply Version of Classical Bias Arrangement



$$I_E = \frac{V_{EE} - V_{BE}}{R_E + R_B / (\beta + 1)}$$

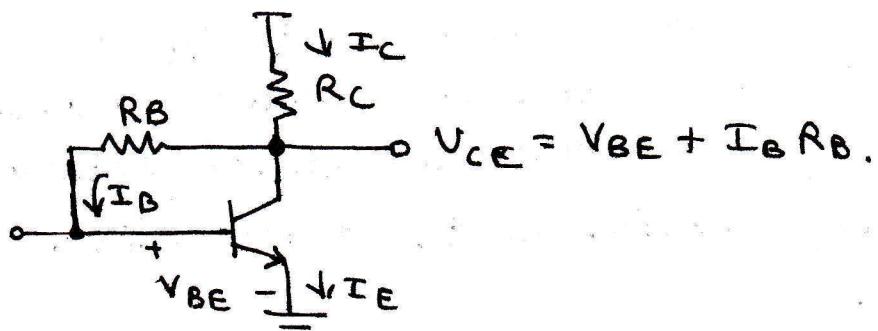Biasing Using a Collector-Base Feedback Resistor



Applying KVL from V_{CC} to ground we get,

$$V_{CC} = I_E R_C + I_B R_B + V_{BE}$$

Why $I_E R_C$. not $I_C R_C$?


$$\Rightarrow V_{CC} = I_E \left[R_C + \frac{R_B}{\beta + 1} \right] + V_{BE}$$

$$\Rightarrow I_E = \frac{V_{CC} - V_{BE}}{R_C + R_B / (\beta + 1)}$$

* Value of R_B determines V_{CB} and hence allowable signal swing,

$$V_{CB} = I_B R_B = I_E \frac{R_B}{\beta + 1}$$

BIASING USING CONSTANT CURRENT SOURCE :-

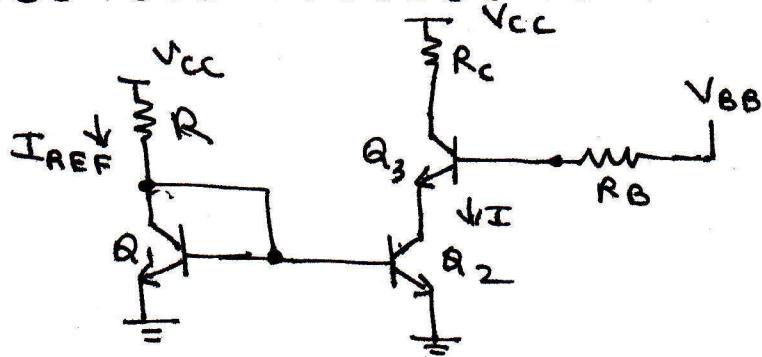

* Q_1 is diode connected.

$$I_{REF} = \frac{V_{CC} - V_{BE}}{R}$$

* Since, Q_1 & Q_2 have same V_{BE} , their collector currents will be equal resulting in,

$$I = I_{REF} = \frac{V_{CC} - V_{BE}}{R}$$

* Arrangement of Q_1 , Q_2 , & R is called current mirror.

SMALL SIGNAL OPERATION AND MODELS :-

Convention :- $v_{BE} = V_{BE} + v_{be}$

$$v_{CE} = V_{CE} + v_{ce}$$


$$i_c = I_c + i_{c_e}$$

$$i_B = I_B + i_{b_e}$$

$$i_E = I_E + i_{e_e}$$

Conceptual circuit to arrive at small signal model :-

At DC (i.e. no ac signal applied).

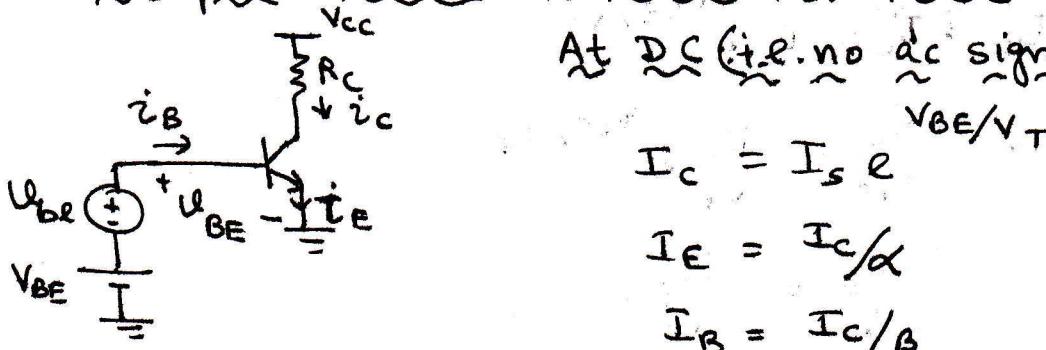

$$I_c = I_s e^{V_{BE}/V_T}$$

$$I_E = I_c/\alpha$$

$$I_B = I_c/\beta$$

$$V_C = V_{CE} = V_{CC} - I_c R_C$$

With ac signal :-

$$v_{BE} = V_{BE} + v_{be}$$

$$\Rightarrow i_c = I_c + i_{c_e}$$

$$\Rightarrow i_c = I_s e^{(V_{BE} + v_{be})/V_T}$$

$$\Rightarrow i_c = I_s e^{V_{BE}/V_T} e^{v_{be}/V_T}$$

$$\Rightarrow i_c = I_c e^{v_{be}/V_T}$$

$$\Rightarrow i_c = I_c \left(1 + \frac{v_{be}}{V_T} \right) \dots \left[\text{By Taylor series expansion with } \frac{v_{be}}{V_T} \ll 1 \right]$$

Thus,

$$i_c = I_c + \frac{I_c}{V_T} u_{be}$$

$$\Rightarrow \text{small signal, } i_c = \frac{I_c}{V_T} u_{be}$$

$$\Rightarrow \text{Transconductance, } g_m = \frac{I_c}{V_T}.$$

* Can you prove that, $g_m = \left. \frac{\partial i_c}{\partial V_{BE}} \right|_{i_c = I_c}$?

Now, $\frac{\partial i_c}{\partial V_{BE}} = I_s e^{\frac{V_{BE}}{V_T}}$

$$\Rightarrow \frac{\partial i_c}{\partial V_{BE}} = \frac{I_s}{V_T} e^{\frac{V_{BE}}{V_T}}$$

$$\Rightarrow \frac{\partial i_c}{\partial V_{BE}} = \frac{I_c}{V_T}.$$

* Can you also prove that, $g_m = \frac{I_c}{V_T}$ with base-width modulation?

* Unlike MOSFET where there is no gate current at DC, we have a base current in BJT at DC.

* Now,

$$i_B = I_B + i_b$$


$$\Rightarrow i_B = \frac{I_c}{\beta} + \frac{I_c}{\beta V_T} u_{be}$$

Thus,

$$i_b = \frac{g_m}{\beta} u_{be}$$

$$\Rightarrow \frac{u_{be}}{i_b} = \frac{\beta}{g_m} = r_\pi = \text{small signal input resistance between base and emitter.}$$

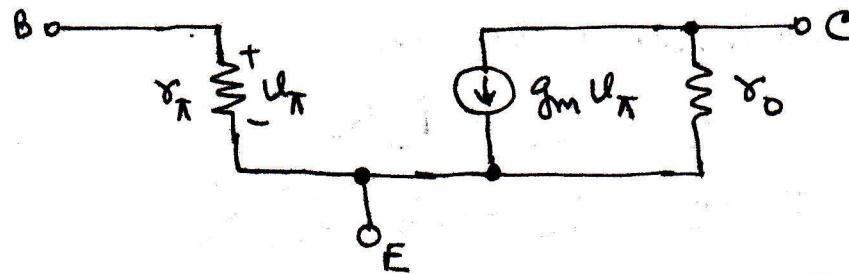Thus, small signal model of BJT is as follows:-



Emitter current & Input resistance at Emitter :-

$$i_E = \frac{i_c}{\alpha} = \frac{I_c}{\alpha} + \frac{i_c}{\alpha}$$

$$\Rightarrow i_E = I_E + i_e$$

$$\text{where, } I_E = \frac{I_c}{\alpha} \text{ and } i_e = \frac{i_c}{\alpha}.$$

$$\text{Now, } i_e = \frac{i_c}{\alpha} = \frac{I_c}{\alpha V_T} \cdot V_{be}$$

$$\Rightarrow i_e = \frac{I_E}{V_T} V_{be}$$

$$\Rightarrow r_e = \frac{V_{be}}{i_e} = \frac{V_T}{I_E}$$

$$\text{We know, } g_m = \frac{I_c}{V_T}. \text{ Thus,}$$

$$r_e = \frac{\alpha}{g_m} \approx \frac{1}{g_m} \quad [\because \alpha \approx 1].$$

Relationship between r_π and r_e .

We know,

$$V_{be} = i_b r_\pi = i_e r_e.$$

$$\Rightarrow r_\pi = \frac{i_e}{i_b} r_e$$

$$\Rightarrow r_\pi = (\beta + 1) r_e.$$

VOLTAGE GAIN:-

Total collector voltage is,

$$U_c = V_{cc} - i_c R_c$$

$$\Rightarrow U_c = V_{cc} - (I_c + i_c) R_c$$

$$\Rightarrow U_c = (V_{cc} - I_c R_c) - i_c R_c$$

$$\Rightarrow U_c = V_c - i_c R_c$$

↓ ↓
 DC bias AC Variation.
 Voltage

Thus,

$$U_c = - i_c R_c$$


$$\Rightarrow U_c = - g_m U_{be} R_c$$

$$\Rightarrow A_u = \frac{U_c}{U_{be}} = - g_m R_c$$

We know, $g_m = \frac{I_c}{V_T}$ resulting in,

$$A_u = - \frac{I_c R_c}{V_T}$$

SEPARATING THE DC AND AC QUANTITIES :-

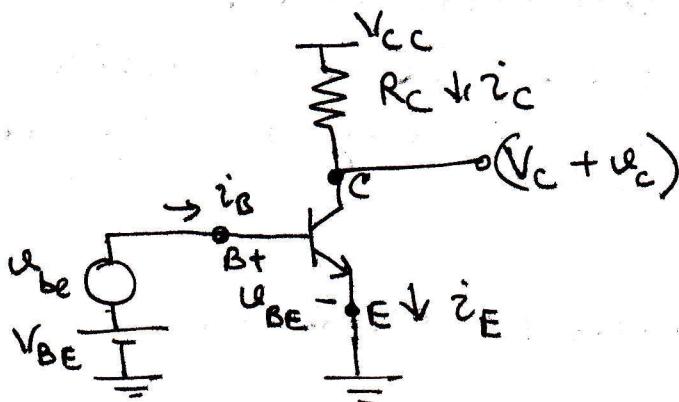

$$V_{BE} = V_{BE} + u_{be}$$

$$u_C = V_C + u_c$$


$$i_B = I_B + i_b$$

$$i_C = I_C + i_c$$

$$i_E = I_E + i_e.$$



DC Equivalent Circuit:-

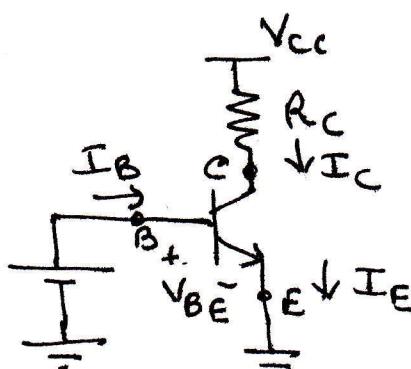Obtains, V_{BE} , V_{CE} , I_C , I_E , and I_B .



AC Equivalent Circuit :- Note that $u_{cc} = V_{CC} + u_{ce}$.

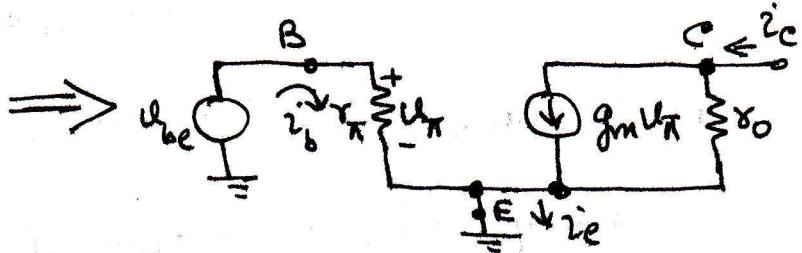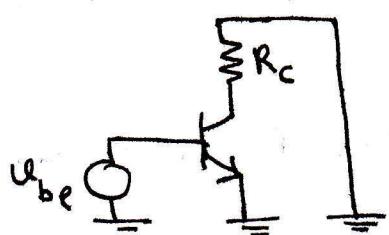But, $u_{cc} = 0 \Rightarrow u_{cc} = V_{CC}$. i.e. AC part of u_{cc} is 0 \Rightarrow a voltage source does not have a.c. variation.



$$\text{where, } r_\pi = \frac{\beta}{g_m}$$

$$\text{and, } g_m = \frac{I_C}{V_T}.$$

STEPS OF THE ANALYSIS

- ① Determine the DC operating point of the BJT i.e. V_{BE} , V_C , and I_C . If the BJT is in active mode then I_B and I_E are given by $I_B = \frac{I_C}{\beta}$ and $I_E = \frac{I_C}{\alpha}$.

- ② Calculate the small signal parameters :-

$$g_m = \frac{I_C}{V_T}$$

$$\gamma_T = \frac{\beta}{g_m}$$

$$\gamma_e = \frac{V_T}{I_E} = \frac{\alpha}{g_m}$$

$$\gamma_o = \frac{V_A}{I_C}$$

- ③ Remove all DC sources i.e.

(a) remove all ~~DC~~ independent DC voltage sources i.e. replace them with short circuit.


(b) remove all independent DC current sources i.e. replace them with open circuit.

REMEMBER ONLY INDEPENDENT VOLTAGE & CURRENT SOURCES.


- ④ Replace the BJT with small signal model.

- ⑤ Analyze the resulting ~~circuit~~ small signal circuit.

Example :- $\beta = 100, V_A = \infty$

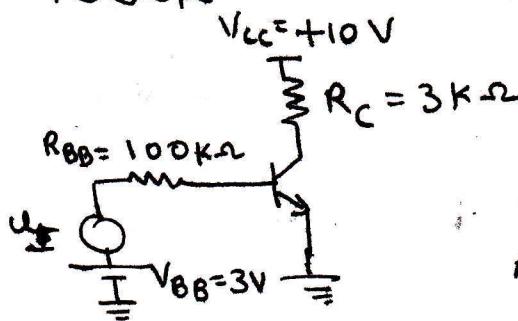

\Rightarrow
DC
Analysis

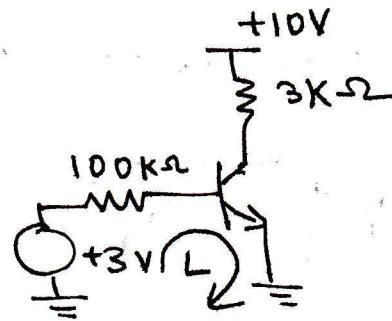

① D.C. Analysis :-

KVL in loop L gives,

$$3 = I_B 100\text{k}\Omega + V_{BE}$$

$$\Rightarrow 3 = I_B 100\text{k}\Omega + 0.7$$

$$\Rightarrow I_B = 23\mu\text{A}.$$

$$\text{Thus, } I_C = 100 \times 23\mu\text{A} = 2.3\text{mA}$$

$$I_E = 2.323\text{mA}.$$

$$V_C = 10 - I_C R_C = 3.1\text{V}.$$


② Computing small signal parameters :-

$$g_m = \frac{I_C}{V_T} = \frac{2.3\text{mA}}{25\text{mV}} = 92\text{mV}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{92 \times 10^{-3}} = 1.09\text{k}\Omega$$

$$r_e = \frac{V_T}{I_E} = \frac{25\text{mV}}{2.323\text{mA}} = 10.8\Omega$$


③ Small signal circuit diagram :-

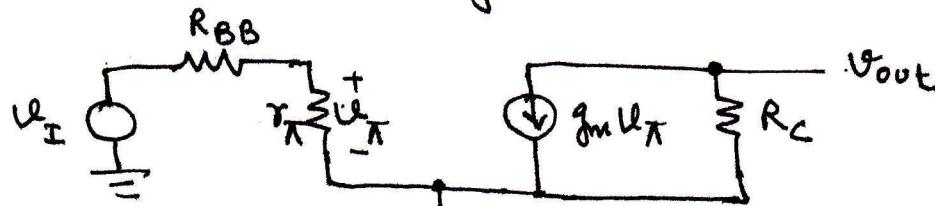

$$\text{Now, } u_\pi = \frac{u_I}{R_{BB} + r_\pi} r_\pi. \Rightarrow u_{out} = -g_m u_\pi R_C$$

$$\Rightarrow A_{v2} = \frac{u_{out}}{u_I} = -\frac{r_\pi}{R_{BB} + r_\pi} g_m R_C = -3.06$$

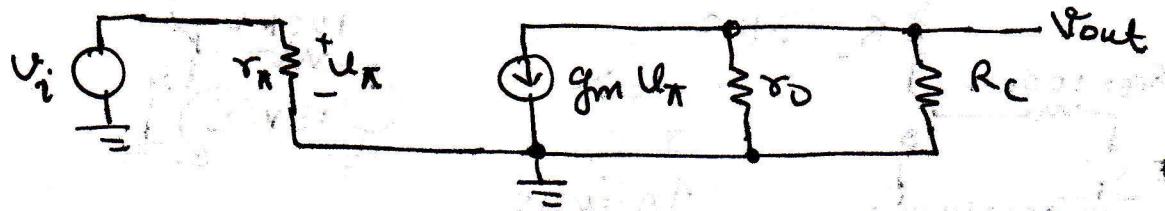In the presence of Early Effect we should have,



$$\text{Gain, } A_u = -g_m (r_o \parallel R_C).$$

* SOLVE EXAMPLE 5.15 → showing the waveforms at various points.