

# Electromagnetic Engineering (EC 21006)

## TUTORIAL - X

### TRANSMISSION LINES -- TIME DOMAIN ANALYSIS

1. In the transmission line of Figure 1,  $R_L = Z_0 = 50\Omega$ , and  $R_g = 25\Omega$ . Determine and plot the voltage at the load resistor and the current in the battery as functions of time by constructing appropriate voltage and current reflection diagrams.




**Figure 1**

2. In the transmission line of Figure 1,  $Z_0 = 50\Omega$ , and  $R_L = R_g = 25\Omega$ . The switch is closed at  $t = 0$  and is *opened again* at time  $t = l/4v$ , thus creating a rectangular voltage *pulse* in the line. Construct an appropriate voltage reflection diagram for this case and use it to make a plot of the voltage at the load resistor as a function of time for  $0 < t < 8l/v$  (note that the effect of opening the switch is to initiate a second voltage wave, whose value is such that it leaves a net current of zero in its wake).
3. In the charged line of Figure 2, the characteristic impedance is  $Z_0 = 100\Omega$ , and  $R_g = 300\Omega$ . The line is charged to initial voltage,  $V_0 = 160\text{ V}$ , and the switch is closed at  $t = 0$ . Determine and plot the voltage and current through the resistor for time  $0 < t < 8l/v$  (four round-trips).




**Figure 2**

4. In the transmission line of Figure 3, the switch is located *midway* down the line and is closed at  $t = 0$ . Construct a voltage reflection diagram for this case, where  $R_L = Z_0$ . Plot the load resistor voltage as a function of time.

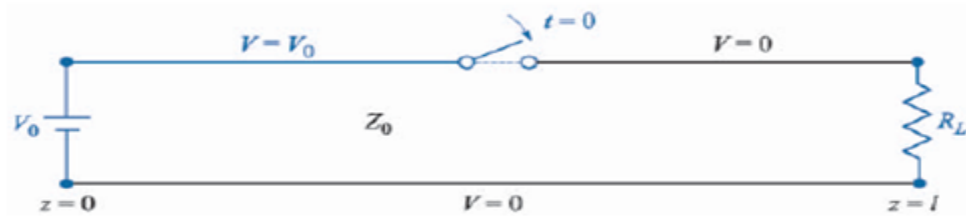


**Figure 3**

5. A simple *frozen wave generator* is shown in Figure 4. Both switches are closed simultaneously at  $t = 0$ . Construct an appropriate voltage reflection diagram for the case in which  $R_L = Z_0$ . Determine and plot the load resistor voltage as a function of time.

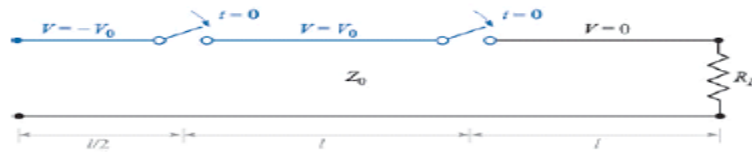


**Figure 4**

6. A  $50\text{-}\Omega$  transmission line having a transit time of  $50\text{ ns}$  connects a pulse generator to a  $150\text{-}\Omega$  load resistance. The internal resistance of the pulse generator is  $10\text{ }\Omega$ , and its voltage magnitude is  $10\text{ V}$  at no load. Determine the variation of the voltage at the midpoint of the line for duration of  $5t_t$  if the pulse width is  $1\text{ ns}$ .
7. A  $2950\text{-m}$ -long, lossless telephone line is subjected to a  $24 u(t)\text{ V}$  source having an internal resistance of  $100\text{ }\Omega$ , as shown in Figure 5. The per-unit-length inductance and capacitance of the line are  $1.15\text{ }\mu\text{H/m}$  and  $10\text{ pF/m}$ , respectively. Sketch the voltage and current waveforms as a function of time at the midpoint when the transmission line is terminated into a load resistance of  $500\text{ }\Omega$ .

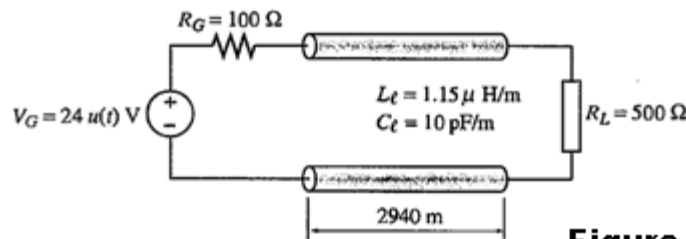

**Figure 5**

8. An  $800\text{-m}$ -long, overhead transmission line having a transit time of  $4\text{ }\mu\text{s}$  is connected to a  $400\text{-m}$ -long cable with a transit time of  $2\text{ }\mu\text{s}$  at point A, as shown in Figure 6. The characteristic resistances of the overhead line and cable are  $200\text{ }\Omega$  and  $50\text{ }\Omega$ , respectively. The receiving end of the cable is open-circuited, and the internal resistance of the source is assumed to be zero. Determine the variation of the voltage for duration of  $30\text{ }\mu\text{s}$  at the receiving end of the cable when the overhead line is subjected to a unit step voltage.

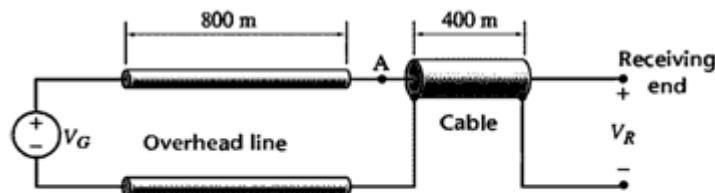

**Figure 6**