

# Introduction to Electronics (Practice paper – 6)

## Topic: Op-Amp

1. Determine the expressions/values of  $v_o$  ( $V_o$ ) in the following circuits:

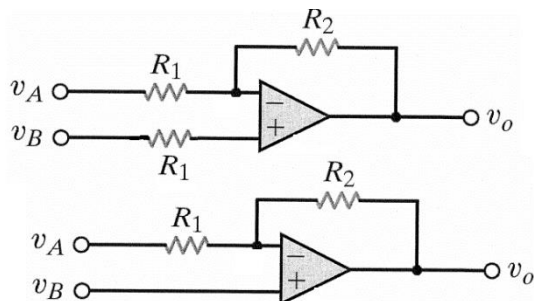


Fig. 1a (i & ii)

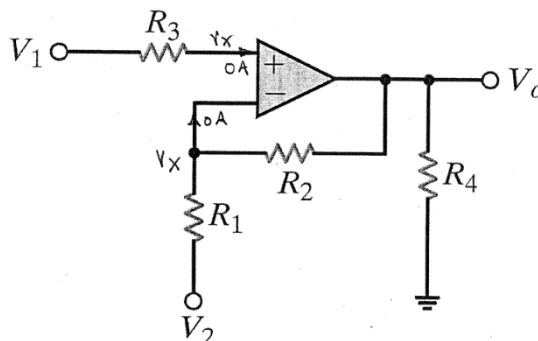


Fig. 1b

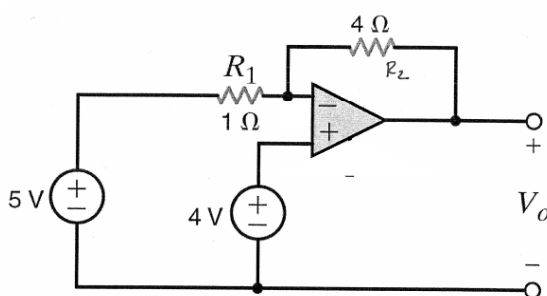


Fig. 1c

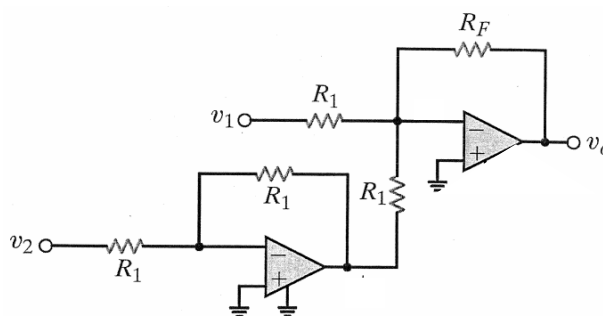


Fig. 1d

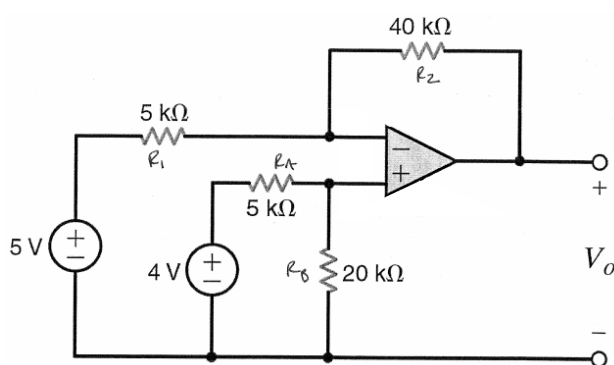


Fig. 1e

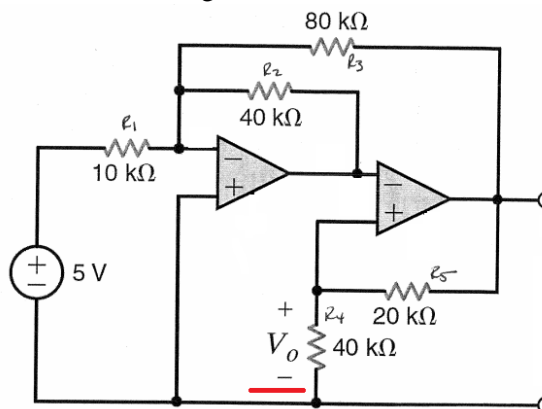


Fig. 1f

2. You have given a bunch of  $10\text{ k}\Omega$  resistors and an Op-Amp. Design a circuit that will produce the following output ( $V_o$ ).  $V_o = -2V_1 - 4V_2$

3. In the Op-Amp circuit shown in Fig. 2, find  $I_o$  and  $I_s$  if  $V_s = 1\text{ V}$  and  $R_L = 1\text{ k}\Omega$ . Also, plot the variation of  $I_o$  with  $R_L$ .

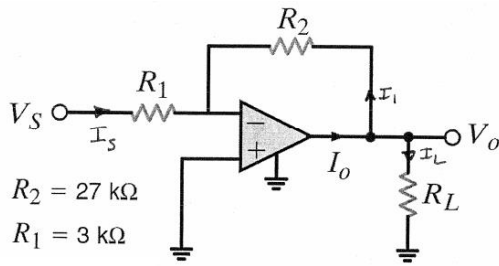


Fig. 2

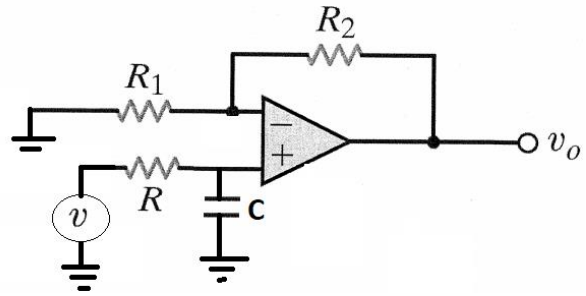


Fig. 3

4. Fig. 3 shows a low-pass filter. Estimate the value of feedback resistor  $R_2$  such that the 'pass-band' gain of the total circuit is 100. Given that  $C = 0.2 \mu\text{F}$  and  $R_1 = 1 \text{ k}\Omega$ . Also calculate the value of resistor  $R$  for realizing a cut-off frequency of 2 kHz.
5. For an Op-Amp, the differential gain ( $A_d$ ) is 100. When 1 V is applied (common) to both the inputs, the output voltage measured is 0.01 V. Calculate the CMRR of the Op-Amp in dB.
6. Consider the circuit in Fig. 4, (a) Derive the expression for the output voltage  $v_O$  in terms of  $v_{I1}$  and  $v_{I2}$ . (b) Determine  $v_O$  for  $v_{I1} = +5 \text{ mV}$  and  $v_{I2} = (-25 - 50 \sin \omega t) \text{ mV}$ .

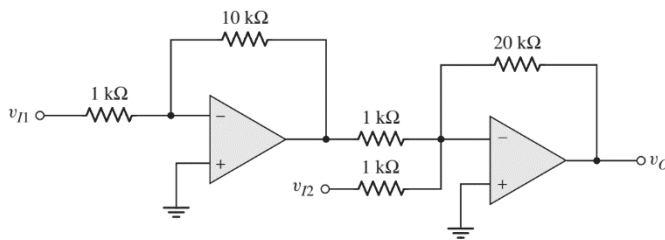


Fig. 4

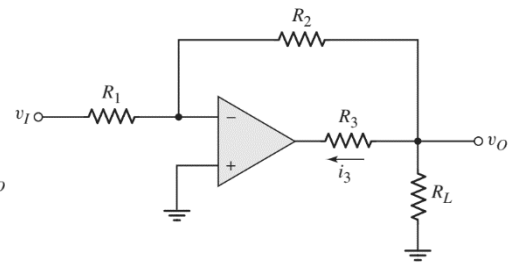


Fig. 5

7. In the circuit shown in Fig. 5, derive the expression for  $i_3$  in terms of  $v_I$ .
8. Consider the circuit shown in Fig. 6. (a) Determine the ideal voltage gain. (b) Find the actual gain if the open-loop gain ( $A_{od}$ ) of the op-amp is  $A_{od} = 5 \times 10^3$ . (c) Determine the required value of  $A_{od}$  in order that the actual voltage gain be within 0.2 percent of the ideal value.

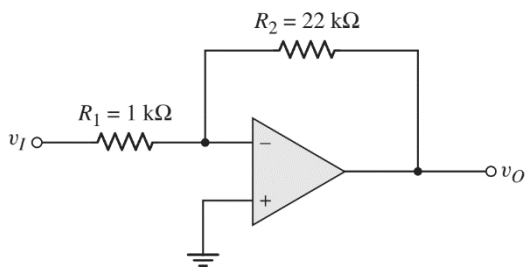


Fig. 6

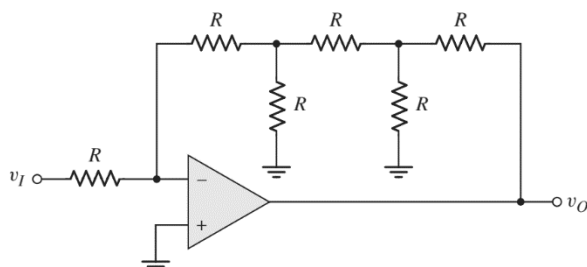


Fig. 7

9. For the inverting op-amp amplifier shown in Fig. 7, determine the gain  $A_v = v_O/v_I$ .
10. The circuit shown in Fig. 8 is a first-order high-pass active filter. Determine how the gain of this circuit [ $A_v = v_O/v_I$ ] is dependent on frequency i.e. find the voltage transfer function.

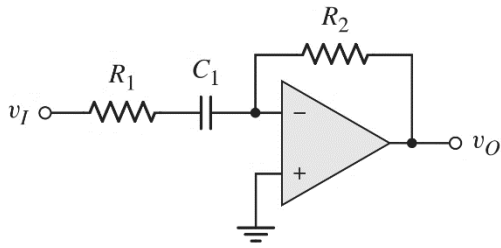


Fig. 8

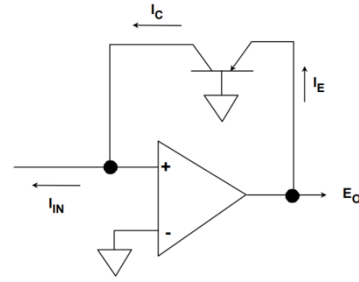


Fig. 9

11. In Fig. 9, show that  $E_0 = \frac{kT}{q} \ln\left(\frac{I_{IN}}{I_{ES}}\right)$ , where,  $I_{ES}$  is the reverse saturation current.
12. If an op-amp has a slew-rate of 5 V/ $\mu$ s, find the full-power bandwidth for a peak output voltage of (a) 5 V, (b) 1.5 V, and (c) 0.4 V
13. An amplifier system is to be designed to provide an undistorted 10 V peak sinusoidal signal at a frequency of  $f = 12$  kHz. Determine the minimum slew rate required for the amplifier.
14. An audio amplifier system is to use an op-amp with an open-loop gain of  $A_{Od} = 2 \times 10^5$  and a dominant-pole frequency of 10 Hz. The maximum closed-loop gain for the audio amplifier is 100. Determine the closed loop bandwidth of the amplifier.
15. For Fig. 10, neatly sketch the output voltage  $V_0$  when  $V_{in}$  is a sine wave of amplitude 2 V (zero to peak). Consider the op-amp as ideal and zero voltage drop across the diode in forward bias.

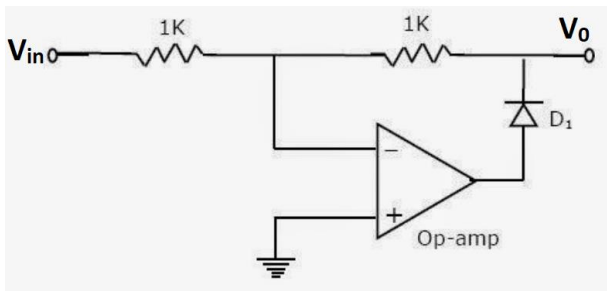


Fig. 10